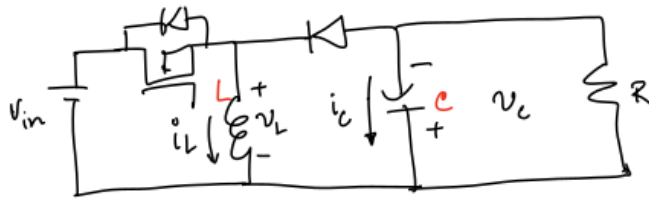



Lecture 3

January 11, 2022



Buck Boost converter

mode 1

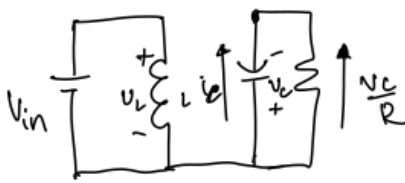

Mode 1


$$v_L = V_{in} = L \frac{di_L}{dt}$$

$$0 = i_C + \frac{v_C}{R}$$

$$0 = C \frac{dv_C}{dt} + \frac{v_C}{R}$$

$$\therefore C \frac{dv_C}{dt} = -\frac{v_C}{R}$$

Mode 2

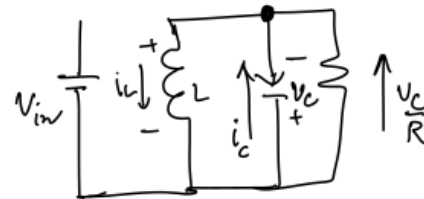

Mode 2

$$v_L = L \frac{di_L}{dt} = -v_C$$

$$i_L = i_C + \frac{v_C}{R}$$

$$\therefore C \frac{dv_C}{dt} = -\frac{v_C}{R} + i_L$$

$$\langle x(t) \rangle_{T_s} = \int_t^{t+T_s} x(\tau) d\tau$$

$$0 = (V_{in})D + (-V_C)D'$$

$$0 = \left(-\frac{v_C}{R}\right)D + \left(-\frac{v_C}{R} + I_L\right)D'$$

Balance Equations

$$\langle v_L(t) \rangle_{T_s} = L \frac{d}{dt} \langle i_L(t) \rangle_{T_s} = [v_L \text{ during mode 1}] d(t) + [v_L \text{ during mode 2}] d'(t)$$

$$= \langle v_{in}(t) \rangle_{T_s} d(t) + \langle -v_C(t) \rangle_{T_s} d'(t)$$

$$= \langle v_{in}(t) \rangle_{T_s} d(t) - \langle v_C(t) \rangle_{T_s} d'(t)$$

$$\langle i_C(t) \rangle_{T_s} = C \frac{d}{dt} \langle v_C(t) \rangle_{T_s} = [i_C \text{ during mode 1}] d(t) + [i_C \text{ during mode 2}] d'(t)$$

$$= \left(-\frac{\langle v_C(t) \rangle_{T_s}}{R} \right) d(t) + \left(-\frac{\langle v_C(t) \rangle_{T_s}}{R} + \langle i_L(t) \rangle_{T_s} \right) d'(t)$$

Notation

$\langle x(t) \rangle_{T_s}$ denotes the average of $x(t)$ over an interval of length T_s

Introduce Perturbation

$$\langle i_L(t) \rangle_{T_s} = I_L + \tilde{i}_L(t)$$

$$\langle v_C(t) \rangle_{T_s} = V_C + \tilde{v}_C(t)$$

$$\langle v_{in}(t) \rangle_{T_s} = V_{in} + \tilde{v}_{in}(t)$$

$$d(t) = D + \tilde{d}(t)$$

$$d'(t) = 1 - d(t)$$

$$= 1 - D - \tilde{d}(t)$$

$$= D' - \tilde{d}(t)$$

Rewrite Balance Equations $v_L(t)$

$$\langle v_L(t) \rangle_{T_s} = L \frac{d}{dt} \langle i_L(t) \rangle_{T_s} = \langle v_{in}(t) \rangle_{T_s} d(t) + \langle -v_C(t) \rangle_{T_s} d'(t)$$

$$L \frac{d}{dt} [I_L + \tilde{i}_L(t)] = [V_{in} + \tilde{v}_{in}(t)] [D + \tilde{d}(t)] - [V_C + \tilde{v}_C(t)] [D' - \tilde{d}(t)]$$

$$L \frac{d}{dt} I_L + L \frac{d}{dt} \tilde{i}_L(t) = V_{in} D + V_{in} \tilde{d}(t) + \tilde{v}_{in}(t) D + \tilde{v}_{in}(t) \tilde{d}(t) - V_C D' + V_C \tilde{d}(t) - \tilde{v}_C(t) D' + \tilde{v}_C(t) \tilde{d}(t)$$

Note $\tilde{v}_C(t) \tilde{d}(t)$ and $\tilde{v}_{in}(t) \tilde{d}(t)$ are very small and can be ignored

Collect similar terms

Large signal terms (DC terms)

$$L \frac{d}{dt} I_L = V_{in} D + -V_C D' = 0$$

$$V_{in} D = V_C D' \text{ where } V_C = V_0$$

$$\therefore V_0 = \frac{V_{in} D}{D'} \quad 1.$$

Linear small signal

$$L \frac{d}{dt} \tilde{i}_L(t) = V_{in} \tilde{d}(t) + \tilde{v}_{in}(t) D + V_C \tilde{d}(t) - \tilde{v}_C(t) D' \quad 2.$$

Rewrite Balance Equations $i_C(t)$

$$\langle i_C(t) \rangle_{T_s} = C \frac{d}{dt} \langle v_C(t) \rangle_{T_s} = \left(\frac{\langle v_C(t) \rangle_{T_s}}{R} \right) d(t) + \left(-\frac{\langle v_C(t) \rangle_{T_s}}{R} + \langle i_L(t) \rangle_{T_s} \right) d'(t)$$

$$C \frac{d}{dt} \langle v_C(t) \rangle_{T_s} = \frac{-\langle v_C(t) \rangle_{T_s}}{R} (d(t) + d'(t)) + \langle i_L(t) \rangle_{T_s} d'(t)$$

$$C \frac{d}{dt} \langle v_C(t) \rangle_{T_s} = \frac{-\langle v_C(t) \rangle_{T_s}}{R} + \langle i_L(t) \rangle_{T_s} d'(t)$$

$$\therefore C \frac{d}{dt} [V_C + \tilde{v}_C(t)] = \frac{-[V_C + \tilde{v}_C(t)]}{R} + [I_L + \tilde{i}_L(t)] [D' - \tilde{d}(t)]$$

Collect similar terms

1. Large signal terms (DC terms)

$$C \frac{d}{dt} V_C = \frac{V_C}{R} + I_L D' = 0$$

$$I_L = \frac{V_C}{RD'} \text{ where } V_C = V_0$$

$$\therefore I_L = \frac{V_0}{RD'} = \frac{I_0}{D'} \quad 3.$$


2. Linear small signal

$$C \frac{d}{dt} \tilde{v}_C(t) = \frac{-\tilde{v}_C(t)}{R} - I_L \tilde{d}(t) + \tilde{i}_L(t) D' \quad 4.$$

Linear small system

$$L \frac{d}{dt} \tilde{i}_L(t) = V_{in} \tilde{d}(t) + \tilde{v}_{in}(t)D + V_C \tilde{d}(t) - \tilde{v}_C(t)D'$$
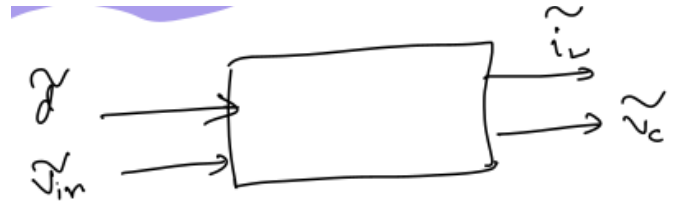
$$C \frac{d}{dt} \tilde{v}_C(t) = \frac{-\tilde{v}_C(t)}{R} - I_L \tilde{d}(t) + \tilde{i}_L(t)D'$$



Want to find $\frac{\tilde{i}_L}{\tilde{d}}, \frac{\tilde{v}_C}{\tilde{d}}$

$$L \frac{d}{dt} \tilde{i}_L(t) = V_{in} \tilde{d}(t) + \tilde{v}_{in}(t)D + V_C \tilde{d}(t) - \tilde{v}_C(t)D'$$

$$L [s \tilde{I}_L(s) - \tilde{i}_L(0)] = V_{in} \tilde{d}(s) + \tilde{v}_{in}(s)D + V_C \tilde{d}(s) - \tilde{v}_C(s)D'$$

control: apply $\tilde{i}_L(0) = 0$ and $\tilde{I}_L(s) = \langle i_L \rangle_{Ts}$

$$sL \tilde{i}_L(s) = V_{in} \tilde{d}(s) + \tilde{v}_{in}(s)D + V_C \tilde{d}(s) - \tilde{v}_C(s)D' \quad 5.$$

$$C \frac{d}{dt} \tilde{v}_C(t) = \frac{-\tilde{v}_C(t)}{R} - I_L \tilde{d}(t) + \tilde{i}_L(t)D'$$

$$sC \tilde{v}_C(s) = \frac{-\tilde{v}_C(s)}{R} - I_L \tilde{d}(s) + \tilde{i}_L(s)D' \quad 6.$$

Solve System

Set $\tilde{v}_{in} = 0$

$$sL \tilde{i}_L(s) = V_{in} \tilde{d}(s) + \tilde{v}_{in}(s)D + V_C \tilde{d}(s) - \tilde{v}_C(s)D'$$

$$\left(sC + \frac{1}{R}\right) \tilde{v}_C(s) = -I_L \tilde{d}(s) + \tilde{i}_L(s)D'$$

Find $\frac{\tilde{i}_L(s)}{\tilde{d}(s)}$

$$\tilde{v}_C(s) = \frac{\tilde{i}_L(s)D' - I_L\tilde{d}(s)}{sC + \frac{1}{R}}$$

$$sL\tilde{i}_L(s) = (V_{in} + V_C)\tilde{d}(s) - \tilde{v}_C(s)D'$$

$$sL\tilde{i}_L(s) = (V_{in} + V_C)\tilde{d}(s) - D'\frac{\tilde{i}_L(s)D' - I_L\tilde{d}(s)}{sC + \frac{1}{R}}$$

$$sL\tilde{i}_L(s) = (V_{in} + V_C)\tilde{d}(s) - \frac{\tilde{i}_L(s)D'^2}{sC + \frac{1}{R}} + \frac{D'I_L\tilde{d}(s)}{sC + \frac{1}{R}}$$

$$\left(sL + \frac{\tilde{i}_L(s)D'^2}{sC + \frac{1}{R}}\right)\tilde{i}_L(s) = (V_{in} + V_C)\tilde{d}(s) + \frac{D'I_L}{sC + \frac{1}{R}}\tilde{d}(s)$$

$$\therefore \frac{\tilde{i}_L(s)}{\tilde{d}(s)} = \frac{(V_{in} + V_C)(sC + \frac{1}{R}) + D'I_L}{s^2 LC + \frac{sL}{R} + D'^2}$$

Similarly find $\frac{\tilde{v}_C(s)}{\tilde{d}(s)}$...