

EE 458/533 – Power Electronics Controls
Homework 2
Due Date: Thursday January 20th 2021

1.

A) $\dot{x} = \begin{bmatrix} f_1(x, u) \\ f_2(x, u) \end{bmatrix} = \frac{d}{dt} \begin{bmatrix} \langle i(t) \rangle \\ \langle v(t) \rangle \end{bmatrix}$ where $u = \begin{bmatrix} d(t) \\ \langle v_g(t) \rangle \end{bmatrix}$

$$\frac{d}{dt} \begin{bmatrix} \langle i(t) \rangle \\ \langle v(t) \rangle \end{bmatrix} = \begin{bmatrix} \frac{1}{L} [\langle v_g(t) \rangle - 2R_{on}\langle i(t) \rangle - \langle v(t) \rangle] d(t) + \frac{1}{L} [-\langle v_g(t) \rangle - 2R_{on}\langle i(t) \rangle - \langle v(t) \rangle] d'(t) \\ \frac{1}{C} \left[\langle i(t) \rangle - \frac{\langle v(t) \rangle}{R} \right] d(t) + \frac{1}{C} \left[\langle i(t) \rangle - \frac{\langle v(t) \rangle}{R} \right] d'(t) \end{bmatrix}$$

$$\frac{d}{dt} \begin{bmatrix} \langle i(t) \rangle \\ \langle v(t) \rangle \end{bmatrix} = \begin{bmatrix} \frac{1}{L} [(2d(t) - 1)\langle v_g(t) \rangle - 2R_{on}\langle i(t) \rangle - \langle v(t) \rangle] \\ \frac{1}{C} \left[\langle i(t) \rangle - \frac{\langle v(t) \rangle}{R} \right] \end{bmatrix}$$

$$\frac{d}{dt} \begin{bmatrix} \langle i(t) \rangle \\ \langle v(t) \rangle \end{bmatrix} = \begin{bmatrix} \frac{1}{L} [2d(t)\langle v_g(t) \rangle - \langle v_g(t) \rangle - 2R_{on}\langle i(t) \rangle - \langle v(t) \rangle] \\ \frac{1}{C} \left[\langle i(t) \rangle - \frac{\langle v(t) \rangle}{R} \right] \end{bmatrix}$$

$$\langle v_L(t) \rangle = L \frac{d}{dt} [I + \langle \hat{i}(t) \rangle] = \left[2[D + \hat{d}(t)][V_g + \langle \hat{v}_g(t) \rangle] - [V_g + \langle \hat{v}_g(t) \rangle] - 2R_{on}[I + \langle \hat{i}(t) \rangle] - [V + \langle \hat{v}(t) \rangle] \right]$$


$$\langle v_L(t) \rangle = L \frac{d}{dt} [I + \langle \hat{i}(t) \rangle] = \left[2DV_g + 2D\langle \hat{v}_g(t) \rangle + 2\hat{d}(t)V_g + 2\hat{d}(t)\langle \hat{v}_g(t) \rangle - V_g - \langle \hat{v}_g(t) \rangle - 2R_{on}I - 2R_{on}\langle \hat{i}(t) \rangle - V - \langle \hat{v}(t) \rangle \right]$$

$$\langle \hat{v}_L(t) \rangle = L \frac{d}{dt} \langle \hat{i}(t) \rangle = \left[2D\langle \hat{v}_g(t) \rangle + 2\hat{d}(t)V_g - \langle \hat{v}_g(t) \rangle - 2R_{on}\langle \hat{i}(t) \rangle - \langle \hat{v}(t) \rangle \right]$$

$$\langle \hat{v}_L(t) \rangle = L \frac{d}{dt} \langle \hat{i}(t) \rangle = \left[(2D - 1)\langle \hat{v}_g(t) \rangle + 2\hat{d}(t)V_g - 2R_{on}\langle \hat{i}(t) \rangle - \langle \hat{v}(t) \rangle \right]$$

$$\langle i_C(t) \rangle = C \frac{d}{dt} [V + \langle \hat{v}(t) \rangle] = \left[[I + \langle \hat{i}(t) \rangle] - \frac{1}{R} [V + \langle v(t) \rangle] \right]$$
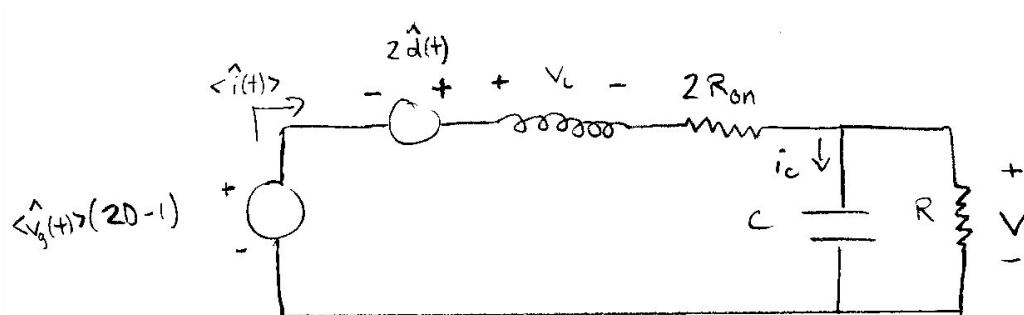
$$\langle \hat{i}_C(t) \rangle = C \frac{d}{dt} \langle \hat{v}(t) \rangle = \left[\langle \hat{i}(t) \rangle - \frac{\langle v(t) \rangle}{R} \right]$$



B) Taking the derivative with respect to x_1 and x_2 , the same values for A and B are found such that $\dot{\hat{x}}(t) = A\hat{x}(t) + B\hat{u}(t)$.

$$\frac{d}{dt}\langle\hat{i}(t)\rangle = \frac{1}{L}\left[(2D-1)\langle\hat{v}_g(t)\rangle + 2\hat{d}(t)V_g - 2R_{on}\langle\hat{i}(t)\rangle - \langle\hat{v}(t)\rangle\right]$$

$$\frac{d}{dt}\langle\hat{v}(t)\rangle = \frac{1}{C}\left[\langle\hat{i}(t)\rangle - \frac{\langle v(t)\rangle}{R}\right]$$

$$A = \left[\begin{array}{cc} \frac{\partial f_1}{\partial x_1} & \frac{\partial f_1}{\partial x_2} \\ \frac{\partial f_2}{\partial x_1} & \frac{\partial f_2}{\partial x_2} \end{array} \right] \Big|_{x,u} = \left[\begin{array}{cc} \frac{\partial f_1}{\partial \langle\hat{i}(t)\rangle} & \frac{\partial f_1}{\partial \langle\hat{v}(t)\rangle} \\ \frac{\partial f_2}{\partial \langle\hat{i}(t)\rangle} & \frac{\partial f_2}{\partial \langle\hat{v}(t)\rangle} \end{array} \right] \Big|_{x,u} = \left[\begin{array}{cc} \frac{-2R_{on}}{L} & \frac{-1}{L} \\ \frac{1}{C} & \frac{-1}{RC} \end{array} \right]$$

$$B = \left[\begin{array}{cc} \frac{\partial f_1}{\partial u_1} & \frac{\partial f_1}{\partial u_2} \\ \frac{\partial f_2}{\partial u_1} & \frac{\partial f_2}{\partial u_2} \end{array} \right] \Big|_{x,u} = \left[\begin{array}{cc} \frac{\partial f_1}{\partial \hat{d}(t)} & \frac{\partial f_1}{\partial \langle\hat{v}_g(t)\rangle} \\ \frac{\partial f_2}{\partial \hat{d}(t)} & \frac{\partial f_2}{\partial \langle\hat{v}_g(t)\rangle} \end{array} \right] \Big|_{x,u} = \left[\begin{array}{cc} \frac{-2V_g}{L} & \frac{2D-1}{L} \\ 0 & 0 \end{array} \right]$$

C)

$$\hat{y}(t) = \hat{x}(t) = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} \langle\hat{i}(t)\rangle \\ \langle\hat{v}(t)\rangle \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} \hat{d}(t) \\ \langle\hat{v}_g(t)\rangle \end{bmatrix}$$

$$\hat{y}(s) = \left(C(sI - A)^{-1}B + E \right) \hat{u}(s)$$

$$G(s) = \begin{bmatrix} G_{id}(s) & G_{ig}(s) \\ G_{vd}(s) & G_{vg}(s) \end{bmatrix} = \begin{bmatrix} \frac{2V_g(CRs+1)}{CLRs^2 + (2CRR_{on}+L)s + 2R_{on}+R} & \frac{(2D-1)(CRs+1)}{CLRs^2 + (2CRR_{on}+L)s + 2R_{on}+R} \\ \frac{2RV_g}{CLRs^2 + (2CRR_{on}+L)s + 2R_{on}+R} & \frac{R(2D-1)}{CLRs^2 + (2CRR_{on}+L)s + 2R_{on}+R} \end{bmatrix}$$

- D) Given $d=0.5$, $G_{ig}(s)$ and $G_{vg}(s)$ will have no response since they have terms of $(2D-1)$. Half the switching frequency is $25\text{kHz}/2 = 12.5\text{kHz}$, however the cross over frequencies occur at frequencies much greater than this.

The system is stable due to large positive phase margin in $G_{id}(s)$. Phase margin shows how much the system gain can be increased before it is unstable. There is also small positive phase margin in $G_{vd}(s)$.

TF	GM (dB)	PM (deg)	WG (Hz)	WP (Hz)	Stability
$G_{id}(s)$	inf	90.01	nan	106,182	yes
$G_{ig}(s)$	inf	inf	nan	nan	yes
$G_{vd}(s)$	inf	2.25	nan	41,180	yes
$G_{vg}(s)$	inf	inf	nan	nan	yes

