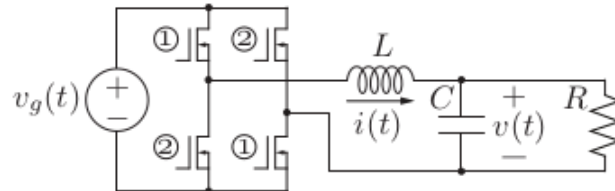



EE 458/533 – Power Electronics Controls, Winter 2022

Homework 1

Due Date: Thursday January 21 2022



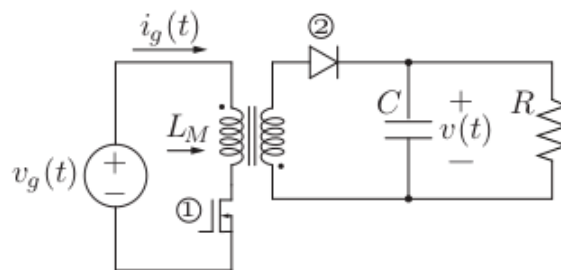Circuit for Problem 1: The single-phase voltage source inverter.



Circuit for Problem 2: The flyback converter.

1. a)

Mode 1

Mode 2

$$x(t) = \begin{bmatrix} f_1(x(t), u(t)) \\ f_2(x(t), u(t)) \end{bmatrix} = \begin{bmatrix} \frac{d}{dt} \langle i(t) \rangle_{T_s} \\ \frac{d}{dt} \langle v(t) \rangle_{T_s} \end{bmatrix}$$

$$x(t) = \begin{bmatrix} \frac{1}{L} [\langle v_g(t) \rangle_{T_s} - \langle v(t) \rangle_{T_s} - 2R_{on} \langle i(t) \rangle_{T_s}] dt + \frac{1}{C} [-\langle v_g(t) \rangle_{T_s} - \langle v(t) \rangle_{T_s} - 2R_{on} \langle i(t) \rangle_{T_s}] d'(t) \\ \frac{1}{C} [\langle i(t) \rangle_{T_s} - \frac{\langle v(t) \rangle_{T_s}}{R}] dt + \frac{1}{C} [\langle i(t) \rangle_{T_s} - \frac{\langle v(t) \rangle_{T_s}}{R}] d'(t) \end{bmatrix}$$

$$b.) L \frac{dI_L}{dt} = (V_g - V - 2R_{on}I_L)D + (-V_g - V - 2R_{on}I_L)D' = 0$$

$$0 = DV_g - D'V_g - V - \frac{2VR_{on}D}{R} + \frac{2VR_{on}D'}{R}$$

$$0 = (2D-1)V_g - V\left(\frac{2R_{on}}{R} + 1\right)$$

$$0 = (2D-1)V_g - V\left(\frac{2R_{on}+R}{R}\right)$$

$$V = \frac{R(2D-1)V_g}{2R_{on}+R}$$

$$C \frac{dV_c}{dt} = \left(I - \frac{V}{R}\right)D + \left(I - \frac{V}{R}\right)D' = 0$$

$$0 = I - \frac{V}{R} \rightarrow I = \frac{V}{R} = \frac{(2D-1)V_g}{2R_{on}+R}$$

$$c.) \quad \dot{\tilde{x}} = A(\tilde{x}) + B(\tilde{u})$$


$$A = \left. \frac{\partial f}{\partial \tilde{x}} \right|_{\substack{\tilde{x} = \bar{\tilde{x}} \\ \tilde{u} = \bar{\tilde{u}}}} = \begin{bmatrix} \frac{\partial f_1}{\partial \tilde{i}_L} & \frac{\partial f_1}{\partial \tilde{v}} \\ \frac{\partial f_2}{\partial \tilde{i}_L} & \frac{\partial f_2}{\partial \tilde{v}} \end{bmatrix} = \begin{bmatrix} -\frac{2R_{on}}{L} & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix}$$

$i_L = I_L, d = D$
 $v_c = V_c, v_{in} = V_{in}$

$$B = \left. \frac{\partial f}{\partial \tilde{u}} \right|_{\substack{\tilde{x} = \bar{\tilde{x}} \\ \tilde{u} = \bar{\tilde{u}}}} = \begin{bmatrix} \frac{\partial f_1}{\partial \tilde{d}} & \frac{\partial f_1}{\partial \tilde{v}_g} \\ \frac{\partial f_2}{\partial \tilde{d}} & \frac{\partial f_2}{\partial \tilde{v}_g} \end{bmatrix} = \begin{bmatrix} \frac{2V_g}{L} & \frac{2D-1}{L} \\ 0 & 0 \end{bmatrix}$$

$i_L = I_L, d = D$
 $v_c = V_c, v_{in} = V_{in}$


2. a)

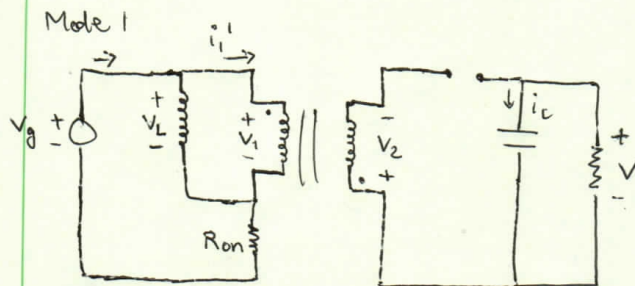

$$i_L + n i_C = 0$$

$$i_L = i_C = 0$$
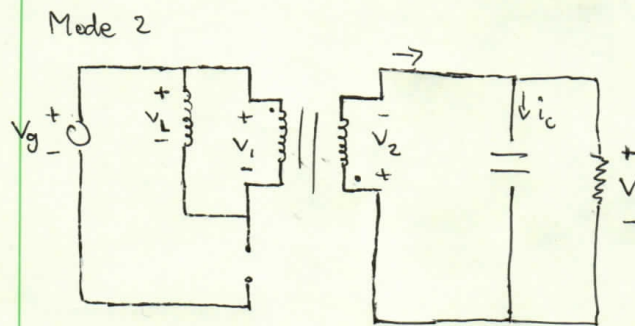
$$V_1 = \frac{V_2}{n} \rightarrow V_2 = n V_1 = n V_g$$



$$x(t) = \begin{bmatrix} f_1(x(t), u(t)) \\ f_2(x(t), u(t)) \end{bmatrix} = \begin{bmatrix} \frac{d}{dt} \langle i(t) \rangle_{T_s} \\ \frac{d}{dt} \langle v(t) \rangle_{T_s} \end{bmatrix}$$

$$x(t) = \begin{bmatrix} \frac{1}{L} \left[\langle V_g(t) \rangle_{T_s} - R_{on} \langle i(t) \rangle_{T_s} \right] d(t) + \frac{1}{L} \left[-\frac{\langle v(t) \rangle_{T_s}}{n} \right] d'(t) \\ \frac{1}{C} \left[-\frac{\langle v(t) \rangle_{T_s}}{R} \right] d(t) + \frac{1}{C} \left[\frac{\langle i(t) \rangle_{T_s}}{n} - \frac{\langle v(t) \rangle_{T_s}}{R} \right] d'(t) \end{bmatrix}$$

$$b.) \quad L \frac{dI_L}{dt} = (V_g - I R_{on}) D + \left(\frac{-V}{n}\right) D' = 0$$

$$0 = V_g D - \frac{n D R_{on} V}{R D'} - \frac{D'}{n} V$$

$$0 = V_g D - V \left(\frac{n D R_{on}}{R D'} + \frac{D'}{n} \right)$$

$$V = \frac{V_g D}{\frac{n D R_{on}}{R D'} + \frac{D'}{n}}$$

$$C \frac{dV_c}{dt} = \left(\frac{-V}{R}\right) D + \left(\frac{I}{n} - \frac{V}{R}\right) D' = 0$$

$$0 = \frac{-V}{R} + \frac{I}{n} D'$$

$$I = \frac{n V}{R D'} = \frac{n}{R D'} \left(\frac{V_g D}{\frac{n D R_{on}}{R D'} + \frac{D'}{n}} \right)$$

$$c.) \quad \dot{\tilde{x}} = A(x - \bar{x}) + B(u - \bar{u})$$



$$A = \frac{\partial f}{\partial \tilde{x}} \bigg|_{\substack{x=\bar{x}, \\ u=\bar{u}}} = \begin{bmatrix} \frac{\partial f_1}{\partial \tilde{i}_L} & \frac{\partial f_1}{\partial \tilde{v}} \\ \frac{\partial f_2}{\partial \tilde{i}_L} & \frac{\partial f_2}{\partial \tilde{v}} \end{bmatrix} = \begin{bmatrix} \frac{-R_{on} D}{L} & \frac{-D'}{nL} \\ \frac{D'}{nC} & \frac{-1}{RC} \end{bmatrix} \bigg|_{\substack{i_L = I_L, d=D \\ v_c = V_c, v_{in} = V_{in}}} \quad n=2$$

$$A = \begin{bmatrix} \frac{-R_{on} D}{L} & \frac{-D'}{nL} \\ \frac{D'}{nC} & \frac{-1}{RC} \end{bmatrix}$$

$$B = \frac{\partial f}{\partial \tilde{u}} \bigg|_{\substack{x=\bar{x}, \\ u=\bar{u}}} = \begin{bmatrix} \frac{\partial f_1}{\partial \tilde{a}} & \frac{\partial f_1}{\partial \tilde{v}_g} \\ \frac{\partial f_2}{\partial \tilde{a}} & \frac{\partial f_2}{\partial \tilde{v}_g} \end{bmatrix} =$$

$$B = \begin{bmatrix} \frac{1}{L}(V_g - IR_{on} + \frac{V}{n}) & \frac{D}{L} \\ \cancel{\frac{-V}{RC}} - \frac{1}{nC} + \cancel{\frac{V}{RC}} & 0 \end{bmatrix}_{n=2} = \begin{bmatrix} \frac{1}{L}(V_g - IR_{on} + \frac{V}{n}) & \frac{D}{L} \\ \frac{-1}{nC} & 0 \end{bmatrix}$$
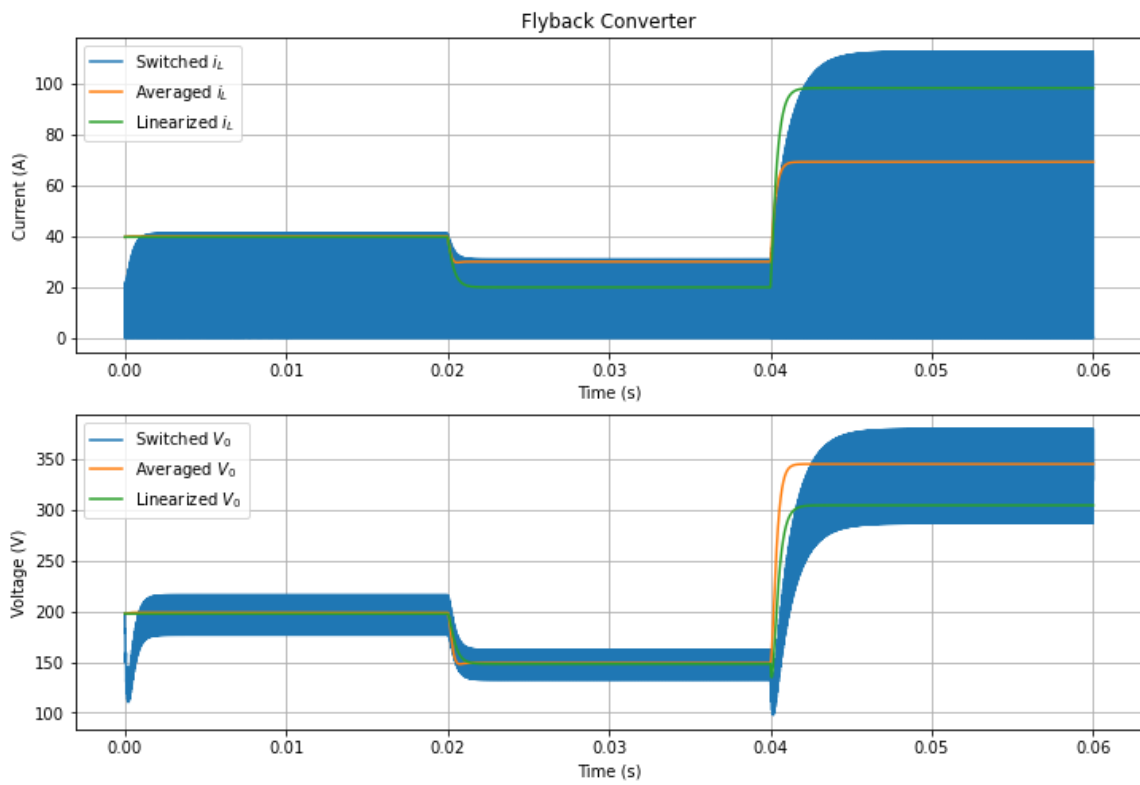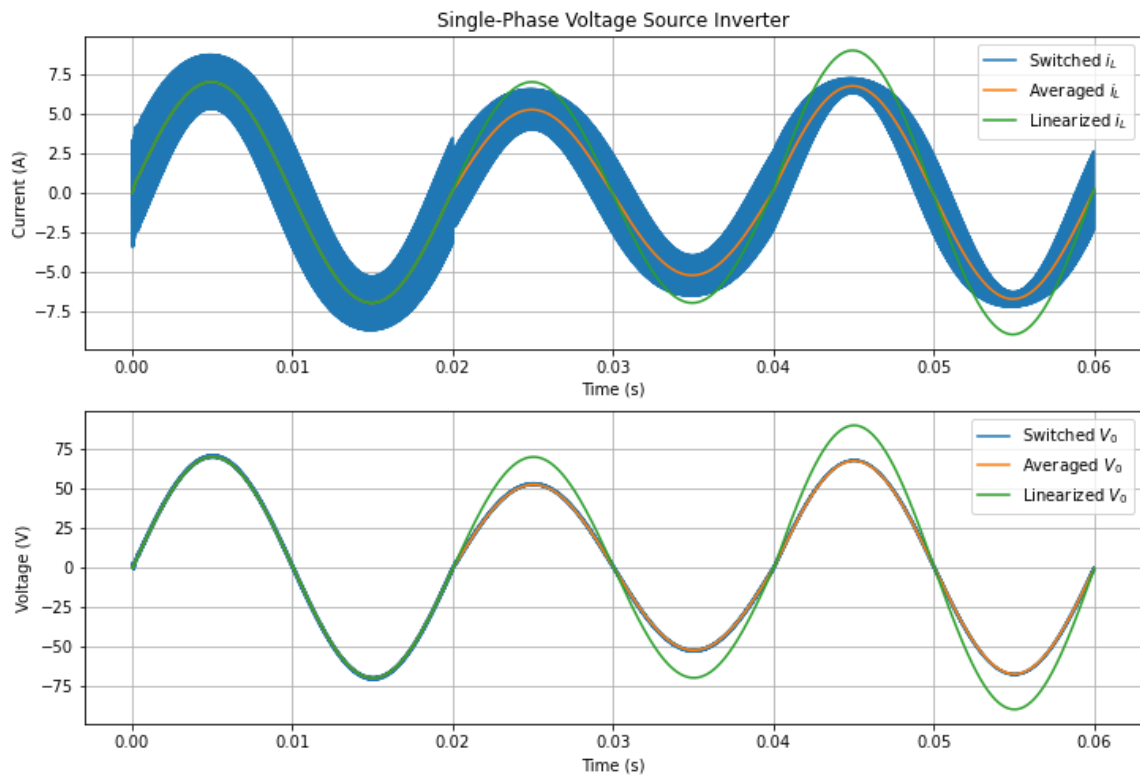
$$B = \begin{bmatrix} \frac{1}{L}(V_g - IR_{on} + \frac{V}{2}) & \frac{D}{L} \\ \frac{-1}{2C} & 0 \end{bmatrix}$$



$$3 \text{ a.) } q = 0.02 = \frac{1}{N_r + 1} \rightarrow N_r = 49$$

$$T_{sw} = 2N_r \cdot T_{clk}$$

$$N_r = \frac{T_{sw}}{2T_{clk}}$$

$$q_r = \frac{1}{N_r + 1} = \frac{1}{\frac{T_{sw}}{2T_{clk}} + 1} = \frac{1}{\frac{f_{clk}}{2f_{sw}} + 1}$$

$$0.02 = \frac{1}{\frac{100 \text{ MHz}}{2f_{sw}} + 1}$$

$$f_{sw} = 1.02 \text{ MHz}$$

$$b.) \quad N_r = \frac{T_{sw}}{2T_{clk}} \rightarrow 2^{N_{pwm}} = \frac{f_{clk}}{2f_{sw}}$$

$$2^{16} = \frac{f_{clk}}{2f_{sw}} \rightarrow f_{sw} = \frac{f_{clk}}{2 \cdot 2^{16}} = \frac{100 \text{ MHz}}{2 \cdot 65,536} = 762 \text{ Hz}$$

$$c.) \quad N_r \leq 2^{N_{pwm}} - 1$$

$$N_r \leq 2^{16} - 1$$

$$N_r \leq 65,535$$

$$q = \frac{1}{N_r + 1} = \frac{1}{65,536} = 1.5 \text{ E-5}$$

$$q = \Delta D = 0.0015 \%$$

$$d.) V_0 = V_{in} \cdot \frac{D}{\frac{nDR_{on}}{RD'} + \frac{D'}{n}}$$

$$\text{and } n=2, R=10, R_{on}=15\text{ m}\Omega$$

$$\Delta V_0 = V_{in} \frac{\Delta D}{\frac{n\Delta DR_{on}}{R(1-\Delta D)} + \frac{(1-\Delta D)}{n}} = V_{in} \frac{1.5E-5}{\frac{2(1.5E-5)(15E-3)}{10(1-1.5E-5)} + \frac{(1-1.5E-5)}{2}}$$

$$\Delta V_0 = 3E-5 V_{in}$$