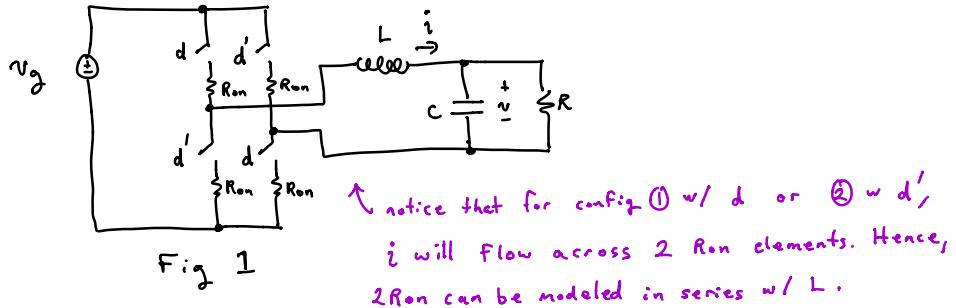


Homework #2

#1) Look @ switched ckt first



a) Average the sw. ports

Following p.9-10 of lecture #4, draw the H-bridge as
two sets of sw. ports

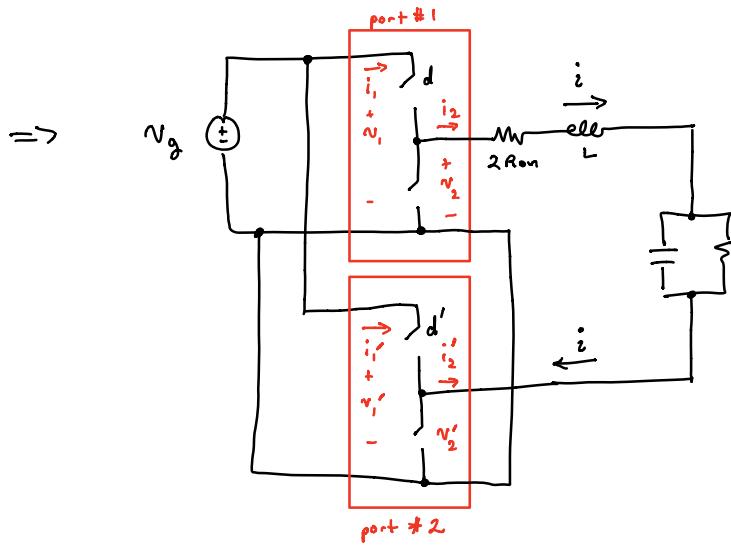


Fig 2

• Avg port #1

$$\langle v_2 \rangle = d \langle v_1 \rangle + d' \cancel{\langle v_0 \rangle^0} \quad (i)$$

$$\langle i_1 \rangle = d \langle i_2 \rangle + d' \cancel{\langle i_0 \rangle^0} \quad (ii)$$

put in xfmr form

$$\frac{\langle N_1 \rangle}{1} = \frac{\langle N_2 \rangle}{d} \Rightarrow \frac{\langle i_1 \rangle}{\langle N_1 \rangle} = \frac{\langle i_2 \rangle}{\langle N_2 \rangle}$$

$\langle i_1 \rangle - d \langle i_2 \rangle = 0$

(of form)

$\frac{\# \text{windings} \times \text{current into}}{\text{coil } 1 \text{ dot } 1} + \frac{\# \text{windings} \times \text{current into}}{\text{coil } 2 \text{ dot } 2} + \dots = 0$

- Avg port #2

$$\langle N'_2 \rangle = d' \langle N'_1 \rangle + d \langle \emptyset \rangle$$


$$\langle i'_1 \rangle = d' \langle i'_2 \rangle + d \langle \emptyset \rangle$$

put in xfmr form

$$\frac{\langle N'_1 \rangle}{1} = \frac{\langle N'_2 \rangle}{d'} \Rightarrow \frac{\langle i'_1 \rangle}{\langle N'_1 \rangle} = \frac{\langle i'_2 \rangle}{\langle N'_2 \rangle}$$


$\langle i'_1 \rangle - d' \langle i'_2 \rangle = 0$

- Draw avg version of Fig 2 :

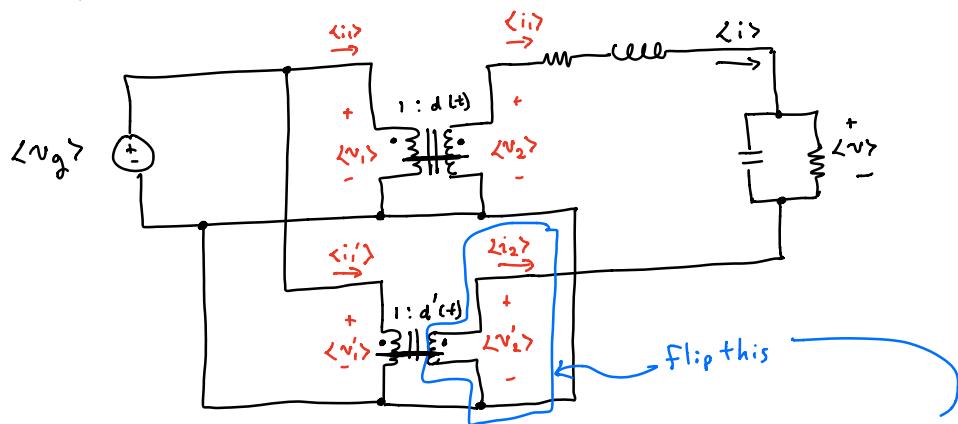

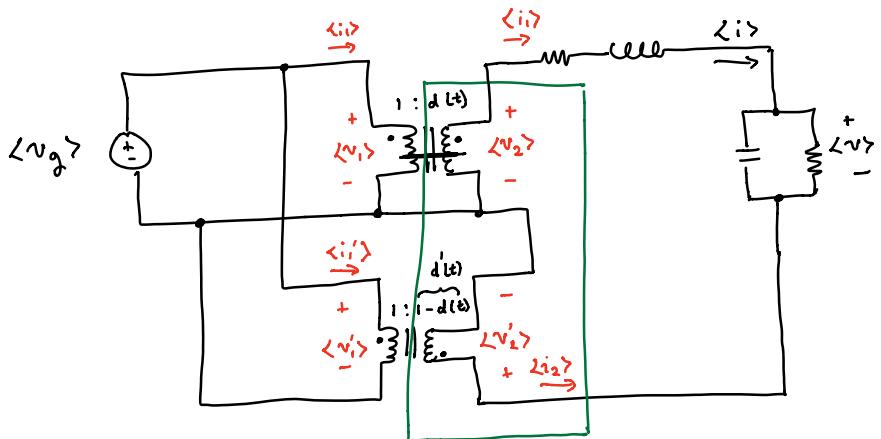Let's manipulate this setup to simplify. First flip secondary coil on port #2. Note dot on that coil flips.





It's easy to see secondary coils in series

Next step is to combine both xfmr into one. 2 series coils w/ $n_1 \neq n_2$ turns are equivalent of one coil w/ $n_1 + n_2$ turns.



To make easier to see method of combining 2 xfmers, focus on bottom xfmr for port #2 ↴

$$\begin{array}{c}
 \text{Circuit diagram of the bottom xfmr:} \\
 \text{Primary: } \frac{\langle i_1' \rangle}{+} \xrightarrow{\parallel} \frac{\langle n_1' \rangle}{-} \xrightarrow{\parallel} \frac{\langle v_2' \rangle}{+} \xrightarrow{\parallel} \frac{\langle i_2' \rangle}{-} \\
 \text{Secondary: } \frac{\langle v_2' \rangle}{+} \xrightarrow{\parallel} \frac{\langle n_2' \rangle}{-} \xrightarrow{\parallel} \frac{\langle i_2' \rangle}{+} \xrightarrow{\parallel} \frac{\langle v_2 \rangle}{-}
 \end{array}
 \quad \frac{\langle n_1' \rangle}{1} = \frac{\langle n_2' \rangle}{1-d} \quad (1) \\
 \Leftrightarrow \langle i_1' \rangle(1) + (-\langle i_2' \rangle)(1-d) = 0 \quad (2)$$

This ckt is a pain b/c dot is on bottom of secondary. Can get equiv xfmr w/ dot on top by multiplying $(1-d)$ turns by (-1) . We get ↴

$$\begin{array}{c}
 \text{Circuit diagram of the bottom xfmr with dot on top:} \\
 \text{Primary: } \frac{\langle i_1' \rangle}{+} \xrightarrow{\parallel} \frac{\langle n_1' \rangle}{-} \xrightarrow{\parallel} \frac{\langle v_2' \rangle}{+} \xrightarrow{\parallel} \frac{\langle i_2' \rangle}{-} \\
 \text{Secondary: } \frac{\langle v_2' \rangle}{+} \xrightarrow{\parallel} \frac{\langle n_2' \rangle}{-} \xrightarrow{\parallel} \frac{\langle i_2' \rangle}{+} \xrightarrow{\parallel} \frac{\langle v_2 \rangle}{-}
 \end{array}
 \quad \frac{\langle n_1' \rangle}{1} = \frac{-\langle n_2' \rangle}{d-1} \quad (3) \\
 \Leftrightarrow \langle i_1' \rangle(1) + \underbrace{\langle i_2' \rangle(d-1)}_{(-\langle i_2' \rangle)(1-d)} = 0 \quad (4)$$

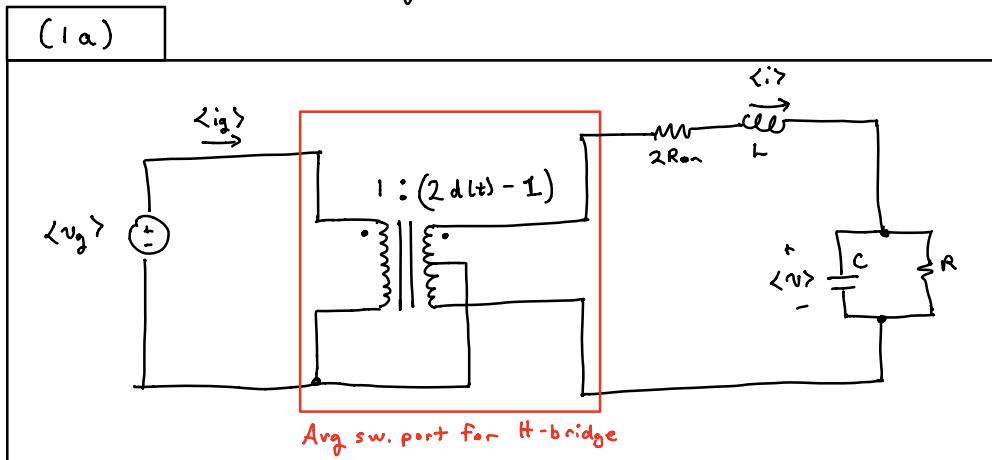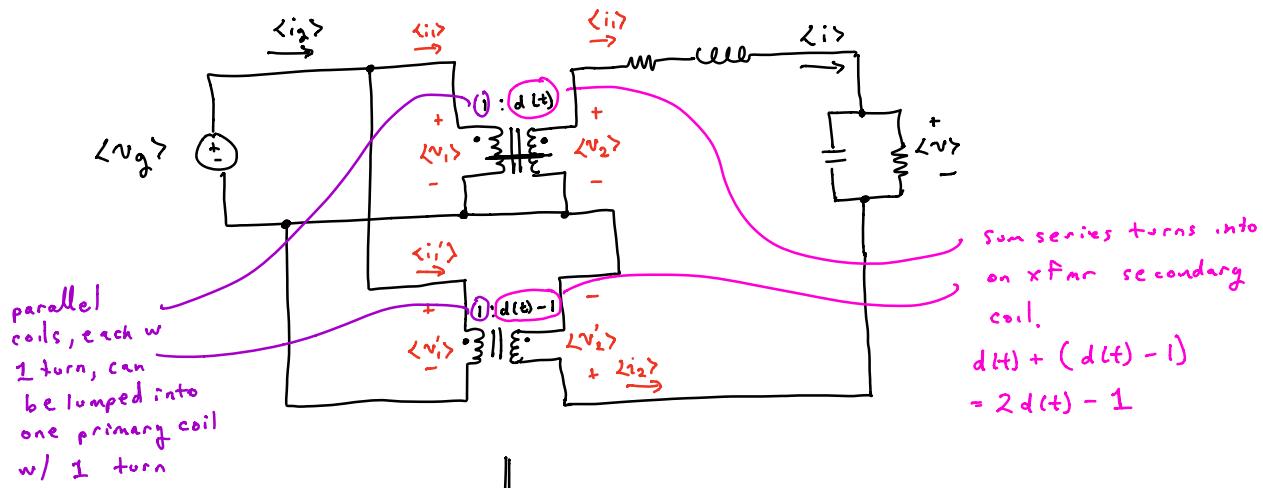Since (1)-(2) ≠ (3)-(4) are equiv, we get



This is the same as in HW 1. But this solution is most complete since it shows that secondary midpoint is with respect to \ominus rail of $\langle v_g \rangle$ supply.

b) Derive small-signal equiv ckt

Focus on Avg sw. port xfrm equiv in (1a)

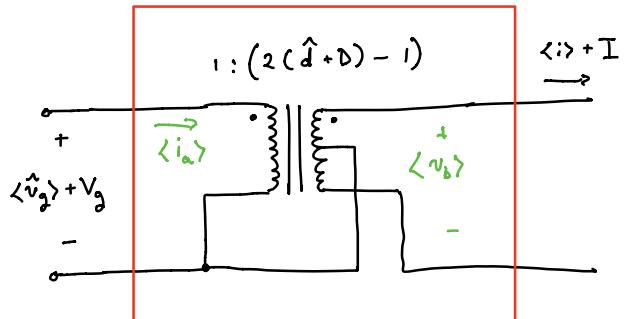


Fig 3

- Let $\langle i_a \rangle$ & $\langle v_b \rangle$ denote input/output of new equiv ckt from (1a).
- $\langle v_b \rangle$ depends on $\langle v_g \rangle$ input
- $\langle i_a \rangle$ depends on $\langle i \rangle$ state
- Compute $\langle v_b \rangle$

$$\begin{aligned}\langle v_b \rangle &= (V_g + \langle \hat{v}_g \rangle)(2(\hat{d} + D) - 1) \\ &= (V_g + \langle \hat{v}_g \rangle)((2D - 1) + 2\hat{d}) \\ &= \underbrace{V_g(2D - 1)}_{\text{dc comp.}} + \underbrace{\langle \hat{v}_g \rangle(2D - 1)}_{\text{1st order linear terms}} + \underbrace{2V_g\hat{d}}_{\text{2nd order}} + \underbrace{2\hat{d}\langle \hat{v}_g \rangle}_{\text{2nd order}} \quad (5) \leftarrow \frac{\text{KVL}}{\text{for secondary}}\end{aligned}$$

Compute $\langle i_a \rangle$

$$\begin{aligned}\langle i_a \rangle &= (I + \langle \hat{i} \rangle)(2(\hat{d} + D) - 1) \\ &= (I + \langle \hat{i} \rangle)((2D - 1) + 2\hat{d}) \\ &= \underbrace{I(2D - 1)}_{\text{dc comp.}} + \underbrace{\langle \hat{i} \rangle(2D - 1)}_{\text{1st order linear terms}} + \underbrace{2I\hat{d}}_{\text{2nd order}} + \underbrace{2\hat{d}\langle \hat{i} \rangle}_{\text{2nd order}} \quad (6) \leftarrow \frac{\text{KCL}}{\text{for primary}}\end{aligned}$$

- Next, discard dc terms in (5) - (6) and also discard V_g
- $\nexists I$ in Fig 3. Use KVL/KCL relations implied in (5) - (6) to get

(1 b)


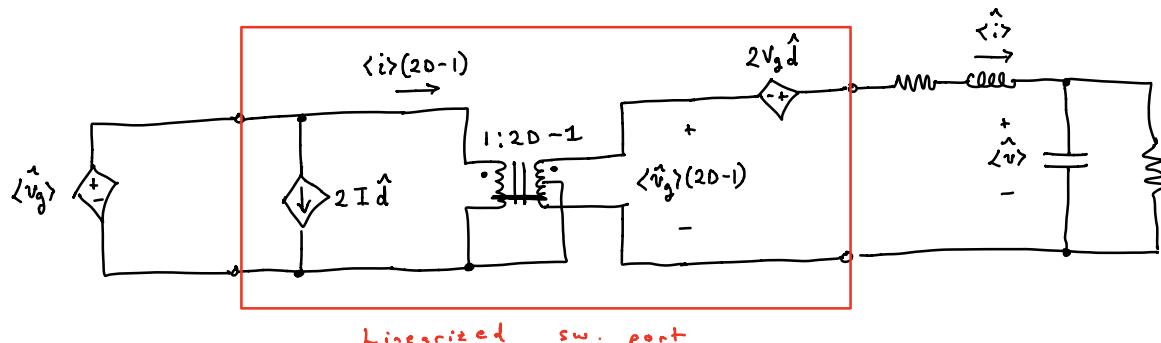


Fig 4

$$(c) \text{ Derive } \frac{d}{dt} \langle \hat{i} \rangle \neq \frac{d}{dt} \langle \hat{v} \rangle.$$

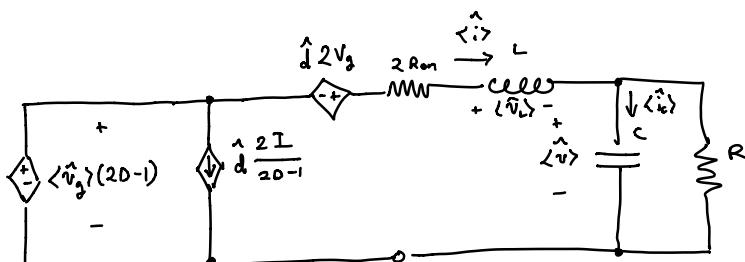Push all ckt elements to right hand side of eqn.



$$\begin{aligned} \frac{d}{dt} \langle \hat{i} \rangle &= \frac{1}{L} \langle \hat{v}_r \rangle \\ &= \frac{1}{L} (\langle \hat{v}_g \rangle (2D-1) + \frac{d}{dt} 2 \hat{V}_g - 2 R_{on} \langle \hat{i} \rangle - \langle \hat{v} \rangle) \end{aligned}$$

¶

$$\begin{aligned} \frac{d}{dt} \langle \hat{v} \rangle &= \frac{1}{C} \langle \hat{i} \rangle \\ &= \frac{1}{C} (\langle \hat{i} \rangle - \langle \hat{v} \rangle / R) \end{aligned}$$

↓ put in matrix form

(1c)

$$\frac{d}{dt} \begin{bmatrix} \hat{i} \\ \hat{v} \end{bmatrix} = \underbrace{\begin{bmatrix} -\frac{2R_{on}}{L} & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix}}_A \begin{bmatrix} \hat{i} \\ \hat{v} \end{bmatrix} + \underbrace{\begin{bmatrix} \frac{2V_0}{L} & \frac{2D-1}{L} \\ 0 & 0 \end{bmatrix}}_B \begin{bmatrix} \hat{d} \\ \hat{v}_2 \end{bmatrix}$$

↑ matches solution in HW 1!

1 d) Given $C = I_{2 \times 2}$ & $E = O_{2 \times 2}$, compute freq domain model.

From Lecture #7, we know:

$$\hat{y}(s) = (C(sI - A)^{-1}B + E)\hat{u}(s)$$

$$* C = I, E = O_{2 \times 2}$$

$$= (sI - A)^{-1}B\hat{u}(s)$$

$$= \left(s \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - \begin{bmatrix} -\frac{2R_{on}}{L} & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix} \right)^{-1} B \hat{u}(s)$$

$$= \begin{bmatrix} s + \frac{2R_{on}}{L} & \frac{1}{L} \\ -\frac{1}{C} & s + \frac{1}{RC} \end{bmatrix}^{-1} B \hat{u}(s)$$

$$* \begin{bmatrix} ab \\ cd \end{bmatrix}^{-1} = \frac{1}{ad-bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$$

$$= \frac{(sI - A)^{-1}}{\left(s + \frac{2R_{on}}{L} \right) \left(s + \frac{1}{RC} \right) - \left(\frac{1}{C} \right) \left(-\frac{1}{L} \right)} \underbrace{\begin{bmatrix} s + \frac{1}{RC} & -\frac{1}{L} \\ \frac{1}{C} & s + \frac{2R_{on}}{L} \end{bmatrix}}_{\textcircled{2}} \underbrace{\begin{bmatrix} \frac{2V_0}{L} & \frac{2D-1}{L} \\ 0 & 0 \end{bmatrix}}_B \hat{u}(s)$$

$$\begin{aligned}
&= \frac{1}{s^2 + s \left(\frac{1}{RC} + \frac{2R_{on}}{L} \right) + \frac{2R_{on}}{RLC} + \frac{1}{LC}} \cdot \frac{\frac{RLC}{RLC}}{\frac{RLC}{RLC}} \quad (*) \\
&= \frac{\frac{RLC}{RLC}}{s^2 RLC + s(L + 2R_{on}RC) + 2R_{on} + R} \left[\begin{array}{l} \cancel{(s + \frac{1}{RC}) (\frac{2V_2}{L})} + \cancel{(-\frac{1}{L})(0)} \cancel{(s + \frac{1}{RC}) (\frac{2D-1}{L})} + \cancel{(\frac{-1}{L})(0)} \\ \cancel{(\frac{1}{C})(\frac{2V_2}{L})} + \cancel{(s + \frac{2R_{on}}{L})(0)} \cancel{(\frac{1}{C})(\frac{2D-1}{L})} + \cancel{(s + \frac{2R_{on}}{L})(0)} \end{array} \right] \hat{u}(cs) \\
&= \frac{1}{s^2 RLC + s(L + 2R_{on}RC) + 2R_{on} + R} \left[\begin{array}{l} \cancel{RLC} (s + \frac{1}{RC}) (\frac{2V_2}{L}) \\ \cancel{RLC} (\frac{1}{C}) (\frac{2V_2}{L}) \end{array} \right] \left[\begin{array}{l} \cancel{RLC} (s + \frac{1}{RC}) (\frac{2D-1}{L}) \\ \cancel{RLC} (\frac{1}{C}) (\frac{2D-1}{L}) \end{array} \right] \hat{u}(cs) \\
&= \frac{1}{s^2 RLC + s(L + 2R_{on}RC) + 2R_{on} + R} \left[\begin{array}{l} 2V_2 (SRC + 1) \\ 2V_2 R \end{array} \right] \left[\begin{array}{l} (2D-1)(SRC+1) \\ (2D-1)R \end{array} \right] \left[\begin{array}{l} \hat{u}_d(cs) \\ \hat{u}_{ng}(cs) \end{array} \right]
\end{aligned}$$


where $G(s) = \begin{bmatrix} G_{id}(s) & G_{ig}(s) \\ G_{rd}(s) & G_{rg}(s) \end{bmatrix}$

and

$G_{id}(s) = \frac{2V_2 (SRC + 1)}{s^2 RLC + s(L + 2R_{on}RC) + 2R_{on} + R}$
$G_{ig}(s) = \frac{(2D-1)(SRC+1)}{s^2 RLC + s(L + 2R_{on}RC) + 2R_{on} + R}$
$G_{rd}(s) = \frac{2V_2 R}{s^2 RLC + s(L + 2R_{on}RC) + 2R_{on} + R}$
$G_{rg}(s) = \frac{(2D-1)R}{s^2 RLC + s(L + 2R_{on}RC) + 2R_{on} + R}$

1e) Re-derive result in (1c) using ckt analysis in s-domain.

Look @ ckt:

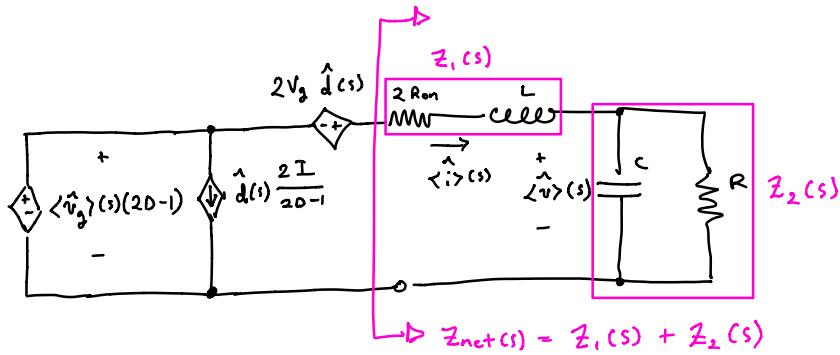

Follow method in Lecture #6:

- First calculate a few things we need later!

$$\square Z_{net}(s) = Z_1(s) + Z_2(s)$$


$$\begin{aligned} &= (2R_{on} + sL) + \left(\frac{1}{sC} \parallel R\right) \\ &= (2R_{on} + sL) + \frac{\frac{1}{sC}R}{R + \frac{1}{sC}} \cdot \frac{sC}{sC} = 2R_{on} + sL + \frac{R}{sRC + 1} \\ &= \frac{(2R_{on} + sL)(sRC + 1) + R}{sRC + 1} \\ &= \frac{s^2RLC + s(2R_{on}RC + L) + 2R_{on} + R}{sRC + 1} \end{aligned}$$

\square Voltage Divider

$$\begin{aligned} &\frac{R \parallel \frac{1}{sC}}{R \parallel \frac{1}{sC} + 2R_{on} + sL} = \frac{\frac{R \frac{1}{sC}}{R + \frac{1}{sC}} \cdot \frac{sC}{sC}}{\frac{R \frac{1}{sC}}{R + \frac{1}{sC}} \cdot \frac{sC}{sC} + 2R_{on} + sL} \\ &= \frac{\frac{R}{sRC + 1}}{s^2RLC + s(2R_{on}RC + L) + 2R_{on} + R} \end{aligned}$$


$$= \frac{R}{s^2 RLC + s(2R_{on}RC + L) + 2R_{on} + R}$$

- Use Superposition

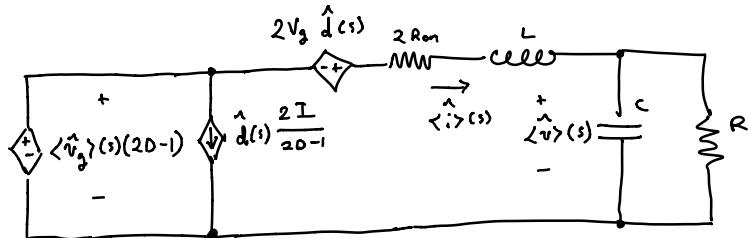


=

Ckt (a) : set $\hat{v}_g = 0$

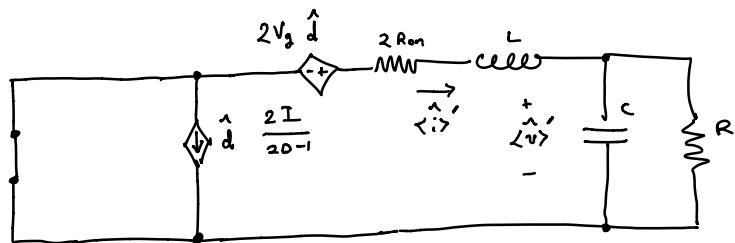

+

Ckt (b) : set $\hat{d} = 0$

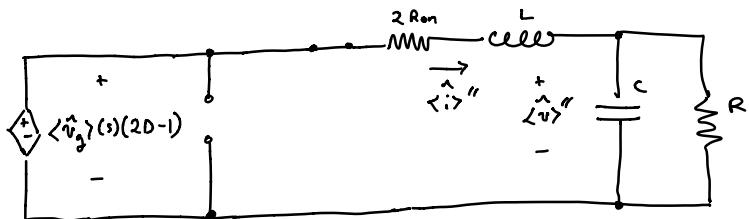


=

Solution

$$\hat{i}(s) = \hat{i}'(s) + \hat{i}''(s)$$

$$\hat{v}(s) = \hat{v}'(s) + \hat{v}''(s)$$

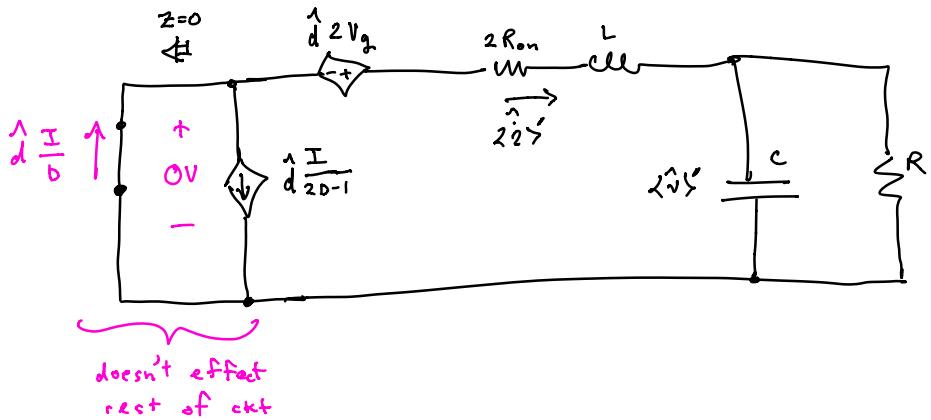- Solve ckt @ for $\langle \hat{i}_2' \rangle(s)$, $\langle \hat{v}_2' \rangle(s)$




$$\begin{aligned}\langle \hat{i}_2' \rangle(s) &= \frac{\langle \hat{v}_2' \rangle(s) 2Vg}{Z_{\text{net}}} \cdot \frac{1}{Z_{\text{net}}} \\ &= \frac{\langle \hat{v}_2' \rangle(s) 2Vg}{s^2 RLC + s(2RonRC + L) + 2Ron + R} \cdot \frac{sRC + 1}{s^2 RLC + s(2RonRC + L) + 2Ron + R}\end{aligned}$$

Get $\langle \hat{v}_2' \rangle$

$$\langle \hat{v}_2' \rangle(s) = \frac{\langle \hat{i}_2' \rangle(s) 2Vg}{s^2 RLC + s(2RonRC + L) + 2Ron + R} \underbrace{\frac{R}{s^2 RLC + s(2RonRC + L) + 2Ron + R}}_{\text{Voltage div.}}$$

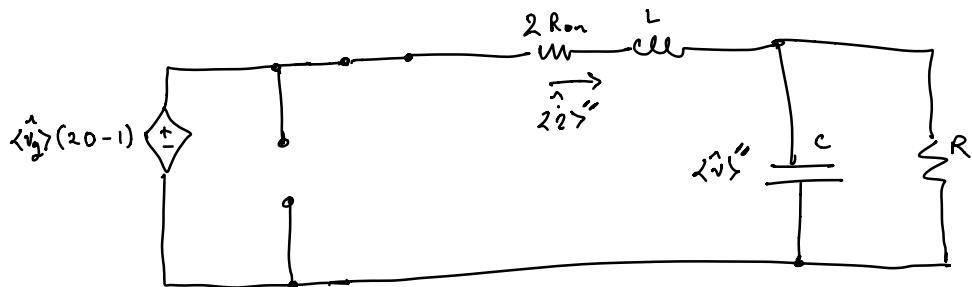- Solve ckt (b) for $\langle \hat{i}_2'' \rangle(s)$, $\langle \hat{v}_2'' \rangle(s)$



Get $\langle \hat{i}_2'' \rangle$

$$\langle \hat{i}''(s) \rangle = \langle \hat{v}_g(s) \rangle (2D-1) \frac{1}{Z_{net}(s)}$$

$$= \langle \hat{v}_g(s) \rangle (2D-1) \frac{sRC + 1}{s^2RLC + s(2R_{on}RC + L) + 2R_{on} + R}$$

Get $\langle \hat{v}'' \rangle$

$$\langle \hat{v}''(s) \rangle = \langle \hat{v}_g(s) \rangle (2D-1) \frac{R}{s^2RLC + s(2R_{on}RC + L) + 2R_{on} + R}$$

$\underbrace{\hspace{10em}}$ $\underbrace{\hspace{10em}}$
voltage div.

- Put together to get soln.

(1e)

$\langle \hat{i}'(s) \rangle = \langle \hat{i}'(s) \rangle + \langle \hat{i}''(s) \rangle$ $= \frac{\langle \hat{v}_g(s) \rangle 2V_g}{s^2RLC + s(2R_{on}RC + L) + 2R_{on} + R} \quad G_{id}(s)$ $+ \langle \hat{v}_g(s) \rangle (2D-1) \frac{sRC + 1}{s^2RLC + s(2R_{on}RC + L) + 2R_{on} + R} \quad G_{ig}(s)$ $\langle \hat{v}(s) \rangle = \langle \hat{v}'(s) \rangle + \langle \hat{v}''(s) \rangle \quad \text{↙ same result as part (1d)!}$ $= \frac{\langle \hat{v}_g(s) \rangle 2V_g}{s^2RLC + s(2R_{on}RC + L) + 2R_{on} + R} \quad G_{vd}(s)$ $+ \langle \hat{v}_g(s) \rangle (2D-1) \frac{R}{s^2RLC + s(2R_{on}RC + L) + 2R_{on} + R} \quad G_{vg}(s)$
