

Lab 2 Lecture Notes

Monday, January 31, 2022 5:12 PM

Agenda:

- Inner current / outer voltage control (Background)
- week 1: controller design
- week 2: implementation and HiL
- week 3: work-time and wrap-up.

1) Background.

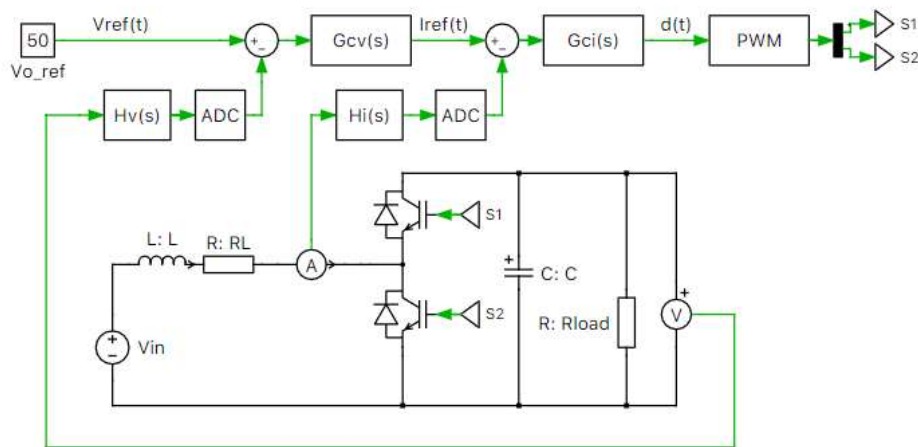


Figure 1: Conceptual diagram of ICOV control for a synchronous boost

* note inputs / outputs

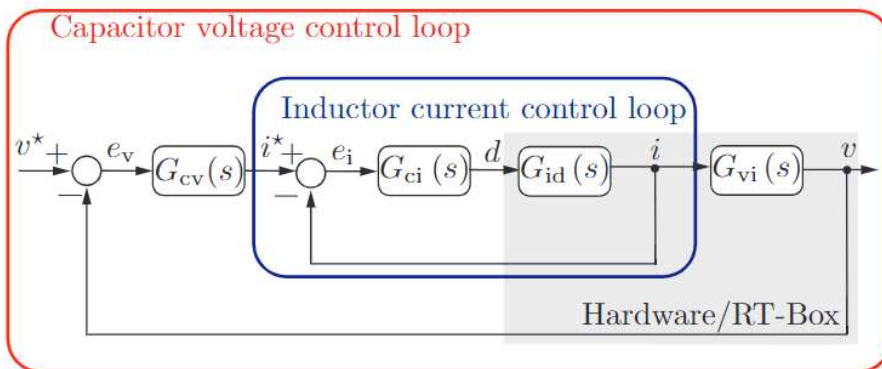


Figure 2: Transfer function diagram of ICOV control

ω_{bw} for IC loop 10x HIGHER than ω_{bw} for OV loop

Why?

- say we have OV @ 1Hz \rightarrow output at highest 1Hz signal
IC @ 10Hz any higher is filtered.

- say we have OV @ 1Hz \rightarrow output at highest 1Hz signal
- IC @ 10Hz any higher is filtered.

\hookrightarrow gain @ 1Hz is high since ω_{bw} is much higher; sees close to DC.

\hookrightarrow IC $\omega_{bw} \leq \frac{\omega_{sw}}{10}$

2) Controller Design: (week 1)

- similar process for IC and OV
 - specific to this problem
 - general solution discussed in lecture.



• IC controller design:

input: i_{ref} output: d

- 1) select $\omega_{c,i} \leq \frac{\omega_{sw}}{10}$
 $\phi_m \leq 60^\circ$ (I'll pick 60°)

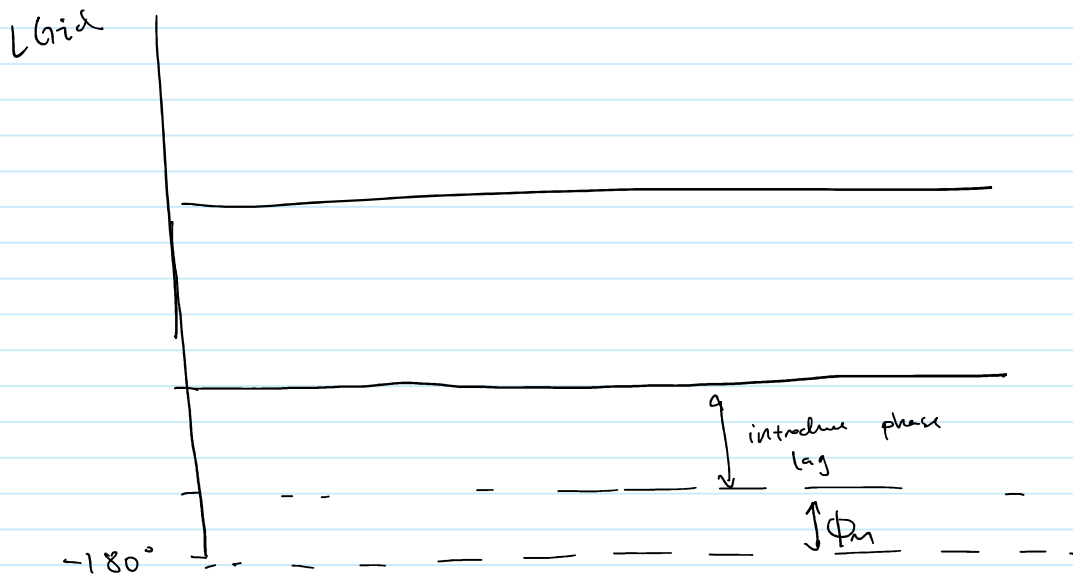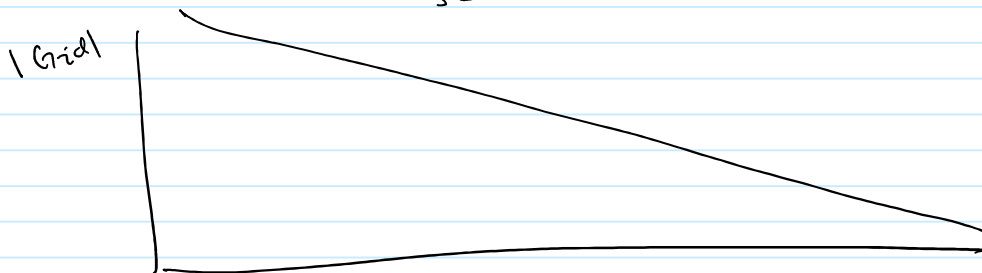- 2) find gain/phase of uncompensated, loop

approx: $G_{idrs} \approx \frac{V_{out}}{sL}$ at high frequency.



3) Use PI controller: $C(s) = (k_p + \frac{k_i}{s})$

$$L_i(s) = C(s) P(s) = C(s) G_{fd}(s)$$

$$\approx (k_p + \frac{k_i}{s}) (\frac{V_{out}}{sL})$$

$$\|L_i(s)\| \Big|_{\omega=\omega_{bw}} = 1$$

$$\angle L_i(s) \Big|_{\omega=\omega_{bw}} = -180^\circ + \phi_m$$

use this to get k_p and k_i

$$\| \frac{V_{out}}{sL} (k_p + \frac{k_i}{s}) \|$$

$$\| \frac{V_{out}}{j\omega_c L} (\frac{j\omega_c k_p + k_i}{j\omega_c}) \|$$

$$\| \frac{V_{out}}{L\omega_c^2} (j\omega_c k_p + k_i) \|$$

$$\frac{V_{out}}{L\omega_c^2} \sqrt{(k_p \omega_c)^2 + k_i^2} = 1$$

$$\frac{L\omega_c^2}{V_{out}} = \sqrt{(k_p \omega_c)^2 + k_i^2}$$

$$\boxed{\frac{L^2 \omega_c^4}{V_{out}^2} = (k_p \omega_c)^2 + k_i^2} \quad (1)$$

$$\angle L_i = \angle (k_p + \frac{k_i}{s}) \frac{V_{out}}{sL} = -180^\circ + \phi_m$$

$$\therefore \angle k_p + \frac{k_i}{s} + \angle \frac{V_{out}}{sL}$$

$$= \angle k_p + \frac{k_i}{j\omega_c} - \frac{\pi}{2}$$

$$\angle k_p + \frac{k_i j\omega_c}{- \omega_c^2} - \frac{\pi}{2}$$

$$\angle k_p - \frac{k_i j}{\omega_c} - \frac{\pi}{2}$$

$$\Rightarrow \arctan\left(\frac{-\frac{k_i}{\omega_c}}{k_p}\right) - \frac{\pi}{2}$$

$$-\arctan\left(\frac{k_i}{\omega_c k_p}\right) - 90^\circ = -180^\circ + \phi_m$$

$$\arctan(x^{-1}) = \frac{\pi}{2} - \arctan(x)$$

$$-(\frac{\pi}{2} - \arctan(\frac{\omega_c k_p}{k_i})) - 90^\circ = -180^\circ + \phi_m$$

$$\arctan\left(\frac{\omega_c k_p}{k_i}\right) - 180^\circ = -180^\circ + \phi_m$$

$$\boxed{\arctan\left(\frac{\omega_c k_p}{k_i}\right) = \phi_m} \quad (2)$$

note: $k_p + \frac{k_i}{s} \cdot G_n (1 + \omega_{PE}) = G_n$

Note: $k_p + \frac{k_i}{s} = G_{PI} (1 + \frac{\omega_{PI}}{s}) = G_c$

Use (1) and (2) to get G_{PI} , ω_{PI}

- Simulate current control.
 - Start file for control in Canvas
 - this is a transfer function model
 - also need to implement w/ switched model

• OV controller design:

input: v_{ref} output: i_{ref}

select $\omega_{c,v} \leq \frac{\omega_{ci}}{10}$

$$\| (k_p + \frac{k_i}{s}) G_{vi} \| = 1 \rightarrow \sqrt{k_p^2 + \frac{k_i^2}{\omega_c^2}} \left[\frac{D'R}{2} - \frac{R_L}{2\omega_c} \right] \quad (3)$$

$$\angle (k_p + \frac{k_i}{s}) G_{vi} = -180^\circ + \phi_m$$

$$\angle k_p + \frac{k_i}{s} + \angle G_{vi} \rightarrow \text{approx } 0 \text{ at low frequency.}$$

$$-\arctan\left(\frac{k_i}{\omega_c k_p}\right) = -180^\circ + \phi_m$$

$$\therefore \arctan\left(\frac{k_i}{\omega_c k_p}\right) - 180^\circ = -180^\circ + \phi_m$$

$$\boxed{\arctan\left(\frac{k_i}{\omega_c k_p}\right) = \phi_m} \quad (4)$$

• Use (3) (4) to get k_p / k_i for voltage controller.

3) Implementation (week 2)

- Set up RT BOX (see auxiliary video)

- scaling

- scale in PICS, send to MEM

- read in ADC pin

- scale to actual numerical value

Scale: 3.3V \rightarrow max ADC voltage

max value + safety

$$i_L: \frac{3.3V}{\dots} - \frac{3.3V}{\dots} \quad V_{out}: \frac{3.3V}{\dots} - \frac{3.3V}{\dots}$$

max value + safety

$$i_L: \frac{3.3V}{10+2A} = \frac{3.3V}{12A} \quad V_{out}: \frac{3.3V}{48+12V} = \frac{3.3V}{60V}$$

$$V_{in}: \frac{3.3V}{24+6V} = \frac{3.3V}{30V}$$

* using $\approx 25\%$ SF

* you can choose these based on your design last quarter

- implement PI in code:

$$z_{err} = i_{ref} - i$$

$$y_{err} = k_p z_{err}$$

→ can also use an array.

$$y_{int} = T_{\text{sample}}(0.5)(z_{err} + z_{err, \text{prev}})k_i + y_{int, \text{prev}}$$

↳ trapezoidal integration

- same idea for V

- saturation

$$\bullet \text{ Saturate } y_{int} \in [-0.95, 0.95]$$

$$\bullet \text{ Saturate } y_i \text{ on max/min duty}$$

$$\bullet \text{ Saturate } y_v \text{ on max/min current}$$

code structure: (Suggested)

Globals / const defines

- state variables for at least 1 previous cycle
- reference variables
- saturation values
- controller gains
- scalings

ADC interrupt:

// voltage control

$$V_{err} = V_{ref} - V_o$$

$$y_{v, err} = V_{err} \cdot k_{p, v}$$

$$y_{int, v} = (T_s \times 0.5)(V_{err} + V_{err, prev})k_{i, v} + y_{int, prev}$$

} PI calculation

if $y_{int, v}$ too high/low:
saturate.

update y_{prev} , $y_{int, prev}$, $V_{err, prev}$, etc.

$$y_v = y_{int} + y_{err}$$

update y_{prev} , $y_{v,ind prev}$, $v_{err prev}$, etc.

$$y_v = y_{int} + y_{pr}$$

if y_v too high/low // y_v is current ref!
saturate

// current control.

$$i_{ref} = y_v$$

repeat PI calculations but for IC loop

saturate y_i if needed // y_i = duty.

update PWM duty register (CMPA)