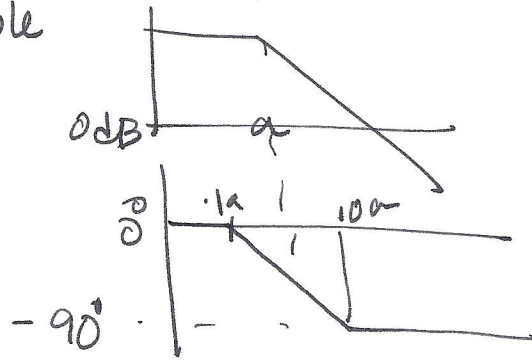



Problem 1

① LHP Pole




Minimum
phase sys
you can
know
phase plot
from gain

LHP Zero

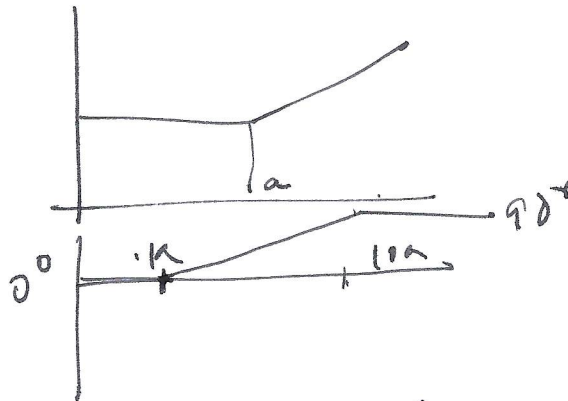

RHP Zero

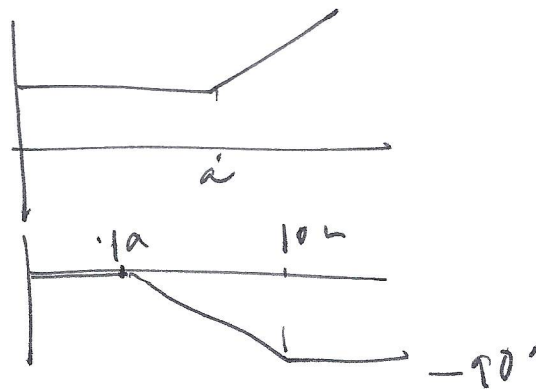

$$(s - a)$$

$$- \tan^{-1} \frac{j\omega}{a}$$

Same gain plot, diff phase plot.


for any minimum phase TF $G(s)$ → gain

$$\angle G(j\omega) = - \frac{\pi}{2} \cdot \frac{d \log_{10} |G(j\omega)|}{d \log_{10} \omega} \text{ radians}$$

one-to-one mapping for minimum phase sys

Problem 1

(2)

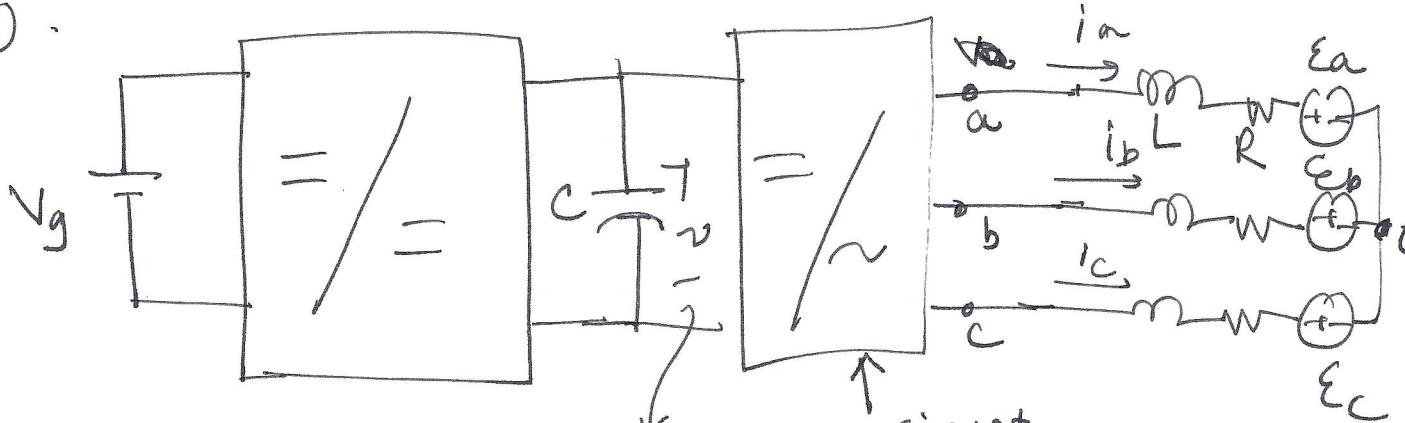

We know,

$$v(t) = C_{vd} d(t) + C_{vg} v_g(t)$$

$$\therefore v_{ao}(t) = v(t) m \sin \omega t$$

$$\text{Let, } v_g(t) = V_g + \underbrace{v_g^0 \sin(\omega_d t)}_{\text{disturbance oscillation}}$$

$$\therefore v_{ao}(t) = [C_{vd} d(t) + C_{vg} v_g(t)] m \sin \omega t$$

we don't want
to study this now ~ 0

$$v_{ao}(t) = C_{vg} \cdot (V_g + v_g^0 \sin(\omega_d t)) m \sin \omega t$$

$$= C_{vg} \cdot V_g \cdot m \sin \omega t + C_{vg} \cdot v_g^0 \cdot m \cdot \sin \omega t \sin(\omega_d t)$$

$$= \underbrace{C_{vg} V_g m \sin \omega t}_{\approx 1} + \frac{C_{vg} v_g^0 m}{2} [\cos(\omega - \omega_d)t - \cos(\omega + \omega_d)t]$$

$\therefore v_{ao}(t)$

has a component we all know,

$$V_{gm} \sin \omega t$$

&

now has another disturbance component,

$$\frac{G_{vg} V_g^{\circ} m}{2} [\cos(\omega - \omega_d)t - \cos(\omega + \omega_d)t]$$

we know,


$$i = \frac{v_{ao}(t) - e_a(t)}{sL + R}$$

If the current controller loop gain,

$$L_i = \left(k_{p,m} + \frac{k_{i,m}}{s} \right) \frac{1}{sL + R}$$

has high gain at $(\omega - \omega_d)$ & $(\omega + \omega_d)$ frequency, we can compensate disturbances at $v_g(t)$.

Problem (3).

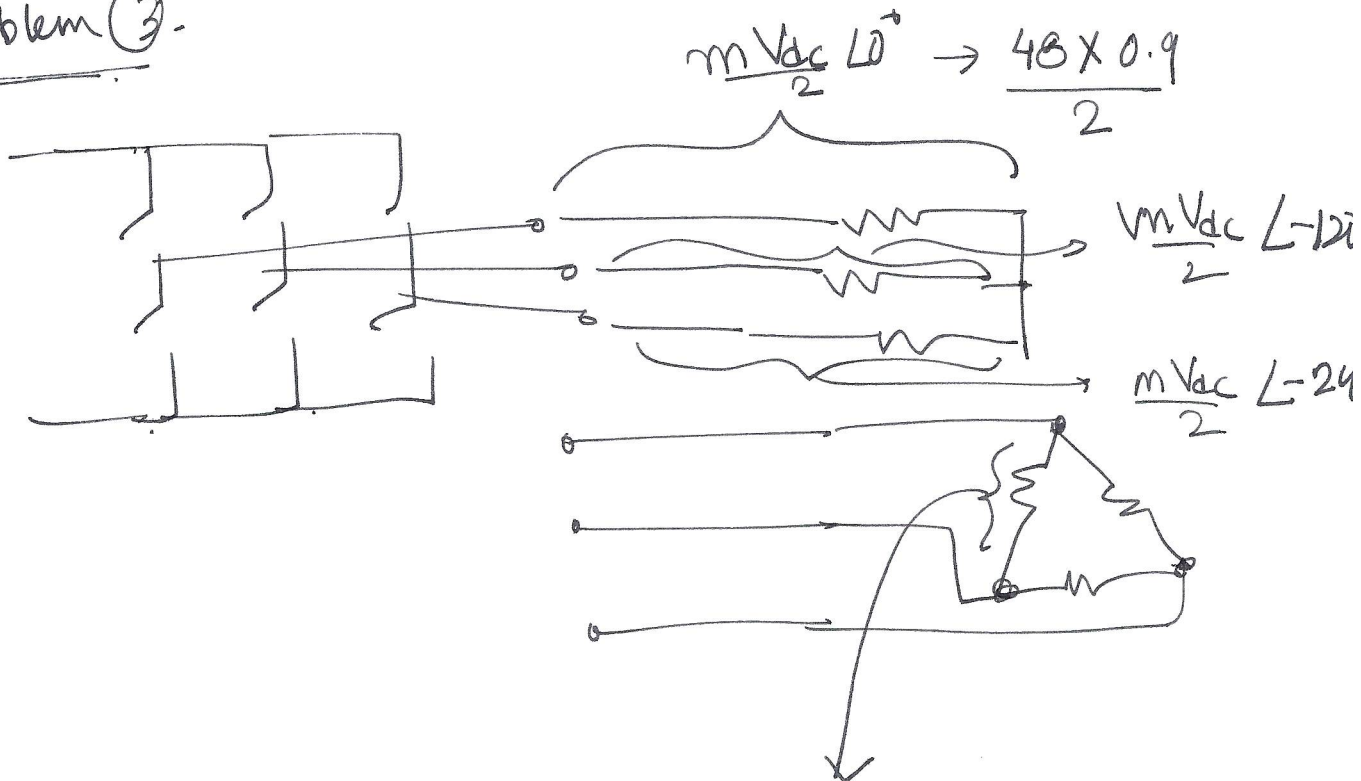

$$\frac{mV_{dc}}{2} \angle 0^\circ - \frac{mV_{dc}}{2} \angle -120^\circ$$

$$= \frac{\sqrt{3} mV_{dc}}{2} \angle 30^\circ$$

Ann
$$Starr = \frac{48 \times 0.9}{2}$$

Delta
$$= \frac{48 \times 0.9 \sqrt{3}}{2}$$

$$C \frac{dv}{dt} \left(1 + \frac{r_{esr}}{R} \right) = i - \frac{v}{R}$$

$$C \frac{dv}{dt} = i \cdot \frac{1}{1 + \frac{r_{esr}}{R}} - \frac{v}{R} \cdot \frac{1}{1 + \frac{r_{esr}}{R}}$$

$$L \frac{di}{dt} = V_{in} - i r_L - v - r_{esr} \cdot C \frac{dv}{dt}$$

$$= V_{in} - i r_L - v - r_{esr} \cdot \left[i \cdot \frac{1}{1 + \frac{r_{esr}}{R}} - \frac{v}{R} \cdot \frac{1}{1 + \frac{r_{esr}}{R}} \right]$$

$$\dot{x} = Ax + Bu$$

$$\begin{bmatrix} \frac{di}{dt} \\ \frac{dv}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{r_L}{L} & -\frac{r_{esr}}{L \left(1 + \frac{r_{esr}}{R} \right)} \\ \frac{1}{C} \cdot \frac{1}{1 + \frac{r_{esr}}{R}} & -\frac{1}{RC} \cdot \frac{1}{1 + \frac{r_{esr}}{R}} \end{bmatrix} \begin{bmatrix} i \\ v \end{bmatrix}$$

$$+ \begin{bmatrix} 0 \\ 0 \end{bmatrix} \frac{1}{L} \begin{bmatrix} 1 \\ 0 \end{bmatrix} \begin{bmatrix} V_{in} \end{bmatrix}$$

$$\left(\frac{sK_{pv} + K_{ir}}{s} \right) \cdot \left(\frac{1}{1 + s\tau_i} \right) \frac{1}{sC}$$


$$s = j\omega$$

$$L_v(j\omega) = \left(\frac{K_{ir} - j\omega K_{pv}}{j\omega} \right) \left(\frac{1}{1 + j\omega\tau_i} \right) \frac{1}{j\omega C}$$

① at $\omega = \omega_g$ (gain cross over freq).

$$|L_v(j\omega)|_{\omega=\omega_g} = 1$$

$$\left| \left(\frac{K_{ir} - j\omega_g K_{pv}}{j\omega_g} \right) \left(\frac{1}{1 + j\omega_g\tau_i} \right) \frac{1}{j\omega_g C} \right| = 1$$

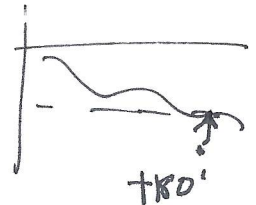

$$\boxed{\frac{\sqrt{K_{ir}^2 + (\omega_g K_{pv})^2}}{\omega_g} \cdot \frac{1}{\sqrt{1 + (\omega_g\tau_i)^2}} \cdot \frac{1}{\omega_g C} = 1} \quad \text{①}$$

② at $\omega = \omega_g$

$$\angle L_v(j\omega) \big|_{\omega=\omega_g} + 180^\circ = PM^\circ$$

$$+ \tan^{-1} \frac{\omega K_{pv}}{K_{ir}} \leftarrow \frac{sK_{pv} + K_{ir}}{s}$$

\swarrow
 -90°

$$\frac{1}{1 + s\tau_i} \quad \frac{1}{sC}$$

\swarrow
 $- \tan^{-1} \omega \tau_i$

\swarrow
 -90°

$$\tan^{-1} \frac{\omega_g k_{pv}}{k_{iv}} - 90^\circ - \tan^{-1} \omega T_i - 90^\circ + 180^\circ = \angle P M^\circ$$

2 eq.

2 unknown - k_{pv} , k_{iv}

Use fsolve/ in MATLAB / python.
solve.

Controller design. Alternative solution.

A

$$\begin{aligned}\frac{L_v}{1+L_v} &= \frac{k_{pv}s + k_{iv}}{CT_i s^3 + Cs^2 + k_{pv}s + k_{iv}} \\ &= \frac{1 + \frac{k_{pv}}{k_{iv}}s}{1 + \frac{k_{pv}}{k_{iv}}s + \frac{C}{k_{iv}}s^2 + \frac{CT_i}{k_{iv}}s^3} \\ &\therefore = \frac{1 + a_1s}{1 + a_1s + a_2s^2 + a_3s^3}\end{aligned}$$

$$a_1 = \frac{k_{pv}}{k_{iv}} \quad a_2 = \frac{C}{k_{iv}} \quad a_3 = \frac{CT_i}{k_{iv}}$$

Look up Maksimovic, Erickson's book

$$\begin{aligned}1 + \tau_1 s + \tau_1 \tau_2 s^2 + \tau_1 \tau_2 \tau_3 s^3 \\ = 1 + (\tau_1 + \tau_2 + \tau_3)s + (\tau_1 \tau_2 + \tau_2 \tau_3 + \tau_1 \tau_3)s^2 + \tau_1 \tau_2 \tau_3 s^3\end{aligned}$$

if and only if $|\tau_1| \gg |\tau_2| \gg |\tau_3|$

For us,

B

$$a_1 \approx \tau_1$$

$$a_2 \approx \tau_1 \tau_2$$

$$a_3 \approx \tau_1 \tau_2 \tau_3$$

$$\tau_1 = \frac{k_{pv}}{k_{iv}}$$

$$\tau_2 = \frac{a_2}{\tau_1} = \frac{C/k_{iv}}{k_{pv}/k_{iv}} = \frac{C}{k_{pv}}$$

$$\tau_3 = \frac{a_3}{\tau_1 \tau_2} = \tau_p$$

If we assume, $\tau_1 \gg \tau_2 \gg \tau_3$

$$\frac{k_{pv}}{k_{iv}} \gg \frac{C}{k_{pv}} \gg \tau_i$$

So,

$$\frac{C}{k_{pv}} \gg \tau_i$$

$$\therefore \boxed{k_{pv} \ll \frac{C}{\tau_i}} \rightarrow$$

$$\boxed{M_1 \gg 1}$$

$$k_{pv} = \frac{C}{M_1 \tau_i}$$

$$\frac{k_{pv}}{k_{iv}} \gg \frac{C}{k_{pv}}$$

$$\therefore \frac{C}{k_{pv}} \gg \frac{C}{k_{pv}}$$

\therefore

$$k_{iv} \ll \frac{k_{pv}^2}{C}$$

$$\boxed{k_{iv} = \frac{k_{pv}^2}{M_2 C}} \quad \text{--- } M_2$$

$M_1 = M_2 = 5$ choose

$$k_{pv} = \frac{C}{5 \tau_i}$$

$$; k_{iv} = \frac{k_{pv}^2}{5 C} = \frac{C}{5^3 \tau_i^2}$$

So then,

C

$$\frac{L_v}{1+L_v} = \frac{1 + a_1 s}{(1 + \cancel{a_1} s) \left(1 + \frac{a_2 s}{a_1}\right) \left(1 + \frac{a_3 s}{a_2}\right)}$$
$$= \frac{1}{1 + \left(\frac{a_2}{a_1} + \frac{a_3}{a_2}\right) s + \frac{a_3}{a_1} s^2}$$

↓
should remind you of

$$= \frac{1}{1 + \frac{2\zeta}{\omega_0} s + \frac{1}{\omega_0^2} s^2}$$

$$\omega_0 = \sqrt{\frac{a_1}{a_3}} = \sqrt{\frac{k_{pv}}{c \tau_i}}$$

2. since, we know, $k_{pv} = \frac{c}{M_1 \tau_i}$

$$\therefore \omega_0 = \frac{1}{\tau_i} \sqrt{\frac{1}{M_1}}$$

2 Damping = $\rho = \frac{\omega_0}{2} \left(\frac{a_2}{a_1} + \frac{a_3}{a_2}\right)$

$$\rho = \frac{1}{2} \sqrt{\frac{k_{pv}}{c \tau_i}} \left(\frac{c}{k_{pv}} + \tau_i\right) \Rightarrow$$


$$p^2 = \frac{k_{pv}}{4c\tau_i} \left(\frac{c^2}{k_{pv}^2} + \tau_i^2 + \frac{2c\tau_i}{k_{pv}} \right) \quad \Downarrow$$

$$= \frac{c}{4\tau_i k_{pv}} + \frac{\tau_i k_{pv}}{4c} + \frac{1}{2}$$

$$= \frac{M_1}{4} + \frac{1}{4M_1} + \frac{1}{2}$$

$$\text{or, } p = \sqrt{\frac{1}{4} \left(M_1 + \frac{1}{M_1} \right) + \frac{1}{2}}$$

(5)

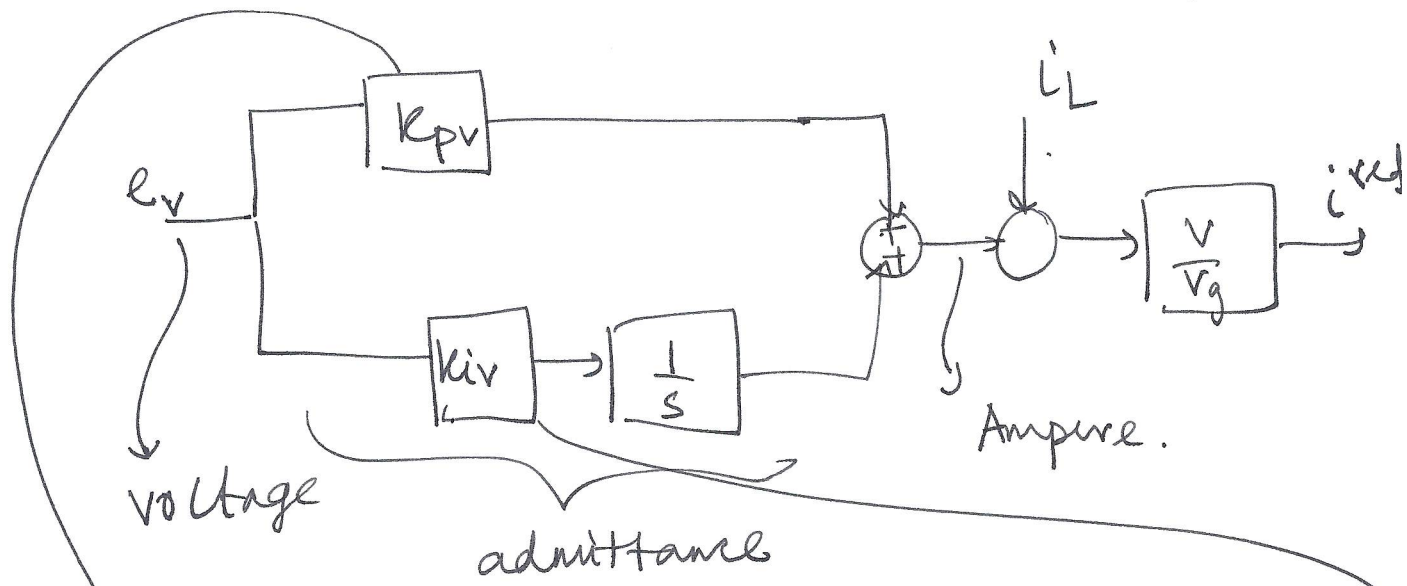

$$K_{pv} = \text{ohm}^{-1} \text{ or mho or siemens } (\Omega^{-1} / \text{V} / \text{s})$$

$$K_{iv} = \text{Admittance} = \frac{K_{iv}}{s}$$


$$\text{Impedance} = \frac{s}{K_{iv}} \equiv s \cdot (L)$$

~~no~~



$$\therefore \frac{1}{K_{iv}} \equiv L$$

$$K_{iv} = L^{-1} \text{ (Henry)}^{-1}$$


LTF

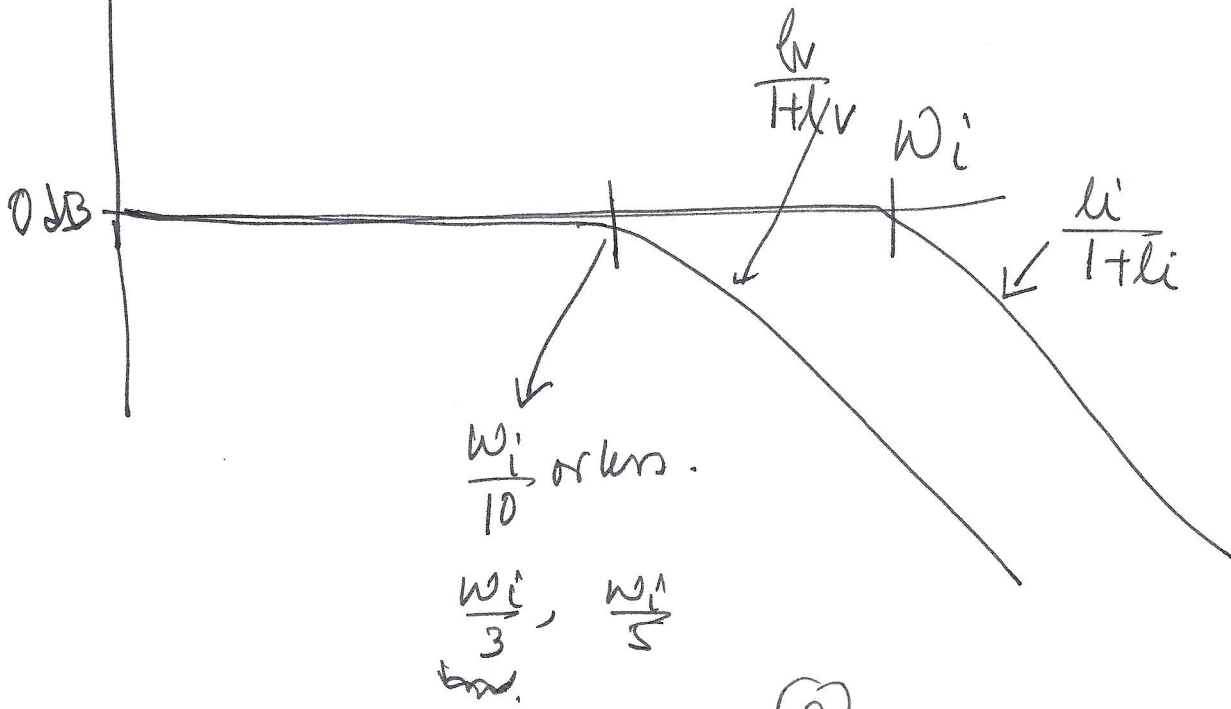

2 (b)

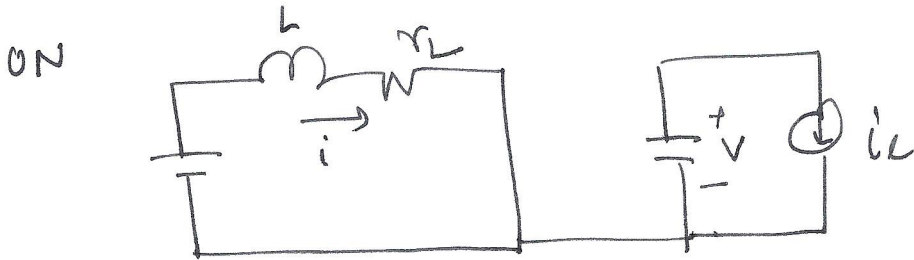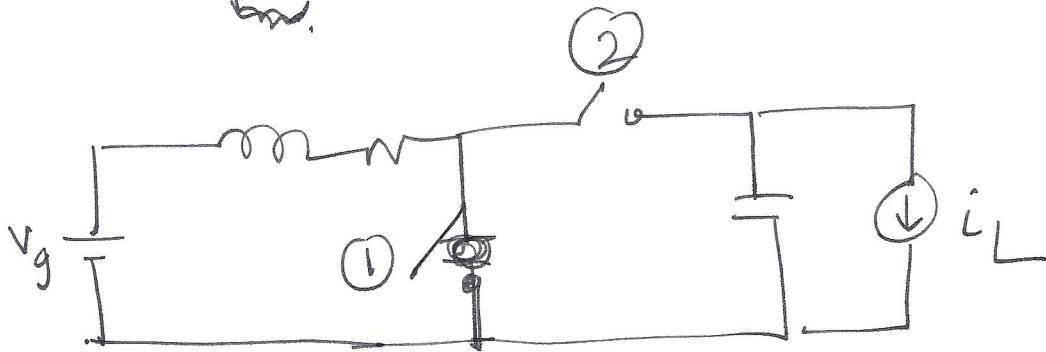
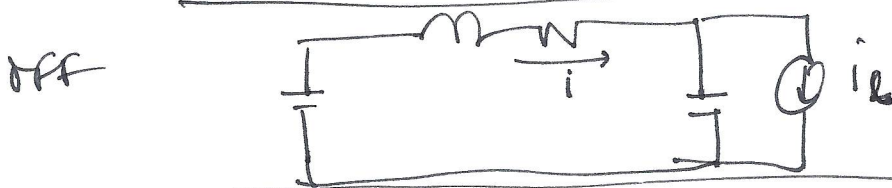
$$\left. \begin{aligned} V_{in} &= L \frac{di}{dt} + i R_L \\ C \frac{dV}{dt} &= -i_L \end{aligned} \right\} (1)$$



$$\left. \begin{aligned} V_{in} &= L \frac{di}{dt} + i R_L + V \\ i &= C \frac{dV}{dt} + i_L \end{aligned} \right\} (2)$$

(7)

At steady state,

$$\left(L \frac{di}{dt} \right)_{(1)} \cdot D + \left(L \frac{di}{dt} \right)_{(2)} D' = 0$$

$$(V_{in} - i_L r_L) D + (V_{in} - i_L r_L - V) D' = 0$$


$$\Rightarrow \boxed{V_{in} - i_L r_L = V \cdot D'} \quad (3)$$

$$\left(C \frac{dv}{dt} \right)_{(1)} D + \left(C \frac{dv}{dt} \right)_{(2)} D' = 0$$

$$(-i_L) D + (i - i_L) D' = 0$$

$$i D' = i_L$$

$$\boxed{i = \frac{i_L}{D'}} \quad (4)$$

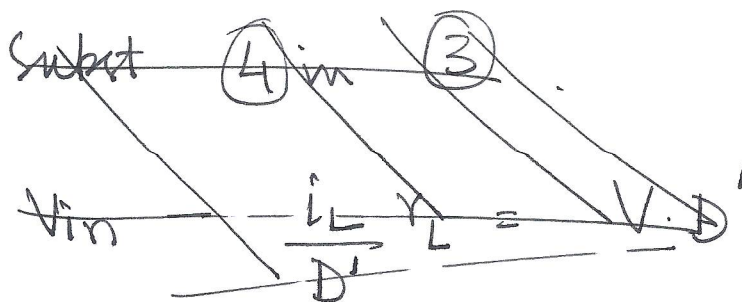

Subst (3) in (4),

$$i = \frac{i_L}{\frac{V_{in} - i_L r_L}{V}} = \underbrace{i \cdot (V_{in} - i_L r_L)}_{\text{quadrant}} = V \cdot i_L$$

$$\boxed{i^2 r_L - i \cdot V_{in} + V \cdot i_L = 0} \quad \rightarrow 2\pi$$


solve

24V

Assume 48V

Use (4) to obtain D'

8

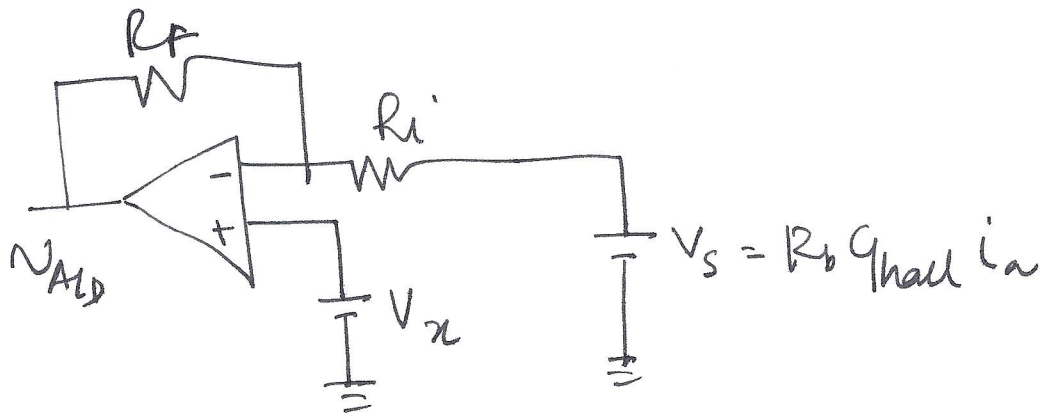

$$V_{AD} = V_x \left(1 + \frac{R_f}{R_i} \right) - \frac{R_f}{R_i} \cdot R_b \cdot Q_{hall} \cdot i_a$$

@ $i_a = 0$, $V_{AD} = V_{FS}/2$

$$V_x \cdot \left(1 + \frac{R_f}{R_i} \right) = \frac{V_{FS}}{2} \quad \text{--- ①}$$

$V_{AD} = \epsilon$ if $i_a = i_{pk}$

$$\epsilon = V_x \left(1 + \frac{R_f}{R_i} \right) - \frac{R_f}{R_i} \cdot R_b \cdot Q_{hall} \cdot i_{pk}$$

from ① $= V_{FS}/2$

$$\epsilon = \frac{V_{FS}}{2} - \left(\frac{R_f}{R_i} \right) \cdot R_b \cdot Q_{hall} \cdot i_{pk}$$

\downarrow \downarrow \downarrow \downarrow
 $3/2$ 75 $\frac{1}{1000}$ 40
 $R_f = \frac{R_f}{R_i} \cdot 100 \text{ k}\Omega$ $?$ $\rightarrow V_x = \frac{V_{FS}/2}{1 + R_f/R_i}$

or,

10

~~i_a~~

$$i_a \approx - m \frac{R_F}{R_i} R_b G_{\text{null}} \frac{2^{12}}{3} i_a +$$

$$= 1 \underbrace{m v_n \left(1 + \frac{R_F}{R_i}\right) \frac{2^{12}}{3} + b}_{=0}$$

$$\therefore b = - m v_n \left(1 + \frac{R_F}{R_i}\right) \frac{2^{12}}{3}$$

$$2, m = - \frac{1}{\frac{R_F}{R_i} R_b G_{\text{null}} \frac{2^{12}}{3}} = - \frac{V_{FS}}{\frac{R_F}{R_i} R_b G_{\text{null}} 2^{12}}$$

$$b = + \left(+ \frac{1}{\frac{R_F}{R_i} R_b G_{\text{null}} \frac{2^{12}}{3}} \right) \cdot v_n \left(1 + \frac{R_F}{R_i}\right) \frac{2^{12}}{3}$$

$$= \frac{v_n \left(1 + \frac{R_F}{R_i}\right)}{\frac{R_F}{R_i} R_b G_{\text{null}}}$$

(11).

$$P_e = \frac{-3}{2} \lambda p_k \omega_c i_q$$

$$\tau_e = -\frac{3}{2} \lambda p_k i_q \frac{P}{2}$$

constant constant

$$J \dot{\omega}_m + B \omega_m = \tau_e - \tau_e^0$$

$$\omega_m = \frac{\tau_e - B \omega_m}{J}$$

constant

$$\begin{cases} J_1 \dot{\omega} + B \omega = \tau \\ J_2 \dot{\omega} + B \omega = \tau \end{cases}$$

~~$J \dot{\omega} = \text{constant}$~~

$$(sJ + B) \omega(s) = \tau(s)$$

$$\omega(s) = \frac{\tau(s)}{sJ + B}$$

for step change in i_q , we get step change in torque $\therefore \tau(s) = \frac{\tau_e}{s}$ $\therefore \omega(s) = \frac{\tau_e}{s(sJ + B)}$

Final value theorem

given, $y(s)$

$$\lim_{t \rightarrow \infty} y(t) = \lim_{s \rightarrow 0} s \cdot y(s)$$

$$W(\infty) = \lim_{t \rightarrow \infty} W(t) = \lim_{s \rightarrow 0} s \cdot W(s)$$

step input torque $= \frac{1}{s}$

$$\frac{T_e}{s} \cdot \frac{1}{sJ+B} = \frac{T_e}{B}$$

proves that irrespective of J ,
the final speed is same.

Initial rate of change.

$$\frac{dw}{dt} \rightarrow s W(s)$$

Initial value theorem.

given $y(s)$

$$\lim_{t \rightarrow 0} \frac{dy(t)}{dt} = \lim_{s \rightarrow \infty} s y(s)$$

$$W(s) = \frac{T(s)}{sJ+B}$$

step change in torque

$$W(s) = \frac{T_e}{s(sJ+B)}$$
$$\therefore \frac{dw}{dt} \rightarrow s W(s) = \frac{T_e}{sJ+B}$$

$$\left. \frac{dw}{dt} \right|_{t=0} = \lim_{t \rightarrow 0} \frac{dW(t)}{dt} = \lim_{s \rightarrow \infty} s \cdot \frac{T_e}{sJ+B} = \lim_{s \rightarrow \infty} \frac{T_e}{J+B/s} = \frac{T_e}{J}$$

\therefore initial slope = $\frac{T_e}{J}$ higher J , lower slope

(13)

Prob 4


(a)

Initial value :-

$$i_L = 0$$



(b)

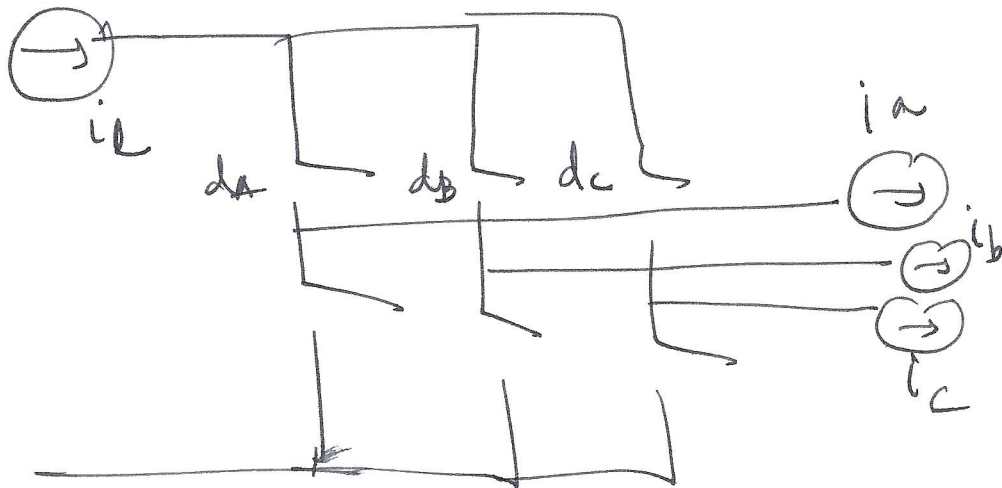

when $d_A = 1$, $i_L = i_a$ (top switch ON)
 $d_A = 0$, $i_L = 0$ (bot switch ON)
 $d_B = 1$, $i_L = i_b$
 $d_B = 0$, $i_L = 0$
 $d_C = 1$, $i_L = i_c$
 $d_C = 0$, $i_L = 0$


Superposition

$$i_L = d_A i_a + d_B i_b + d_C i_c$$


Same a sensor !!

(K)

4c

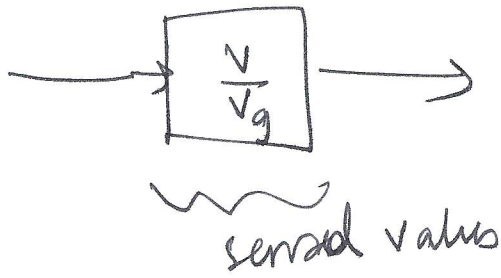

v/s

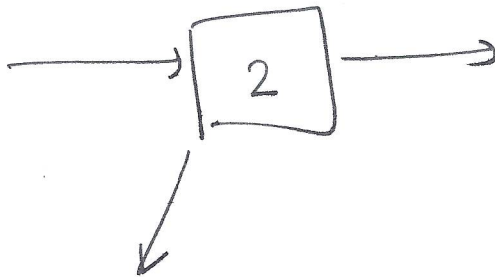

does not have dynamics of v, v_g
so, "quieter" — less noisy.