

# EE 458/533 – Power Electronics Controls, Winter 2022

## Homework 5

**Due Date:** Friday March 3rd 2022, 4:30pm PT

**Problem 1:** Consider a boost converter where the winding and MOSFET on resistances are lumped into  $R_L$ . The diagrams in Figs. 1(a) represents the version used in lab and 1(b) represent the improved control structure that implements feed-forward. Below, you will model the improved controller and then compare it to the lab implementation. Assume all sensing path gains are equal to 1 and that a PI controller is used.


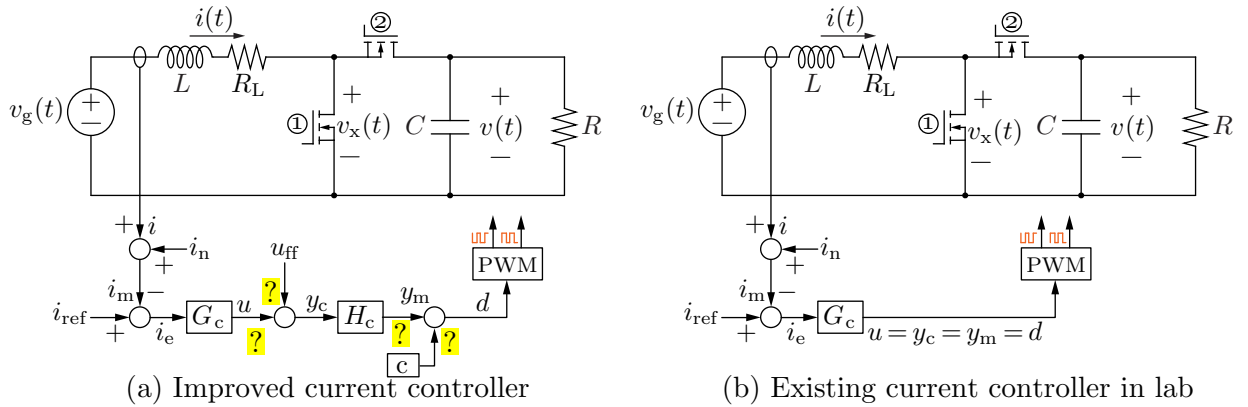



Figure 1: Boost converter with current control.

Perform the following:

- Derive the voltage  $\langle v_x(t) \rangle$  (average value of  $v_x(t)$  over one switching period) in terms of duty,  $d$  and output voltage,  $\langle v(t) \rangle$
- Derive the KVL in the input loop to obtain a relationship between  $v_g(t) (= \langle v_g(t) \rangle)$ ,  $L$ ,  $R_L$ ,  $\langle v_x(t) \rangle$  and  $\langle i(t) \rangle$ .
- Assume the controller,  $G_c$  produces an output,  $d$ , verify that Fig. 2 (a) shows the correct implementation of your KVL derived in the preceding question.
- We want to implement feed-forward to simplify our plant transfer function to be only  $1/(sL + R_L)$  so that the controller design becomes simplified as in Fig. 2 (c). To achieve this, sketch or provide a numerical relationship between the controller output,  $u$ , and the actual duty ratio,  $d$ , that goes into the PWM block. (Note under all circumstances,  $0 < d < 1$ ). Compare the relationship you have derived with Fig. 1 (a) to identify  $H_c$ ,  $c$ ,  $u_{ff}$  and the signs of the sum blocks shown with ?.
- Design your controller,  $G_c$  by plant-inversion formulae to achieve a bandwidth of 1/10-th of your switching frequency.

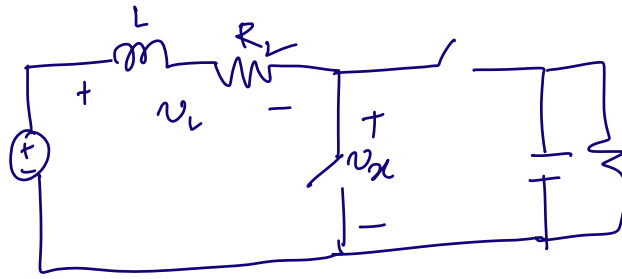

$$0 < t < T_{ON}$$

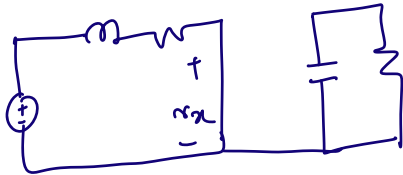


$$v_x = 0$$

$$\therefore \langle v_x \rangle = 0 \cdot d + \langle v \rangle \cdot d'$$

$$\langle v_x \rangle = \langle v \rangle \cdot d'$$

$$T_{ON} < t < T_{SW}$$

$T_{OFF}$

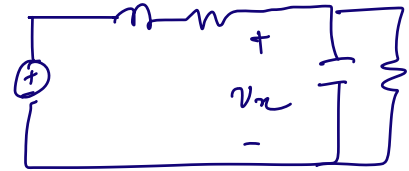


$$v_x = V$$


$$\langle V_{in} \rangle = L \frac{d\langle i \rangle}{dt} + \langle i \rangle R_L + \langle v_x \rangle$$

$$\text{or, } \langle V_{in} \rangle - \langle v \rangle d' = L \frac{d\langle i \rangle}{dt} + \langle i \rangle R_L$$
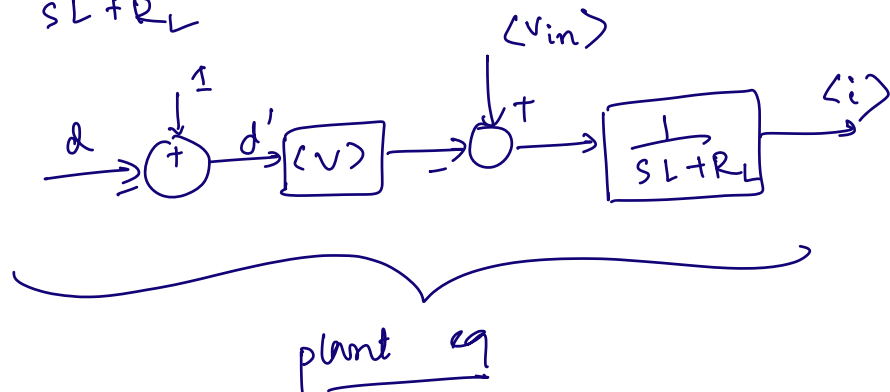
$$\text{or, } \frac{\langle V_{in} \rangle - \langle v \rangle d'}{sL + R_L} = \langle i \rangle$$



Method 1 to derive FF

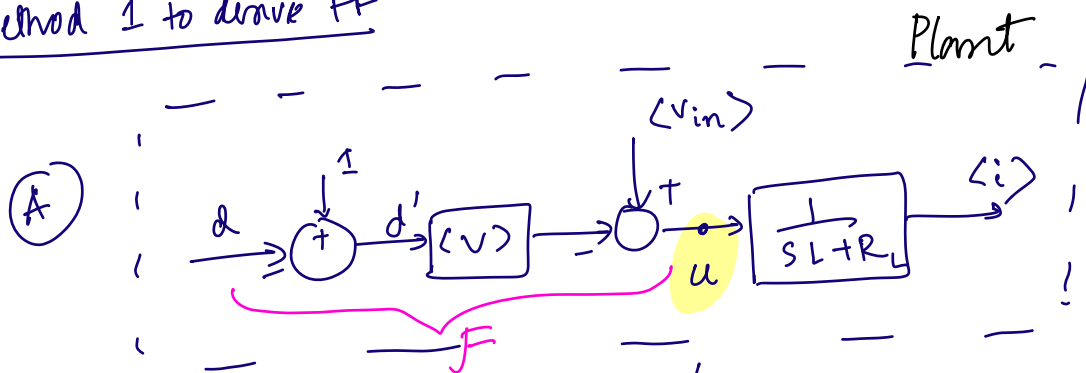


$$u = \langle v_{in} \rangle - \langle v \rangle d'$$

$$= \langle v_{in} \rangle - \langle v \rangle (1-d)$$


$$\therefore (1-d)\langle v \rangle = \langle v_{in} \rangle - u$$


$$\Rightarrow 1-d = \frac{\langle v_{in} \rangle - u}{\langle v \rangle}$$
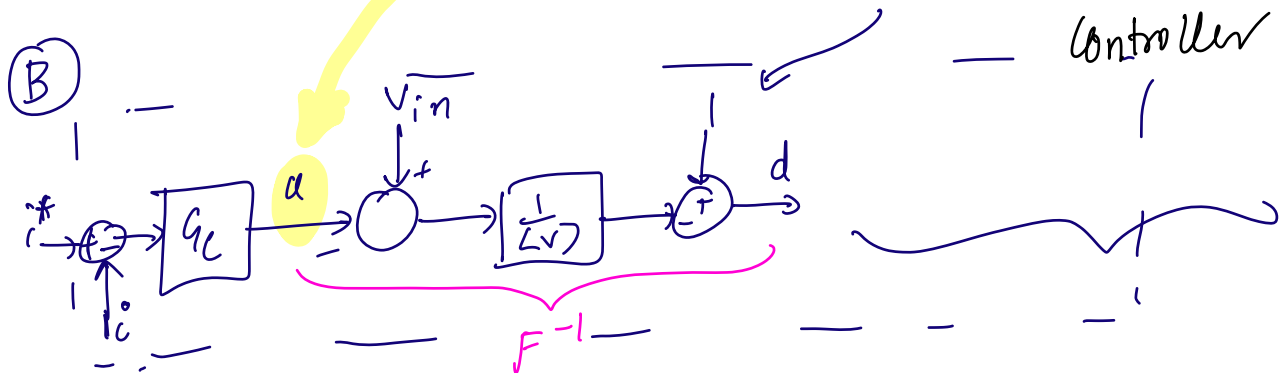
$$\therefore d = 1 - \frac{\langle v_{in} \rangle - u}{\langle v \rangle}$$



Combining (A) & (B),

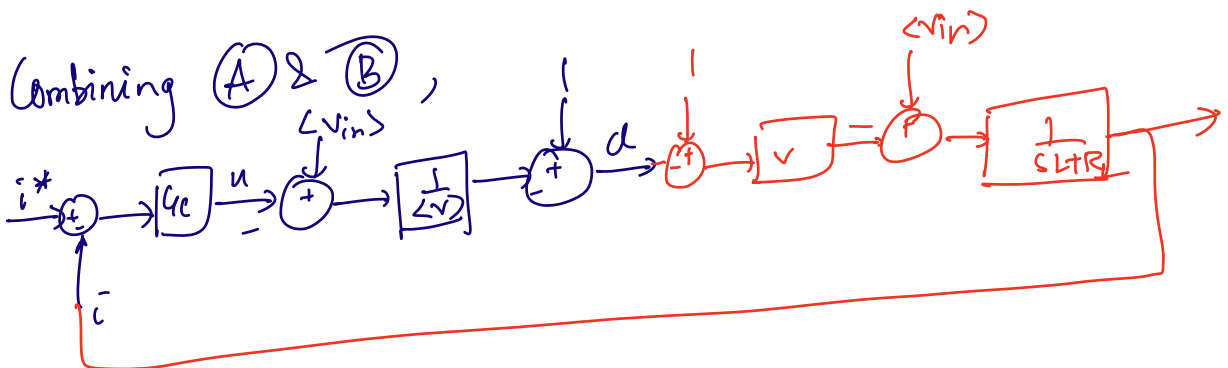

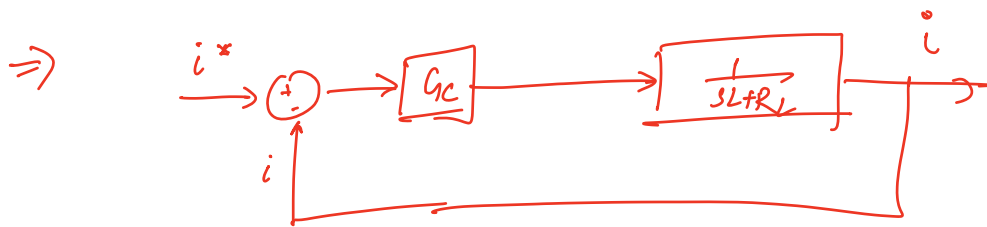

$$H = \frac{1}{(sL+R)}$$

$$u_{ff} = v_{in}$$

$$C = 1$$

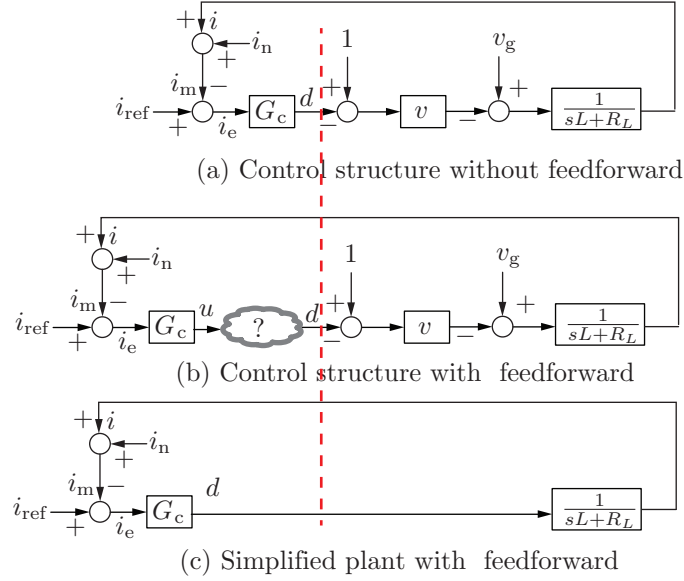


Figure 2: Control simplification with feed-forward. On the right side of the red-dashed line is your plant and on the left is your controller.


**Problem 2:** Simulate the improved implementation in Problem 1 where  $V_g = 24 \text{ V}$ ,  $f_s = 10 \text{ kHz}$ ,  $L = 1.3 \text{ mH}$ ,  $R_L = 60 \text{ m}\Omega$ ,  $C = 250 \text{ }\mu\text{F}$ , and  $R = 10 \text{ }\Omega$ . Use the white noise block<sup>1</sup> to simulate the current sensor noise. Initialize your simulation with a reference of  $i_{\text{ref}} = 3 \text{ A}$  such that the states are all in steady-state and the error,  $i_e$ , is zero. Perform the following:


- (a) Create a switched simulation for improved implementation in Fig. 1 with and without feedforward where the following events below occur. Use your control gains from 2(a). Overlay the  $i(t)$  waveforms for with and without feedforward (for without feedforward, use the controller you developed in lab) on the same plot to facilitate comparison. Comment on how they differ.
  - At  $t = 5 \text{ ms}$ ,  $i_{\text{ref}}$  changes from  $3 \text{ A} \rightarrow 5 \text{ A}$ .
  - At  $t = 10 \text{ ms}$ ,  $v_g$  changes from  $24 \text{ V} \rightarrow 28 \text{ V}$ .
  - At  $t = 15 \text{ ms}$ ,  $R$  changes from  $10 \text{ }\Omega \rightarrow 15 \text{ }\Omega$ .

<sup>1</sup>Configure the white noise block with zero mean, 50 mA standard deviation, and sample time  $T_s$ .

**Problem 3:** We will build on the results from Homework 4, Using Faraday's Law, give the expressions for the induced back EMF voltages,  $e_a$ ,  $e_b$ ,  $e_c$ , within the a, b, and c phase windings, respectively. In addition, draw the equivalent circuits looking into the a, b, and c windings where the back EMFs,  $e_a$ ,  $e_b$ ,  $e_c$ , are clearly labeled along with the speed-dependent voltages  $\mathcal{E}_a$ ,  $\mathcal{E}_b$ ,  $\mathcal{E}_c$  and inductive voltage drops. Be careful with all circuit element polarities.

- Class Lecture

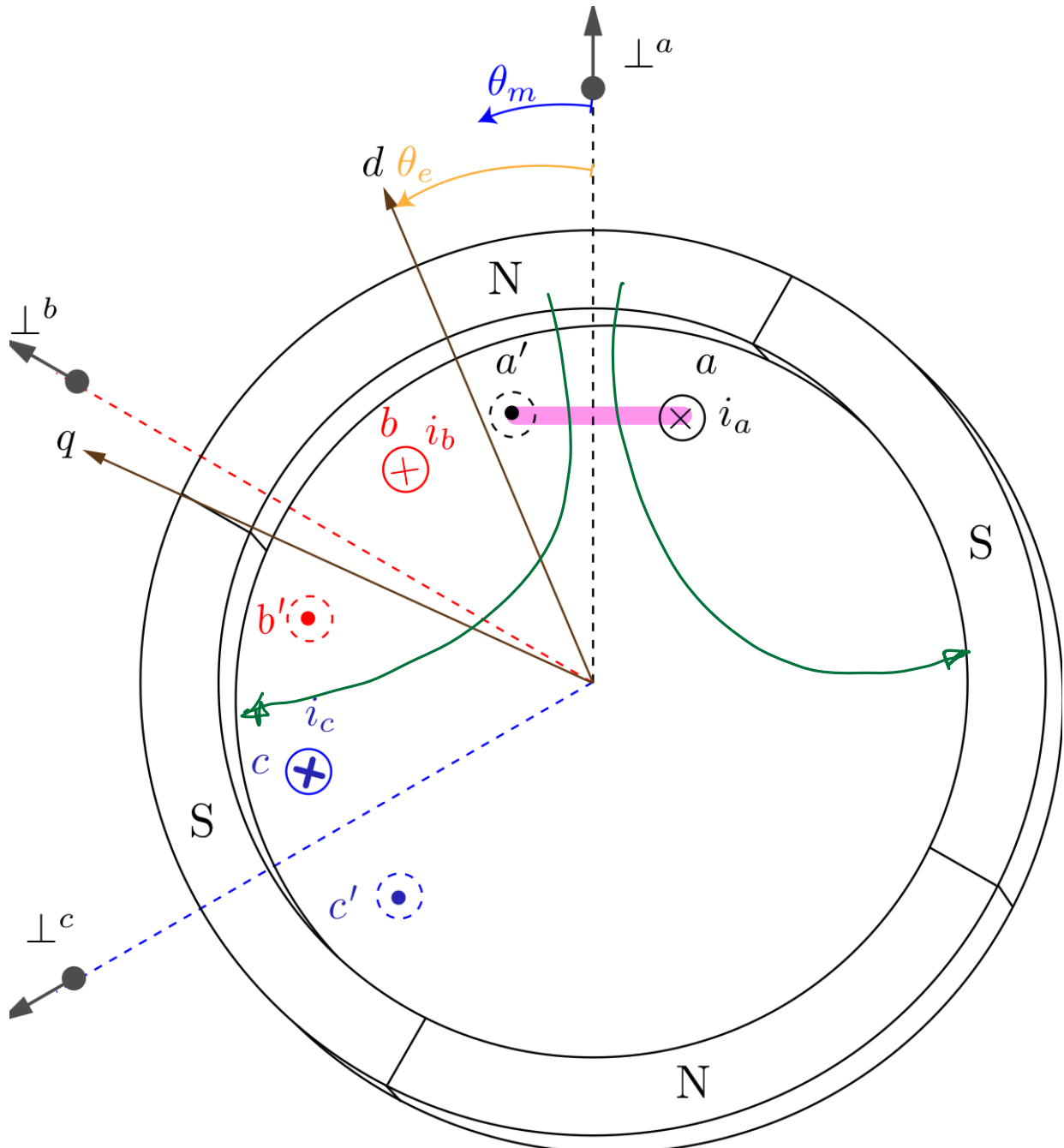

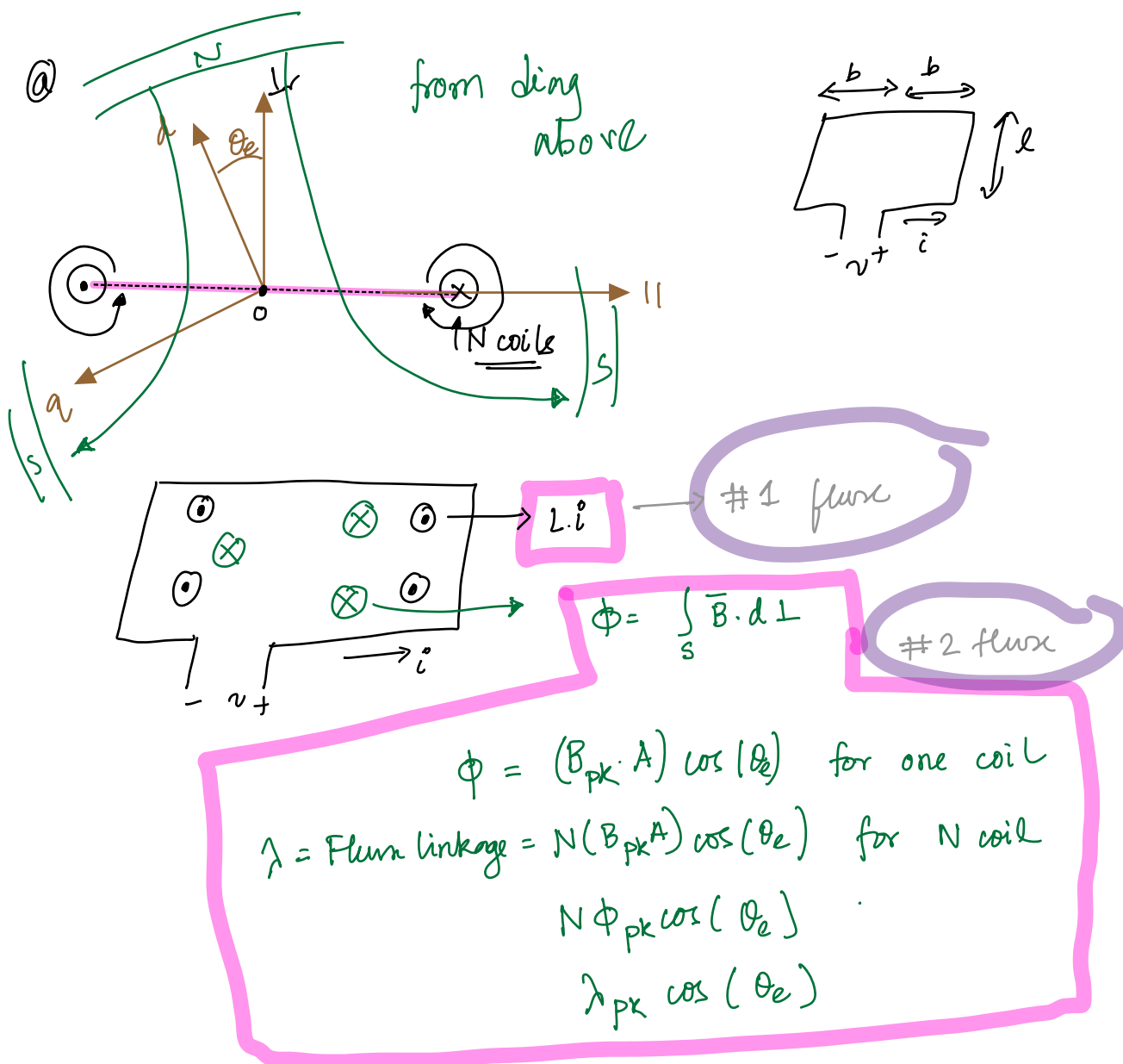

\* Remember, sign convention  
 ccw for arrow coming out of paper.

So, net flux linkage coming out of paper is a function of angle  $\theta_e$

$$\therefore \lambda(\theta_e) = -N \cdot \phi_{pk} \cos(\theta_e) + Li$$

(sign convention to accommodate the  $\odot$  rotation)



Induced emf :-

$$- \frac{d\lambda(\theta_e)}{dt} = - \frac{d}{dt} \left[ -\lambda_{pk} \cos\left(\theta_m \frac{P}{2}\right) + Li \right]$$


$$= \lambda_{pk} \cdot \frac{d}{dt} \left\{ \cos\left(\theta_m \frac{P}{2}\right) \right\} - L \frac{di}{dt}$$

$$= -\lambda_{pk} \sin\left(\theta_m \frac{P}{2}\right) \frac{P}{2} \frac{d(\theta_m)}{dt} - L \frac{di}{dt}$$

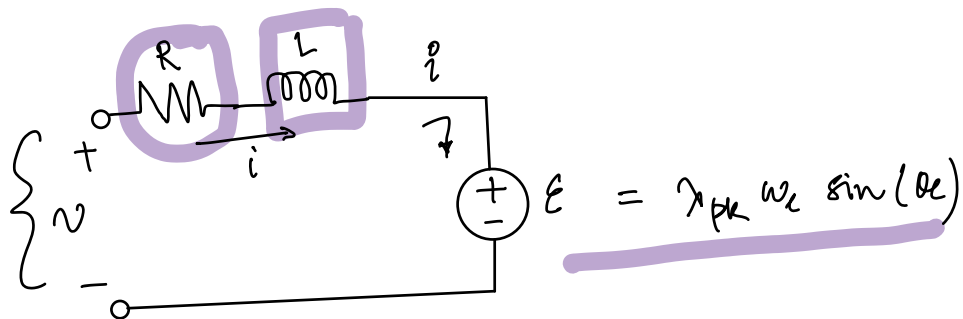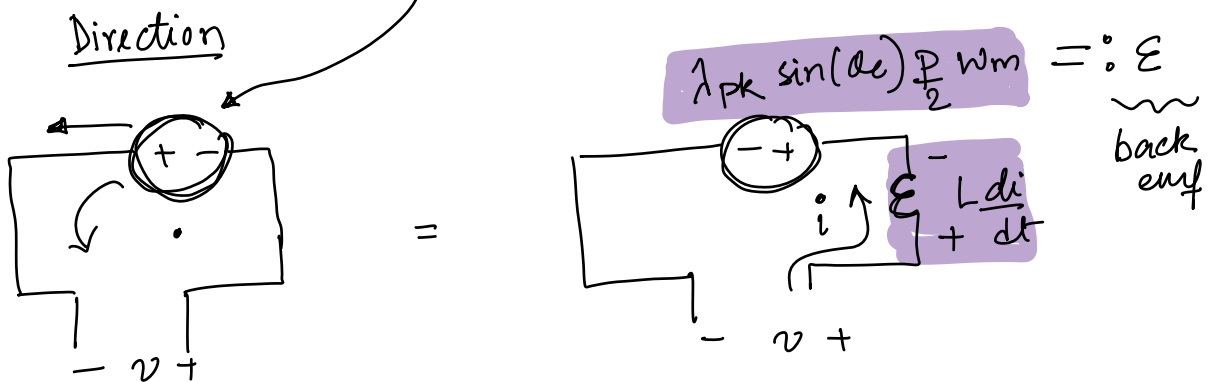
$$= \underbrace{(-\lambda_{pk} \sin(\theta_e) \frac{P}{2} \omega_m)}_{\lambda_{pk} \sin(\theta_e) \omega_e} - L \frac{di}{dt}$$





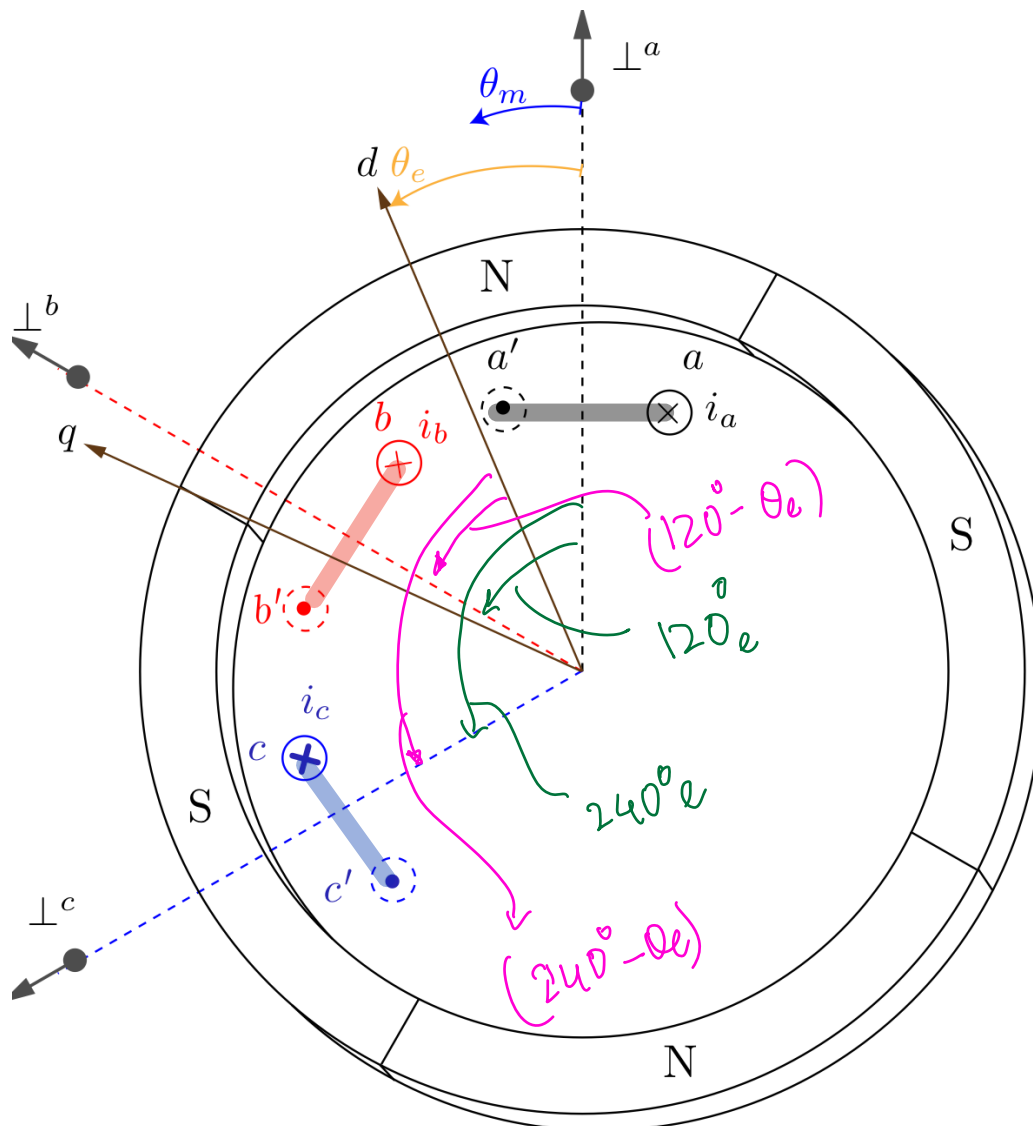

(c) For three sets of coil.

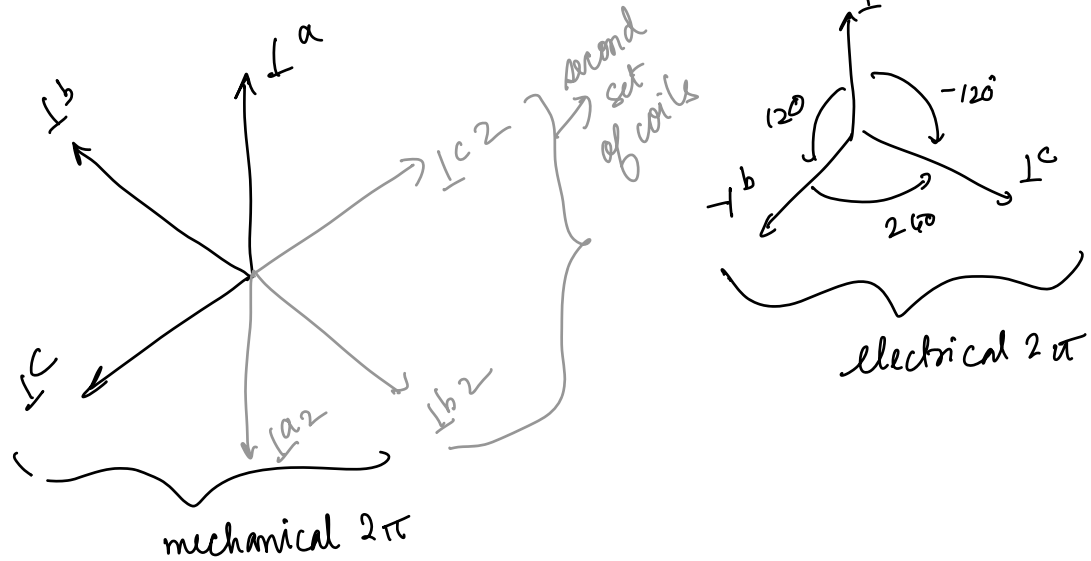

$$\lambda_{a_1 a_2} = -\lambda_{pk} \cos(\theta_e) + L_{ia}$$

$$\lambda_{b_1 b_2} = -\lambda_{pk} \cos\left(\theta_e - \frac{2\pi}{3}\right) + L_{ib} = -\lambda_{pk} \cos\left(\theta_e - \frac{2\pi}{3}\right) + L_{ib}$$

$$\lambda_{c_1 c_2} = -\lambda_{pk} \cos\left(\theta_e - \frac{4\pi}{3}\right) + L_{ic} = -\lambda_{pk} \cos\left(\theta_e - \frac{4\pi}{3}\right) + L_{ic}$$

induced emf:-

$$\text{Coil } a_1 a_2: \left(-\frac{d\lambda_{a_1 a_2}}{dt}\right) = -\lambda_{pk} \omega_e \sin(\theta_e) - L \frac{di_a}{dt}$$

$$\text{Coil } b_1 b_2: \left(-\frac{d\lambda_{b_1 b_2}}{dt}\right) = -\lambda_{pk} \omega_e \sin\left(\theta_e - \frac{2\pi}{3}\right) - L \frac{di_b}{dt}$$

$$\text{Coil } c_1 c_2: \left(-\frac{d\lambda_{c_1 c_2}}{dt}\right) = -\lambda_{pk} \omega_e \sin\left(\theta_e - \frac{4\pi}{3}\right) - L \frac{di_c}{dt}$$

$\underbrace{\hspace{10em}}_{\text{speed dependent emfs}}$   
 $\underbrace{\hspace{10em}}_{\text{not back emfs.}}$

