


Lecture 18 (March 3)

o HW 5 due now (submission open till midnight today)

o HW 6 due 10th March.

Current Sensing

& Voltage Sensing.

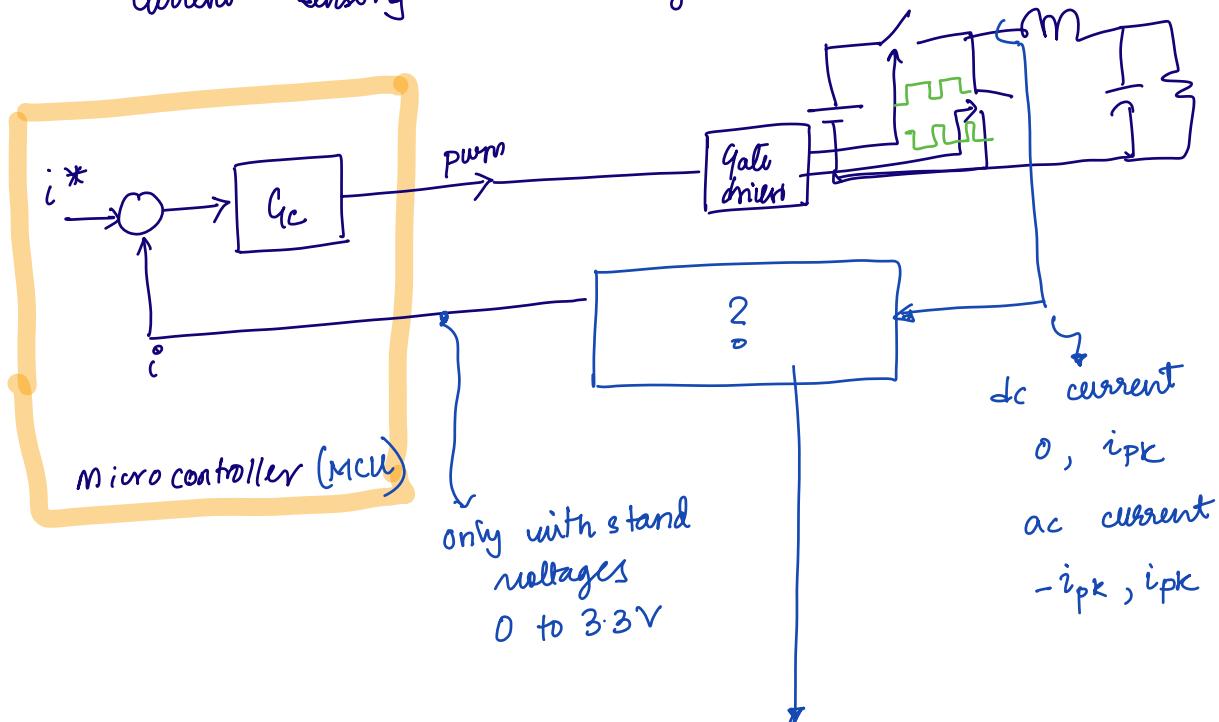

current \longrightarrow voltage conversion
(circuit) (for microcontroller)


① Sense resistor. (R_s)

' i ' - inductor current.

$i \cdot R_s = v_s$ = drop across the sense resistor.

If $0 < v_s < 3.3V$, you can directly feed this to MCU.

Inside MCU,

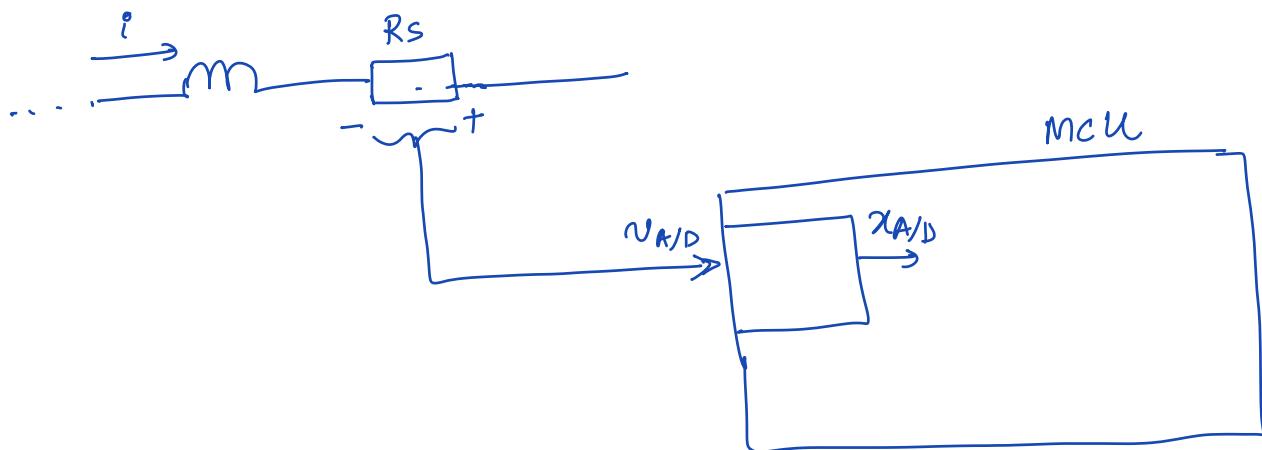

$$x_{A/D}[k] = \text{round} \left(\frac{v_{A/D}}{V_{FS}} \cdot 2^{n_{ADC}} \right) \rightarrow 12 \text{ bits}$$


3:3


$$x_{A/D} \xrightarrow[?]{\circ} i[k]$$

$i[k]$ = inductor current at the k-th sample


$$i[k] = \left[x_{A/D}[k] \cdot \frac{V_{FS}}{2^{n_{ADC}}} \right] \xrightarrow{R_s} \frac{i}{R_s}$$

If $R_s i > 3.3V$,

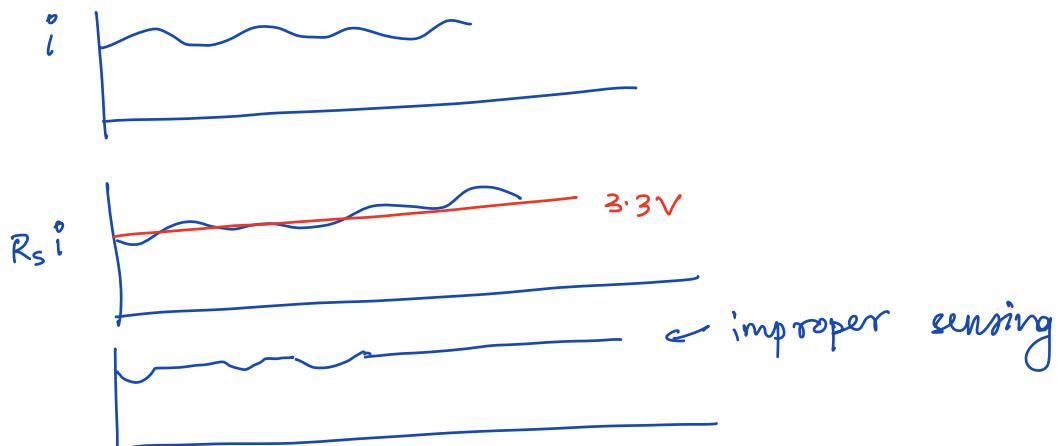

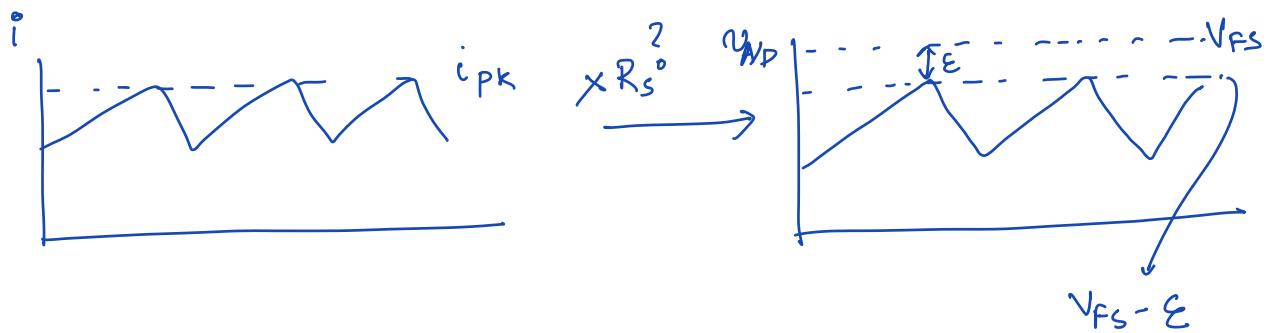

AC currents




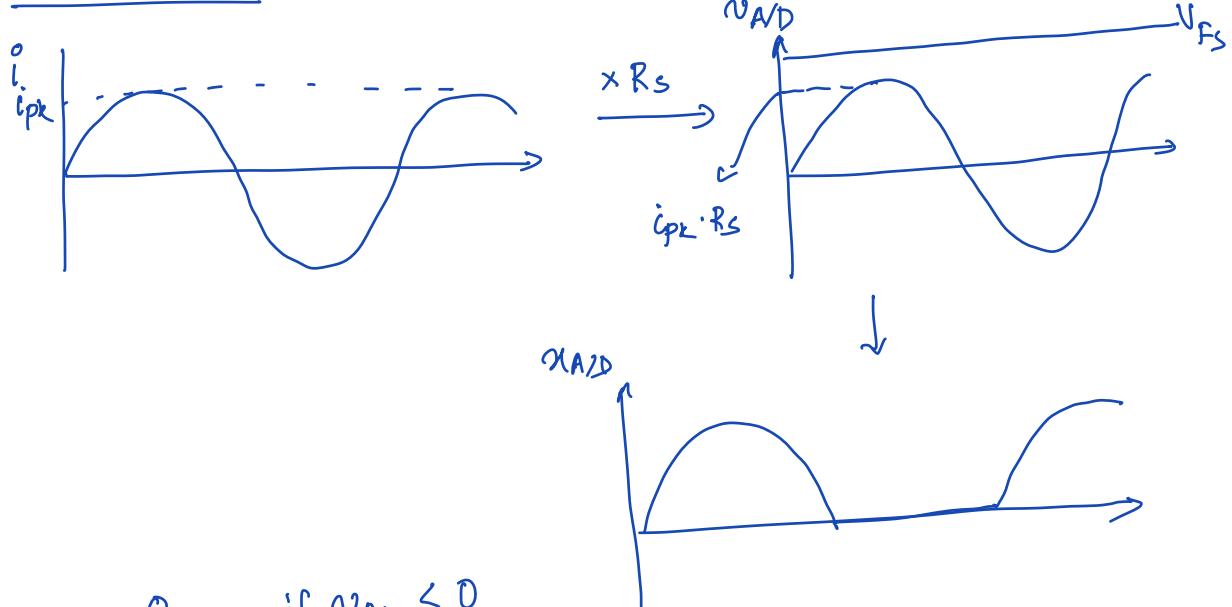


$$v_{AD} = 0 \quad \text{if } v_{AD} < 0$$

$$= \frac{v_{AD}}{V_{fs}} 2^{n_{ADC}} \quad \text{if } 0 \leq v_{AD} \leq v_{fs}$$

$$= 2^{n_{ADC}} - 1 \quad \text{if } v_{AD} > v_{fs}$$

AC 5730

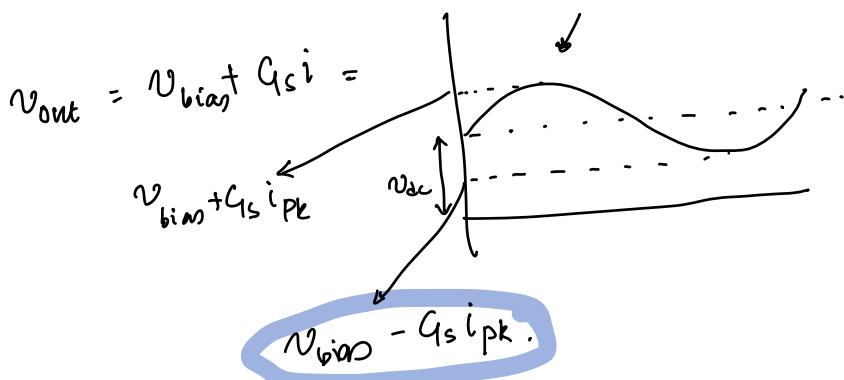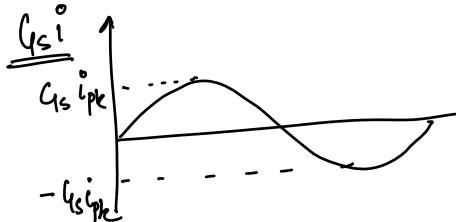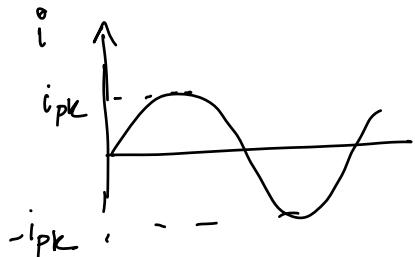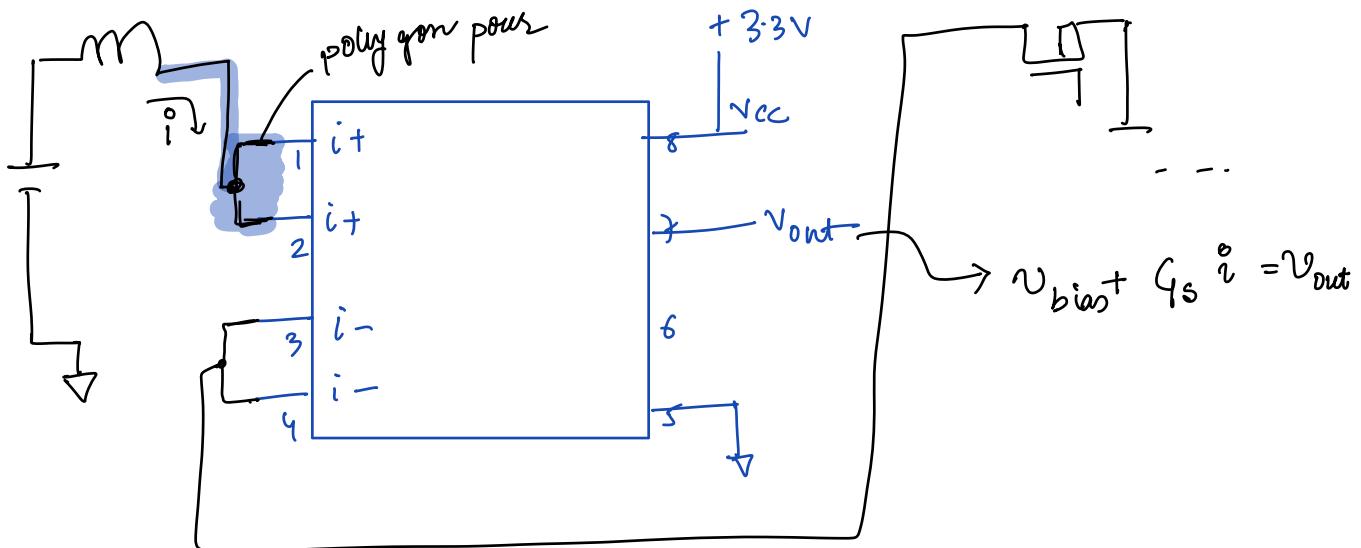

Q O/P has to be strictly positive : became $0 < v_{A/D} < 3\%$.

$$v_{bias} - G_s i_{pk} > 0$$

$$v_{bias} > G_s i_{pk}$$

$$\therefore i_{pk} < \frac{v_{bias}}{G_s}$$

$$V_{bias} + G_s i_{pk} < V_{cc}$$


$$V_{bias} = \frac{V_{cc}}{2}$$


~~eq~~ ACS730 $\rightarrow 3V = V_{cc}$

&, $V_{bias} = 1.5\text{ V.}$

$$G_s = 0.1, 0.15, 0.2 \dots$$

Most General current sensing circuit.

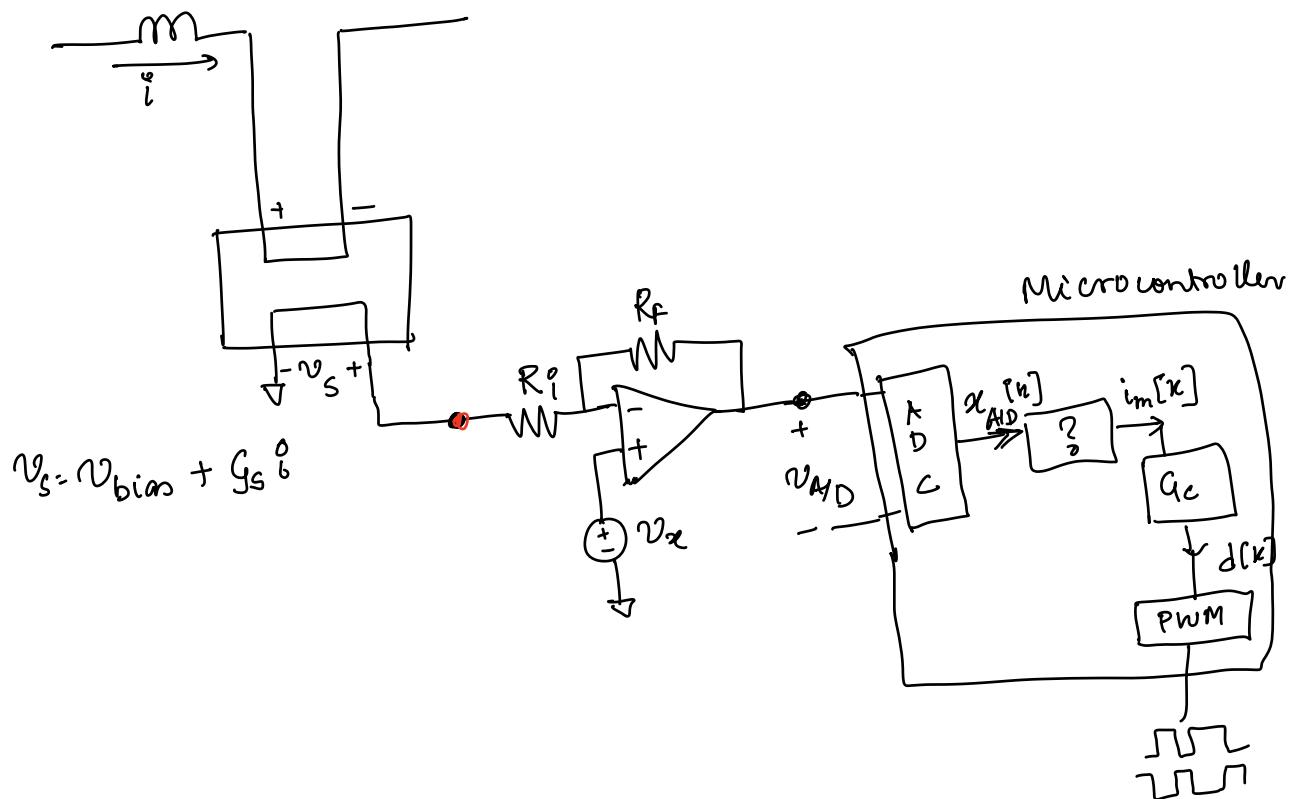

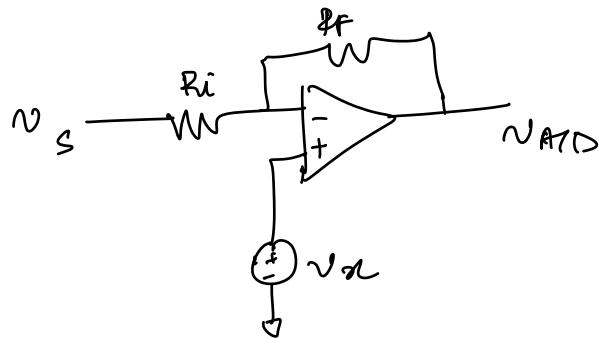

Superposition

$$(1) \quad v_x = 0$$

$$(v_{A/D}) \Big|_{v_x=0} = -\frac{R_f}{R_i} v_s$$

$$(2) \quad v_s = 0$$

$$(v_{A/D}) \Big|_{v_s=0} = \left(1 + \frac{R_f}{R_i}\right) v_x$$

So, net $v_{A/D}$ obtained by superposition:


$$v_{A/D} = (v_{A/D}) \Big|_{v_x=0} + (v_{A/D}) \Big|_{v_s=0}$$

$$= -\frac{R_f}{R_i} v_s + \left(1 + \frac{R_f}{R_i}\right) v_x$$

$$\left[\because v_s = v_{bias} + g_s i \right]$$

$$\hookrightarrow v_{A/D} = -\frac{R_f}{R_i} (v_{bias} + g_s i) + \left(1 + \frac{R_f}{R_i}\right) v_x \quad \text{--- (1)}$$

$$0 < v_{AID} < v_{FS}$$

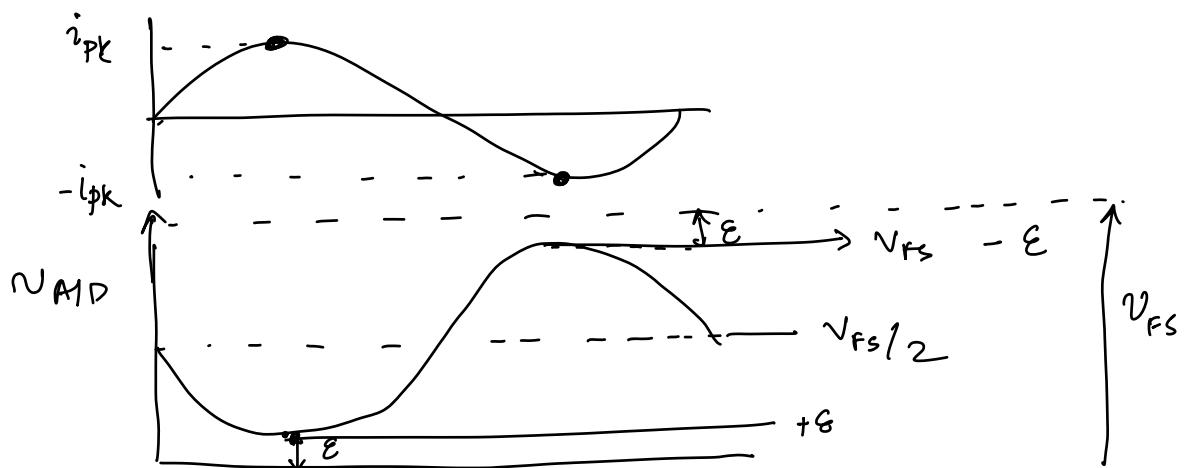

① If $i = 0$,

$$\underline{v_{AID}} = \underline{v_{FS}/2}$$

From eq ① we can write

$$\underline{v_{AID}} = -\frac{R_f}{R_i} (v_{bias} + g_s i) + \left(1 + \frac{R_f}{R_i}\right) v_x$$

$$\boxed{\frac{v_{FS}}{2} = -\frac{R_f}{R_i} v_{bias} + \left(1 + \frac{R_f}{R_i}\right) v_x} \quad \text{--- (2)}$$

Design choices: $\underline{R_f/R_i}, \underline{v_x}$

(2) condition ①


$$\left\{ \begin{array}{l} \text{if } i = i_{PK}, \quad v_{AID} > \epsilon \\ i = -i_{PK}, \quad v_{AID} < v_{FS} - \epsilon \end{array} \right.$$

$$v_{AID} = -\frac{R_f}{R_i} v_{bias} + \left(1 + \frac{R_f}{R_i}\right) v_x - \frac{R_f}{R_i} G_s i$$

$v_{FS}/2$

$$v_{AID} = \frac{v_{FS}}{2} - \frac{R_f}{R_i} G_s i$$
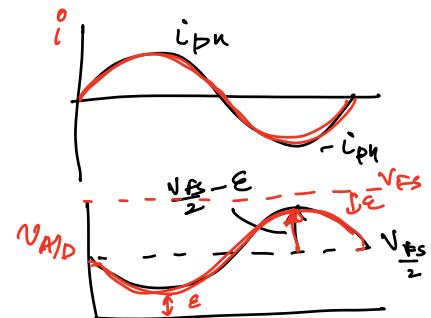
$$\frac{v_{FS}}{2} - \frac{R_f}{R_i} G_s i_{PK} > \epsilon$$



$$\text{or, } \frac{v_{FS}}{2} - \epsilon > \frac{R_f}{R_i} G_s i_{PK}$$


$$\therefore \boxed{\frac{R_f}{R_i} < \frac{1}{G_s i_{PK}} \left(\frac{v_{FS}}{2} - \epsilon \right)} = ③$$

$$\frac{R_f}{R_i} = \frac{1}{G_s i_{PK}} \left(\frac{v_{FS}}{2} - \epsilon \right)$$

A) Choose $\frac{R_f}{R_i}$ by Eq ③

B) Substitute $\frac{R_f}{R_i}$ from A) in Eq ② to get v_x .

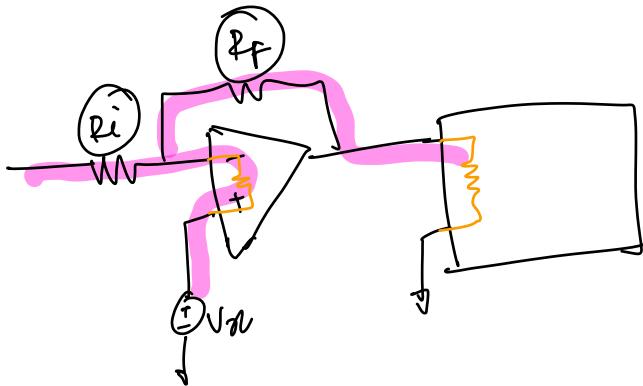C) How to get R_f & R_i from $\frac{R_f}{R_i}$?



$R_i, R_F \ll R_{\text{leakage}}$.

$$R_i, R_F \sim \underline{10 \text{ kOhm}}, \underline{1 \text{ kOhm}}$$

Inside the microcontroller,

$$\alpha_{A/D} = \text{round} \left(\frac{V_{A/D}}{V_{FS}} \cdot 2^{n_{A/D}} \right)$$

$$\alpha_{A/D} = \text{round} \left(- \underbrace{\frac{R_F}{R_i} (V_{\text{bias}} + G_S i) + \left(1 + \frac{R_F}{R_i} \right) V_A}_{V_{FS}} \cdot 2^{n_{A/D}} \right)$$



$$= \text{round} \left(\underbrace{\left(\frac{V_{FS}}{2} - \frac{R_F}{R_i} G_S i \right)}_{V_{FS}} \cdot 2^{n_{A/D}} \right)$$

$$= \text{round} \left(\left(\frac{1}{2} - \frac{R_F}{R_i} \frac{G_S}{V_{FS}} i \right) \cdot 2^{n_{A/D}} \right)$$

$\underbrace{\phantom{\left(\frac{1}{2} - \frac{R_F}{R_i} \frac{G_S}{V_{FS}} i \right)}}_F \cdot 2^{n_{A/D}}$

$$v_{A/D} \rightarrow f^{-1} \rightarrow \underbrace{i[k]}$$

5:28 pm

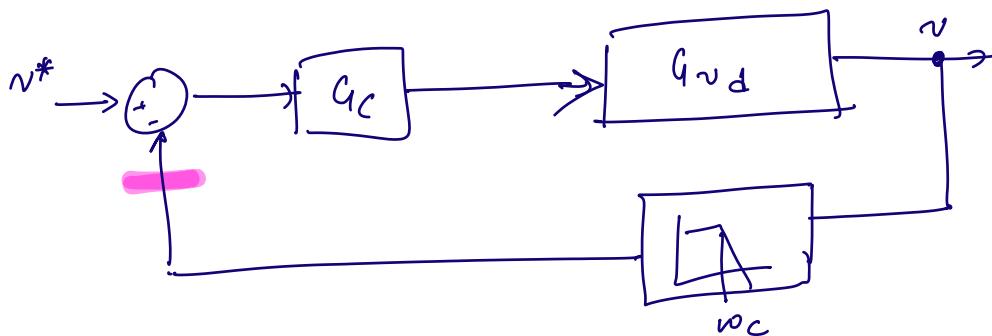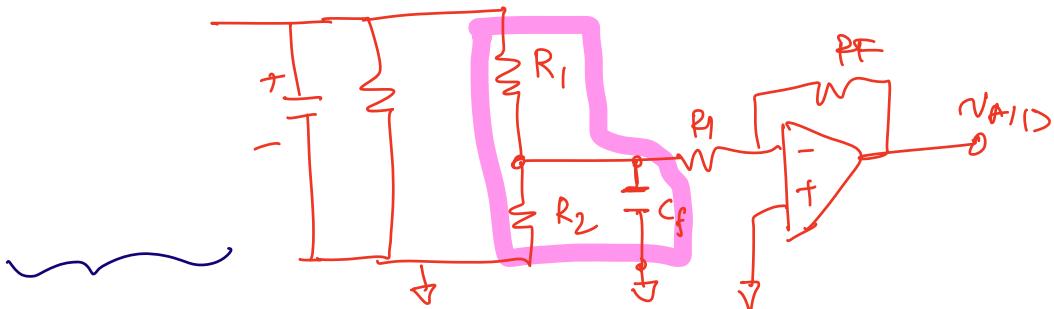

$$\omega_c = \frac{1}{C_f R_f}$$

If $\omega_c \approx \omega_{gv}$ \leftarrow voltage control bandwidth.

ω_c = filter cut off frequency \gg control bandwidth
of the inductor current / cap voltage

MHz range cut off frequency

$$v_{A/D} \rightarrow x_{A/D}[k]$$

① Low pass filter $x_{A/D}$ digitally -



$$x_{A/D}^0 = \frac{S}{S + W_C} x_{A/D}$$

② moving average filter

$$x_{A/D}^0 = \frac{x_{A/D}[k] + x_{A/D}[k-1]}{2}$$

Never try this

$$③ x_{A/D}^0 = x_{A/D}[k] \& (FFF0)$$

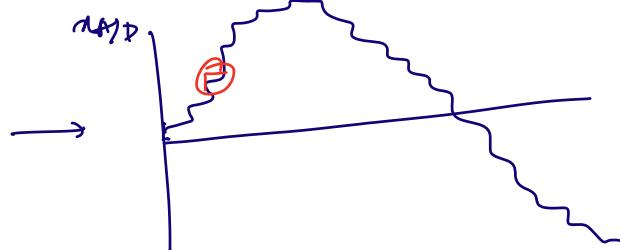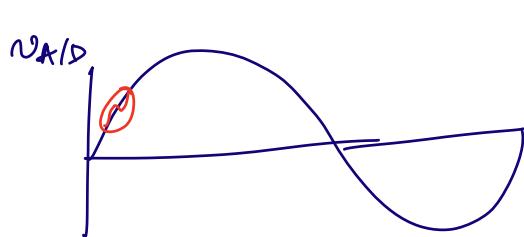


digital
9 → bin
1001

F F F
1111 1111 1111 0000
MSB LSB


LSB = least significant bit

MSB

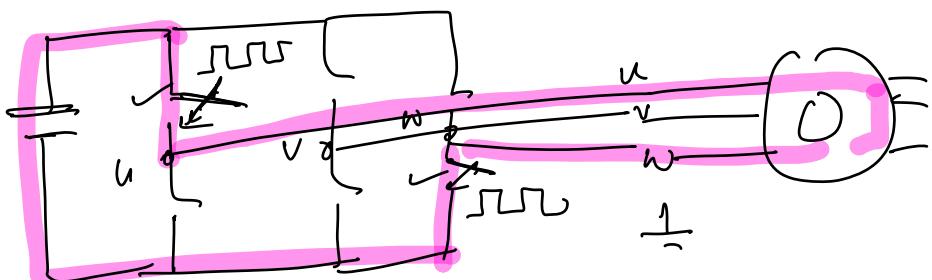

6-step driving – Hall sensors feedback




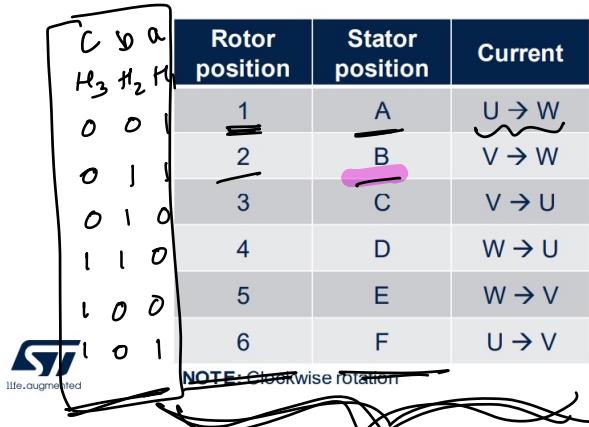
The **Hall sensors** detects the rotor position returning a digital or analog signal. The information is used to move the stator magnetic field in the next position.



Rotor position

Rotor position	Stator position	Current
1	A	$U \rightarrow W$
2	B	$V \rightarrow W$
3	C	$V \rightarrow U$
4	D	$W \rightarrow U$
5	E	$W \rightarrow V$
6	F	$U \rightarrow V$

NOTE: Clockwise rotation

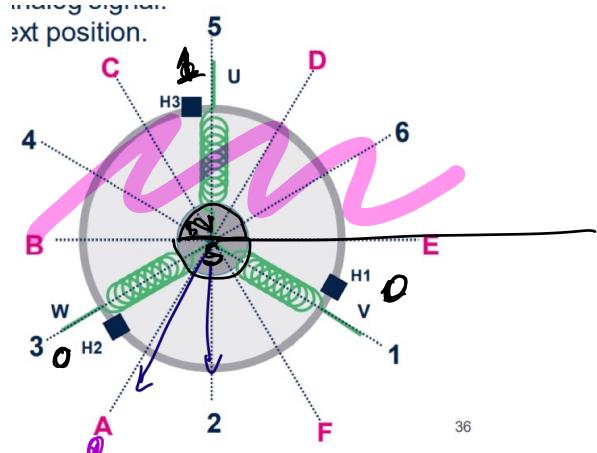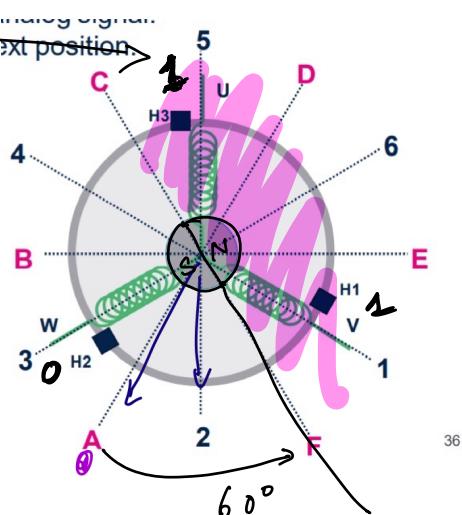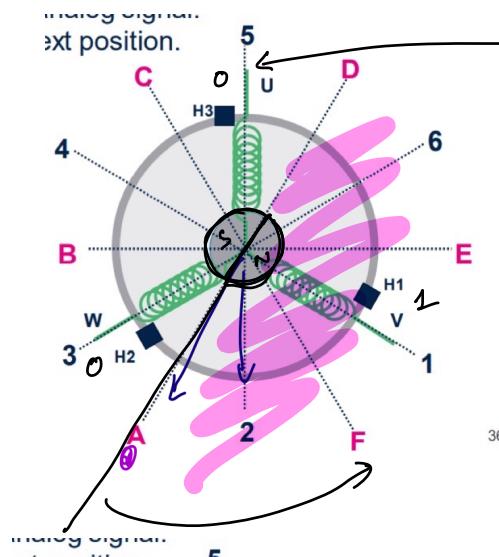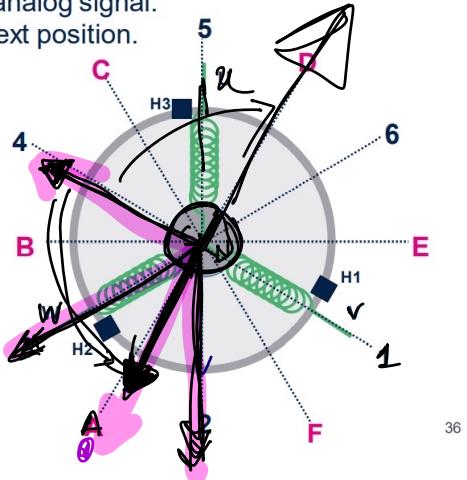



counter = 0 when H_1, H_2, H_3 no change
 counter ++
 counter stops when any one of H_1, H_2, H_3 changes

$$\begin{aligned}
 \text{time} &= \text{counter} \times t_{\text{sample}} \\
 &= (\text{counter}) \left(\frac{1}{2 f_{\text{sw}}} \right) \\
 &= \text{counter} \cdot 50 \mu\text{s.} \quad \times
 \end{aligned}$$

rotation between any 1 Hall effect sensor
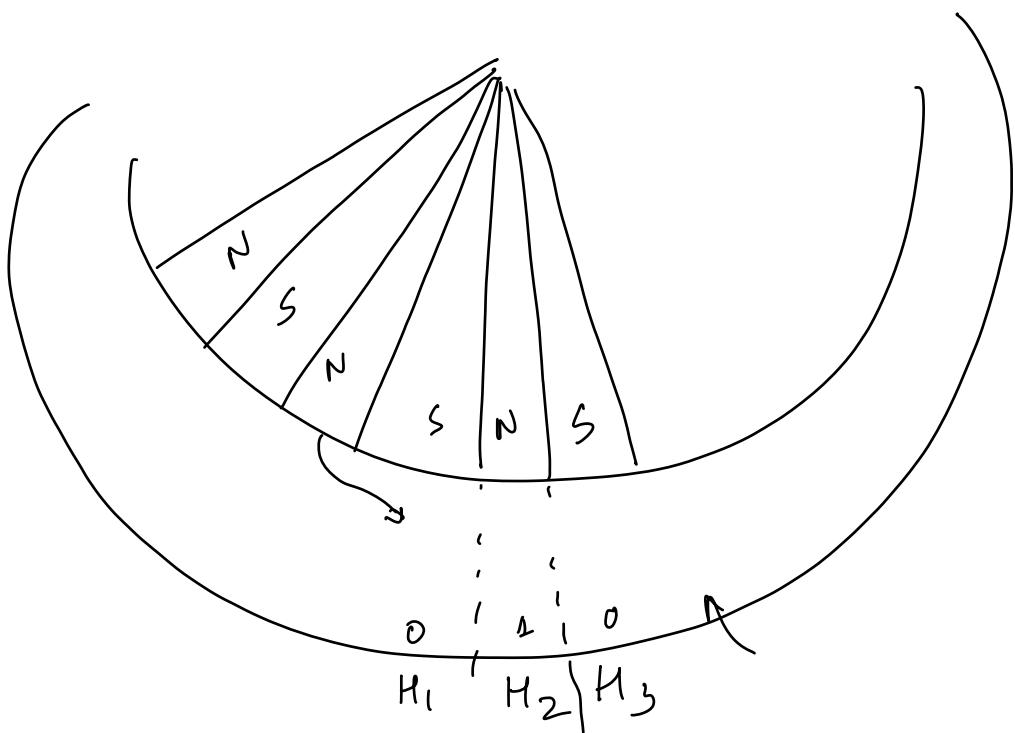
$$\begin{aligned}
 \text{charge} &= \frac{2\pi}{6} = \frac{\pi}{3} \\
 \omega_{\text{electrical}} &= \frac{\pi/3}{(\text{counter}) (50\mu\text{s})} \text{ rad/s}
 \end{aligned}
 \quad \left. \right\}$$



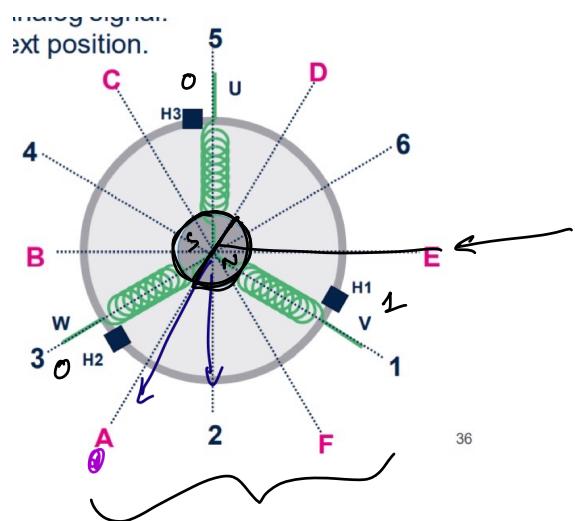


36

- Because of the Hall sensors, the angle θ updates every 60° .

θ	H ₃	H ₂	H ₁
0°	0	0	1
60°	0	1	0
120°	1	0	0
180°	1	0	1
240°	0	1	1
300°	1	1	0
360°	0	0	0

$\theta_i = 0^\circ$ *
 $\theta = \theta_i + \int w \cdot dt$
 $\theta_i = 60^\circ$
 $\theta = \theta_i + \int v \cdot dt$

- (*) Who said 001 → corresponds to 0° .

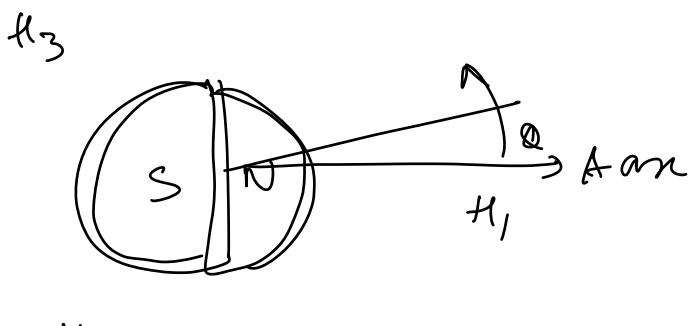

④ At very high speeds,
hall effect sensor outputs can get
missed.

So, your speed & angle estimation might
not work.