### **Lab2** Presentation

Rahul Mallik
University of Washington


#### Main theme

#### **RT-Box Preliminaries**

- Build an PLECS boost converter model
- Learn how to make it compatible with RT-Box simulation
- Run in open loop using PWM. Use ADC to only sense the voltages and currents but not do any actual control



## Circuit

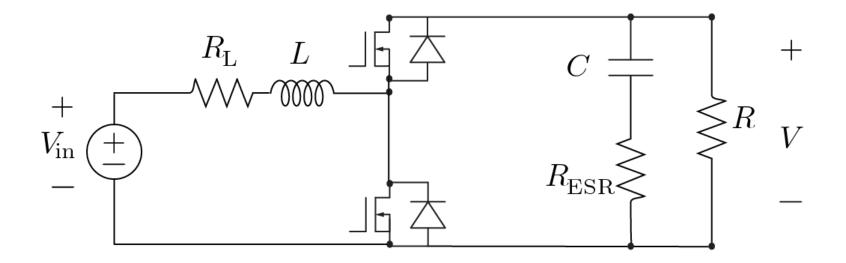




Making it compatible with RT-Box




### The PLECS model

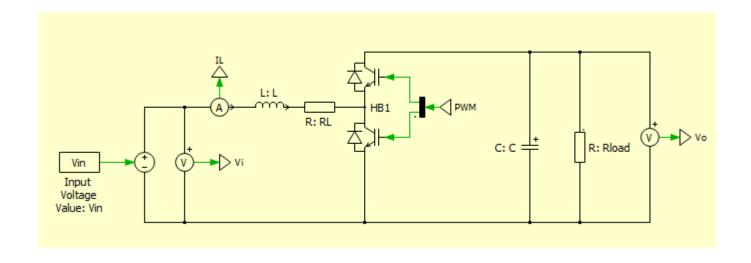



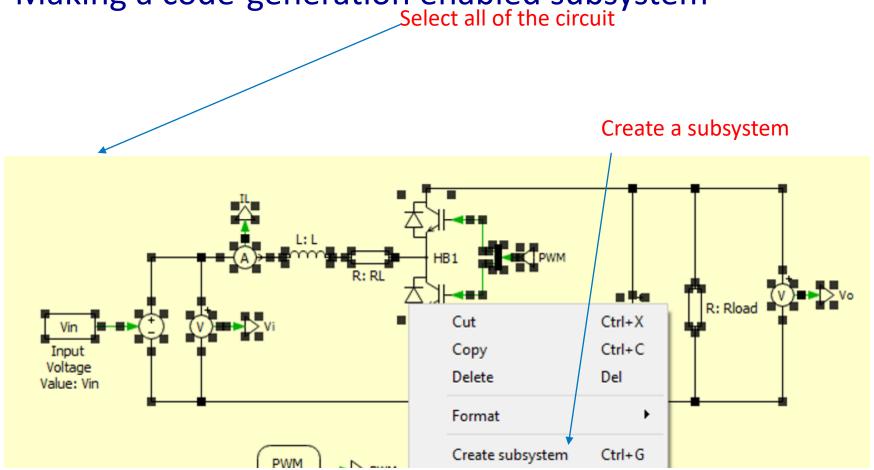
# Making a code-generation enabled subsystem Select all of the circuit





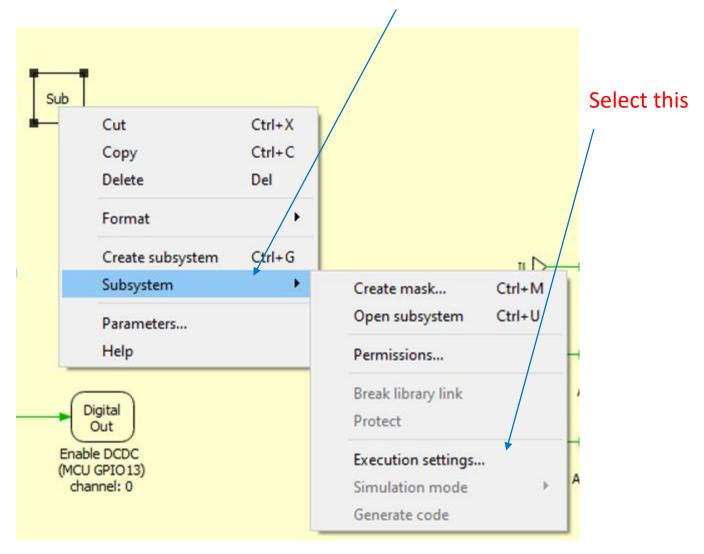
# Making a code-generation enabled subsystem Select this





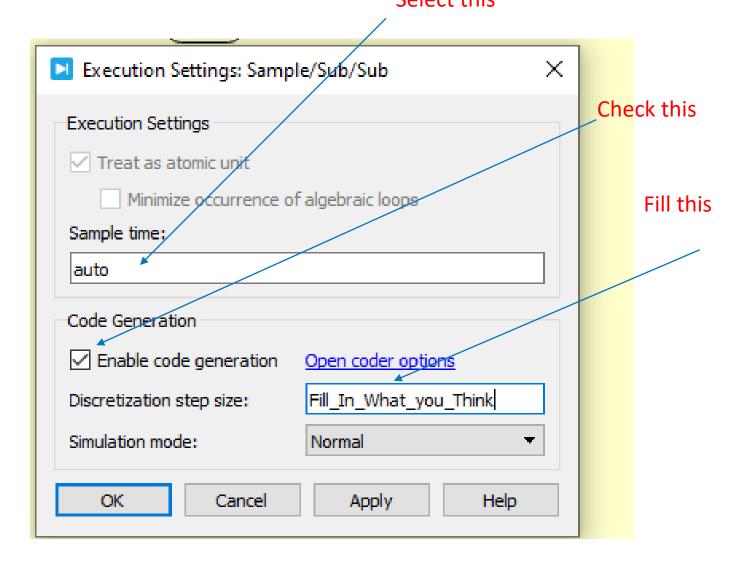
# Making a code-generation enabled subsystem Select this






#### PWM capture

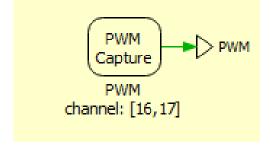


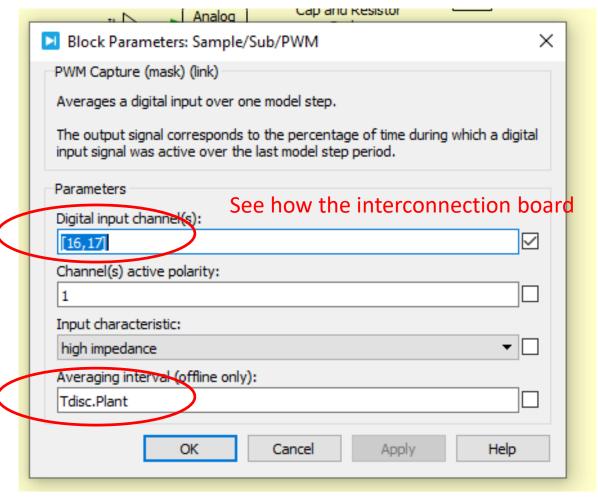
This is the real time discretization paper






#### **ADC Block**

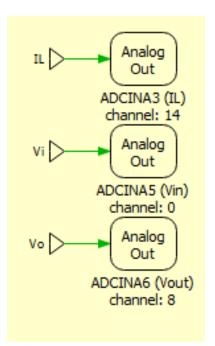

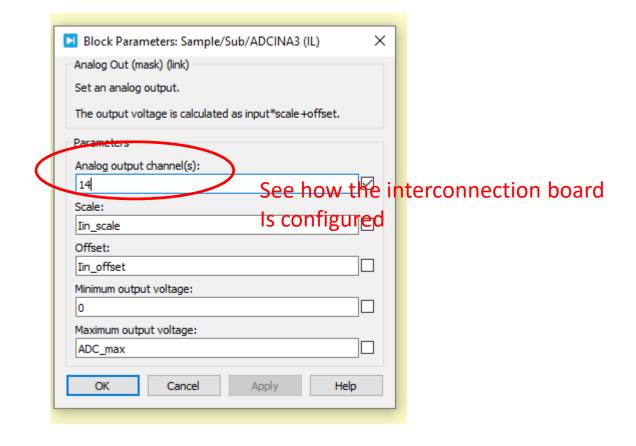




## The whole system

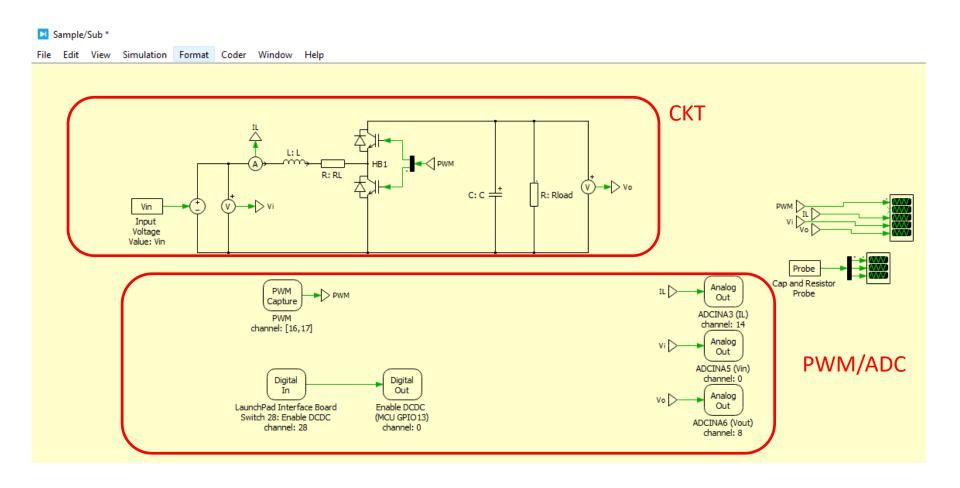


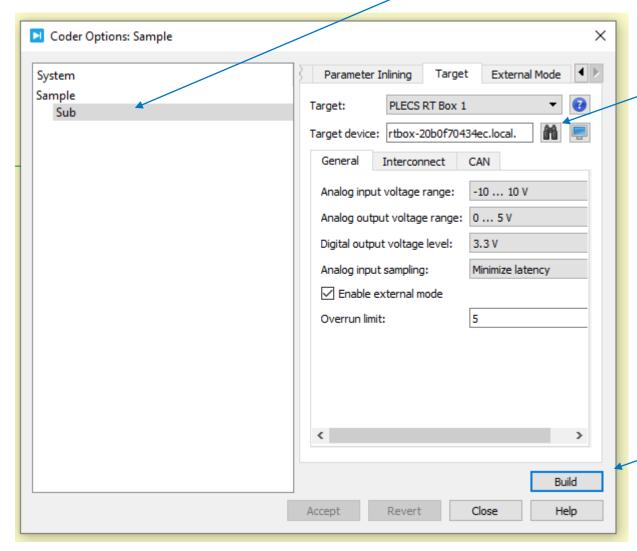
## Go to "Coder" Tab on the menu bar at top and get this Your sub module



Use this to find your RT Box

Click on this to upload code

