

Lecture 20 (10th March)

Finals will be released Friday midnight / Saturday early morning.

You will have approx. 72 hrs. to solve

HW 6 due now. (if you want extension, mail me - max possible till midnight today).

Finals

(Lecture simulation)

- It is heavily reliant on motor modeling simulation
- Use as much as possible from HW 5, 6.
- Main aim of finals is digital control & system integration.

boost + motor model

simulation ~ as close to hardware implementation as possible


- Less focus on control design
- 10 marks for conceptual question.

- Try your best to attempt all problems.
 - partial marks.
- Contact me by Teams.
ask away anything


① Sensor

Current Sensor.

(Hall effect sensor - flavour A)

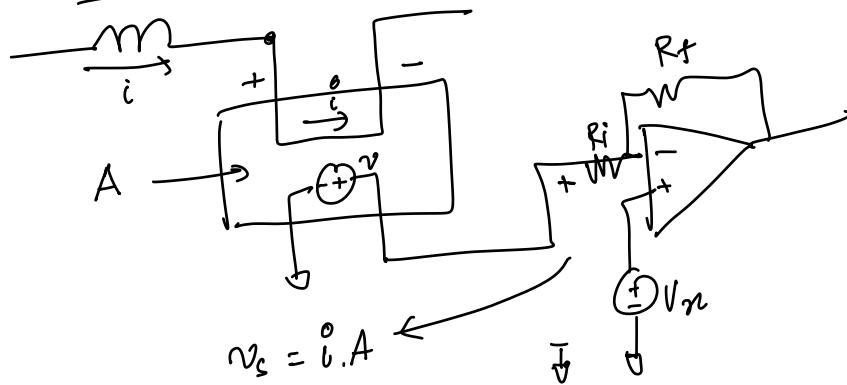


(sensor - flavour B)

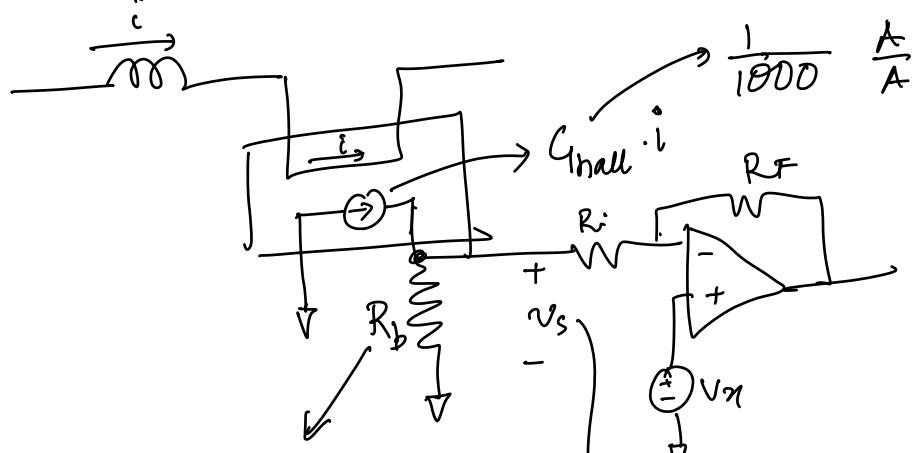

burden / bleeder
resistor




$$V_S = R_b \cdot G_{Hall} \cdot i$$

new gain.

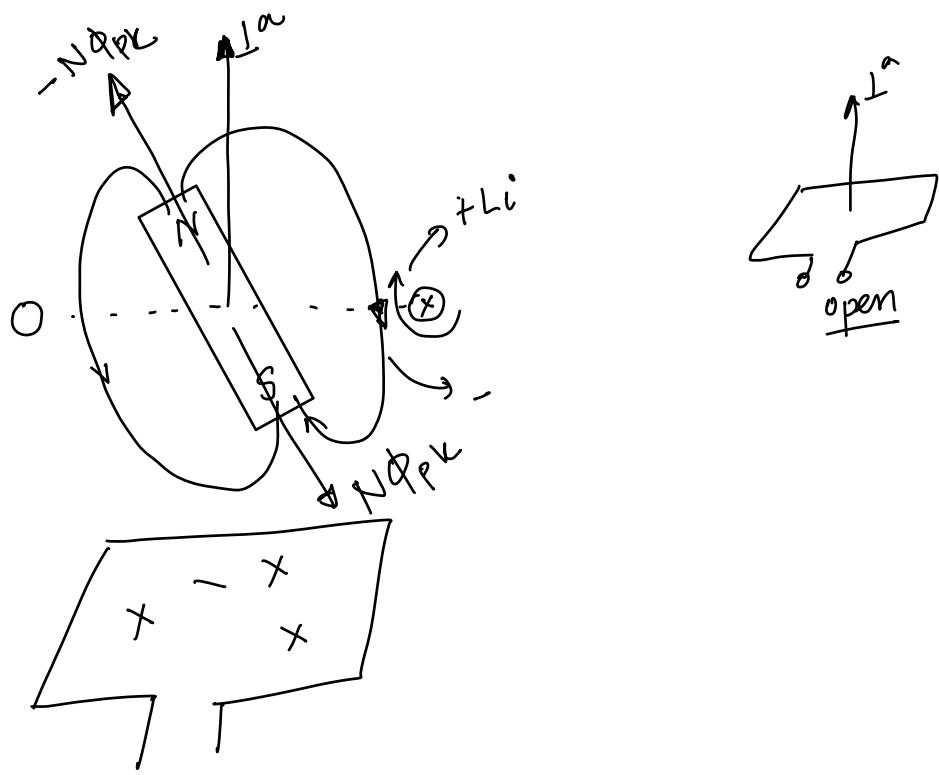



Input Filter design

Buck Converter

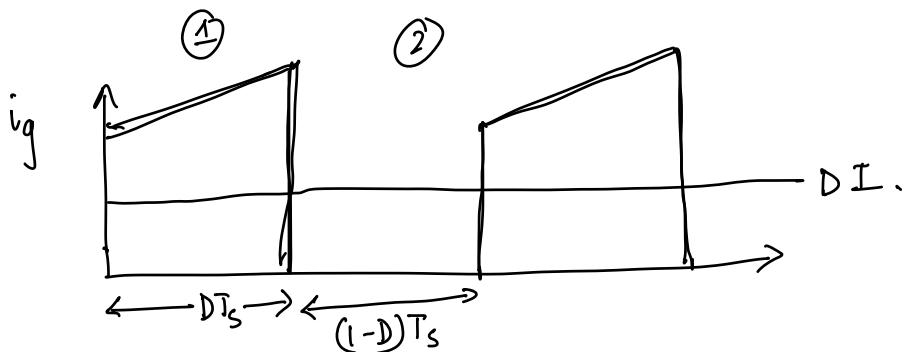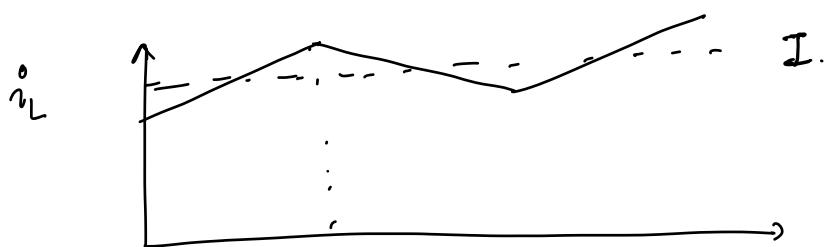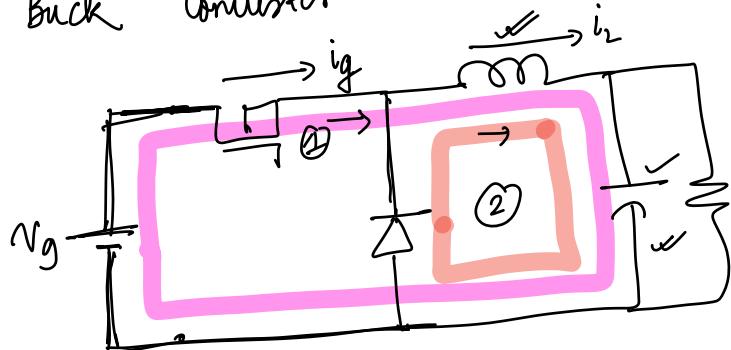


$$i_p(t) = \underbrace{DI}_{\text{DC}} + \sum_{k=1}^{\infty} \frac{2I}{k\pi} \sin(k\pi D) \cos(k\omega t)$$

conducted electromagnetic interference.

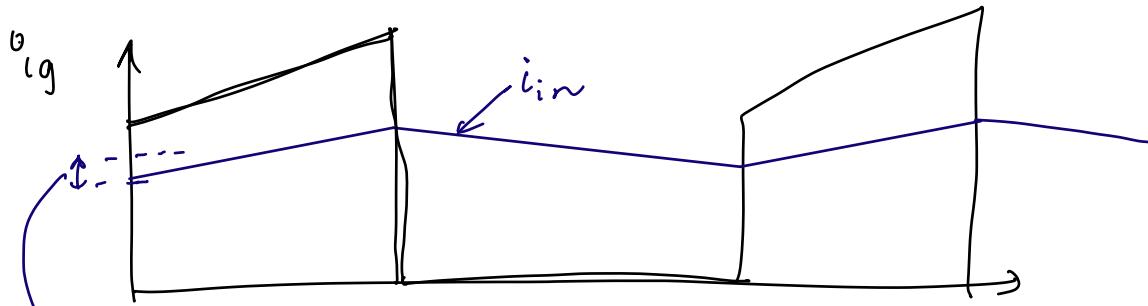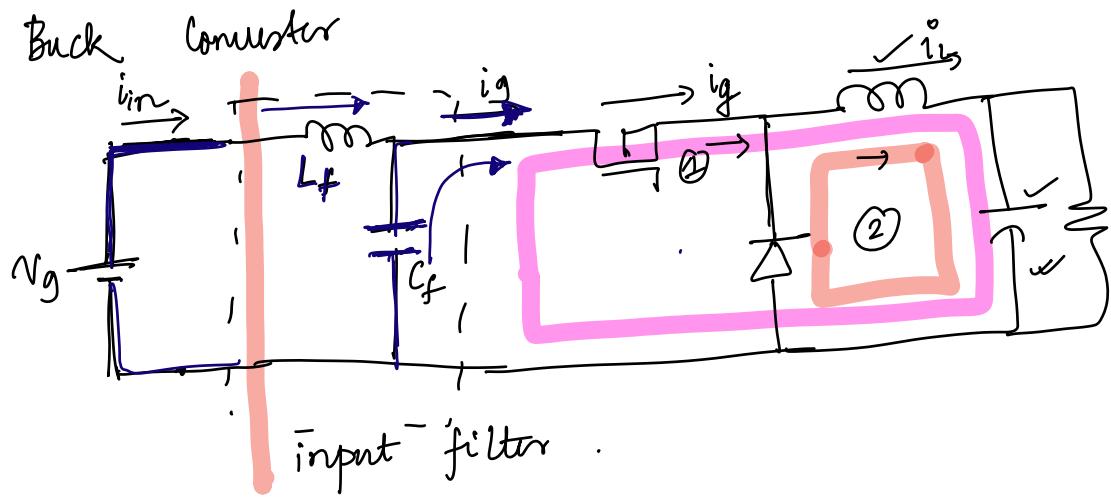
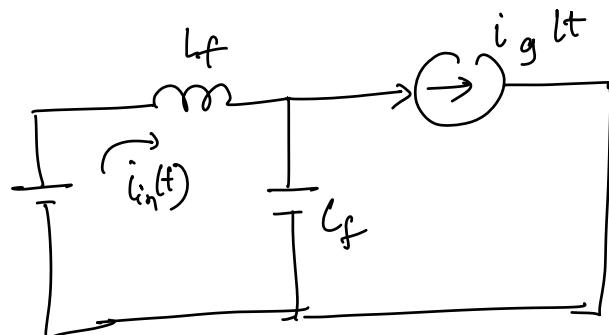
$$\Delta i_{in} \sim 10 \mu A \text{ to } 100 \mu A.$$




$$i_{in}(s) = \underbrace{i_g(s)}_{H(s)} \cdot \frac{\frac{1}{sC_f}}{sL_f + \frac{1}{sC_f}} = i_g(s) \cdot \frac{1}{s^2L_fC_f + 1}$$

$H(s) = \underbrace{\text{filter transfer function}}$

$$i_{ig}(t) = \underbrace{DI}_{dc.} + \sum_{k=1}^{\infty} \frac{2I}{k\pi} \sin(k\pi D) \cos(k\omega t)$$

$$i_{in}(t) = \underbrace{D \cdot H(0) \cdot I}_{dc.} + \sum_{k=1}^{\infty} \boxed{\underbrace{H(k\omega t)}_{L}} \cdot \frac{2I}{k\pi} \sin(k\omega t) \cos(k\omega t)$$

Buck Converter

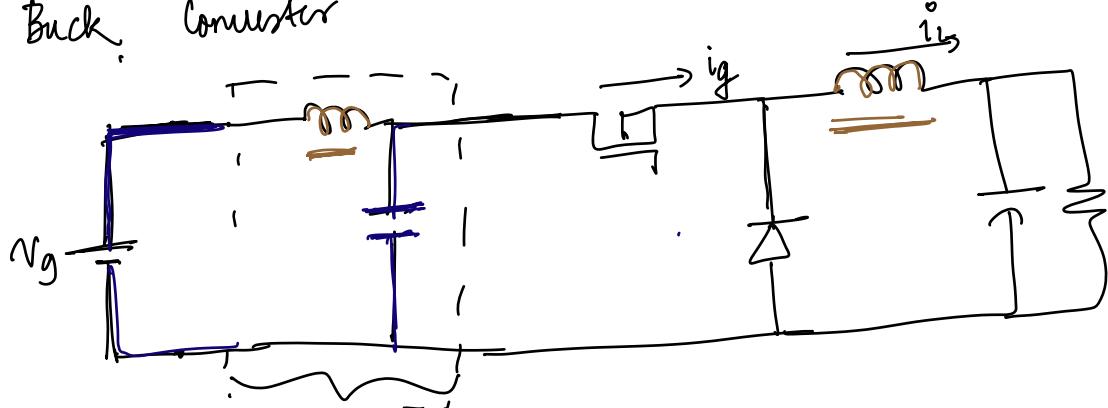

$$G_{vd} = \left. \frac{\tilde{v}}{\tilde{d}} \right|_{\tilde{v}_g = 0}$$

$$G_{id} = \left. \frac{\tilde{i}}{\tilde{d}} \right|_{\tilde{v}_g = 0}$$

- ① Design your controller by imagining that there is no input filter.
- ② Now force the input filter to satisfy 2 design criterias.




$$G_{Vd} \left| \begin{array}{l} \text{with input filter} \end{array} \right. = G_{Vd} \left| \begin{array}{l} \text{without input filter} \end{array} \right. \cdot \frac{\left(1 + \frac{Z_0(s)}{Z_N(s)} \right)}{\left(1 + \frac{Z_0(s)}{Z_D(s)} \right)}$$




$Z_0(s)$ = output impedance of the input filter

$\left. \begin{array}{l} Z_N(s) \\ Z_D(s) \end{array} \right\}$ parameters are tabulated in book.


→ Table 10.1
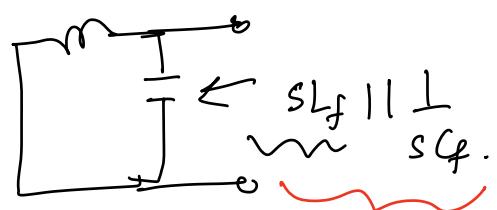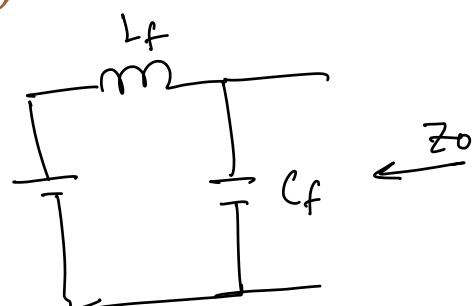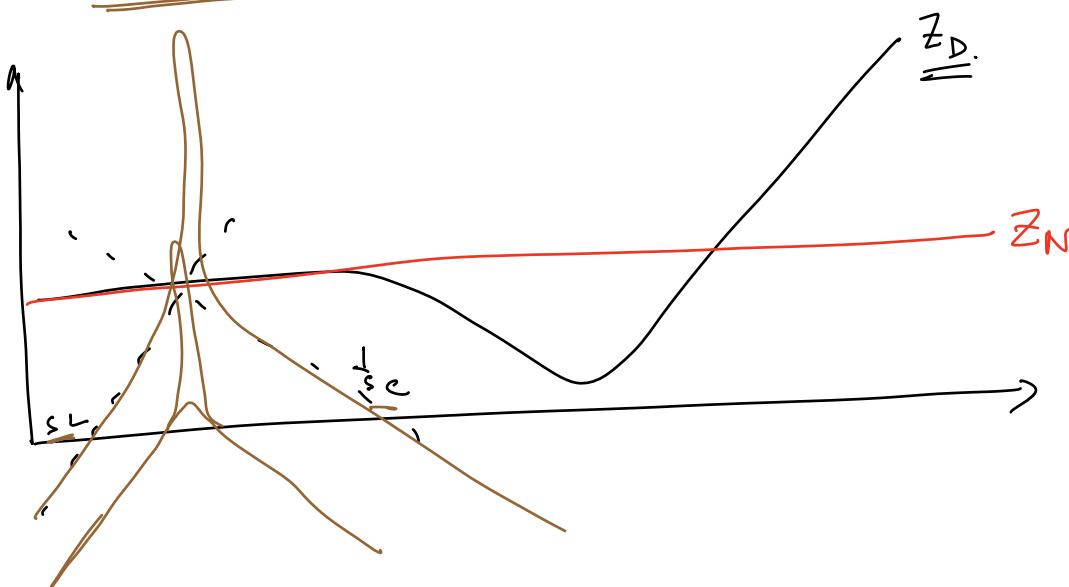
$$\underline{Z_0 \ll Z_N} ; \underline{Z_0 \ll Z_D}$$




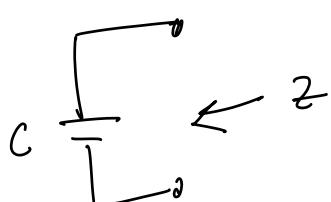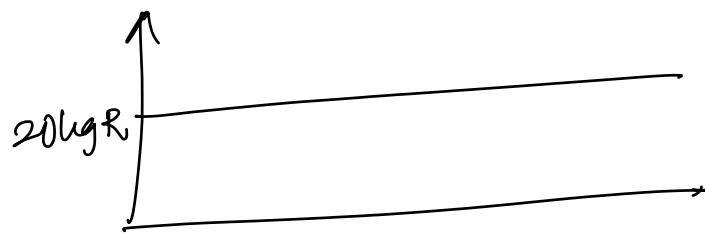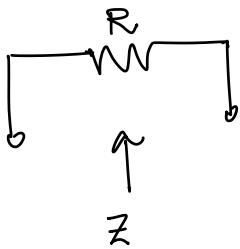



$$Z = \frac{1}{sC}$$




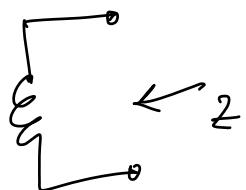






$$Z = sL$$




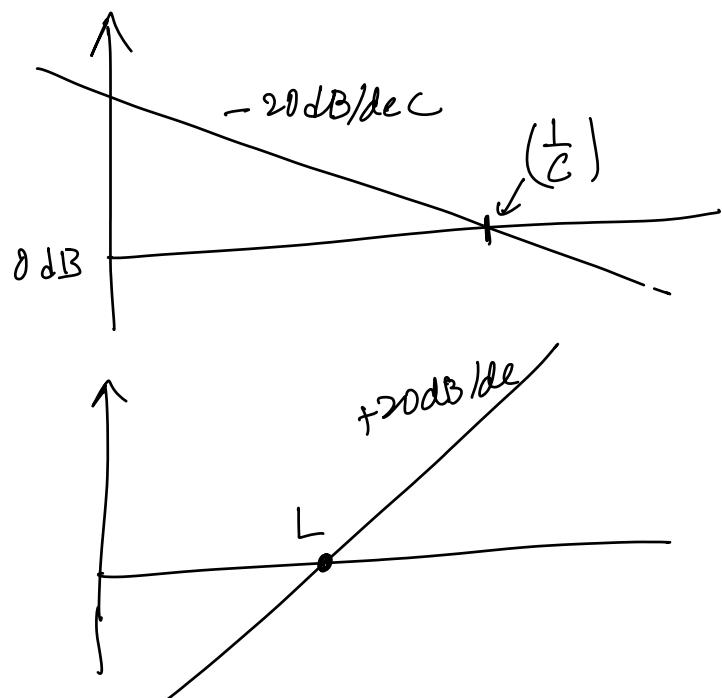


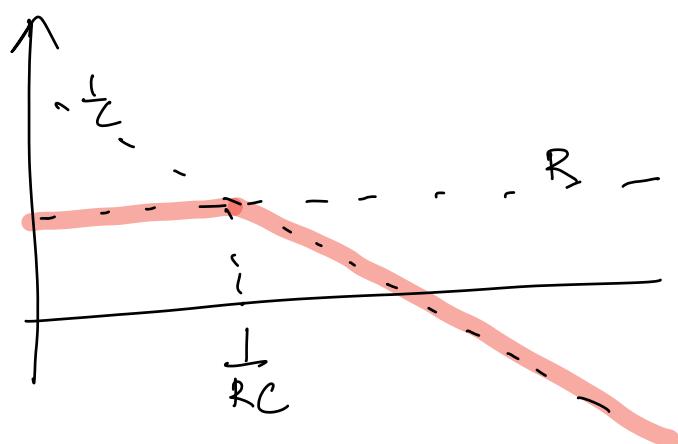
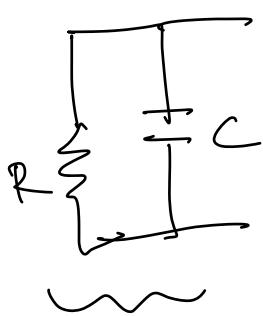
① Asymptotes in parallel = minimum
" " series = maximum



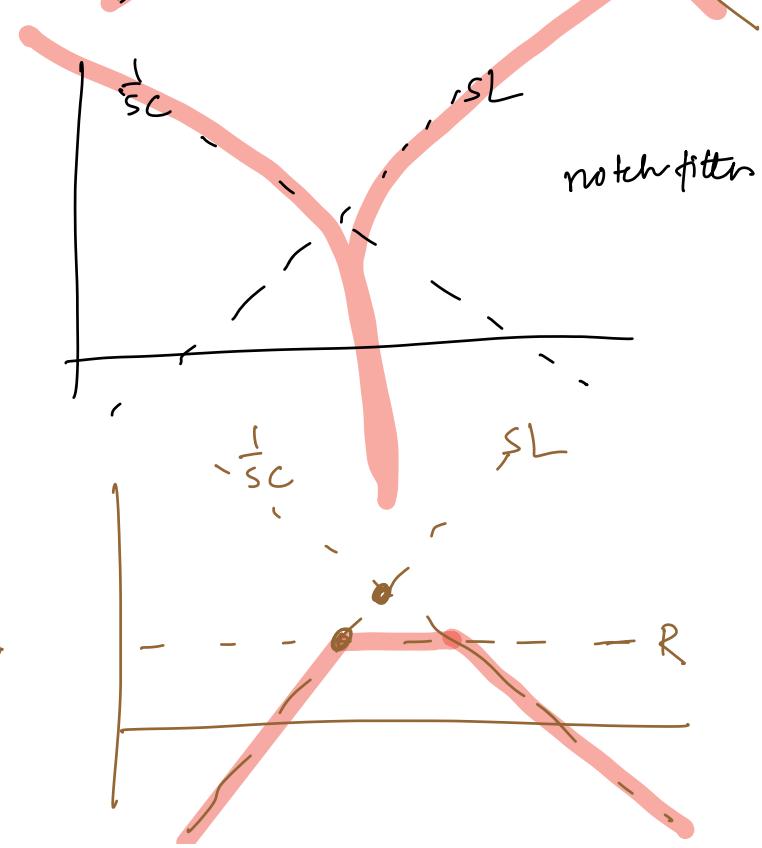
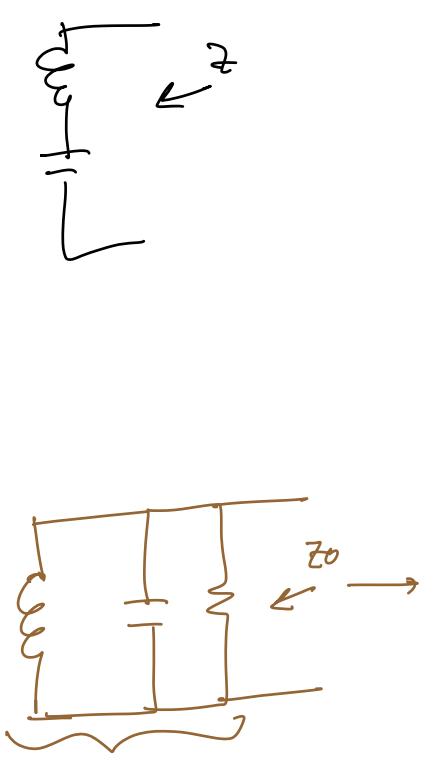
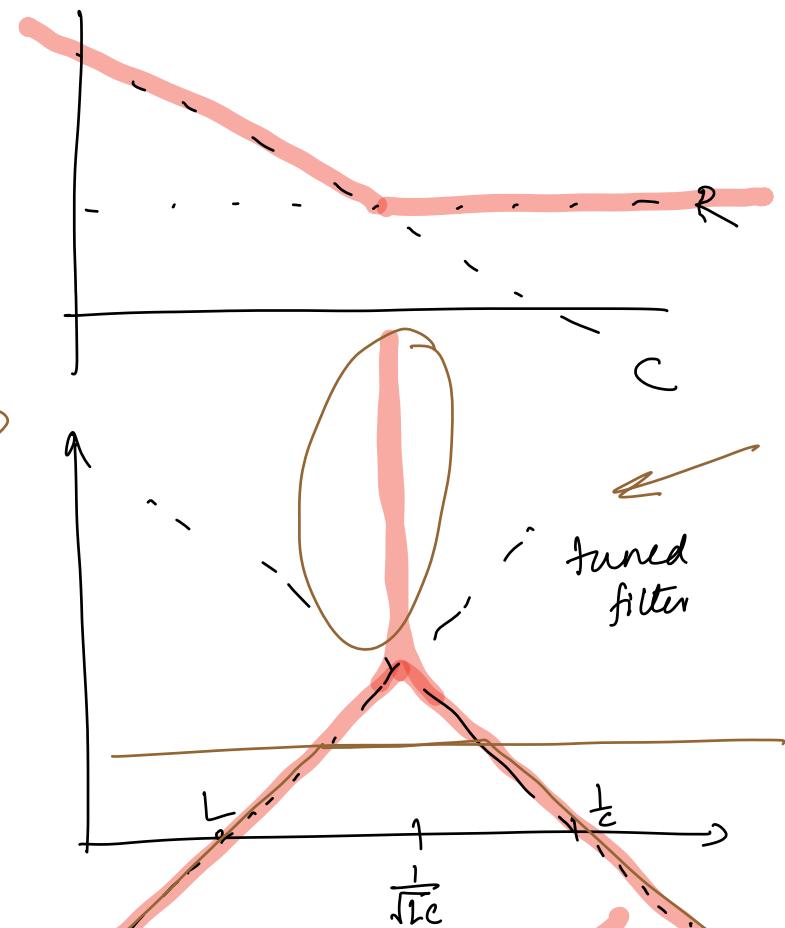
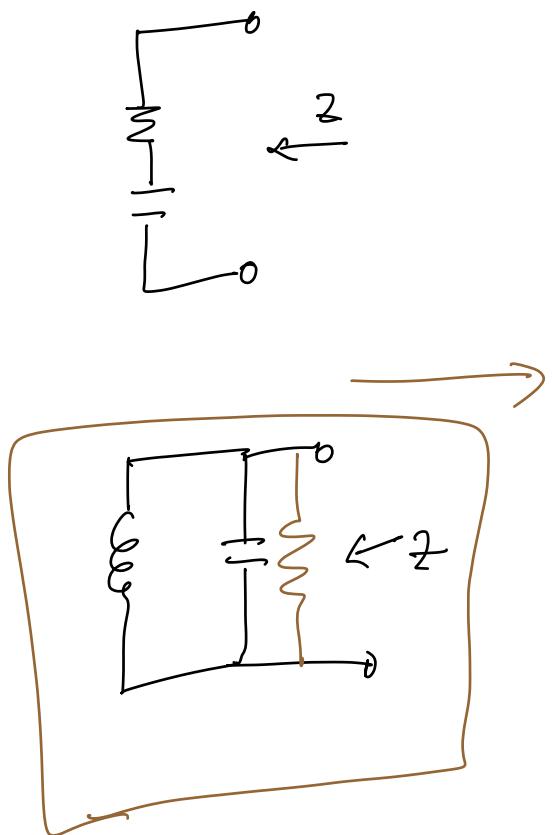


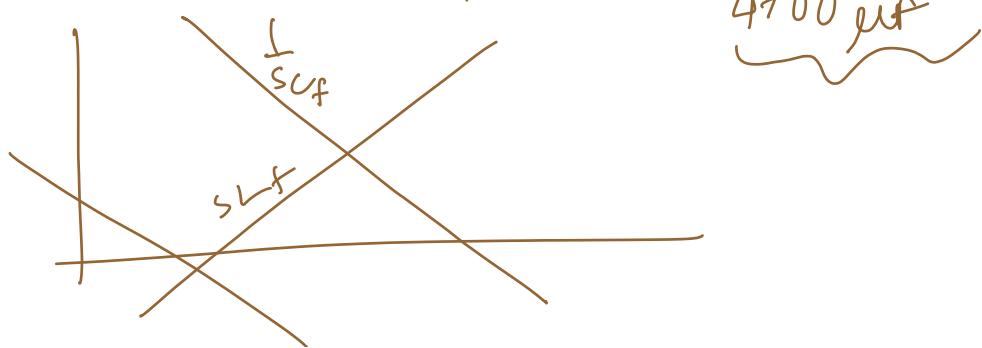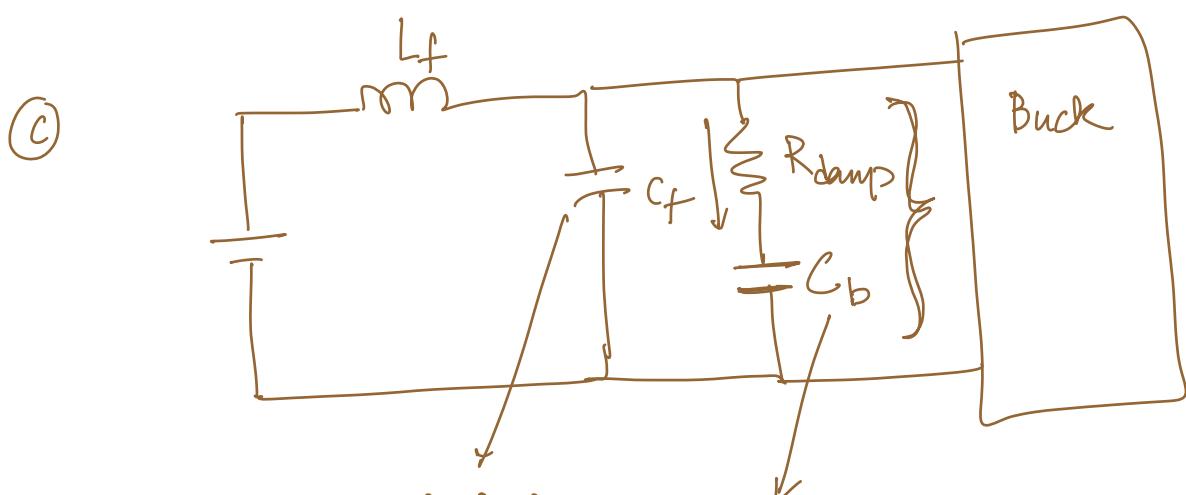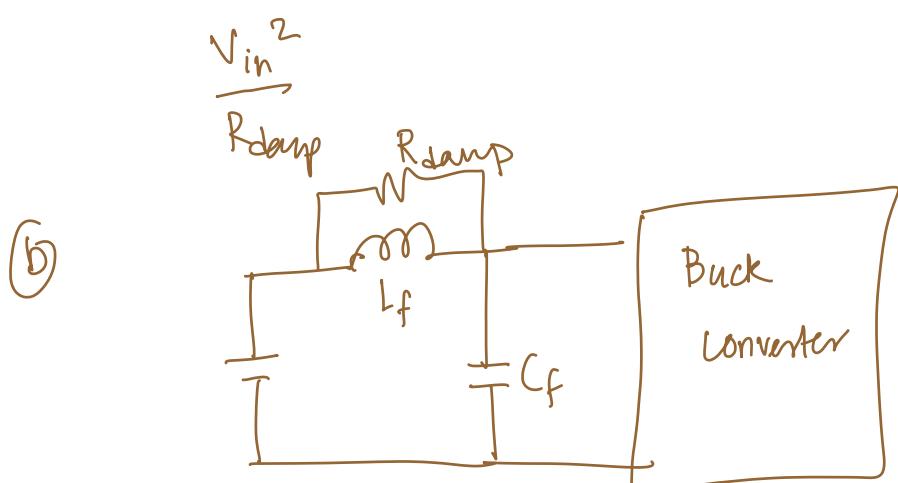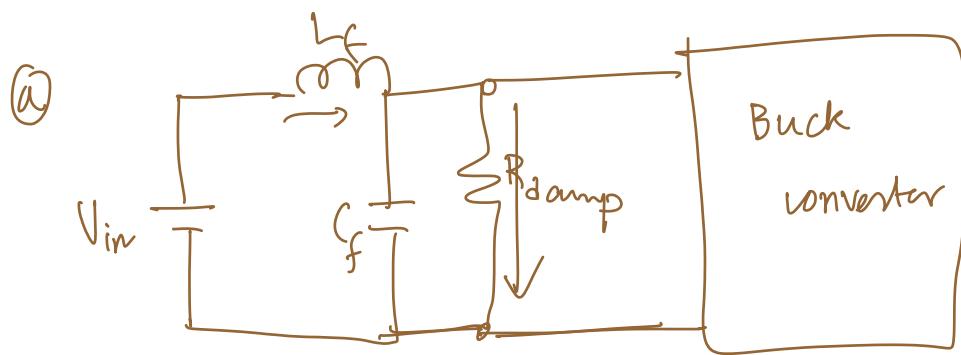

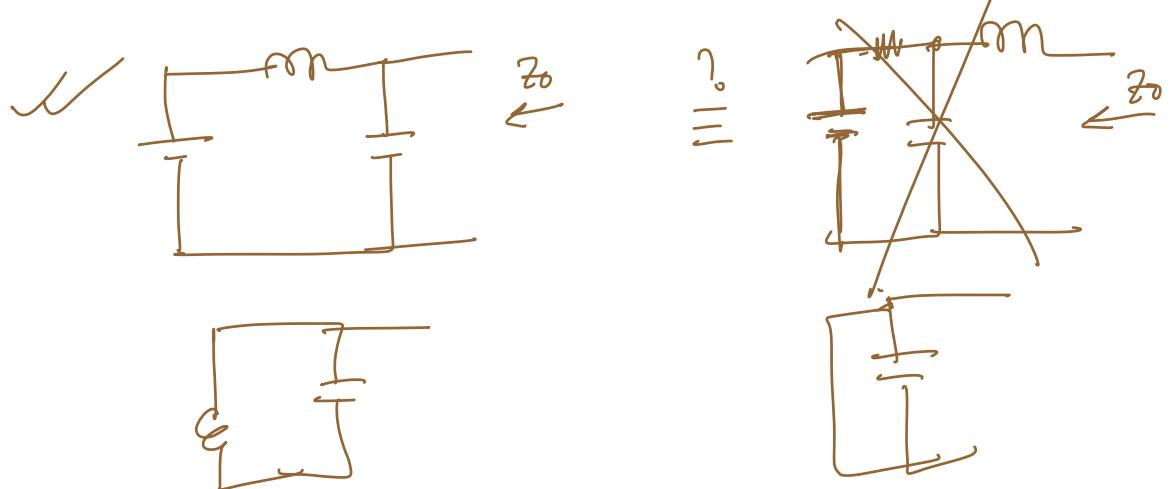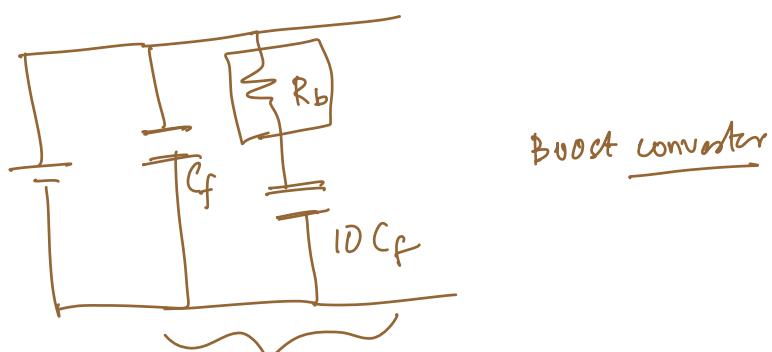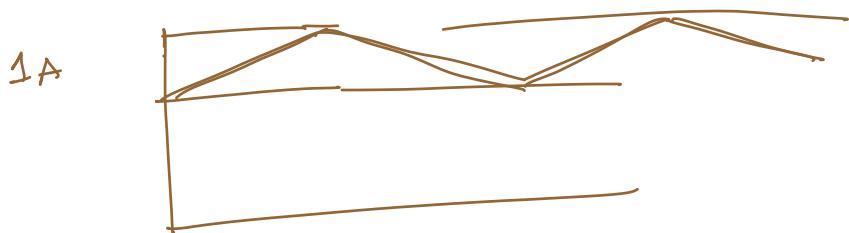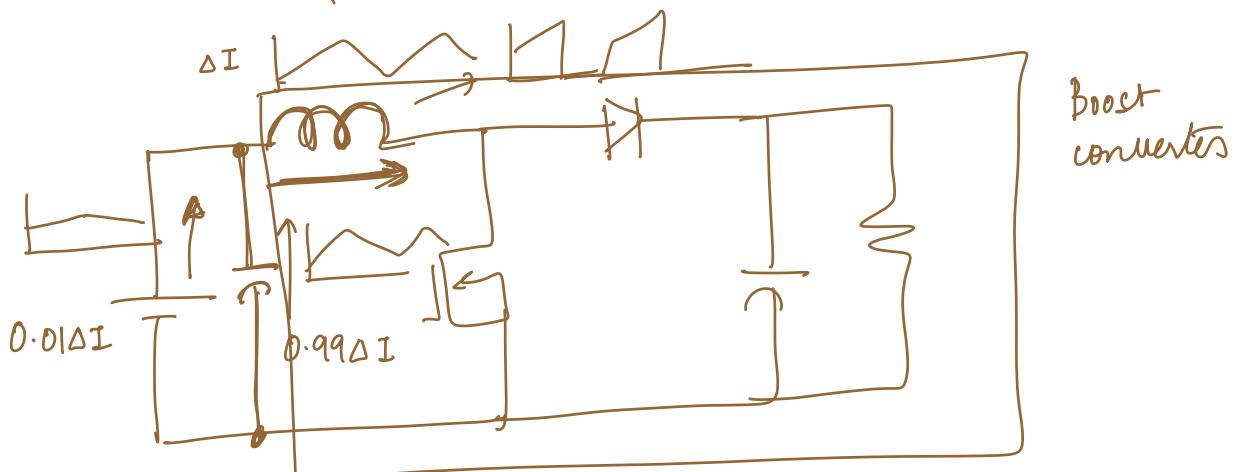

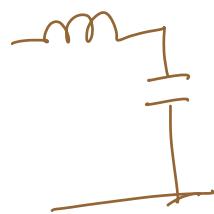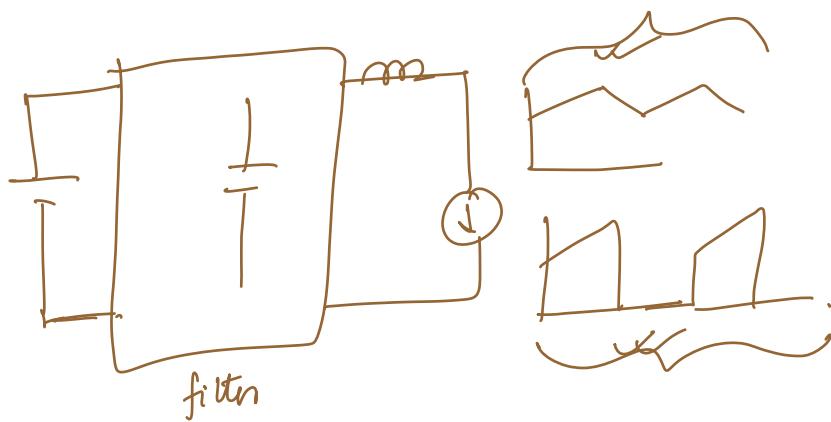


5:40pm

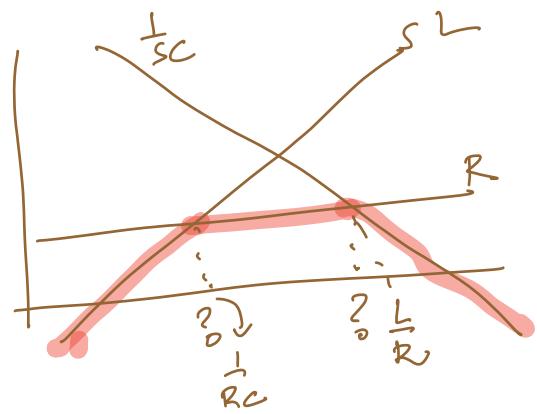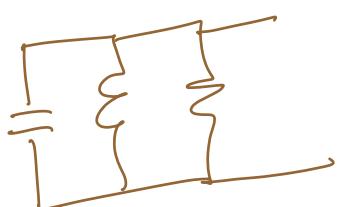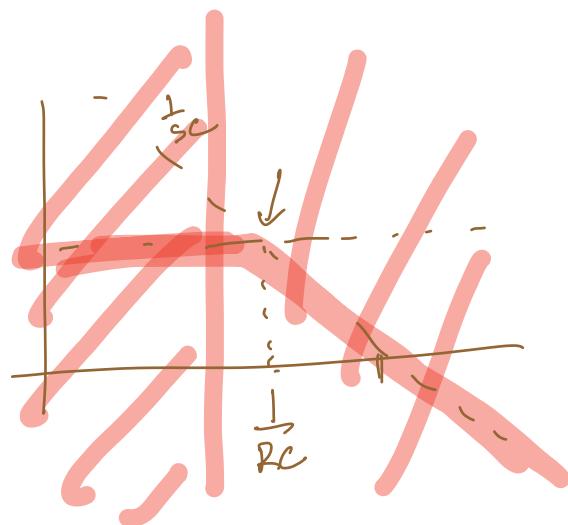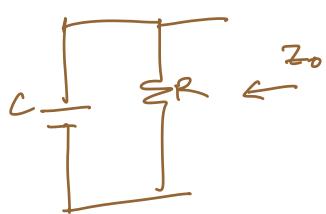

$$\textcircled{1} \quad \text{CC.} \quad \frac{1}{1+s\tau_i}$$

Boost converter :

After implementing feed forward

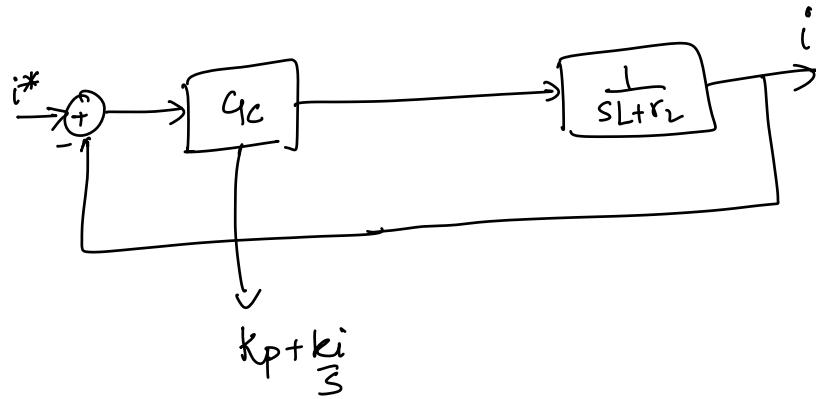

$$l = \underbrace{\frac{w_{gi}}{s}}_{\text{Gain}} \quad l = \left(k_p + \frac{k_i}{s} \right) \cdot \left(\frac{1}{sL+r_L} \right)$$

$$\frac{w_{gi}}{s} = \left(\frac{sk_p + \frac{k_i}{s}}{s} \right) \cdot \frac{1}{sL+r_L}$$

$$i^* \xrightarrow{i} i$$

$$i = \frac{l}{1+l} \cdot i^* = \frac{\frac{w_{gi}}{s}}{1+\frac{w_{gi}}{s}} i^*$$



$$i = \frac{w_{gi}}{s+w_{gi}} i^* \quad w_{gi} = \frac{w_{sw}}{10}$$

$$i = \frac{1}{s/w_{gi} + 1} i^* \quad = \frac{2\pi \cdot f_s}{10}$$


$$= \frac{2\pi \cdot 10 \times 10}{10}$$

$$\dot{i}^* = \frac{1}{s\zeta_i + 1} i^* \quad \leftarrow \text{Closed loop T.F.}$$
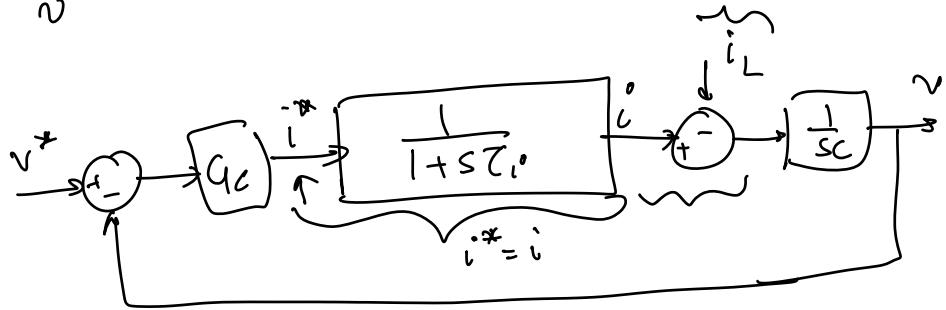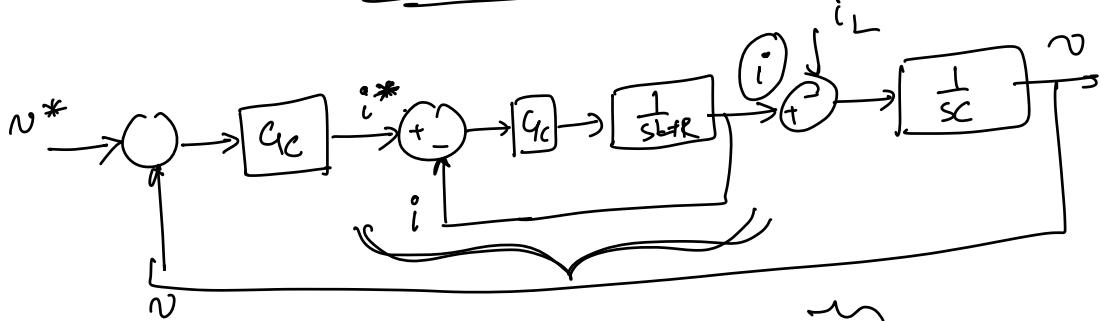
$$\tau_i = \frac{1}{\omega_{gi}} = \frac{10}{\omega_s w}$$





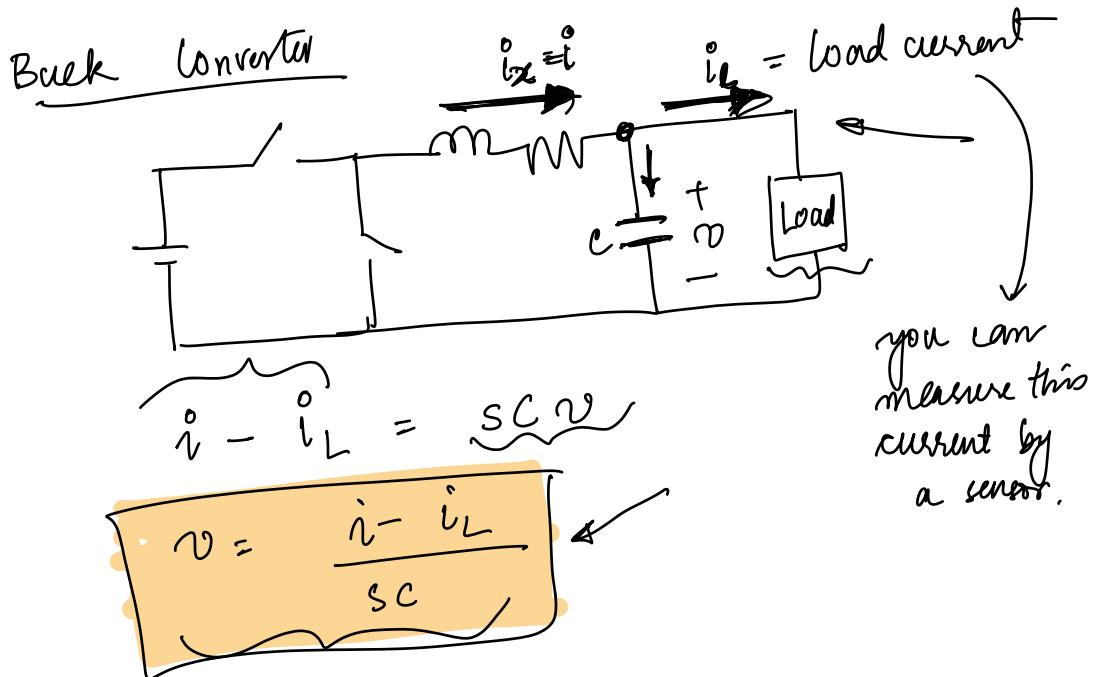inner current control \rightarrow activation signal = d (duty ratio)
 outer voltage " \rightarrow " $v = i^*$ (inner CC reference)



Boost Converter
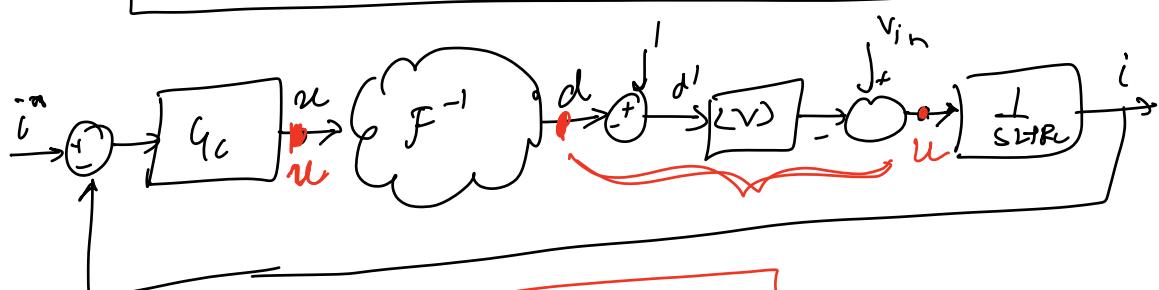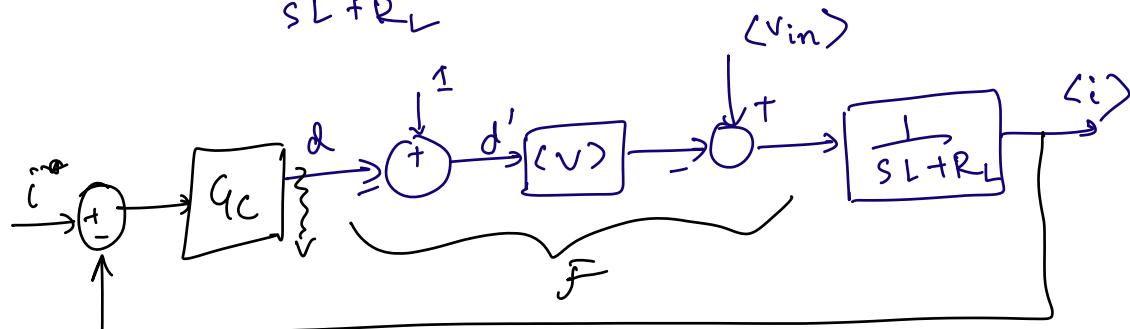
$$n, \quad \frac{(v_{in}) - (\nu)d}{sL + R_L} = \langle i \rangle$$



$$u = v_{in} - (1-d)v \quad F$$


$$u = V_{in} - (1-d)V$$

$$u - V_{in} = -(1-d)V$$

$$-(u - V_{in}) = (1-d)V$$

$$-\frac{(u - V_{in})}{V} = 1-d$$
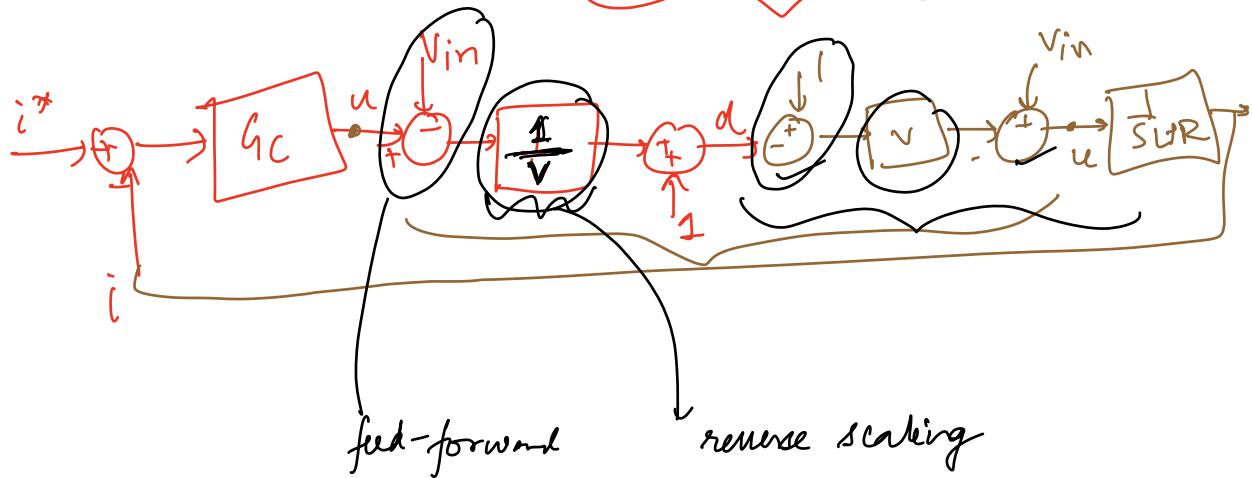
$$\therefore d = 1 + \frac{(u - V_{in})}{V}$$



$\max (\text{anode voltage}, 0.001)$