


Lecture 19

HW 6 (final few) is due Thursday 10th March
finals will be released after that.

Suggestion : Use the HW solution - simulation,
derivation etc for finals.

① Circuit Equivalents for controller.


Buck converter

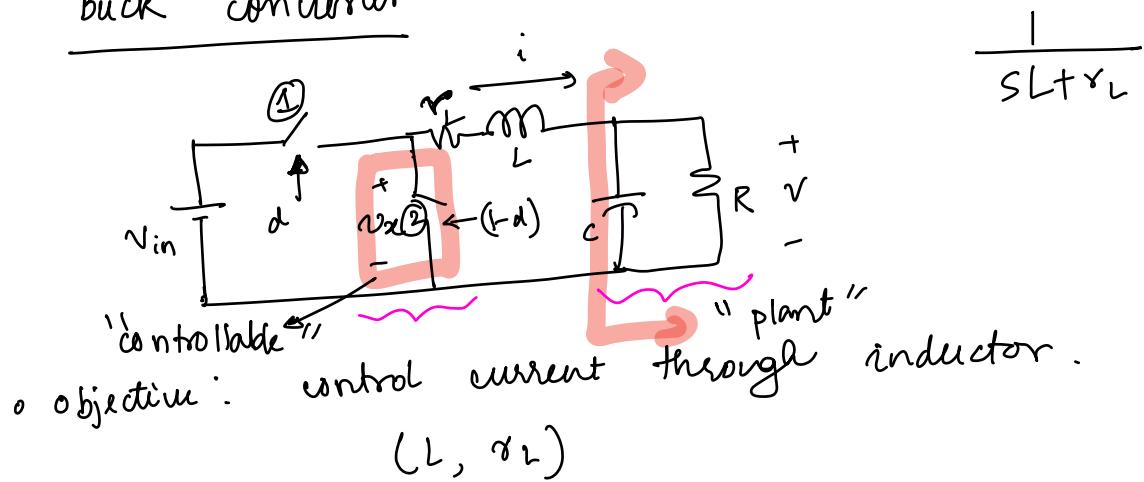


$$v_x = v_{in} \quad (d=1) \leftarrow \text{during } ① \text{ ON}$$


$$v_x = 0 \quad (d=0) \leftarrow \text{during } ② \text{ ON}$$
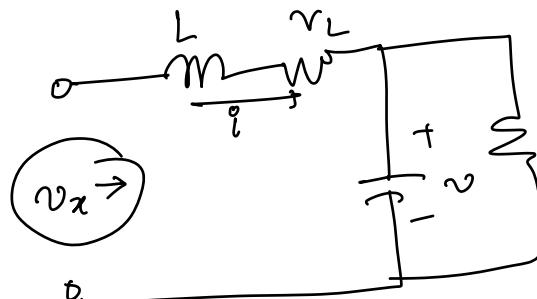
$$\therefore \langle v_x \rangle = v_{in} \cdot d + 0 \cdot (1-d) = v_{in} \cdot d$$




$$\frac{v_x - v}{sL + r_L} = i$$

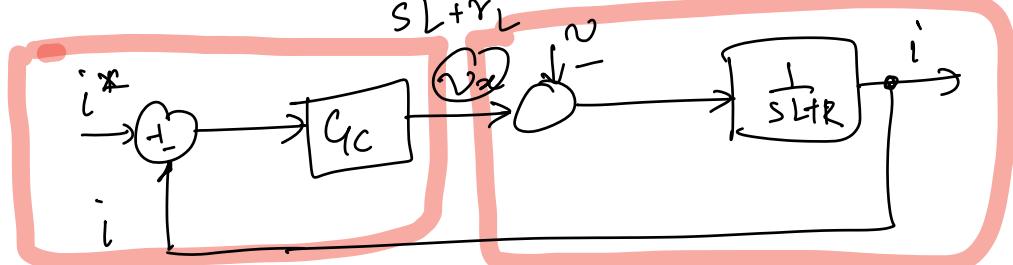

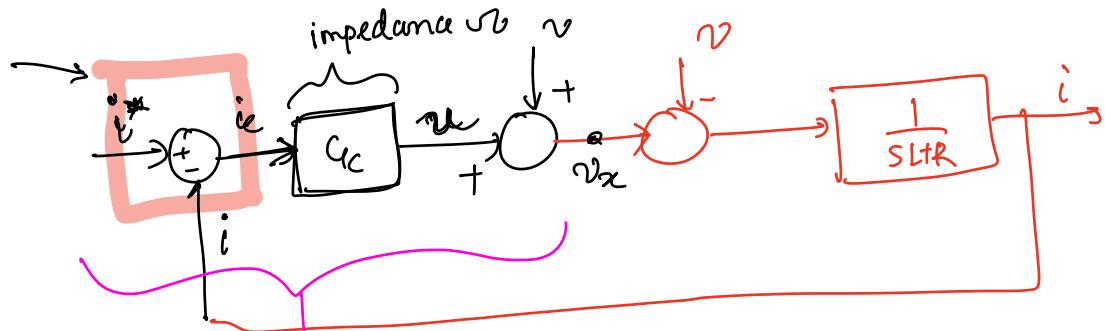

controller implementation.

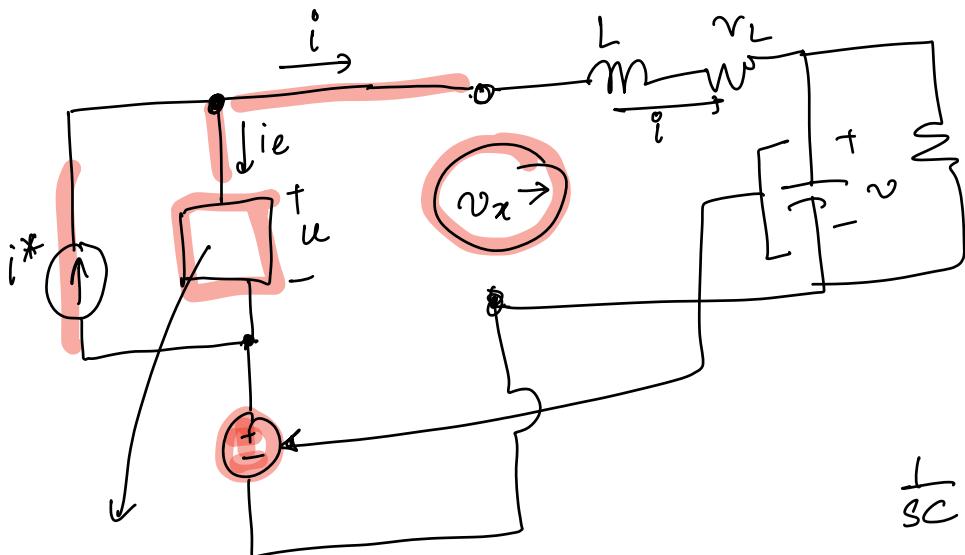

$$(K_p + \frac{K_i}{s}) i_e = u_{\text{voltage}}$$

voltage

$$\frac{K_i}{s} = \text{impedance}$$

K_p = resistor


$$I = C \frac{dU}{dt}$$

$$\frac{K_i}{s} i_e = u_{\text{voltage}}$$


$$I = SC \cdot V$$

$$\frac{K_i}{s} \cdot i_e = u_i \Rightarrow$$

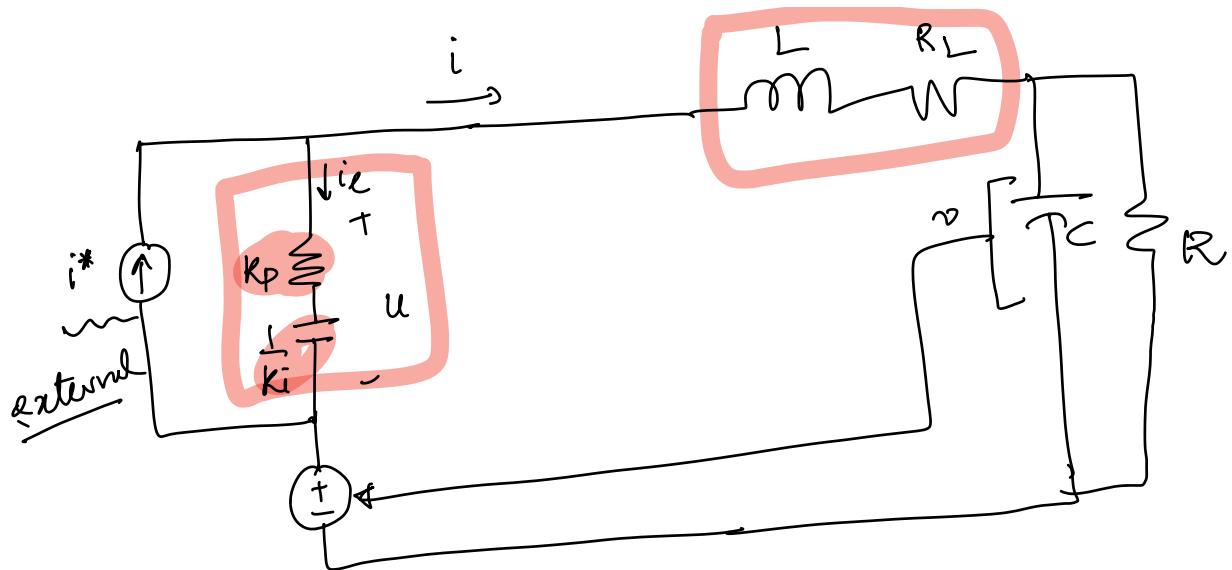
$$i_e = s \cdot \left(\frac{1}{K_i} \right) \cdot u_i$$



voltage control

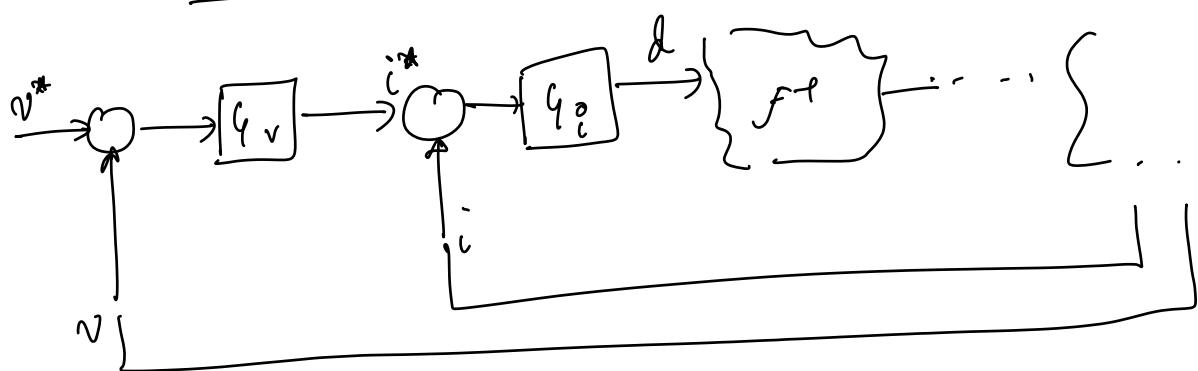


Buck converter

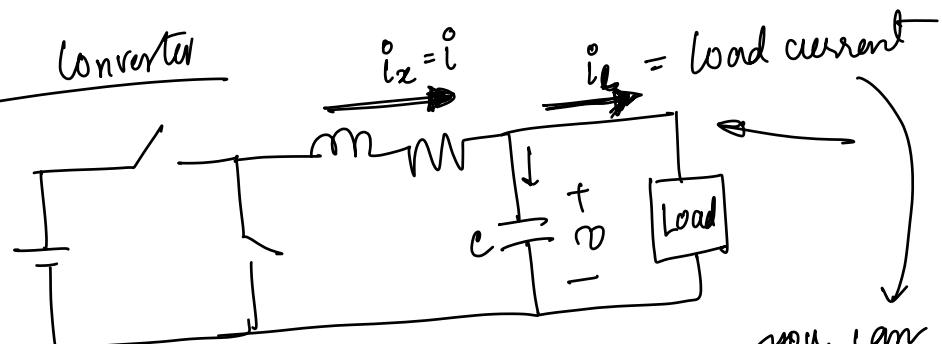





$$i - i_L = SCv$$

$$v = \frac{i - i_L}{SC}$$

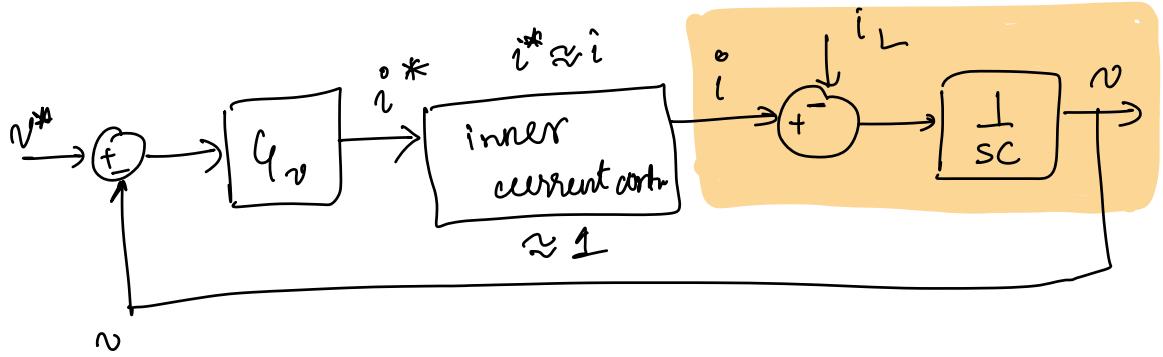
you can
measure this
current by
a sensor.



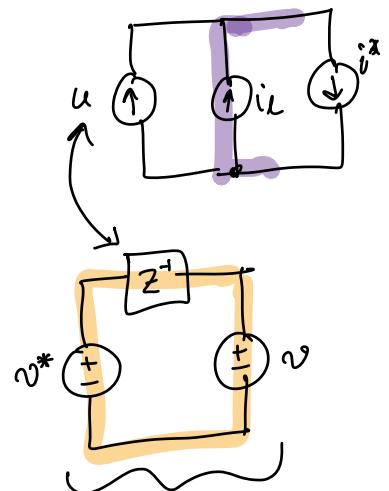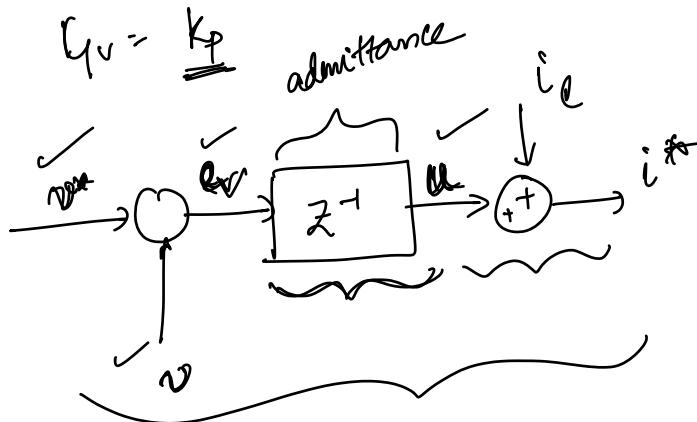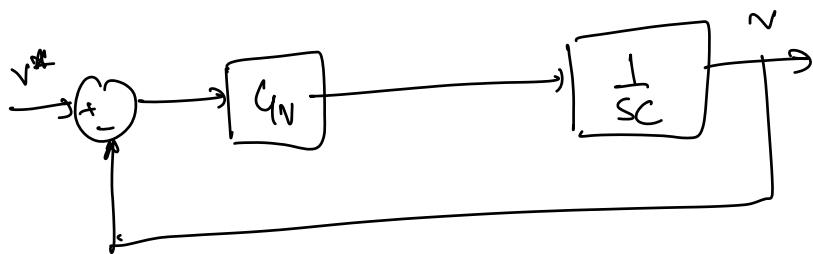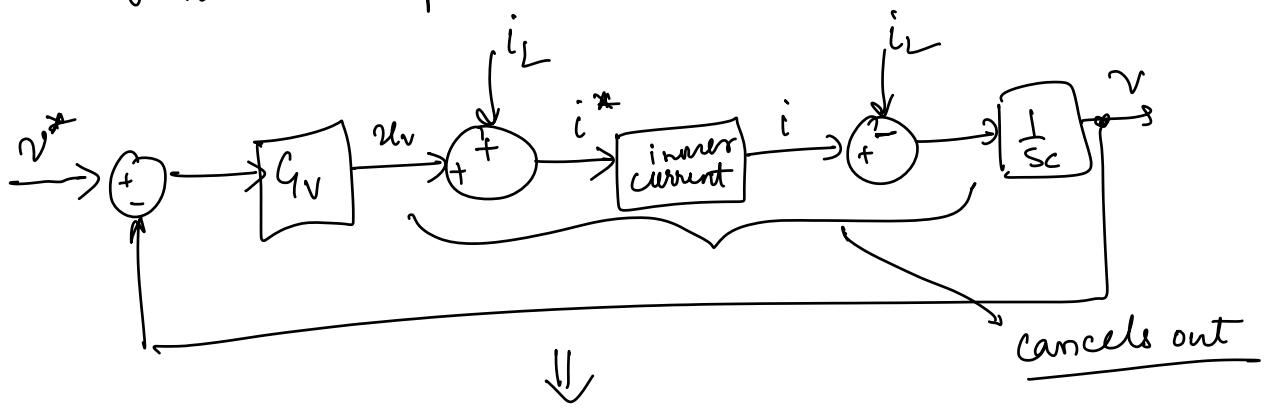If I want my plant transfer function to be $\frac{1}{sC}$
I need to implement feed forward to cancel i_2




Circuit Equivalent

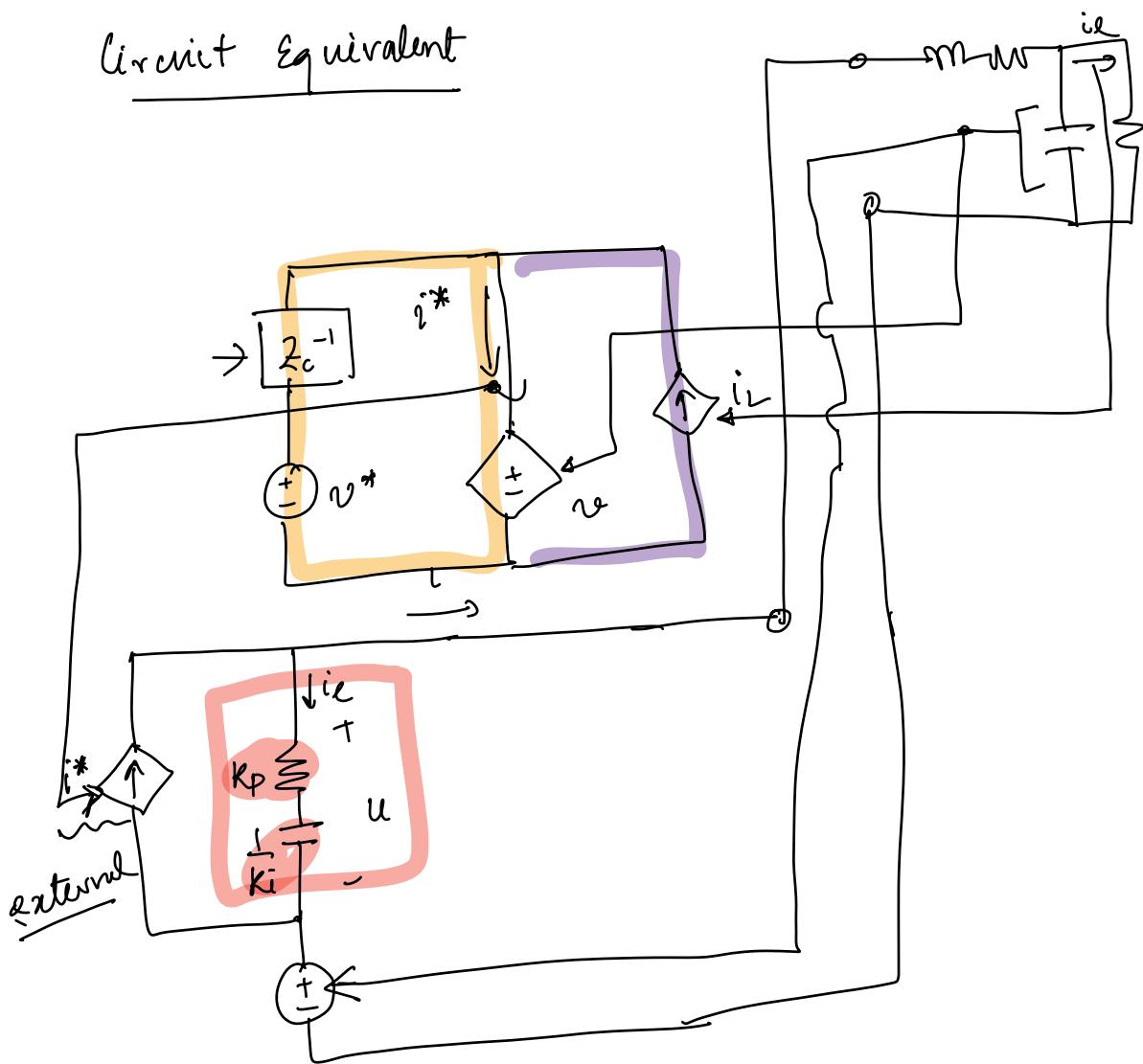



$$u = Z^{-1} \cdot ev$$

$$u = \left(K_{PV} + \frac{K_{IV}}{s} \right) ev$$

↙ current ↴ admittances

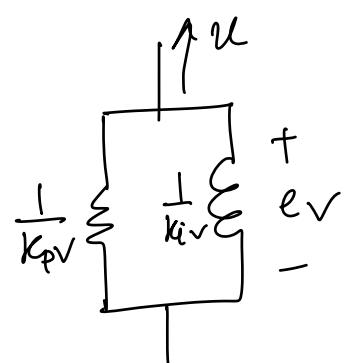

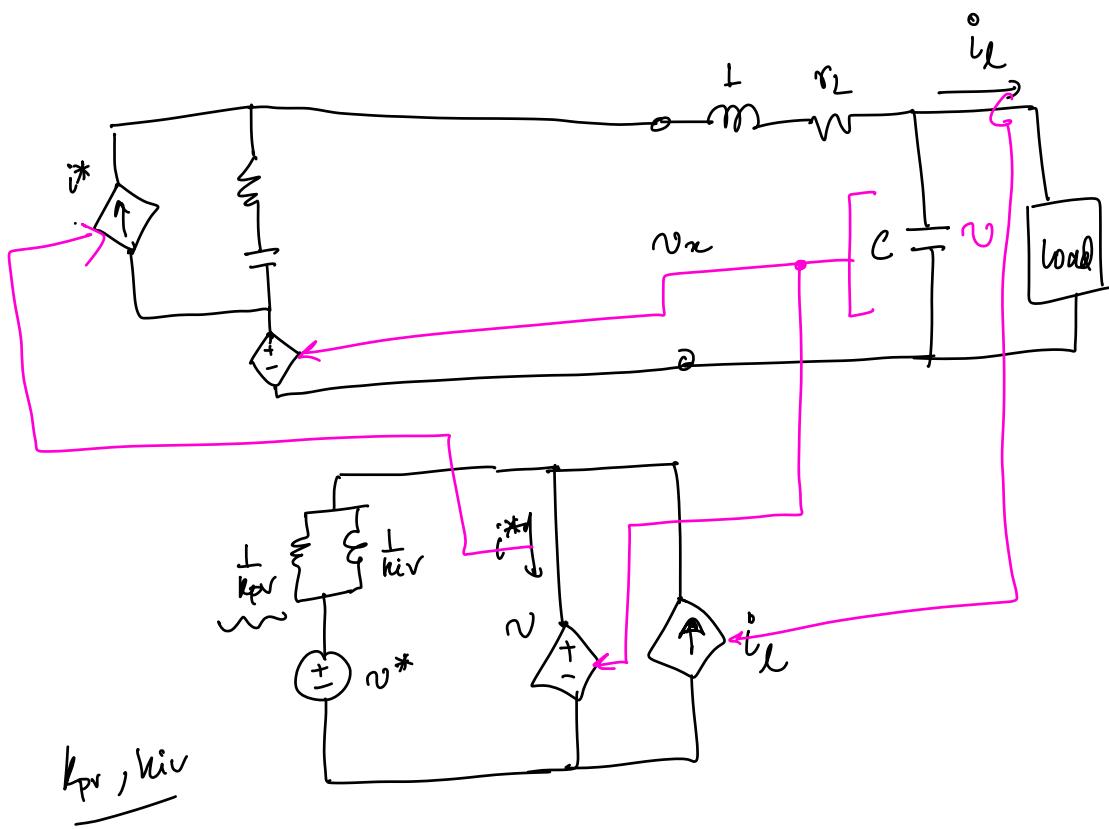

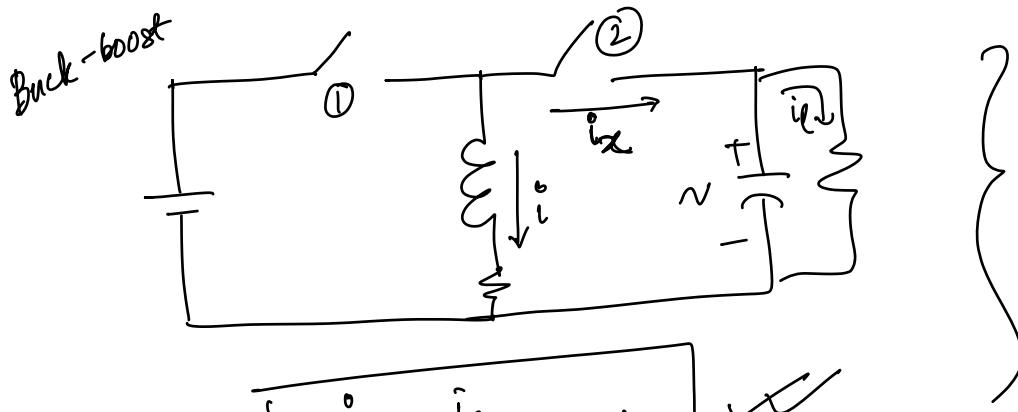


$$\frac{i_x - i_e}{sc} = n \quad \checkmark$$

when ① is ON, $i_m > 0$
 ② is ON, $i_x = -i_L$

$$\begin{aligned}\therefore \langle i_x \rangle &= 0 \cdot d + (-i_L) \cdot d' \\ &= -i_L d'\end{aligned}$$

$$\frac{-i_L d' - i_e}{sc} = n$$

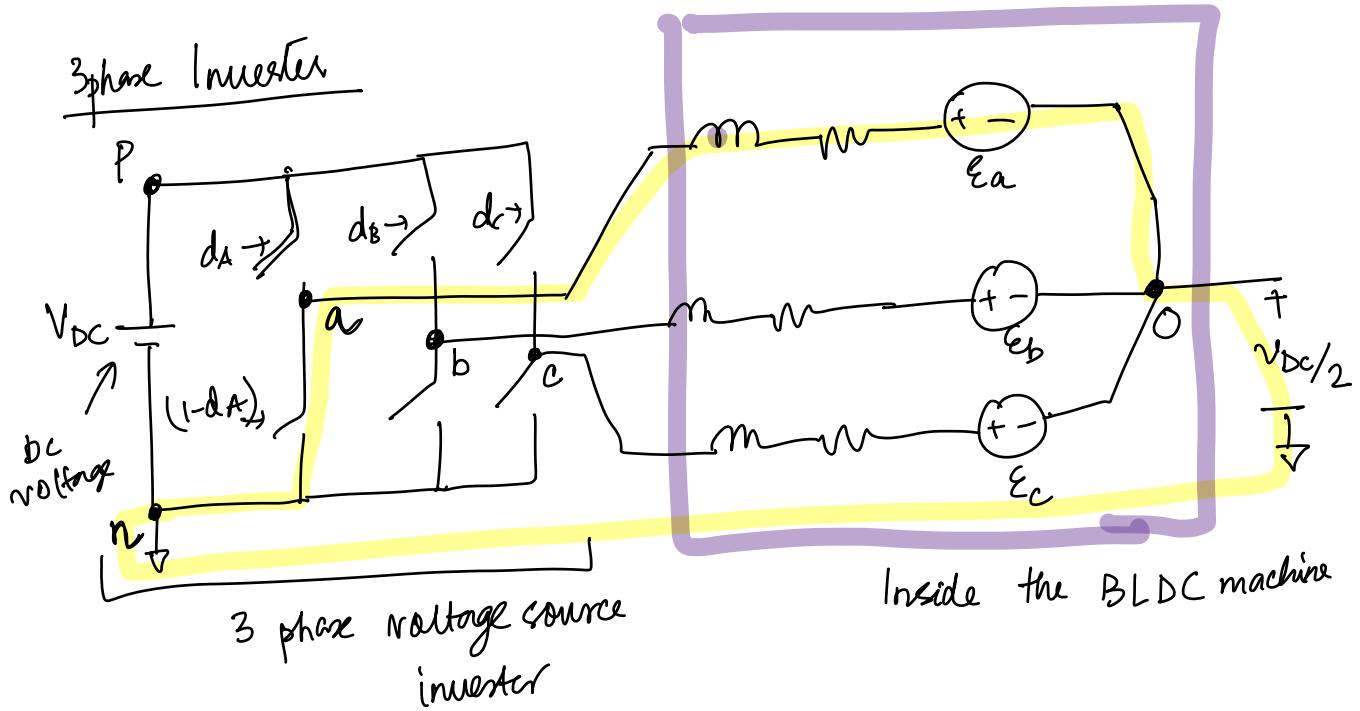

$$d_A = \underbrace{0.5 + 0.5 m \sin \omega t}_{0 < d_A < 1}$$

$$d_B = 0.5 + 0.5 m \sin(\omega t - 2\pi/3) \quad -1 < m < 1.$$

$$d_C = 0.5 + 0.5 m \sin(\omega t - 4\pi/3)$$




$$\langle v_{an} \rangle = d_A \cdot v_{ac} + (1-d_A) \cdot 0$$



$$= (0.5 + 0.5 m \sin \omega t) v_{dc}$$

$$= 0.5 v_{dc} + 0.5 m \sin \omega t v_{dc}$$

$$\langle v_{an} \rangle = \langle v_{ao} \rangle + \langle v_{on} \rangle$$
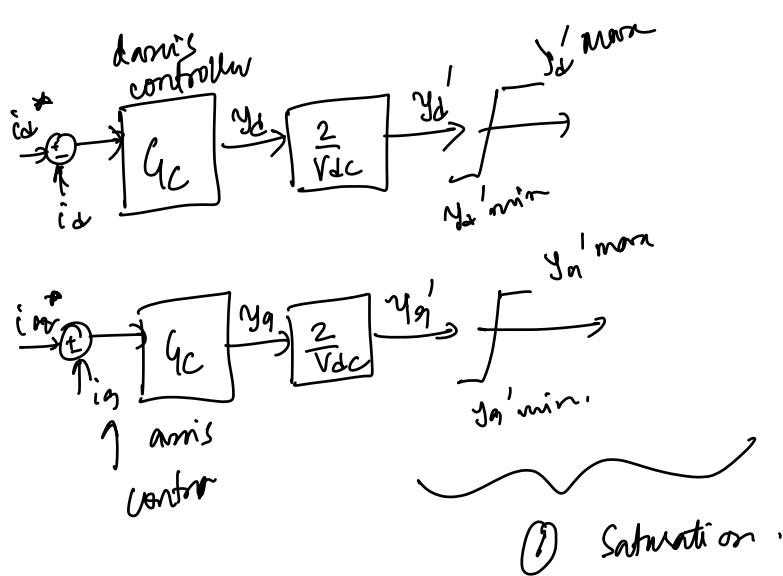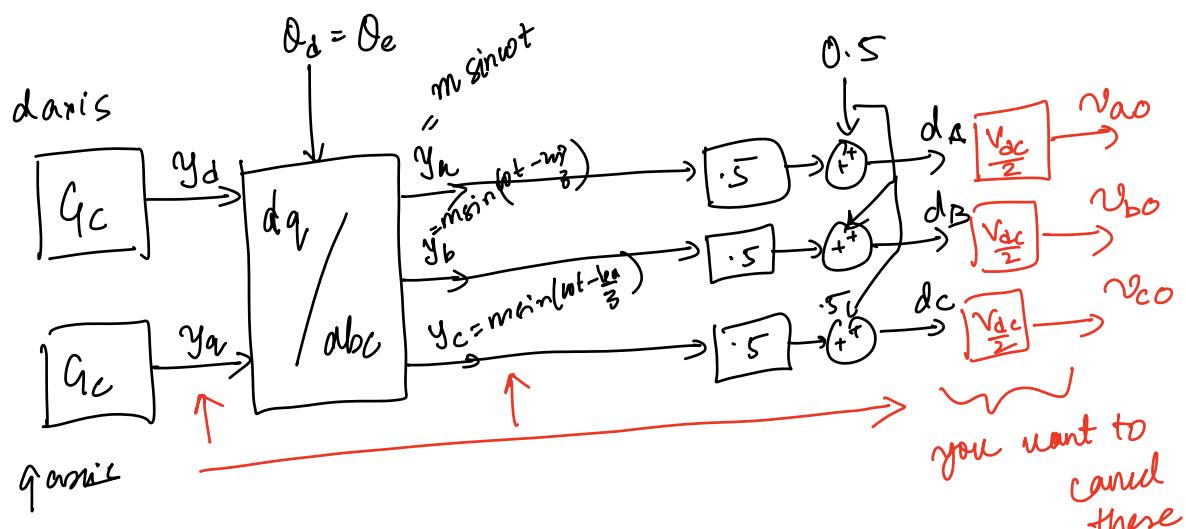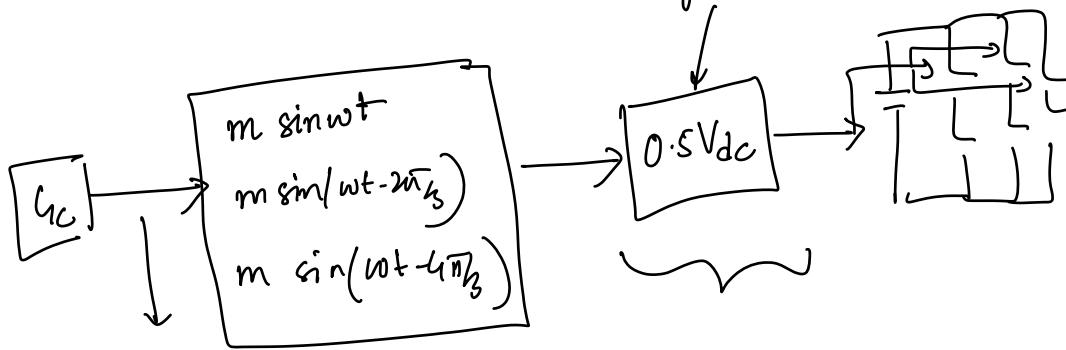
$$\langle v_{ao} \rangle = 0.5 m \sin \omega t V_{dc} \text{ gain due to inverter}$$



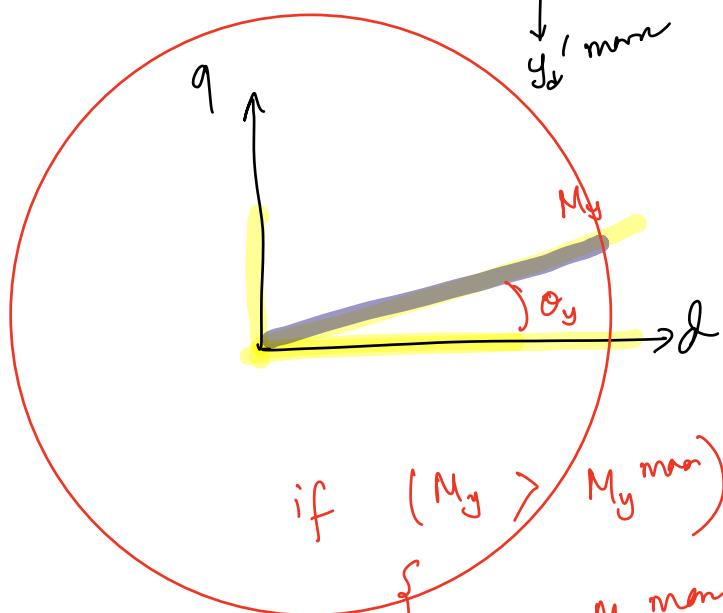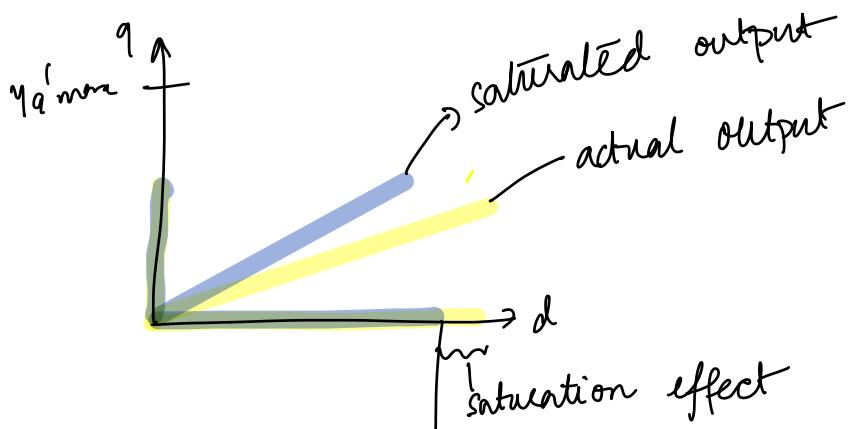

$$M_y = \sqrt{y_d'^2 + y_q'^2}$$



$$\theta_y = \tan^{-1} \frac{y_q'}{y_d'}$$


if $(M_y > M_y^{\text{max}})$


$$\left\{ \begin{array}{l} M_y = M_y^{\text{max}} ; \\ \end{array} \right.$$


O/P: $y_d'' = M_y \cdot \cos \theta_y$

$$y_q'' = M_y \sin \theta_y$$

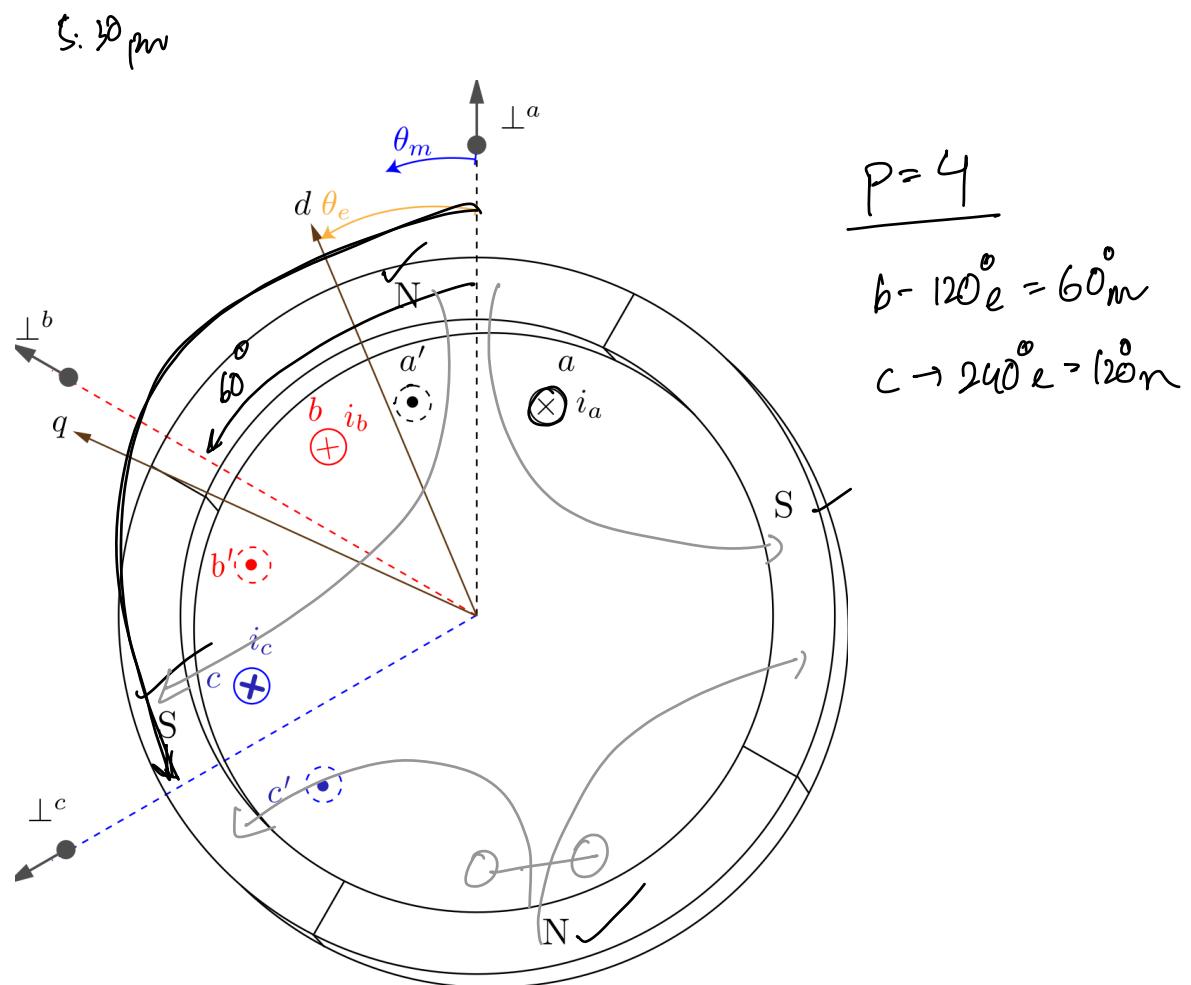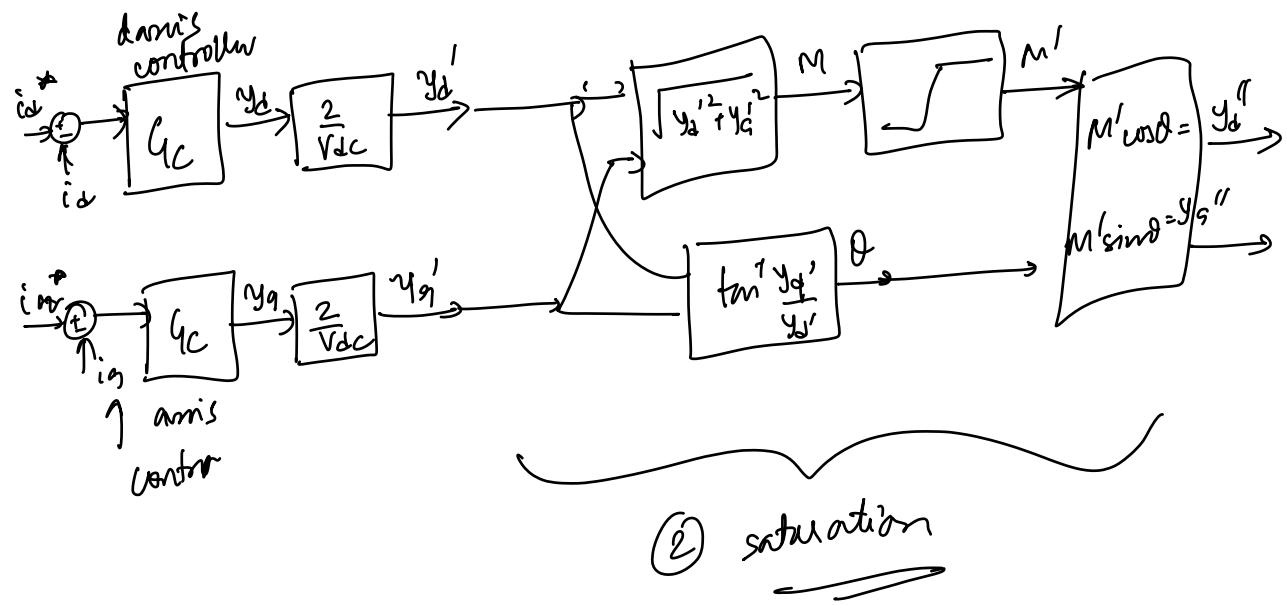

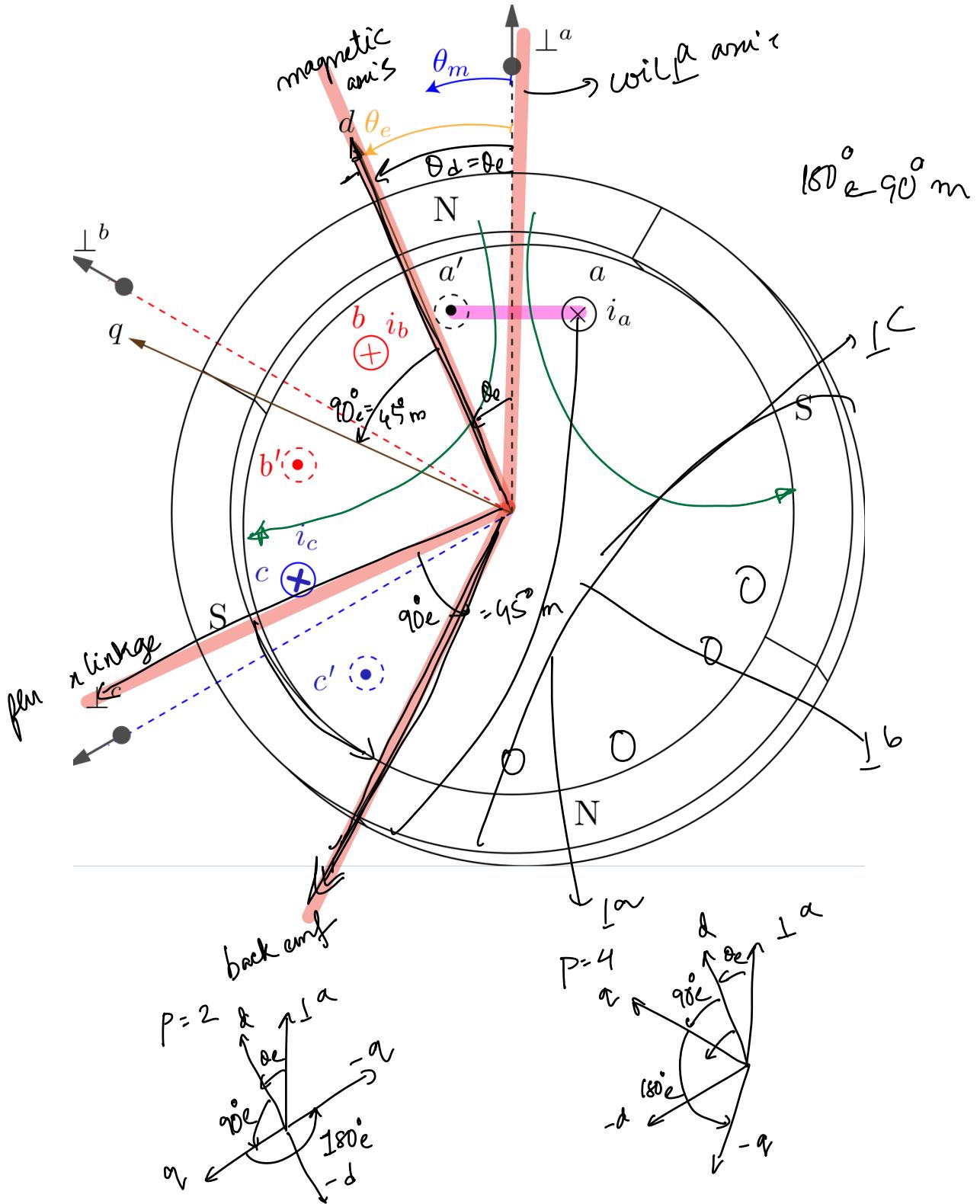


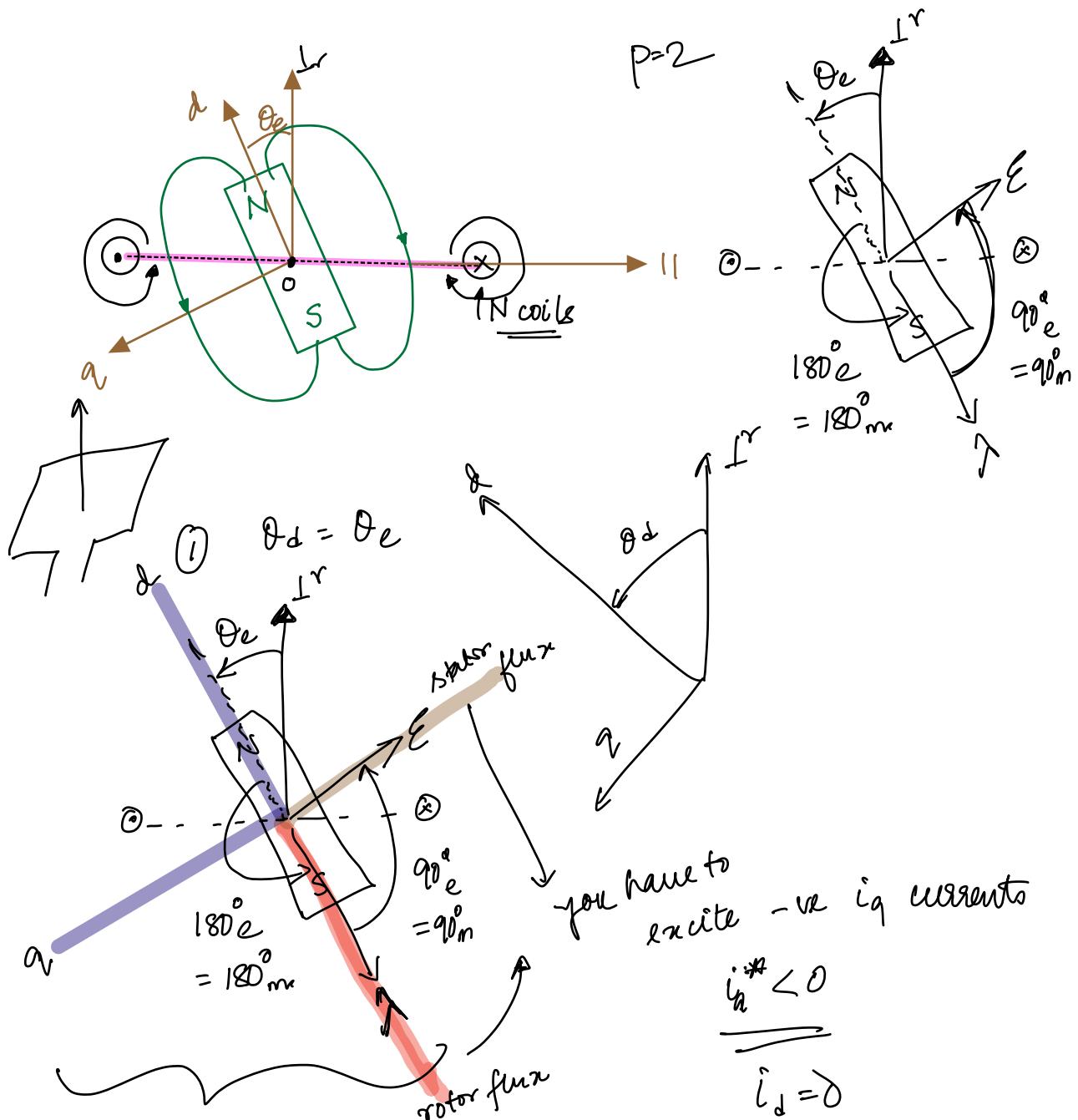

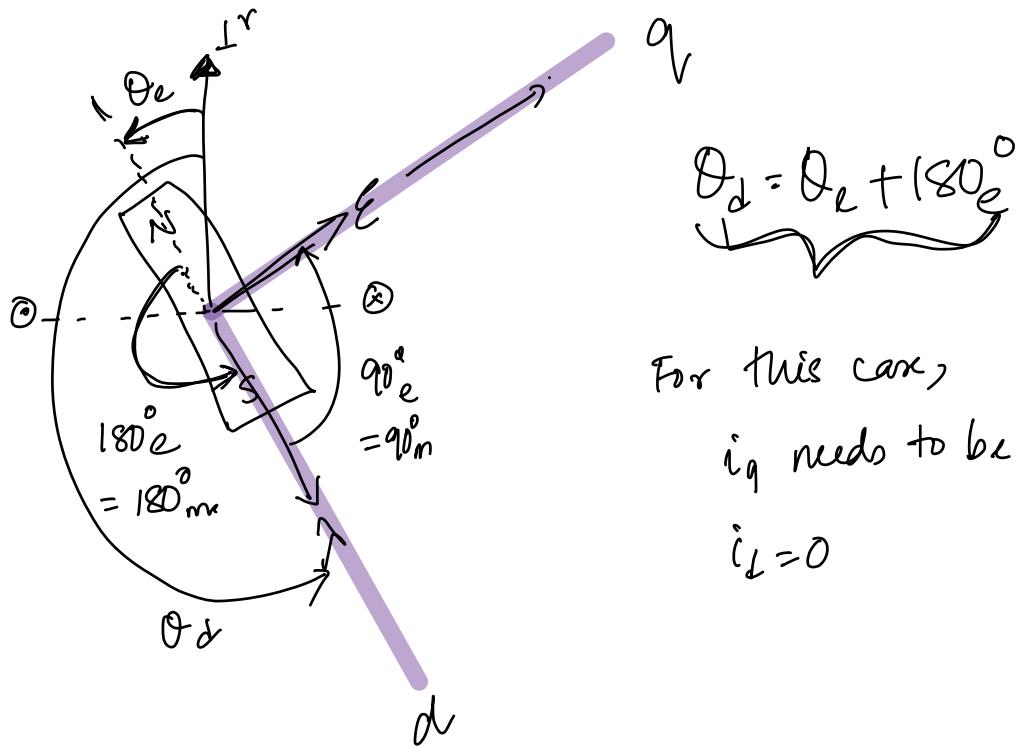

$$\theta_d = \theta_e + 180^\circ$$

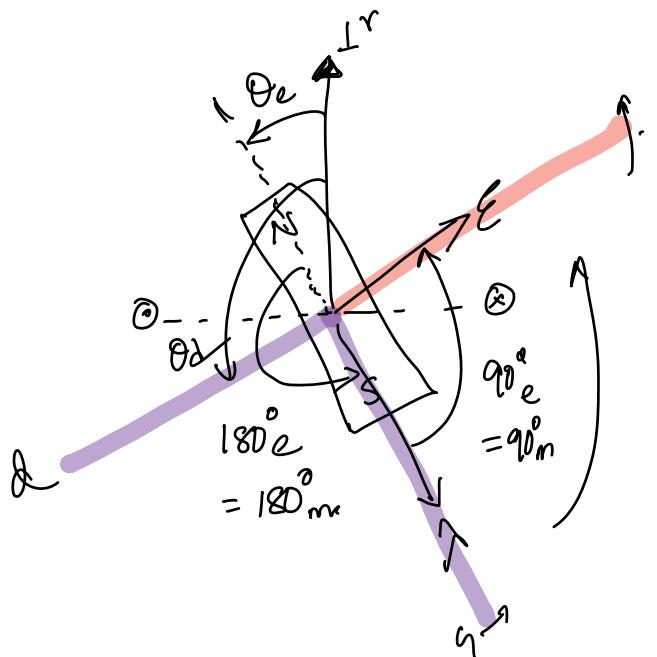
For this case,
 i_q needs to be true
 $i_d = 0$



$$\underline{\theta_d = \theta_e + 90^\circ}$$


i_d^* L-ve

$$\underline{i_q^* = 0}$$

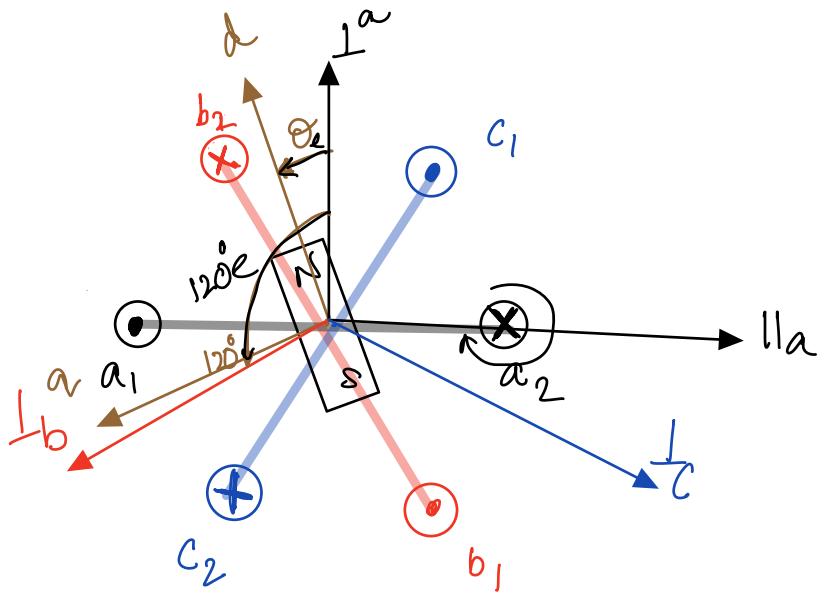


a_1 a_2


correct connection

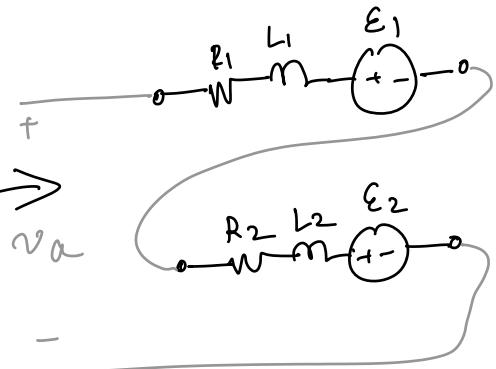

a'_1 a'_2

wrong connection

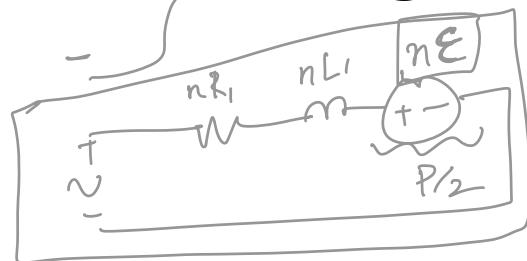

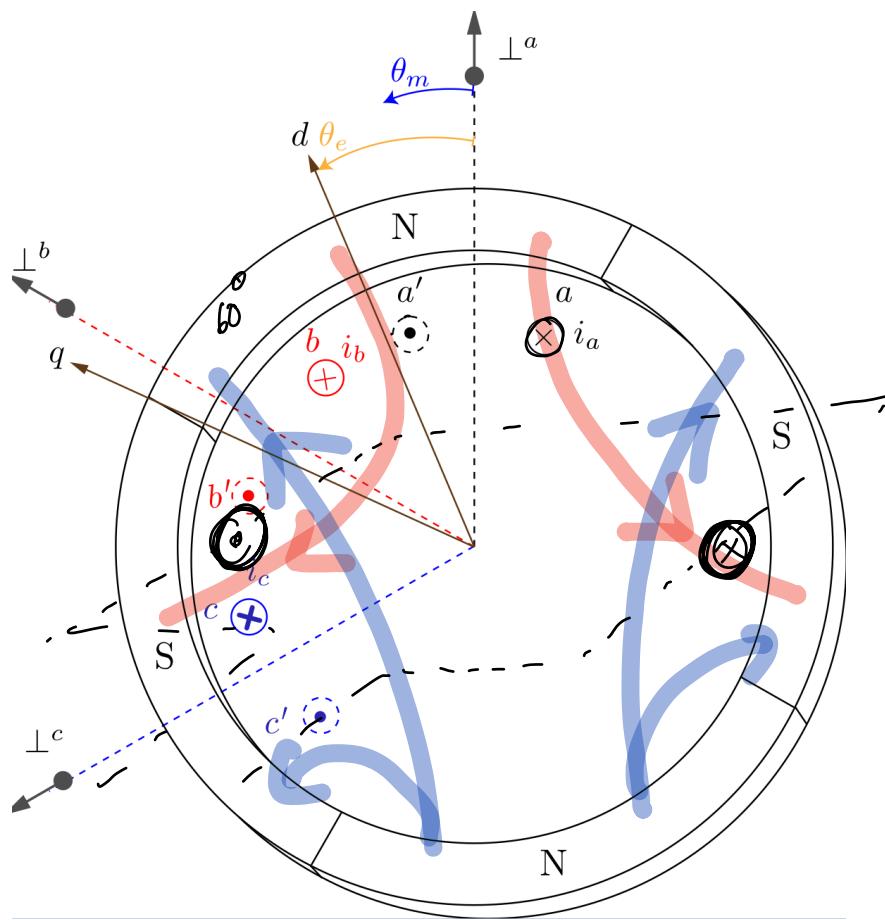

Effect of right half zeros

Minimum phase $s/s = s/s$ that does not have

- delay (e^{-2s})
- Right half zeros
- Right half pole


Non minimum phase $s/s \rightarrow$

$$P_{NMP}(s) = \underbrace{(a-s)}_{\text{right half zero}} \underbrace{P_M(s)}_{\text{minimum ph. transfer func.}}$$


$$= \frac{a-s}{a+s} \cdot \underbrace{(a+s) P_M(s)}_{\text{minimum ph. transfer func.}}$$

$$P_{NMP}(s) = \underbrace{\frac{a-s}{a+s}}_{\text{Blaschke Product}} \cdot P_{MP}(s)$$

$$B.P = \frac{a-s}{a+s}$$

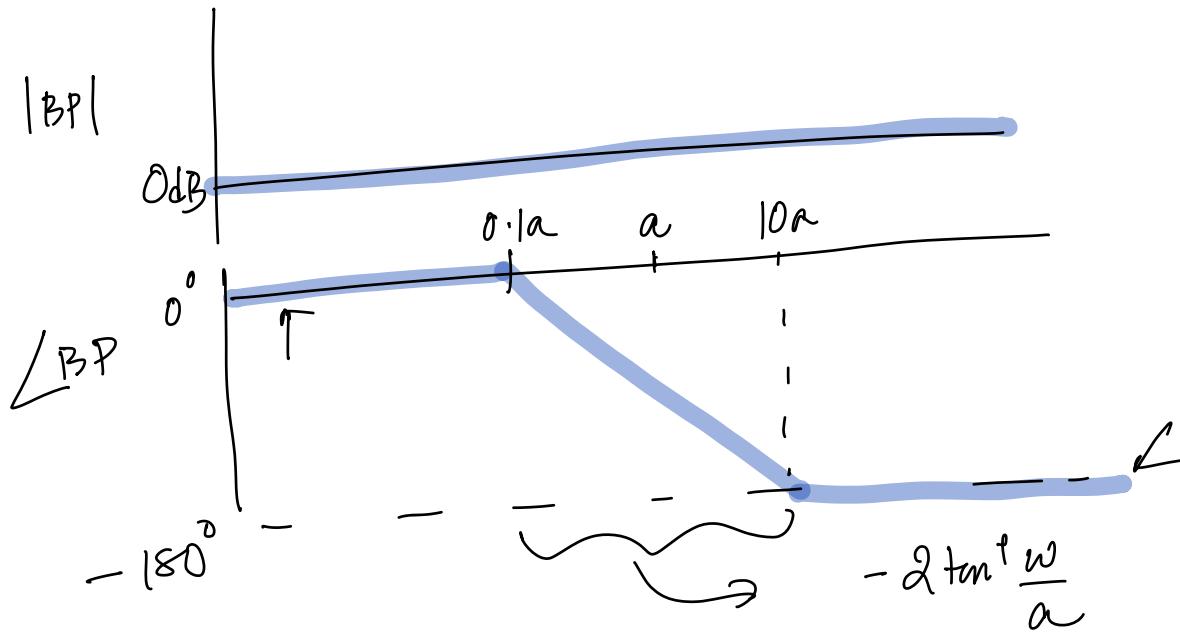

Let's say you have a plant

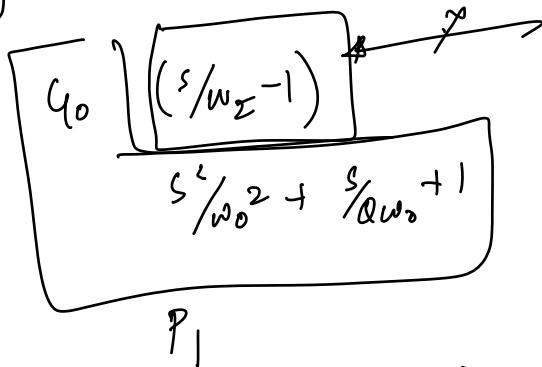


$$\textcircled{1} \quad P_{MP} = (s/w_2 + 1) \cdot P_1$$

\textcircled{2} Design controller for P_{MP} ,

let's call that controller $= C_{MP}$

$$l_{MP} = C_{MP} P_{MP}$$

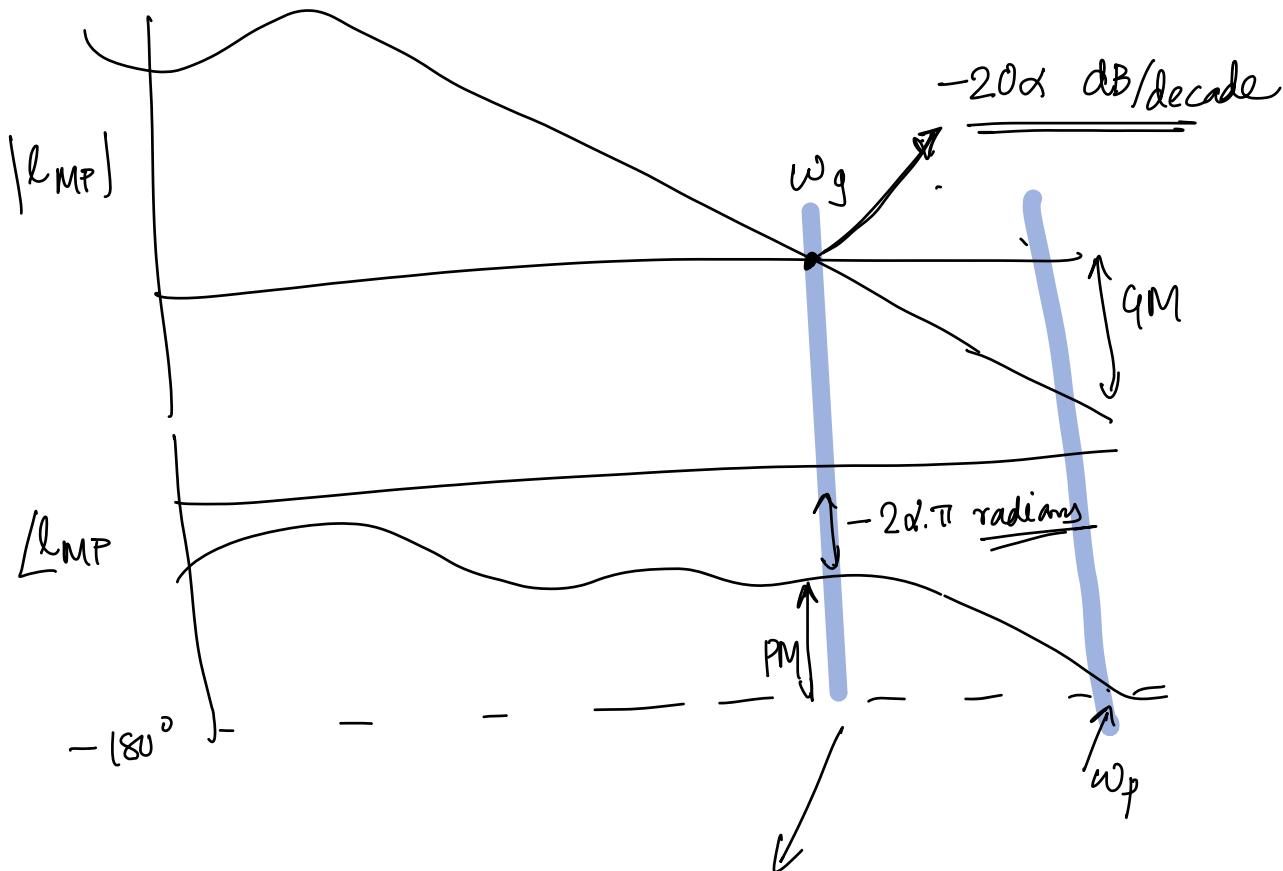


$$\angle L_{NMP} = \angle L_{MP} - 2\tan^{-1} \frac{\omega}{\alpha}$$

At gain crosses over from



$$\begin{aligned} \angle L_{NMP}(\omega_{gc}) &= -2\alpha\pi - 2\tan^{-1} \frac{\omega_{gc}}{\alpha} \\ &= -\pi + PM \end{aligned}$$
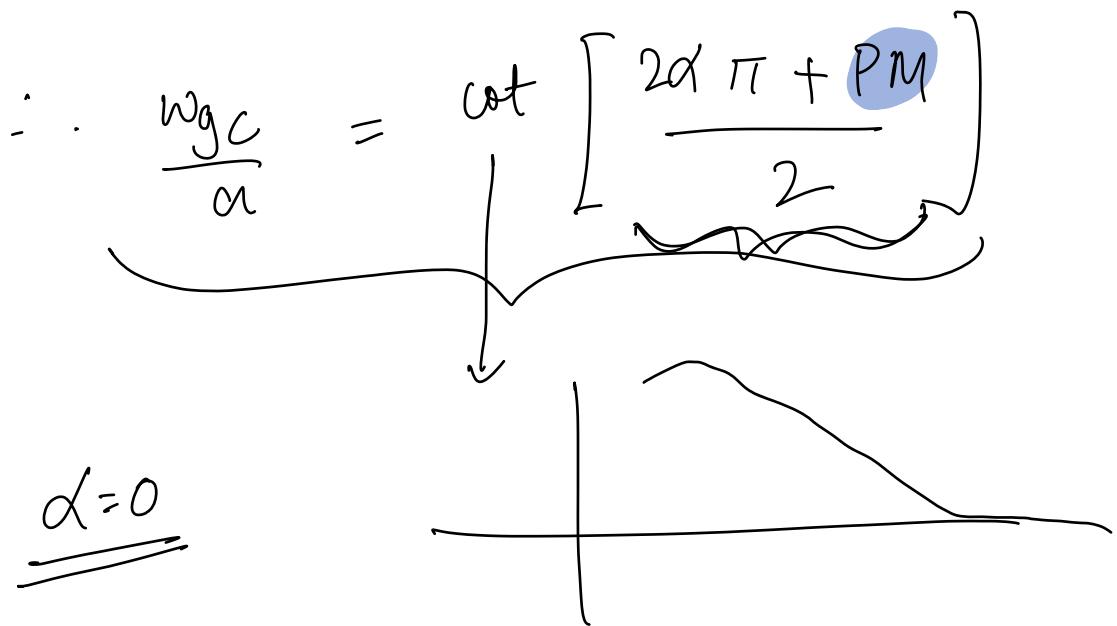
$$\therefore \tan^{-1} \left(\frac{w_{gc}}{\alpha} \right) = \frac{(1-2\alpha)\pi - PM}{2}$$



$$w_{gc} = \alpha \cot \left[\frac{PM}{2} \right]$$

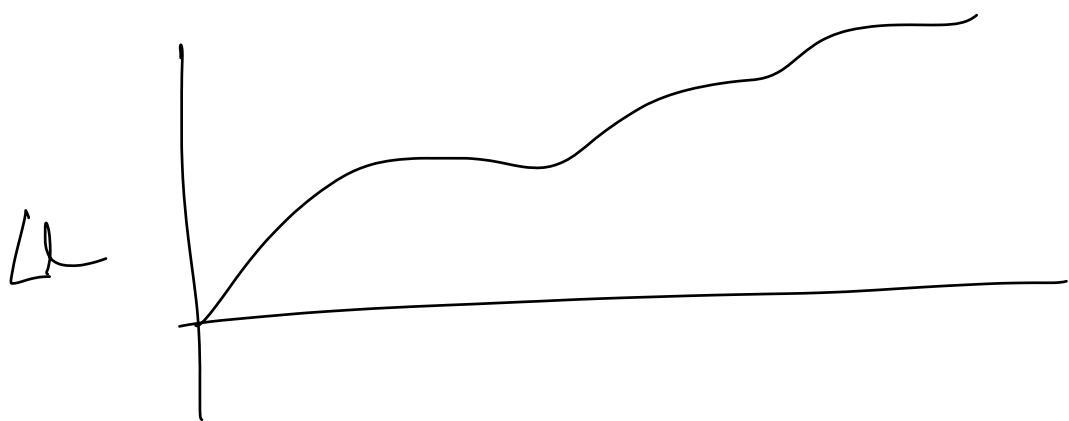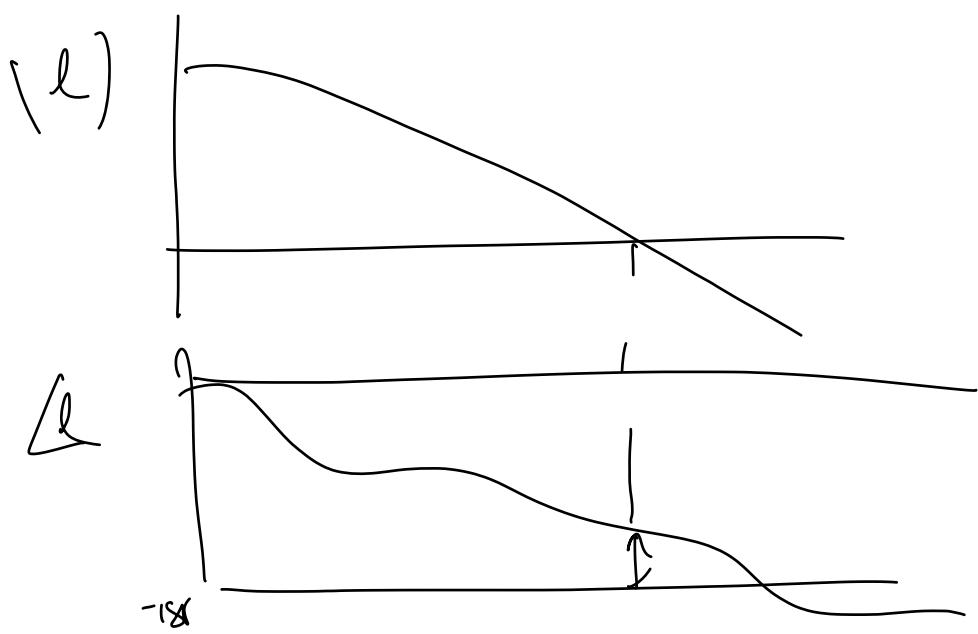Maximum gain crossover freq that you can get for a certain PM.




C
controller P
plant

$$\underline{l} = C \cdot P \rightarrow \text{use this for bode plot, nyquist}$$


$$CLTF = \frac{O/P}{I/P} = \frac{\underline{l}}{1+\underline{l}}$$
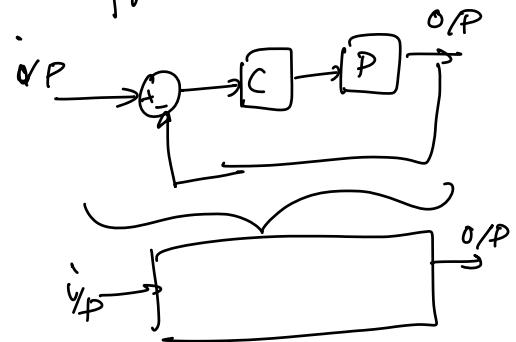
$$CLTF = \frac{\underline{l}}{1+\underline{l}}$$



If $(1+\underline{l})$ has any right half pole

{ p2map(CLTF) Sanity check }

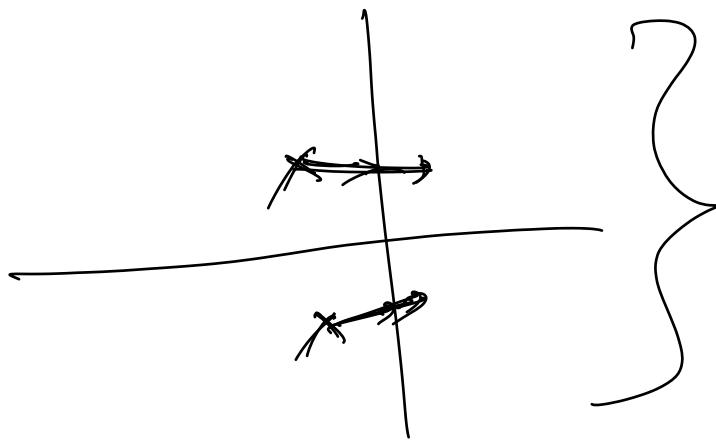

$$l = \frac{n(s)}{d(s)}$$
$$\frac{l}{1+l} = \frac{n/d}{1+n/d} = \frac{n(s)}{\overline{n(s)+d(s)}}$$