

Lecture 5 (18th Jan 2022)

Thursday before class

+ 24 hour extension. (Assignment 1).

HW2 will be uploaded on Thursday.

Step 1

Write down the state eq in mode ①, ② & combine them to get the "average" (over a switching cycle) model.

Average Model:

$$L \frac{d\langle v_L(t) \rangle_{T_S}}{dt} = (\text{v}_L \text{ in mode ①}) dt + (\text{v}_L \text{ in mode ②}) d'(t).$$

$$C \frac{d\langle v_C(t) \rangle_{T_S}}{dt} = (\text{i}_C \text{ in mode ①}) dt + (\text{i}_C \text{ in mode ②}) d'(t).$$

Specific example of buck boost.

$$\langle v_L(t) \rangle_{T_S} = L \frac{d}{dt} \langle v_L(t) \rangle_{T_S} = (\langle v_{in}(t) \rangle_{T_S}) \cdot dt - (\langle v_C(t) \rangle_{T_S}) d'(t)$$

$$\begin{aligned} \langle v_C(t) \rangle_{T_S} &= C \frac{d}{dt} \langle v_C(t) \rangle_{T_S} = \left(-\frac{\langle v_C(t) \rangle_{T_S}}{R} dt \right) + \left(-\frac{\langle v_L(t) \rangle_{T_S}}{R} + \langle i_L(t) \rangle_{T_S} \right) d'(t) \\ &= -\frac{\langle v_C(t) \rangle_{T_S}}{R} + \langle i_L(t) \rangle_{T_S} \cdot d'(t). \end{aligned}$$

How do we simulate this in PLECS?

$$L \frac{d \langle i_L \rangle}{dt} = \langle v_{in} \rangle d - \langle v_C \rangle d'$$

$$C \frac{d \langle v_C \rangle}{dt} = -\frac{\langle v_C \rangle}{R} + \langle i_L \rangle d'.$$


$$\dot{x} = f(x)$$



$$x = \begin{bmatrix} \langle i_L \rangle \\ \langle v_C \rangle \end{bmatrix}$$

these are still variables of time, I am just using a shorthand.

② Solve an ODE

③ Circuit representation.

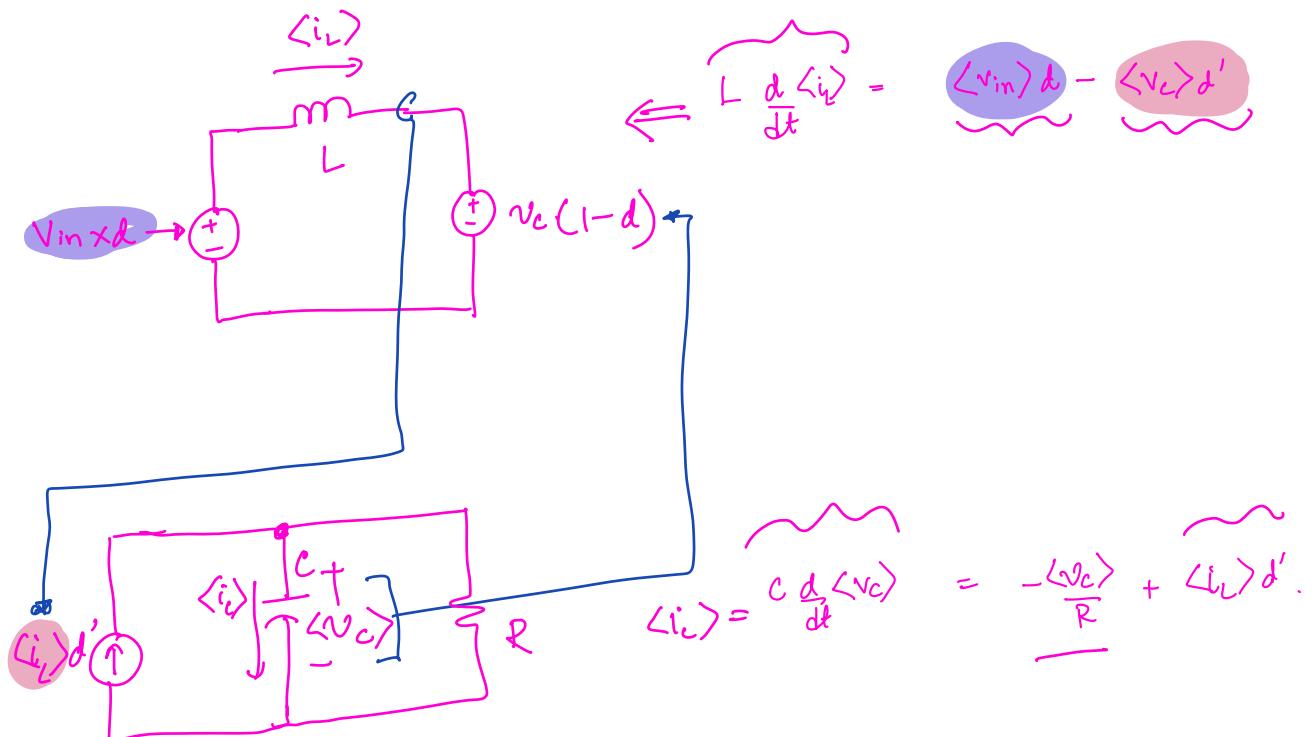

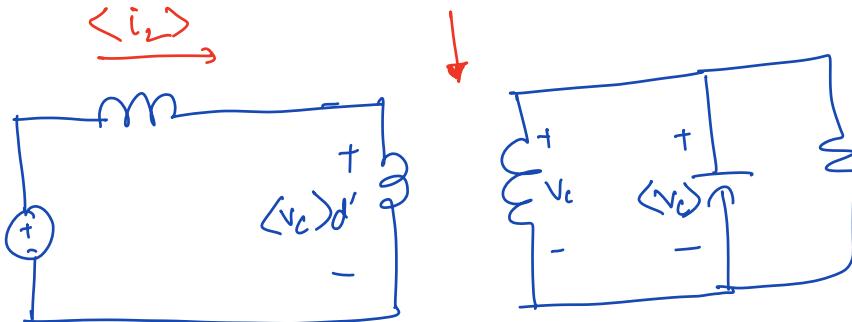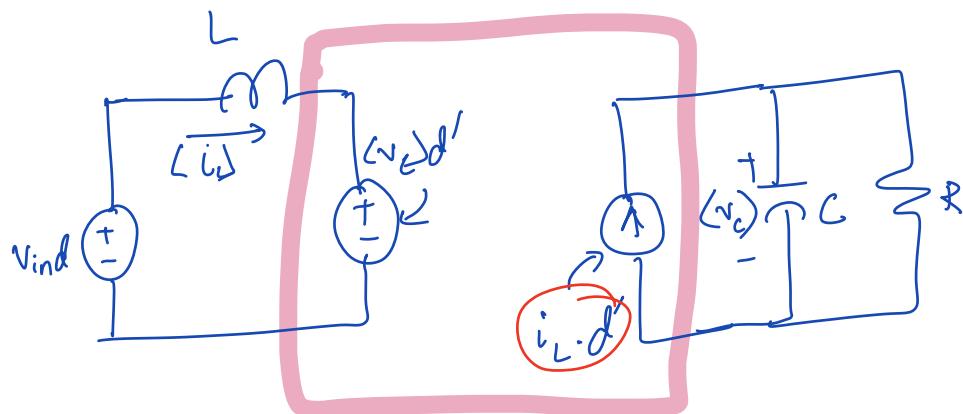

$$n_1 = ? \quad d'$$

$$n_2 = ? \quad 1$$

No. of turns

$$\begin{matrix} + \\ v_1 \\ - \end{matrix} \quad \begin{matrix} + \\ v_c \\ - \end{matrix}$$

$$n_1 : n_2$$

$$d' : 1$$

$$\begin{matrix} + \\ v_1 \\ - \end{matrix} \quad \begin{matrix} + \\ v_2 \\ - \end{matrix}$$

$$n_1, n_2$$

$$\frac{v_1}{n_1} = \frac{v_2}{n_2}$$

$$n_1 i_1 = n_2 i_2$$

$$d' \langle i_c \rangle$$

$$(1) \quad \underline{(i_c \cdot d')}$$

Step 2. Obtain the steady state value. (\bar{x}, \bar{u})
or, (x, u)

$$L \frac{d \langle i_L \rangle}{dt} = \langle v_{in} \rangle d - \langle v_c \rangle d'$$

$$C \frac{d \langle v_c \rangle}{dt} = -\frac{\langle v_c \rangle}{R} + \langle i_L \rangle d'$$

$$v_{in} = V_{in} + \tilde{v}_{in}$$

$$L \frac{d (I_L + \tilde{i}_L)}{dt} = (V_{in} + \tilde{v}_{in}) (D + \tilde{d}) - (V_c + \tilde{v}_c) (D' - \tilde{d}')$$

$$C \frac{d (V_c + \tilde{v}_c)}{dt} = -\frac{(V_c + \tilde{v}_c)}{R} + (I_L + \tilde{i}_L) (D' - \tilde{d}')$$

Only solve for large signal part

$$L \frac{d I_L}{dt} = V_{in} D - V_c D' = 0 \quad \therefore V_c = \frac{V_{in} \cdot D}{D'}$$

$$C \frac{d V_c}{dt} = -\frac{V_c}{R} + I_L D' = 0 \quad I_L = \frac{V_c}{R \cdot D'}$$

$$u = \begin{bmatrix} D \\ V_{in} \end{bmatrix} = \bar{u} \quad x = \begin{bmatrix} I_L \\ V_c \end{bmatrix} = \bar{x} \quad = \begin{bmatrix} V_c / (R \cdot D') \\ \frac{V_{in} D}{D'} \end{bmatrix} = \bar{x}$$

$$= \begin{bmatrix} \frac{V_{in} D}{R D'^2} \\ \frac{V_{in} D}{D'} \end{bmatrix}$$

Step 3 Obtain A & B to get the linearized average model.

$$\ddot{\tilde{x}} = A(\tilde{x} - \bar{x}) + B(u - \bar{u}) \quad \begin{aligned} \tilde{x} &= x - \bar{x} \\ \tilde{u} &= u - \bar{u} \end{aligned}$$

$$A = \left. \frac{\partial f}{\partial \tilde{x}} \right|_{\begin{array}{l} x=\bar{x}, \\ u=\bar{u} \end{array}} \quad B = \left. \frac{\partial f}{\partial \tilde{u}} \right|_{\begin{array}{l} x=\bar{x}, \\ u=\bar{u} \end{array}}$$

$$x = \begin{bmatrix} \langle i_L \rangle \\ \langle v_C \rangle \end{bmatrix} \quad u = \begin{bmatrix} d \\ \langle v_{in} \rangle \end{bmatrix}$$

$$f = \begin{bmatrix} f_1(x, u) \\ f_2(x, u) \end{bmatrix}$$

$$L \frac{d \langle i_L \rangle}{dt} = \langle v_{in} \rangle d - \langle v_C \rangle d'$$

$$C \frac{d \langle v_C \rangle}{dt} = -\frac{\langle v_C \rangle}{R} + \langle i_L \rangle d'$$

$$f_1 = \underbrace{\langle v_{in} \rangle d - \langle v_C \rangle d'}_L$$

$$d' = 1 - d \quad \frac{\partial d'}{\partial d} = -1$$

$$\frac{v_{in}}{L} + \frac{v_C}{C}$$

$$f_2 = -\frac{\langle v_C \rangle}{RC} + \frac{\langle i_L \rangle d'}{C}$$


$$A = \left[\begin{array}{cc} \frac{\partial f_1}{\partial \tilde{i}_L} & \frac{\partial f_1}{\partial \tilde{v}_C} \\ \frac{\partial f_2}{\partial \tilde{i}_L} & \frac{\partial f_2}{\partial \tilde{v}_C} \end{array} \right] = \begin{bmatrix} 0 & -\frac{D'}{L} \\ \frac{D'}{C} & -\frac{1}{RC} \end{bmatrix} \quad D, V_{in}$$

$i_L = I_L, d = D$
 $v_C = V_C, v_{in} = V_{in}$

$$B = \begin{bmatrix} \frac{\partial f_1}{\partial x} & \frac{\partial f_1}{\partial v_{in}} \\ \frac{\partial f_2}{\partial x} & \frac{\partial f_2}{\partial v_{in}} \end{bmatrix} \Big|_{i_L} = \begin{bmatrix} \frac{v_{in} + v_c}{L} & \frac{P}{L} \\ -\frac{1}{C} & 0 \end{bmatrix}$$

∴ $\dot{x} = A(x - \bar{x}) + B(u - \bar{u})$

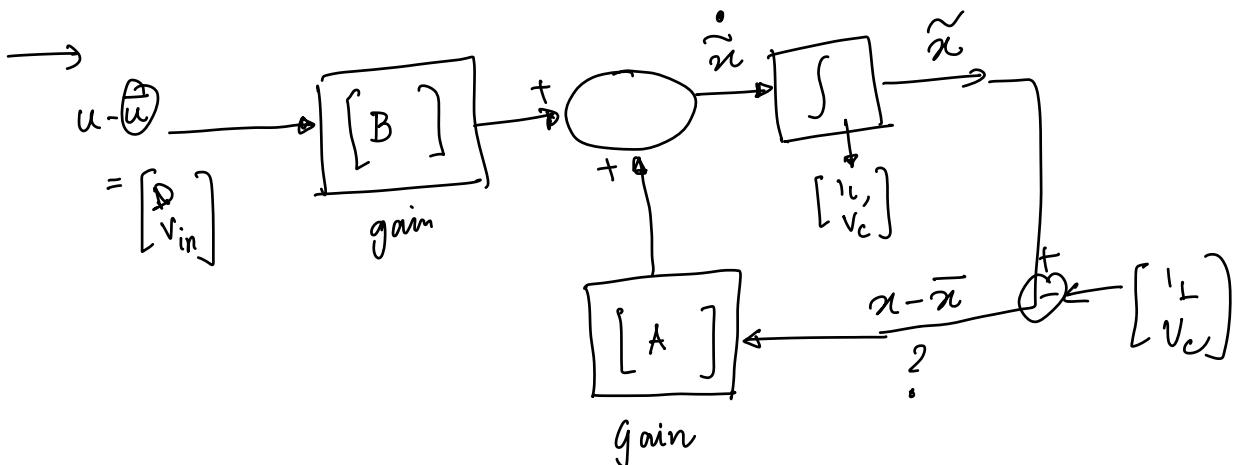You know A, B for a particular D, V_{in} .



$$\dot{x} = f(x, u)$$

$$\dot{x} = f(\bar{x}, \bar{u}) + \underbrace{\frac{\partial f}{\partial x} \cdot (x - \bar{x})}_{A} + \underbrace{\frac{\partial f}{\partial u} \cdot (u - \bar{u})}_{B}$$


$$x - \bar{x} = \tilde{x}$$

$$x = \bar{x} + \tilde{x}$$


$$\begin{aligned} \dot{x} &= \underbrace{\frac{\partial f}{\partial x}}_{=0} \cdot \tilde{x} + \tilde{\dot{x}} \\ &= 0 \end{aligned}$$

$$\dot{x} = A\tilde{x} + B\tilde{u}$$

PLECS simulation

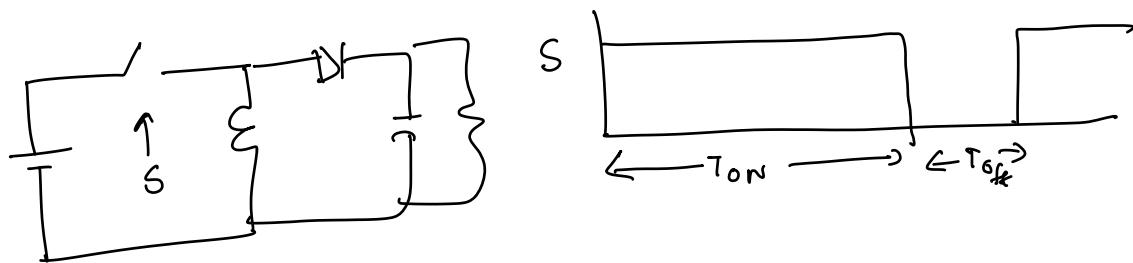


Fixed simulation step size



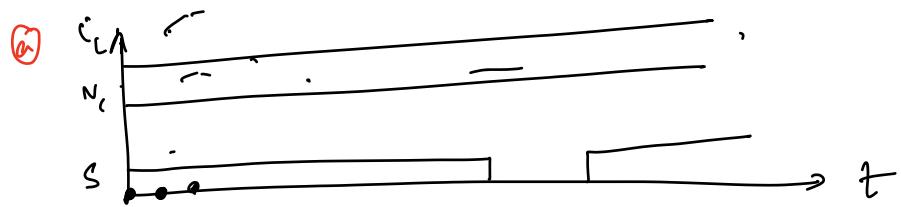


too large time steps - bad results
 too small " " " → good " unnecessarily long simulation

(b) Variable time step.

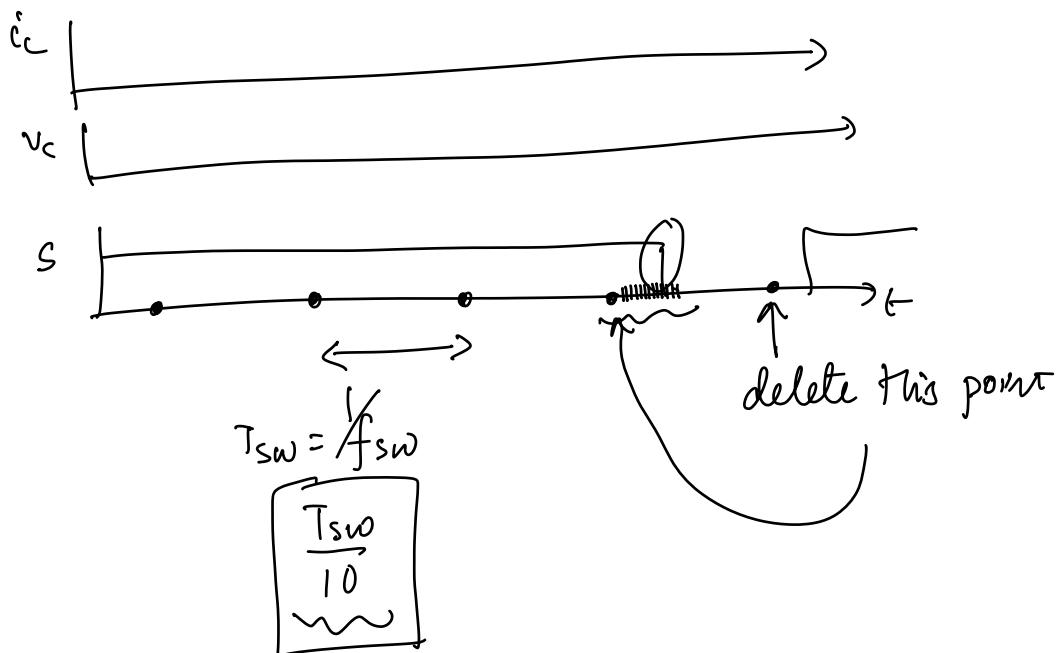


Control

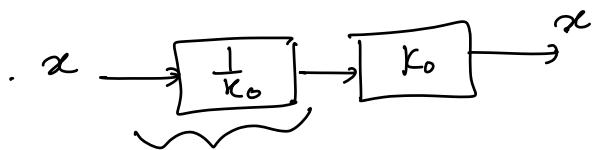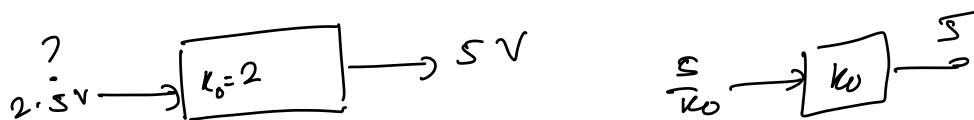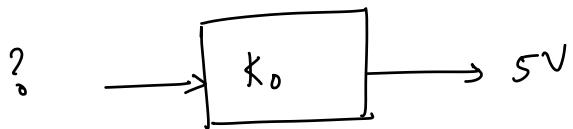


open loop control

Buck converter - cheap.

on-off control / bang-bang control.

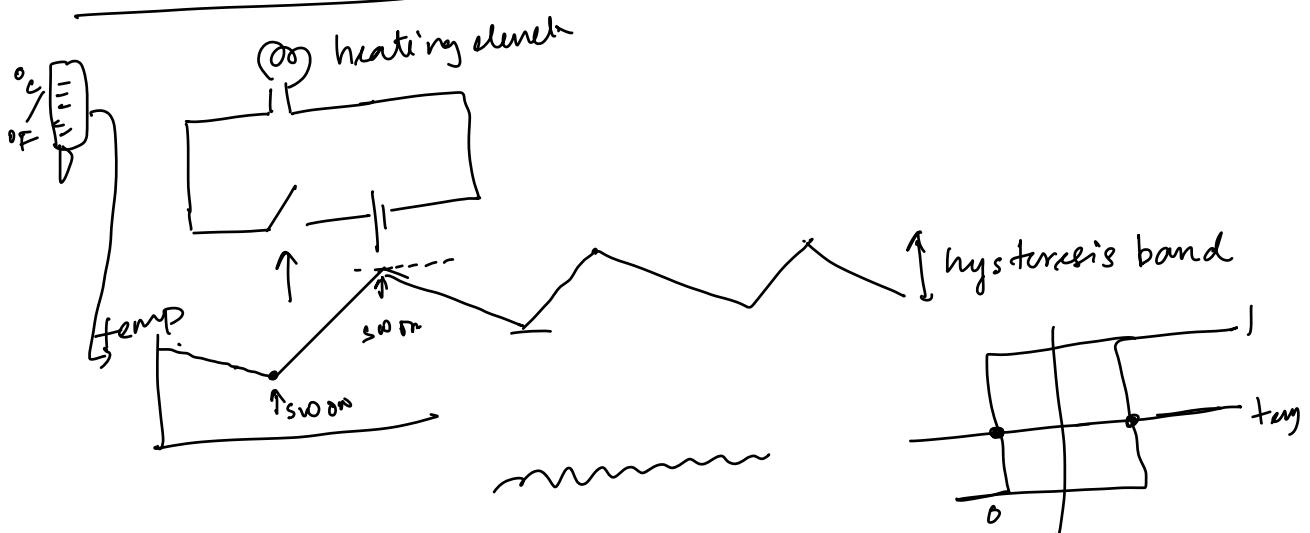


Closed Loop


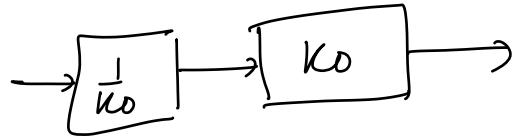


$$I \rightarrow [0.1] \rightarrow [10] \rightarrow 1V$$
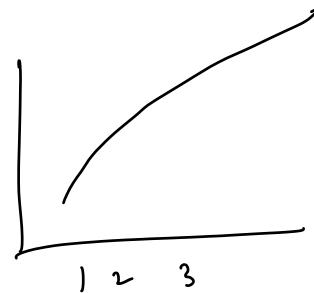
$$I \rightarrow [0.1] \rightarrow [8] \rightarrow 0.8V$$



$$(0(1 + T^{0.001}))$$

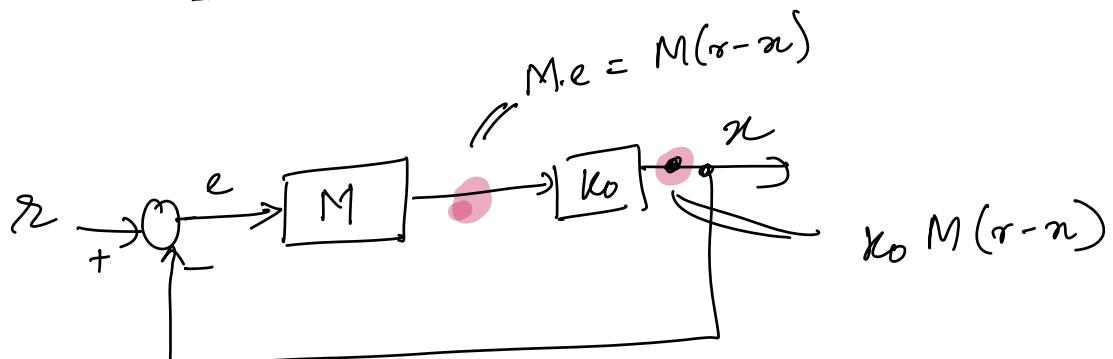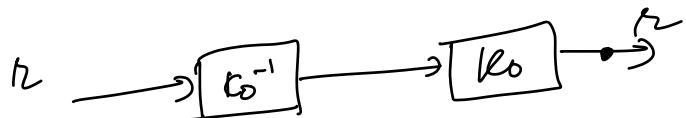

(ideally $r = n$ is what I want.)

$$e = r - n$$

$$K_0 M(r - n) = n$$

$$K_0 Mr - K_0 Mn = n$$


$$k_0 M r = (k_0 M + 1) x$$

$$\therefore x = \frac{k_0 M r}{1 + k_0 M}$$


$$x = r \cdot \frac{1}{1 + \frac{1}{k_0 M}}$$

when $M \rightarrow \infty$, $x \approx r$.


Basic of closed loop control sys.

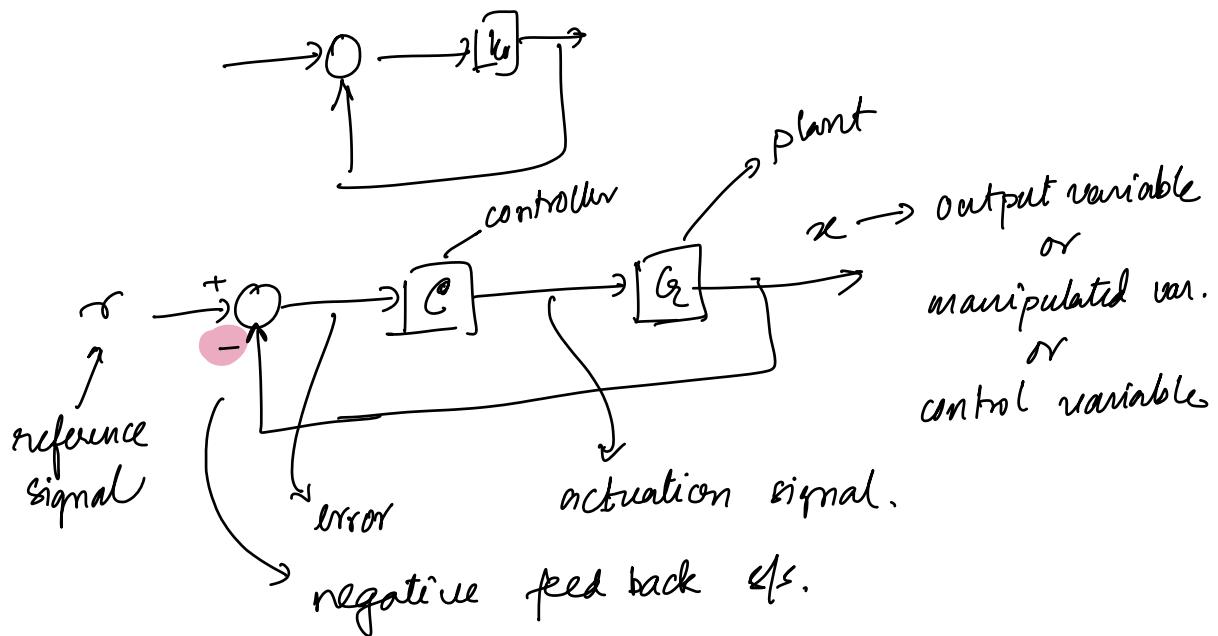
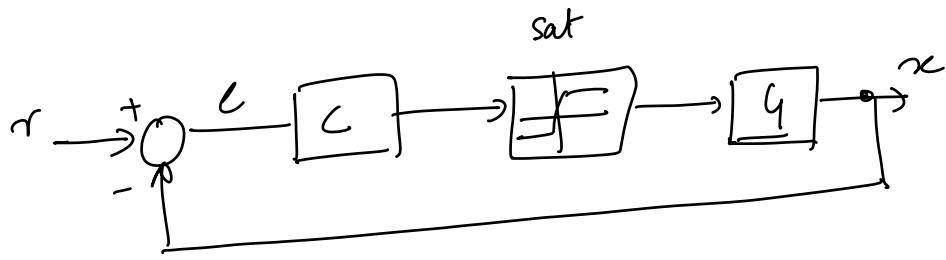
$$x = \frac{G_2 \cdot C}{1 + G_2 \cdot C} \cdot r$$




disturbance

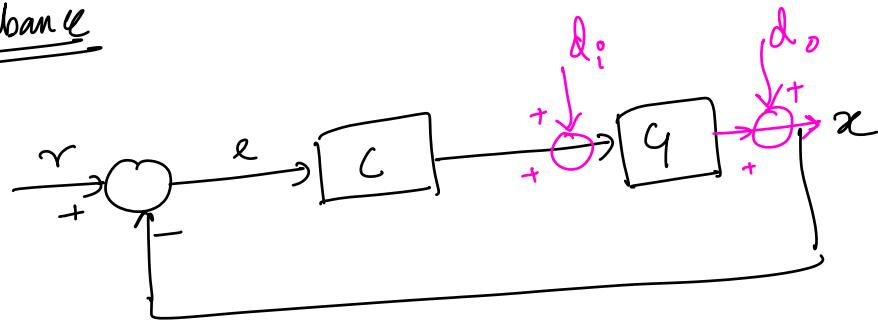

$$x = \frac{G}{1+GC} d_i$$

$$x = \dots r$$

$$x = \frac{1}{1+GC} d_o$$

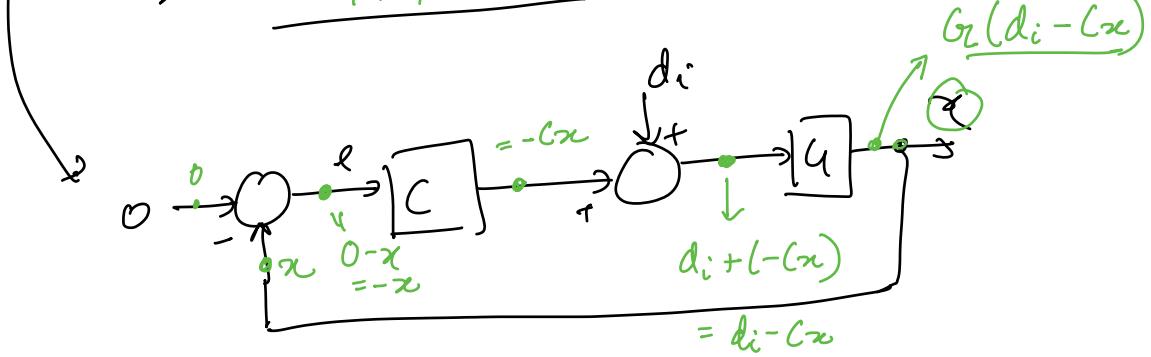

$$G(d_i - Cx) = x$$

$$\Rightarrow G \cdot d_i - G \cdot Cx = x$$

$$G \cdot d_i = (GC + 1)x$$

$$\therefore x = \frac{G}{1+GC} d_i \quad \left| \begin{array}{l} n = \frac{1}{1+GC} d_o \end{array} \right.$$

We do not want disturbance to impact the output variable
(n)


So, I do not want d_i/d_o to impact x

$$x = \underbrace{\text{very small}}_{\text{d}_i \text{ or } d_o} d_i \text{ or } d_o.$$

$$x = \frac{1}{1+GC} d_o = \frac{1}{GC} d_o \text{ if } G \text{ is large, } \underline{x=0}$$

$$x = \frac{G}{1+GC} d_i = \frac{G d_i}{G C} = \frac{1}{C} d_i = 0.$$

$G \text{ is large} \therefore GC \gg 1$

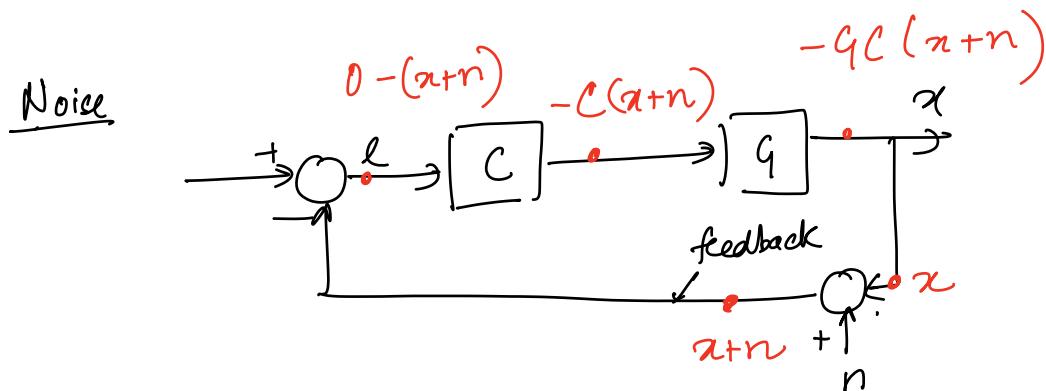

$$-G C (x+n) = n$$

$$-G C n = (1+G C) n$$

$$\therefore x = -\frac{G C}{1+G C} \cdot n.$$

C large, $x = -\frac{G \cdot C}{G \cdot C} n = -n.$
(Controller)

Simultaneously large controller gain (C)
ensures

- ① reference tracking
- ② disturbance rejection
- ③ enhances noise.

$$x = \underbrace{\frac{G_C}{1+GC} r}_{\text{rare}} + \underbrace{\frac{1}{1+GC} d_o}_{\checkmark} + \underbrace{\frac{G}{1+GC} d_i}_{\uparrow \text{sensitivity}} - \underbrace{\frac{G_C}{1+GC} n}_{\checkmark}$$

$$x = \underbrace{T r}_{\begin{matrix} \uparrow \\ \text{Complementary} \\ \text{Sensitivity} \end{matrix}} + \underbrace{S d_o}_{\uparrow \text{Sensitivity}} - T n$$