

Lab 2 Lecture Notes Clean

Monday, January 31, 2022 5:12 PM

Agenda:

- Inner current / outer voltage control (Background)
- week 1: controller design
- week 2: implementation and HiL
- week 3: work-time and wrap-up.

1) Background.

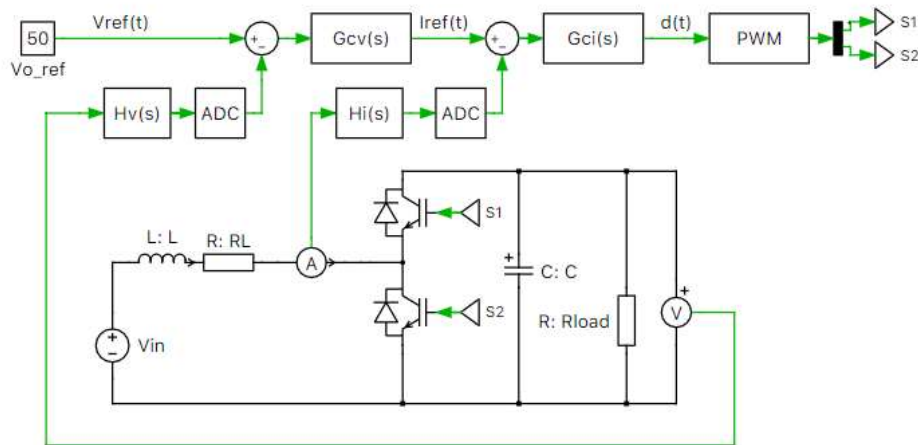


Figure 1: Conceptual diagram of ICOV control for a synchronous boost

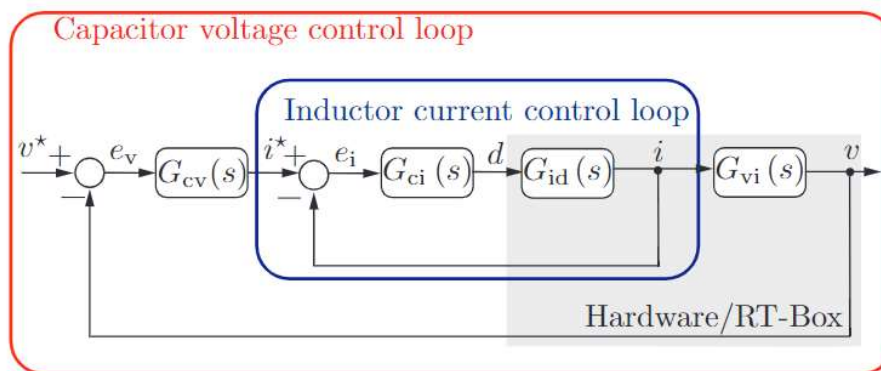


Figure 2: Transfer function diagram of ICOV control

ω_{bw} for IC loop 10x HIGHER than ω_{bw} for OV loop

Why?

2) Controller Design: (week 1)

- similar process for IC and OV
 - specific to this problem
 - general solution discussed in lecture.


• IC controller design:

input: i_{ref} output: d

1) select t_{ci} , ϕ_m

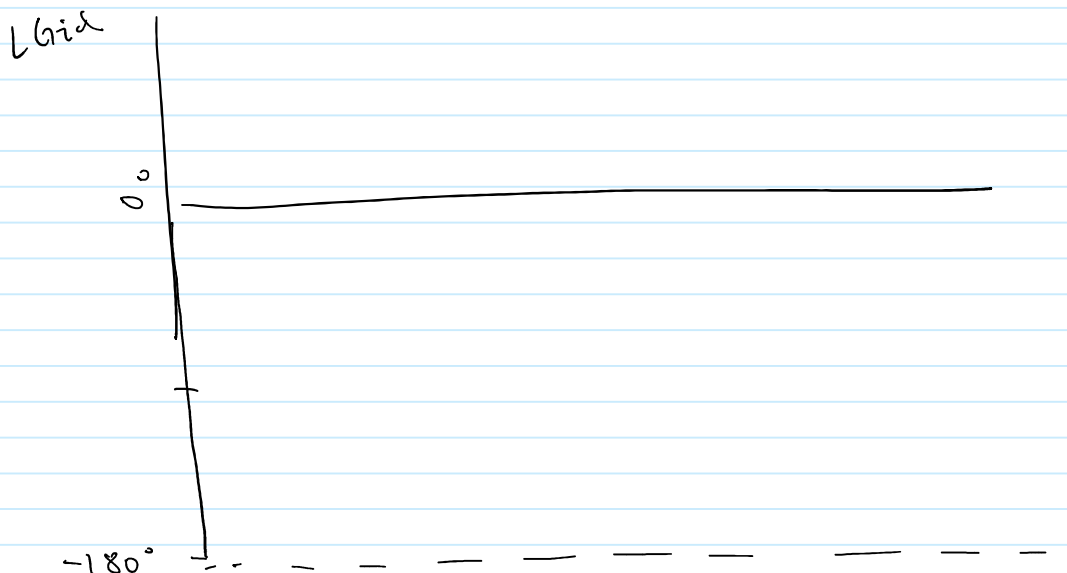2) find gain/phase of uncompensated, loop

approx: $G_{ids} \approx \frac{V_{out}}{sL}$ at high frequency.



3) Use PI controller: $C(s) = (k_p + \frac{k_i}{s})$

$$L_i(s) = C(s) P(s) = C(s) G_{ref}(s)$$

$$\approx (k_p + \frac{k_i}{s}) (\frac{V_{out}}{sL})$$

$$\|L_i(s)\| \Big|_{\omega=\omega_{bw}} = 1$$

$$\angle L_i(s) \Big|_{\omega=\omega_{bw}} = -180^\circ + \phi_m$$

} use this to
get k_p and k_i

$$\| \frac{V_{out}}{sL} (k_p + \frac{k_i}{s}) \|$$

$$\angle L_i = \angle (k_p + \frac{k_i}{s}) \frac{V_{out}}{sL} = -180^\circ + \phi_m$$

note: $k_p + \frac{k_i}{s} = G_{PE} (1 + \omega_{PE}) = G_r$

note: $k_p + \frac{k_i}{s} = G_{PI} \left(1 + \frac{\omega_{PI}}{s}\right) = G_c$

Use (1) and (2) to get G_{PI} , ω_{PI}

- Simulate current control.
 - Start file for control in Canvas
 - this is a transfer function model
 - also need to implement w/ switched model

• OV controller design:

input: v_{ref} output: i_{ref}

select $\omega_{c,v} \leq \frac{\omega_{ci}}{10}$

$$\| (k_p + \frac{k_i}{s}) G_{vi} \| = 1 \rightarrow \boxed{\sqrt{k_p^2 + \frac{k_i^2}{\omega_c^2}} \left[\frac{DR}{2} - \frac{R_L}{2\omega_c} \right]} \quad (3)$$

$$\angle (k_p + \frac{k_i}{s}) G_{vi} = -180^\circ + \phi_m$$

$$\angle k_p + \frac{k_i}{s} + \angle G_{vi} \rightarrow \text{approx } 0 \text{ at low frequency.}$$

$$-\arctan\left(\frac{k_i}{\omega_c k_p}\right) = -180^\circ + \phi_m$$

$$\therefore \arctan\left(\frac{k_i}{\omega_c k_p}\right) - 180^\circ = -180^\circ + \phi_m$$

$$\boxed{\arctan\left(\frac{k_i}{\omega_c k_p}\right) = \phi_m} \quad (4)$$

• Use (3) (4) to get k_p / k_i for voltage controller.

3) Implementation (Week 2)

- Set up RT BOX (see auxiliary video)

- scaling

- scale in PEGS, send to MEM

- read in ADC pin

- scale to actual numerical value

Scale: $\frac{3.3V}{\text{max value} + \text{safety}} \rightarrow \text{max ADC voltage}$

• you can choose them based on your design last quarter

- implement PI in code:

- same idea for V

- saturation

• saturate y_{int} $[-0.95, 0.95]$

• saturate y_i on max/min duty

• saturate y_v on max/min current

code structure: (Suggested)

Globals / Const defines

- state variables for at least 1 previous cycle
- reference variables
- saturation values
- controller gains
- scalings

ADC interrupt:

// voltage control

$$V_{err} = V_{ref} - V_o$$

$$Y_{pr} = V_{err} \cdot k_{p,v}$$

$$y_{int,v} = (Ts/0.5)(V_{err} + V_{err,prev})k_{i,v} + y_{int,prev}$$

if $y_{int,v}$ too high/low:
saturate.

update y_{prev} , $y_{int,prev}$, $V_{err,prev}$, etc.

$$y_v = y_{int} + y_{pr}$$

if y_v too high/low // y_v is current ref!
saturate

if y_v too high/low // y_v is current ref!
saturate
// current control.
 $i_{ref} = y_v$
repeat PI calculations but for DC loop
saturate y_i if needed // $y_i = \text{duty}$.
update PWM duty register (CMPA)