

EE 458 – Power Electronics Controls, Winter 2021

Homework 3

Due Date: Thursday February 3rd, 2022, 4:30pm PT

Problem 1: For the given boost converter circuit in Fig. 1, assume the following,

1. The input voltage V_{in} is perfectly stiff.
2. The duty ratio $d(t)$ represents the time for which S_1 is turned ON. For the complement, $1 - d(t)$, S_2 is turned ON.
3. Output capacitor is ideal, lossless.
4. Assume $R_L = 0$

Let us assume the ratio of small signal output voltage to duty ratio transfer function is defined as follows,

$$G_{vd}(s) = G_o \frac{1 - \frac{s}{\omega_z}}{1 + \frac{s}{Q\omega_o} + \left(\frac{s}{\omega_o}\right)^2}.$$

Specify the values of G_o , ω_z , Q , and ω_o analytically in terms of the circuit parameters R, L, C and the nominal duty ratio, D , the nominal output voltage, V .

 


Figure 1: Boost converter circuit for Problem 1.

[Refer to *Fundamentals of Power Electronics E&M*, pp 300, Table 8.2 to check your solution.]

Problem 2: We operate the boost converter of Problem 1 at the following nominal conditions : $V_{in} = 24V$, output voltage = 48V, output power = 250 W, $f_{sw} = 100$ kHz, $L = 1.25mH$, $C = 250\mu F$.

Does the stability of the system $G_{vd}(s)$ with no compensation (controller, $C(s) = 1$) increases, decreases, or remains unaffected when

- You redesign inductance, L to reduce the current ripple of $i(t)$ shown in Figure 1.
- You change the output power to 100 W.

- You change the switching frequency to 10 kHz.
- You change the output voltage to be at 30 V.

You might use bode plots of $G_{vd}(s)$ with these operating conditions to explain, or give an intuitive explanation.

Problem 3: Consider the transfer functions

$$G_1(s) = G_o \frac{1}{1 + \frac{s}{\omega_1}}, \quad G_2(s) = \frac{1}{1 + \frac{s}{\omega_2}}.$$

where $G_o = 100$, $f_1 = \omega_1/(2\pi) = 1$ kHz, and $f_2 = \omega_2/(2\pi) = 10$ kHz. For the questions below, your frequency axes should be in Hz, amplitude in dB, and phase in degrees.

- Sketch the Bode plots for G_1 and G_2 using the linear asymptote approximations for both amplitude and phase.
- Using your result from (a) sketch the Bode plot for the product $G_1(s)G_2(s)$. You can use a computer to check your result.

Problem 4: In this problem we will study the complete digital control loop. In the questions on the next page, assume

- $f_{\text{clk}} = T_{\text{clk}}^{-1} = 100 \text{ MHz}$, and the switching period is $T_s = (100 \text{ kHz})^{-1}$.
- Asymmetric leading edge modulation is used, N_r is the maximum counter value, and the counter increments every clock cycle.
- The ADC has $n_{\text{A/D}} = 12$ bits and the ADC pin can sample an analog voltage between 0 V and $V_{\text{FS}} = 3 \text{ V}$.
- The time interval between the ADC start of conversion (SOC) and end of conversion (EOC) takes 50 clock cycles. Denote this time as $T_{\text{A/D}}$. The SOC is triggered each time the DPWM counter resets to N_r .
- The arithmetic to carry out the controller code consumes 500 clock cycles. Denote this time as T_{comp} .
- After the processor finishes the controller arithmetic, the a new value of $x_c[n]$ is available where $x_c[n]$ will eventually be loaded into the DPWM compare register. Before the value of $x_c[n]$ is loaded into the DPWM compare register, it is held temporarily in a shadow register. The time this value is held in the shadow register is called T_{hold} .
- The value of $x_c[n]$ is read into the DPWM compare register when the counter resets to N_r . The cumulative time between the ADC SOC and when $x_c[n]$ is written into the DPWM compare register is denoted as T_{ctrl} where $T_{\text{ctrl}} = T_{\text{A/D}} + T_{\text{comp}} + T_{\text{hold}}$.
- The time interval between when $x_c[n]$ is read into the DPWM module and the next transition in the PWM pin $c(t)$ is called T_{mod} .

Answer the questions below:

- If the voltage on the ADC pin, $v_{A/D}$, is 0.75 V, what digital integer value, $x_{A/D}$, will the ADC produce?
- What is the voltage resolution, $q_{A/D}$, of the ADC analog input?
- Compute T_{hold} and the ratio $T_{\text{hold}}/T_{\text{ctrl}}$. What does the value of $T_{\text{hold}}/T_{\text{ctrl}}$ tell us about the computational burden on the processor? What happens to the ratio $T_{\text{hold}}/T_{\text{ctrl}}$ as the controller requires more computations?
- Compute T_{ctrl} , T_{mod} , and T_d . Express your results in terms of T_{clk} and D .
- Sketch the binary PWM output $c(t)$ and sampled ADC value $x_{A/D}$ waveforms onto Figure 2. Overlay $x_{A/D}$ on the same plot as $v_{A/D}$.
- Add the following items onto Figure 2: Label the maximum feasible integer value of $x_{A/D}$ vertical axis, specify the DPWM counter maximum N_r , label the duty D , and the delays T_{ctrl} and T_{mod} . Also draw the delays $T_{A/D}$, T_{comp} , and T_{hold} within T_{ctrl} and try to draw them to scale.

 


Figure 2: Digital system waveforms for Problem 3.