
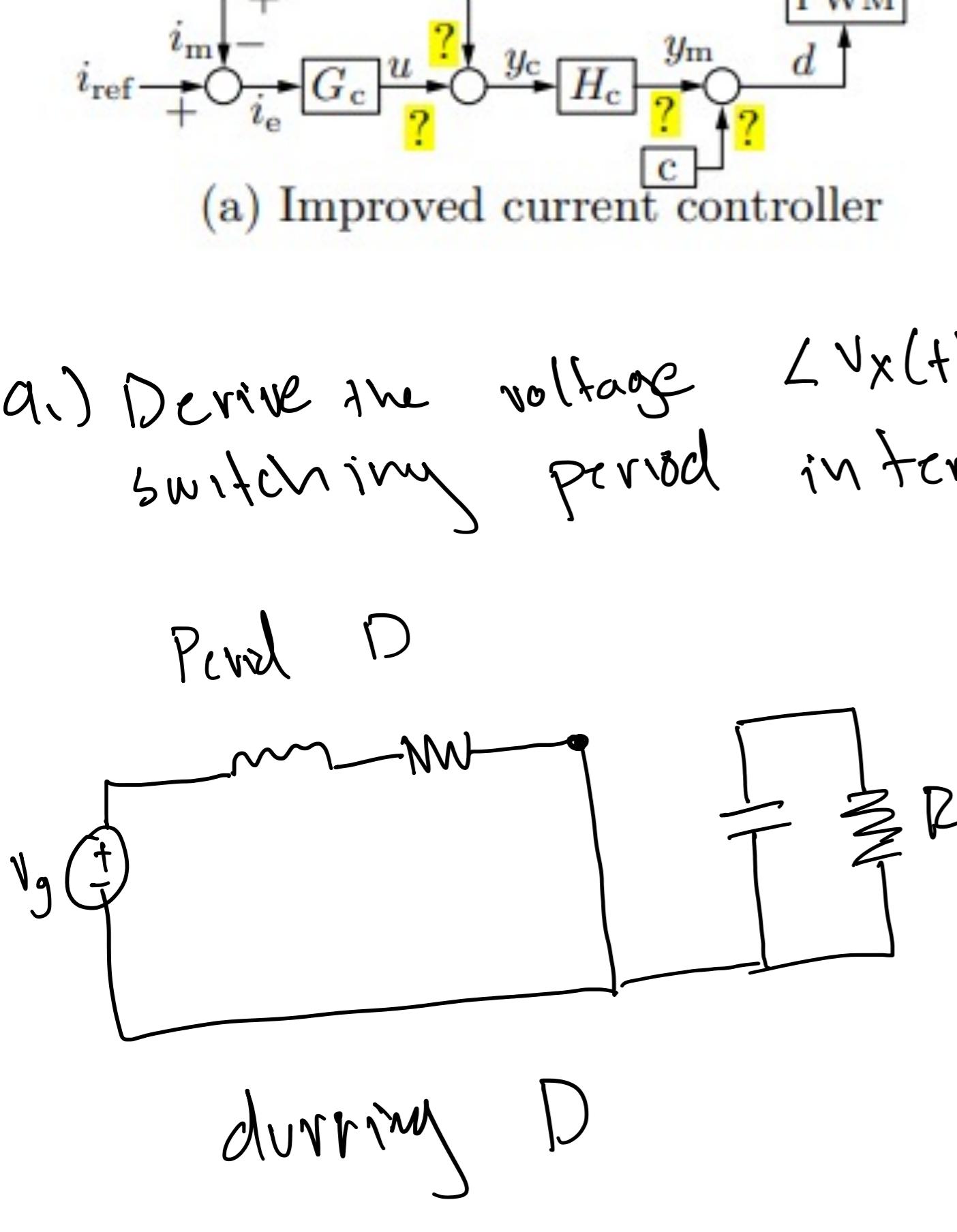


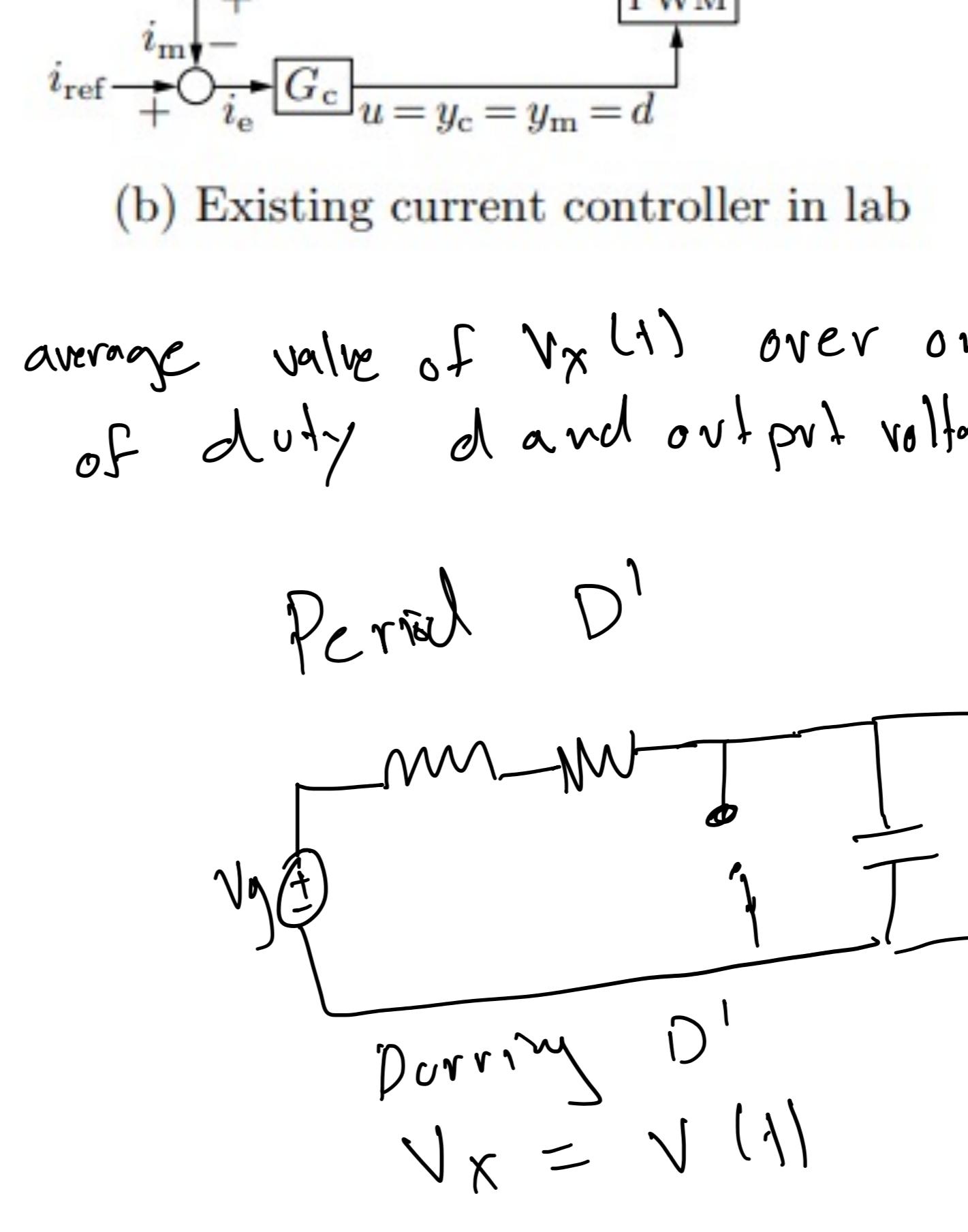→ Boost converter
 • Winding + magnet on resistances lumped into R_L
 • i_{in} → control variable
 • i_b → feed forward structure




(a) Improved current controller




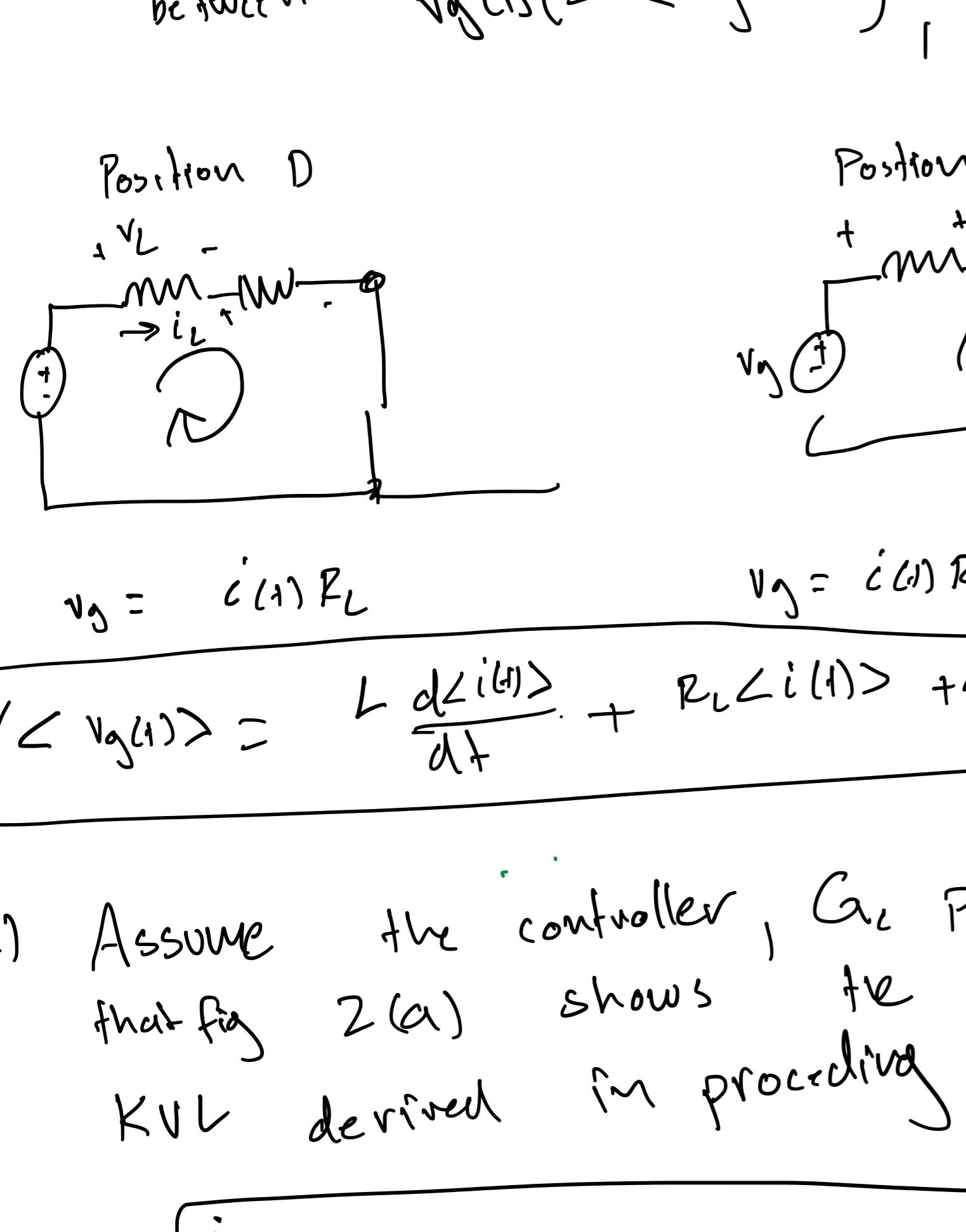(b) Existing current controller in lab

a.) Derive the voltage $\langle v_x(t) \rangle$ average value of $v_x(t)$ over one switching period in terms of duty d and output voltage $v(t)$




$$v_x = 0$$

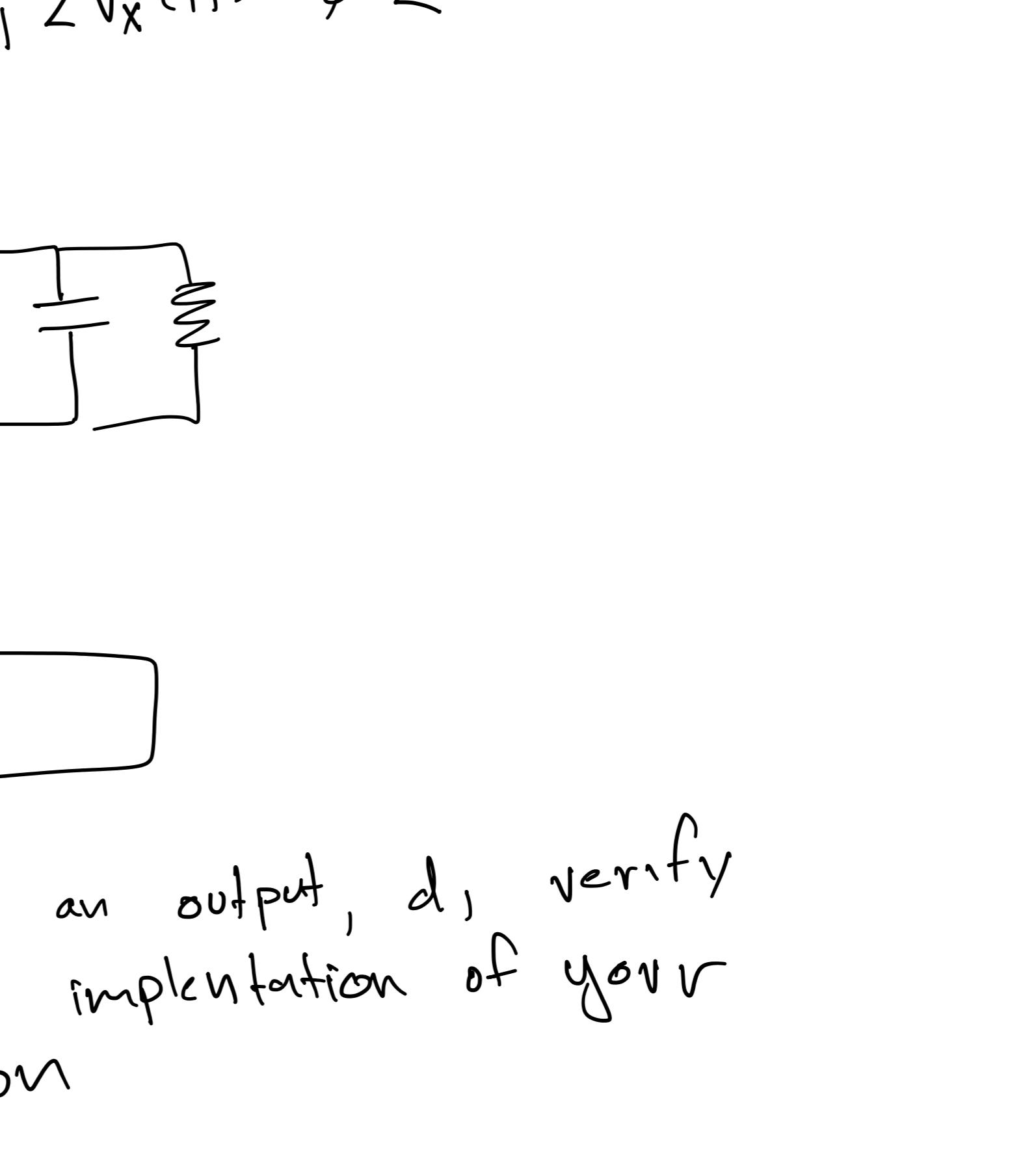


$$\langle v_x(t) \rangle = \langle v(t) \rangle [1 - d]$$

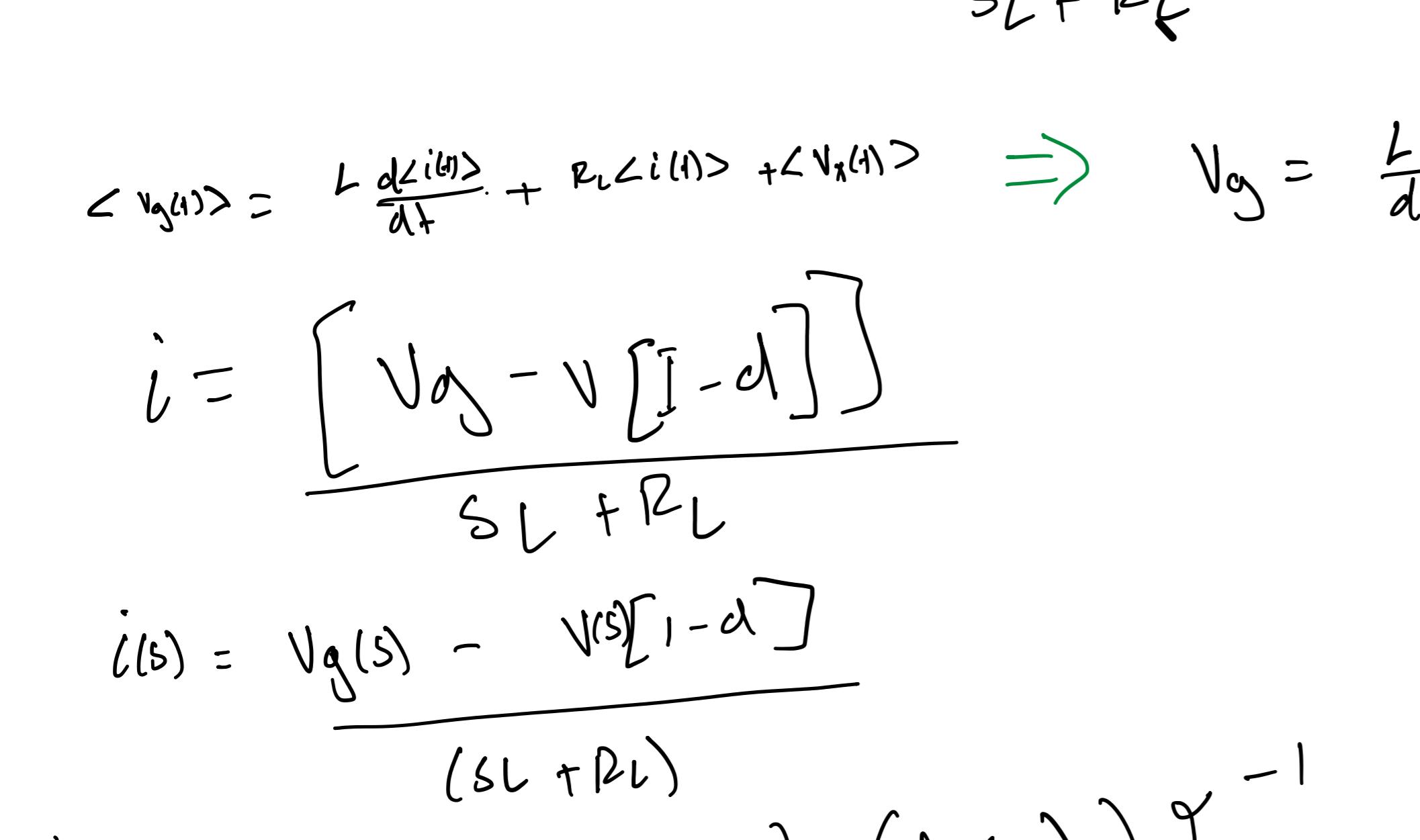b.) Derive KVL in the input loop to obtain a relationship between $v_g(s) (= \langle v_g(t) \rangle)$, L , R_L , $\langle v_x(t) \rangle$ & $\langle i(t) \rangle$



$$\langle v_g(s) \rangle = L \frac{d\langle i(s) \rangle}{dt} + R_L \langle i(s) \rangle + \langle v_x(s) \rangle$$

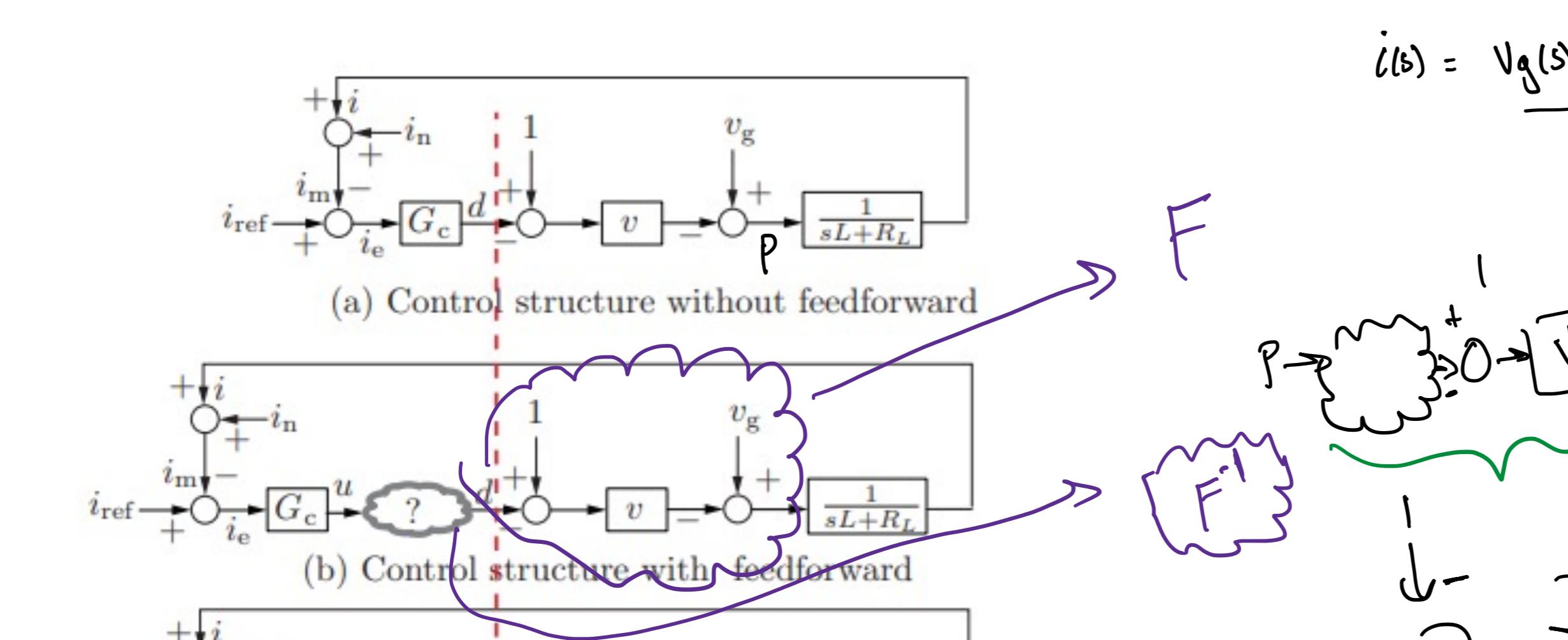c.) Assume the controller, G_c , produces an output, d , verify that fig 2(a) shows the correct implementation of your KVL derived in proceeding question



$$\langle v_g(s) \rangle = L \frac{d\langle i(s) \rangle}{dt} + R_L \langle i(s) \rangle + \langle v_x(s) \rangle \Rightarrow v_g = \frac{L di}{dt} + i R_L + v_x$$

$$i = \frac{v_g - v[1-d]}{sL + R_L}$$

$$i(s) = \frac{v_g(s) - v[1-d]}{sL + R_L}$$

$$d = \frac{(sL + R_L)i(s) + v(s)[1-d(s)]}{sL + R_L} = \frac{(v_g(s))}{sL + R_L}$$


$$d = \frac{1}{sL + R_L} \left[v_g(s) - v[1-d] \right]$$

$$\frac{1}{sL + R_L} \left((sL + R_L)i(s) + v(s)[1-d(s)] \right) = \frac{1}{sL + R_L} \left[v_g(s) \right]$$

$$\frac{1}{sL + R_L} \left(L \frac{di}{dt} + i(s)R_L + v(s)[1-d(s)] \right) = \frac{1}{sL + R_L} \left[v_g(s) \right]$$

$$\frac{L \frac{di}{dt}}{sL + R_L} + i(s)R_L + v(s)[1-d(s)] = v_g(s) \quad \checkmark$$

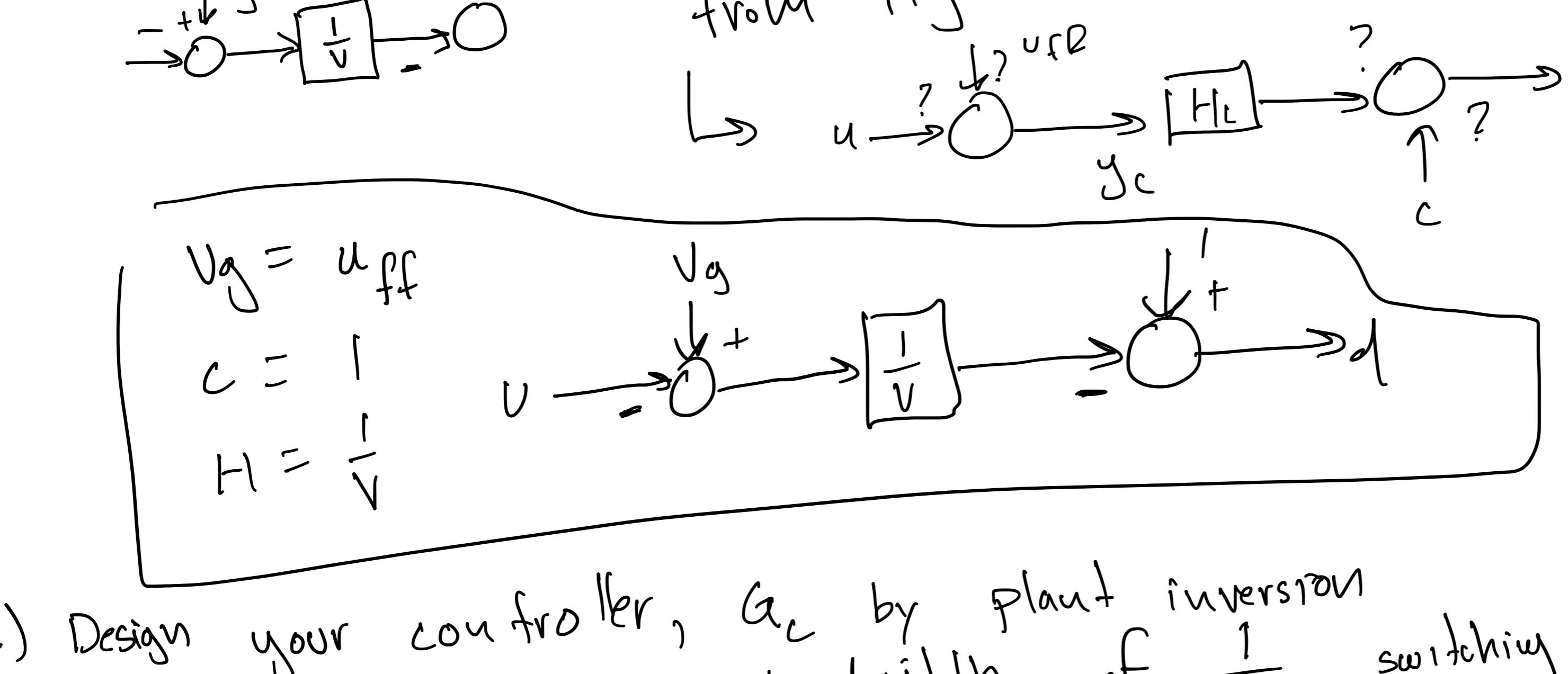d.) We want to implement Feed-Forward to simplify transfer function
 $\rightarrow \frac{1}{sL + R_L}$
 so that the controller design becomes simplified as in Fig 2c



$$d = 1 - \left(\frac{v_g - v}{V} \right)$$

$$d = \frac{v_g - v[1-d]}{sL + R_L}$$

$$d = \frac{v_g - v + v[1-d]}{sL + R_L}$$

$$d = \frac{v_g - v + v - v[1-d]}{sL + R_L}$$

$$d = \frac{v_g - (-x+1)V}{sL + R_L}$$

$$d = \frac{v_g - (-x+1)V}{sL + R_L}$$

Provide a numerical relationship between controller output v and actual duty ratio d , that goes into PWM block

0 < d < 1, compare the relationship with fig 1a.
 to identify H_c , C_{eff} and the signs of the sum blocks shown with ?

$$d = G_c \frac{1}{sL + R_L}$$

$$a = L$$

$$b = R_L$$

$$d = \frac{v_g - (-x+1)V}{sL + R_L}$$

$$d = \frac{(k_p s + k_i)}{sL + R_L} \cdot \frac{1}{sL + R_L}$$

$$d = \frac{w_g}{s} \cdot \frac{1}{sL + R_L}$$

$$d = \frac{w_g}{s} \quad \checkmark$$

$$G_c = \text{controller} = \frac{k_p s + k_i}{s} = \frac{w_g L s + w_g R_L}{s} = \frac{w_g (L s + R_L)}{s}$$

$$w_g = \frac{\omega_{sw}}{10}$$


$$\omega = 2\pi f$$

$$\frac{\omega}{2\pi} = f$$

$$G_c = \frac{\omega_{sw} (L s + R_L)}{10 s}$$

$$G_c = \frac{f_{sw} (L s + R_L)}{20 \pi s}$$
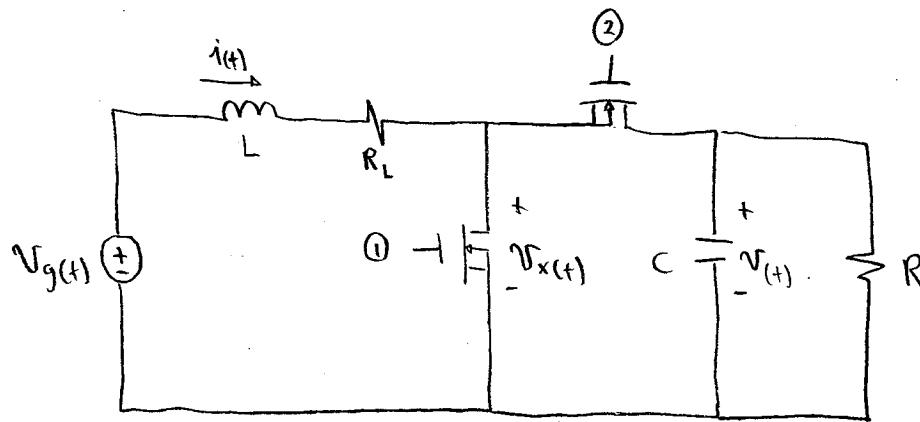
$$k_p = \frac{10,000 \cdot 2\pi}{10} \cdot 0.001^2$$



$$a) \langle V_x(t) \rangle = (0) d + \langle V_{(t)} \rangle (1-d)$$

$$\boxed{\langle V_x(t) \rangle = (1-d) \langle V_{(t)} \rangle}$$


$$b) \boxed{\langle V_g(t) \rangle = L \frac{d \langle i(t) \rangle}{dt} + R_L \langle i(t) \rangle + V_x(t)}$$

$$c) V_g(s) = sL i(s) + R_L i(s) + V_x(s) ; \quad V_x(s) = (1-d) V(s)$$


$$V_g(s) = sL i(s) + R_L i(s) + (1-d) V(s)$$

$$i(s) (sL + R_L) = V_g(s) - (1-d) V(s)$$
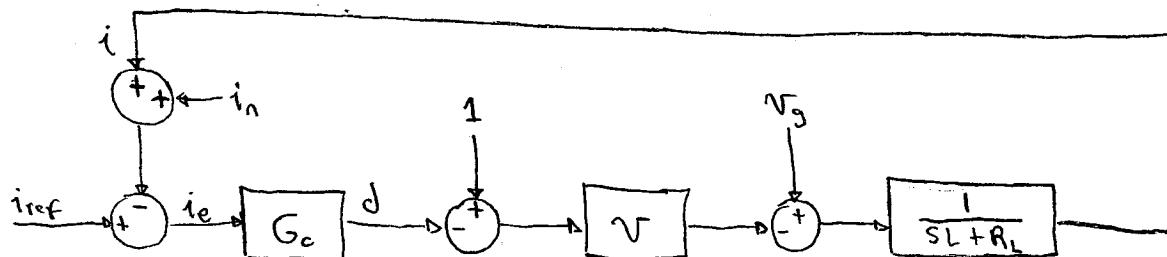
$$\boxed{i(s) = \frac{V_g(s) - (1-d)V(s)}{sL + R_L}}$$



d)

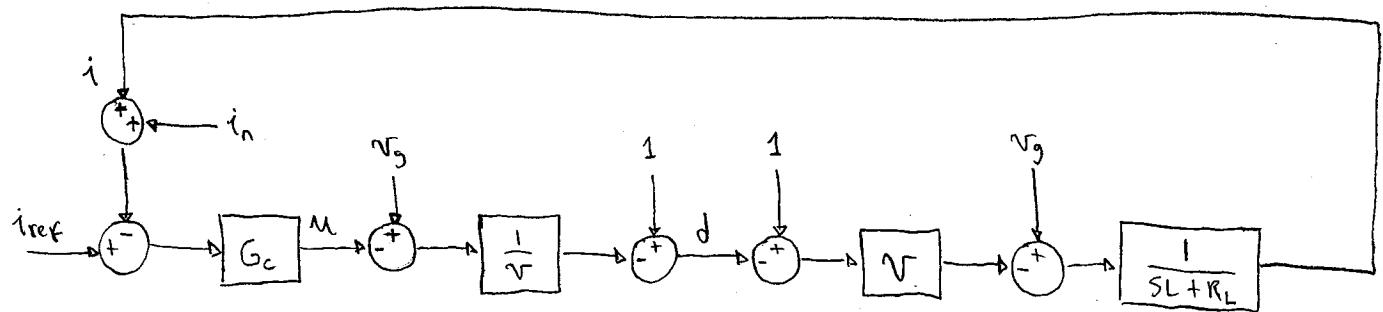


$$i(s) = \frac{V_g(s) - (1-d)V(s)}{sL + R_L} \leftarrow V_g - (1-d)V = u$$

$$\frac{V_g - u}{V} = (1-d)$$

$$d = 1 - \frac{V_g - u}{V}$$

For figure 1(a)

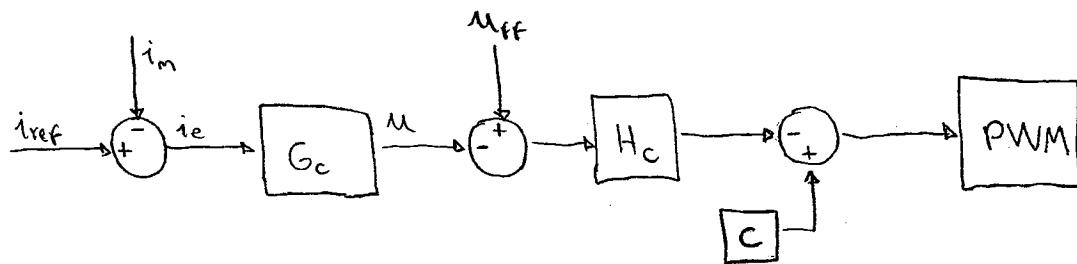

$$H_c = \frac{1}{V}$$

$$M_{ff} = V_g$$

$$C = 1$$

$$e) G_c p = \frac{\omega_g}{s}$$

$$G_c = \frac{\omega_g}{s} \frac{1}{p} \quad ; \quad p = \frac{1}{sL + R_L}$$

$$G_c = \frac{\omega_g}{s} \frac{1}{\frac{1}{sL + R_L}}$$

$$G_c = \frac{\omega_g (sL + R_L)}{s} = \frac{\omega_g L s + \omega_g R_L}{s} = \omega_g L + \frac{\omega_g R_L}{s}$$

$$G_c = k_p + \frac{k_i}{s} \rightarrow k_p = \omega_g L \quad ; \quad \omega_g = 0.1 \quad \omega_{sw} = 0.1(2\pi) f_{sw}$$

$$k_i = \omega_g R_L \quad \omega_g = 0.2\pi f_{sw}$$

$$k_p = 0.2\pi f_{sw} L$$

$$k_i = 0.2\pi f_{sw} R_L$$

$$G_{c(s)} = k_p + \frac{k_i}{s} = \frac{k_p s + k_i}{s} = \boxed{\frac{0.2\pi f_{sw} L s + 0.2\pi f_{sw} R_L}{s}}$$


Problem 2

$$k_p = 0.2\pi f_{sw} L = 0.2(\pi)(10 \times 10^3)(1.3 \times 10^{-3}) = 8.168$$


$$k_i = 0.2\pi f_{sw} R_L = 0.2(\pi)(10 \times 10^3)(60 \times 10^{-3}) = 376.991$$

$$G_{c(s)} = \frac{8.168 s + 376.991}{s}$$


Problem #2:

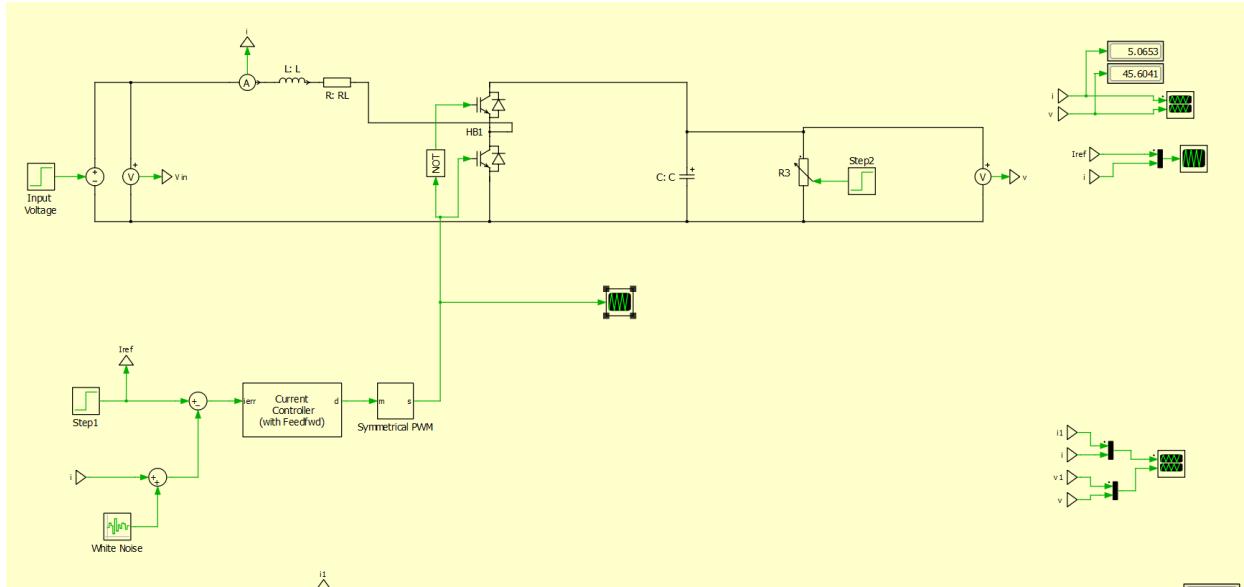



Controller With Feedforward:

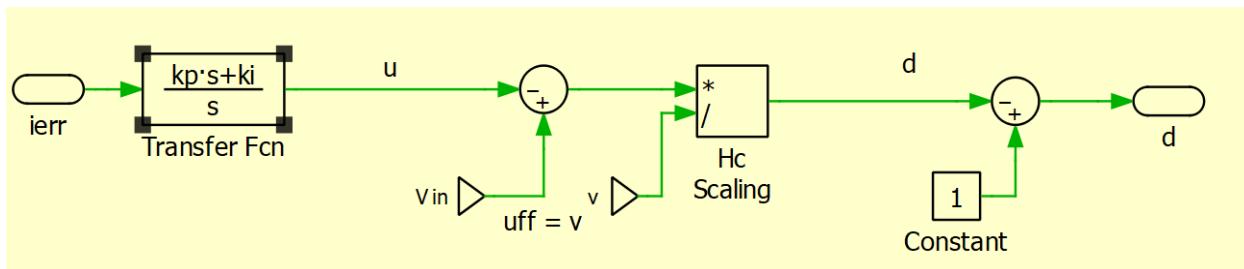


Controller Without Feedforward:

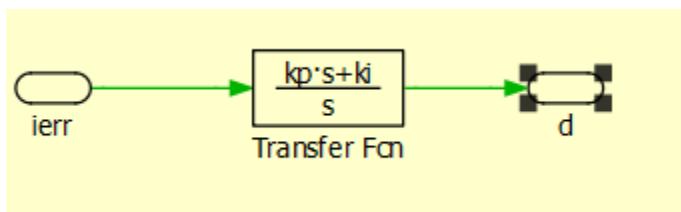

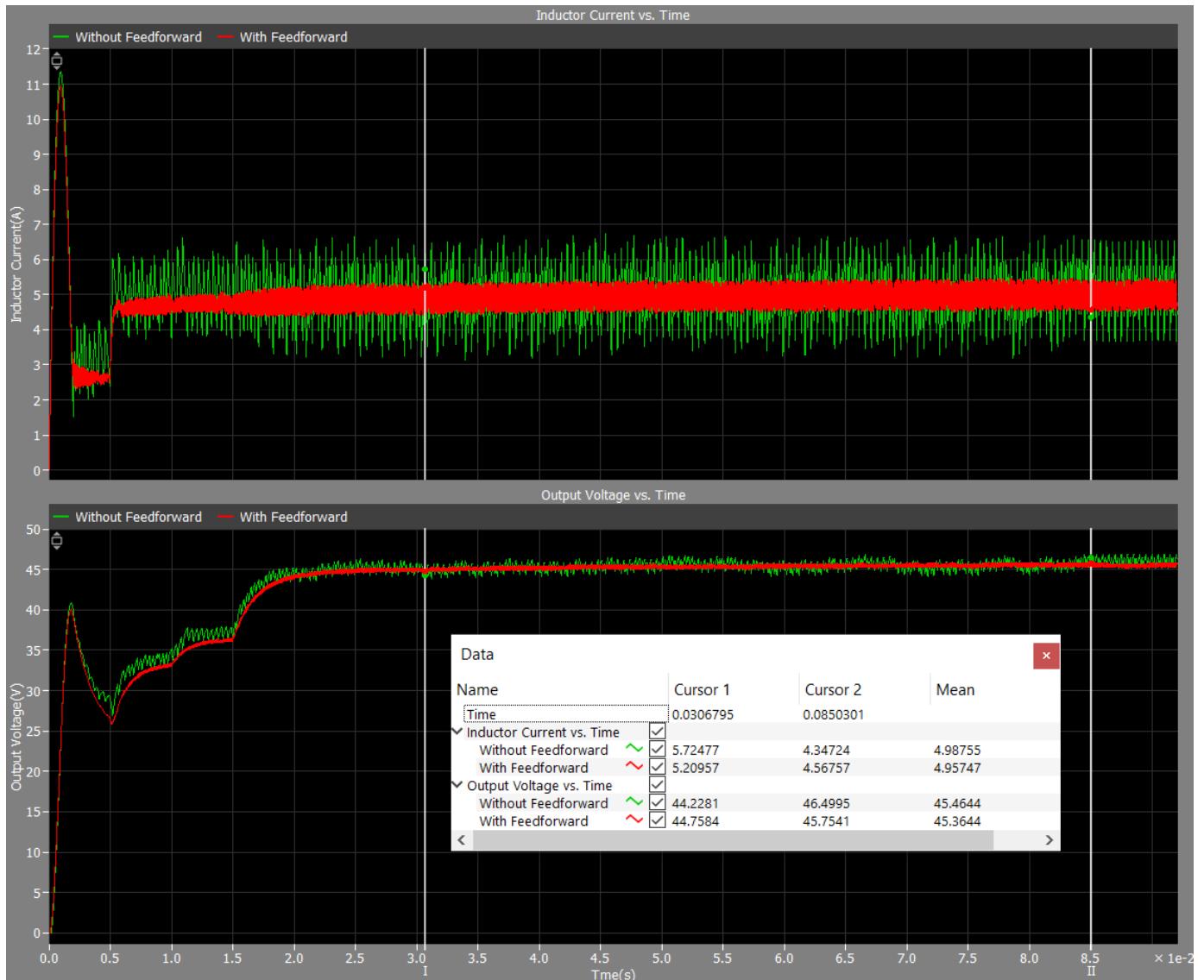

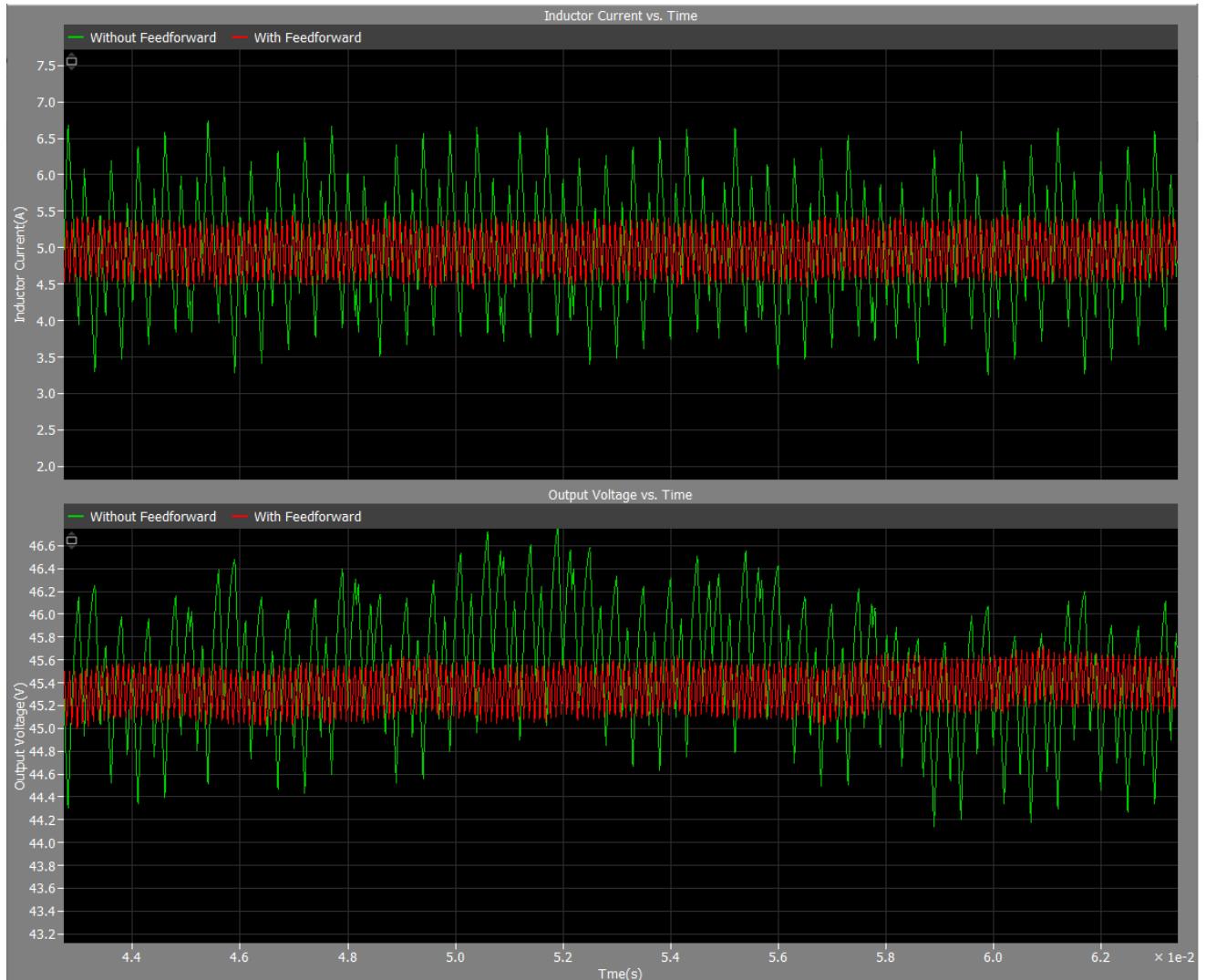

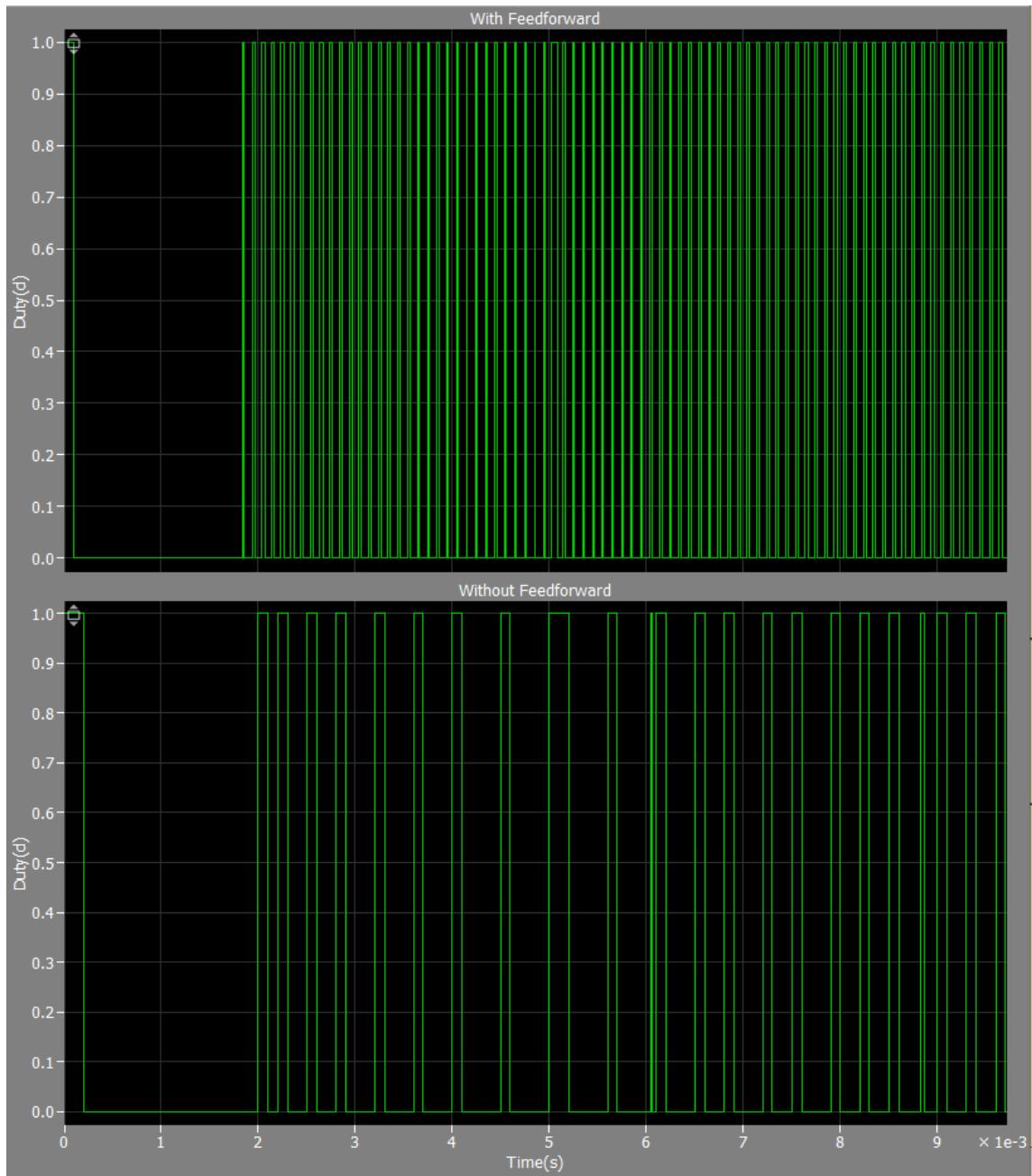


The controller with forward feedback has a much quicker response time and has less than half the current and voltage ripple. Additionally, the output signal varies less with input white noise.




Problem 2 (Rohit Gujarathi)

PROBLEM 2





Conventional Controller


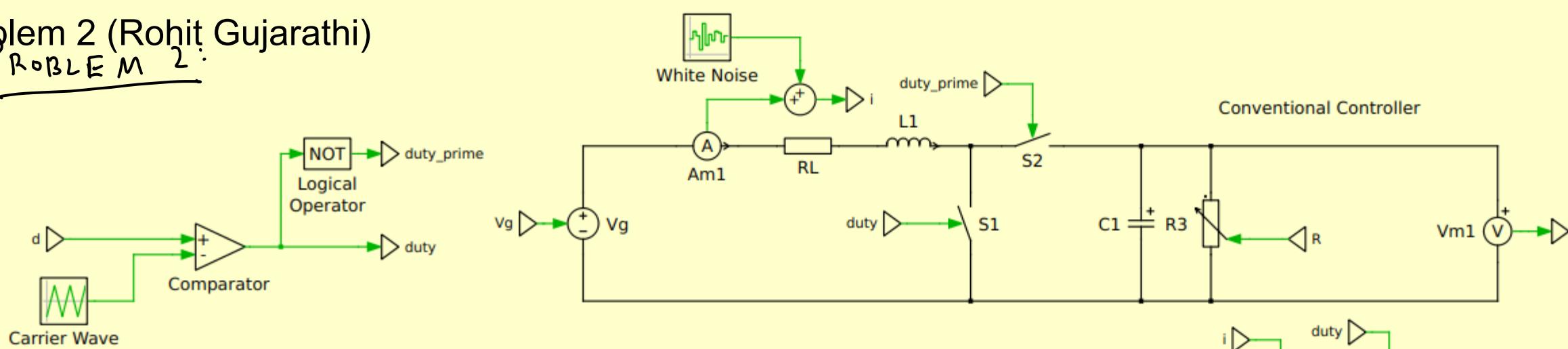


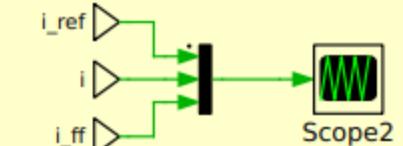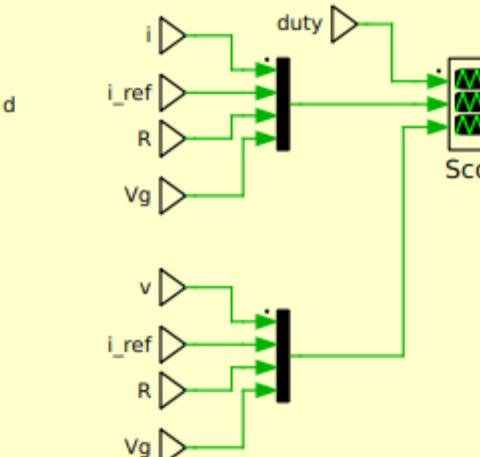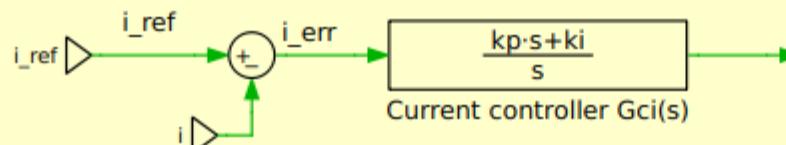V_g
 V_g _control
 i _ref
 i _ref_control
 R
 R _control



d
 d
 $Carrier\ Wave$

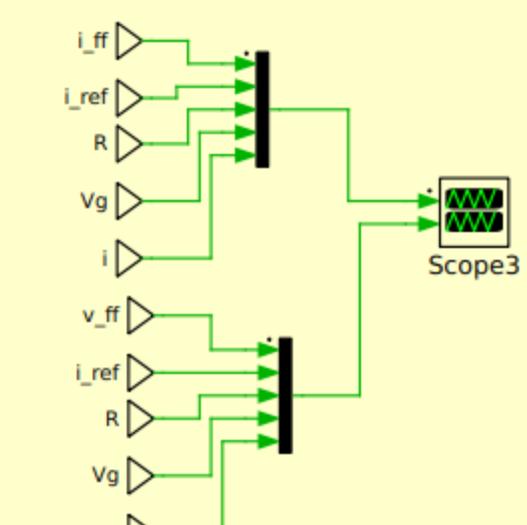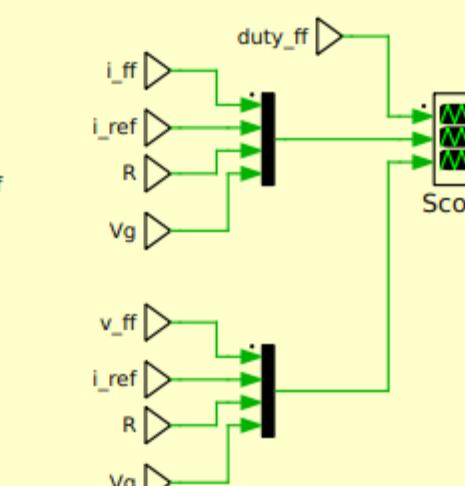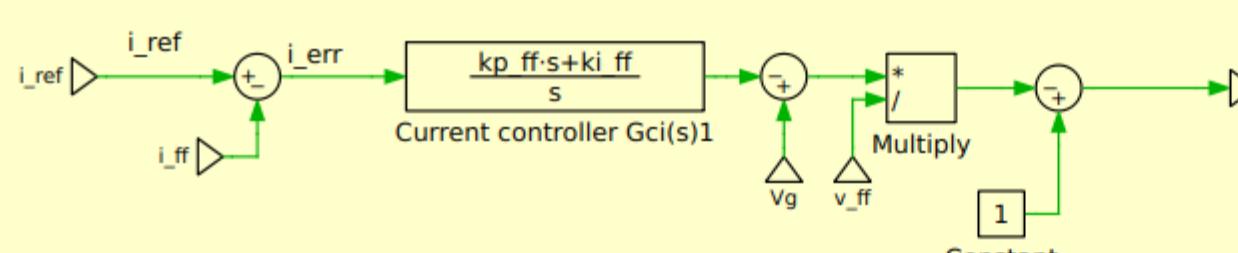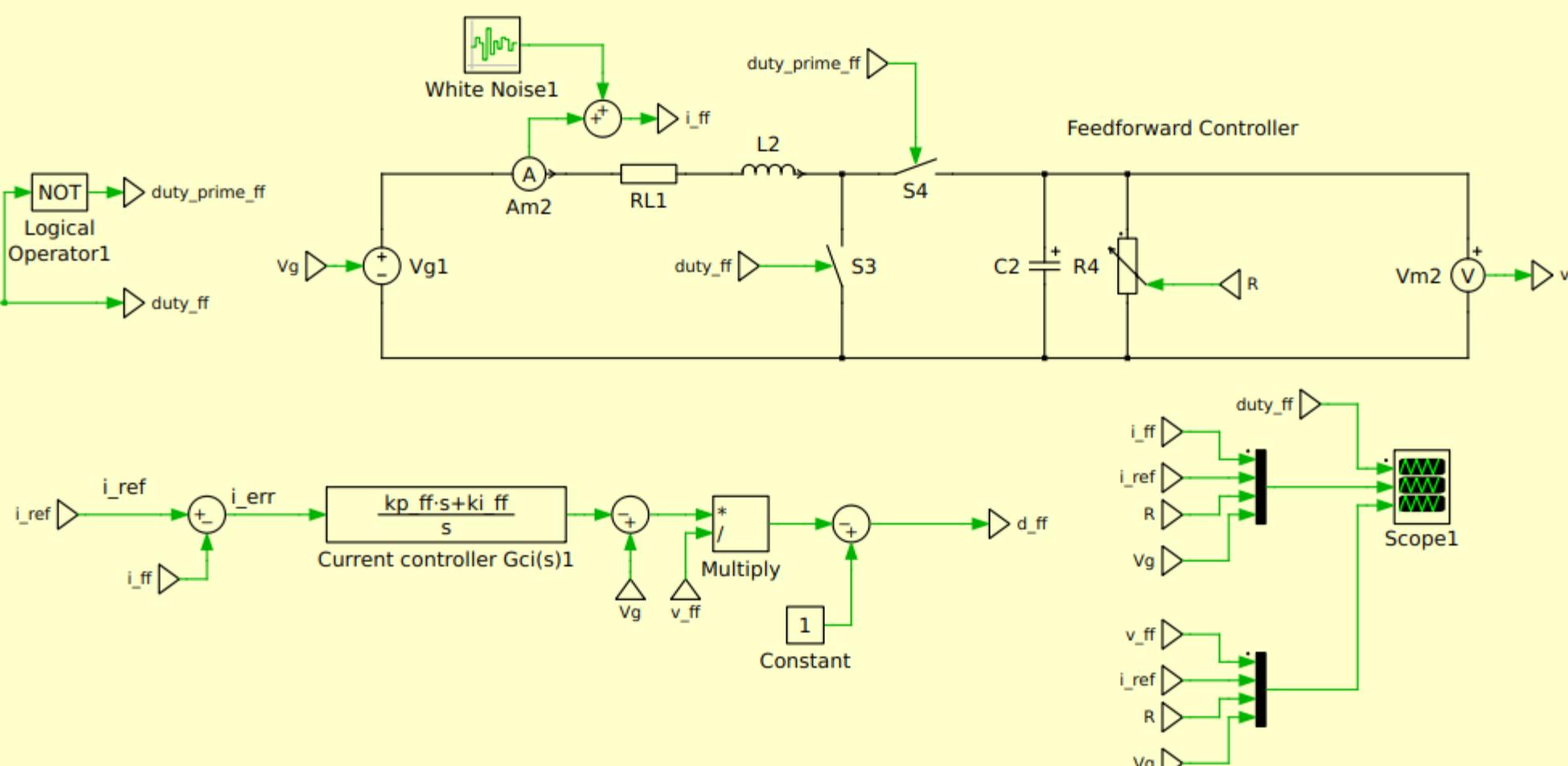

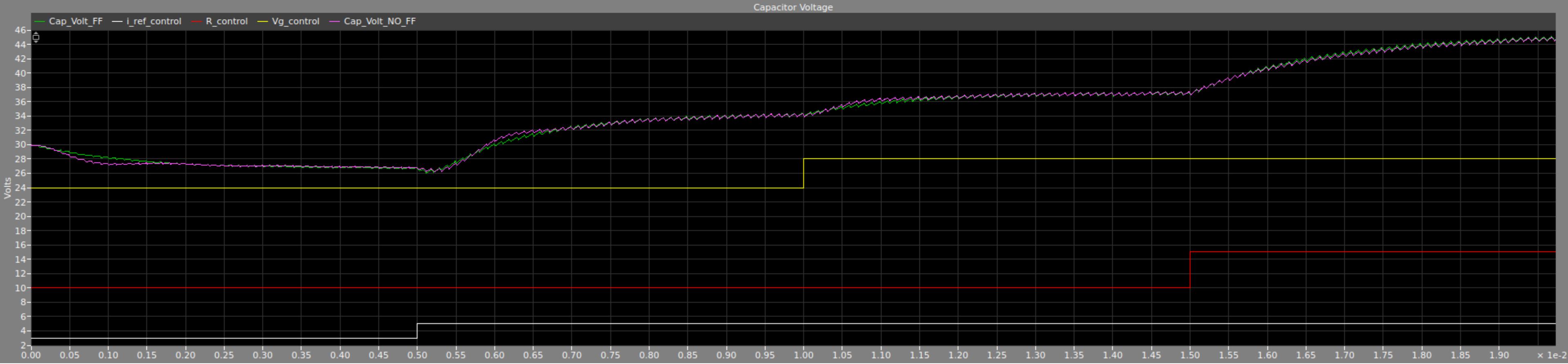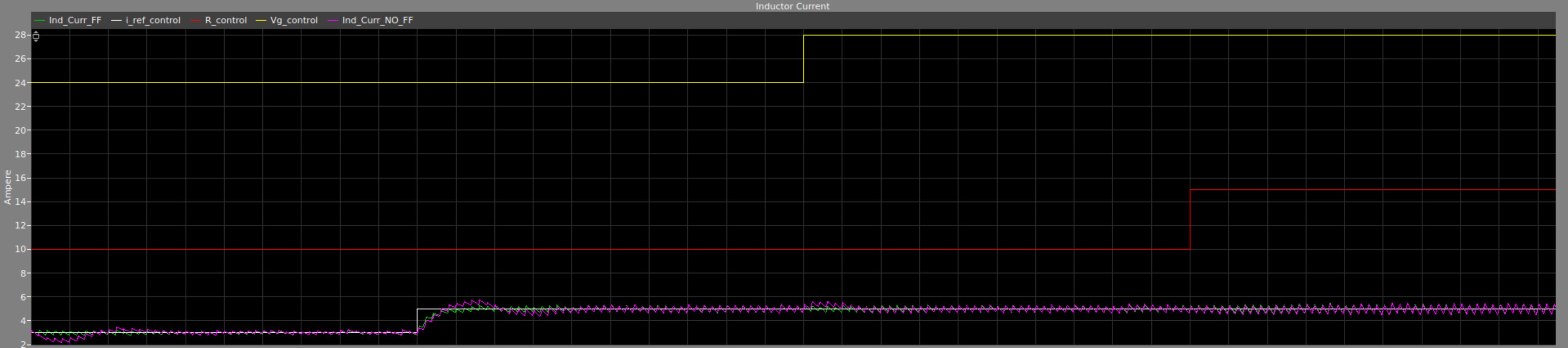

Differences

- The settling time is the same in both cases.
- The overshoot has reduced in case of feed forward.
- The risetime is the same in both cases.
- Feedforward is better at rejecting changes in V_g as can be seen at 10ms. There is a bump in the control without feedforward.
- Both are similar in rejecting changes in R .
- The control without feedforward is quick to respond to changes making the response "jerky".

Problem 3: We will build on the results from Homework 4, Using Faraday's Law, give the expressions for the induced back EMF voltages, e_a , e_b , e_c , within the a, b, and c phase windings, respectively. In addition, draw the equivalent circuits looking into the a, b, and c windings where the back EMFs, e_a , e_b , e_c , are clearly labeled along with the speed-dependent voltages \mathcal{E}_a , \mathcal{E}_b , \mathcal{E}_c and inductive voltage drops. Be careful with all circuit element polarities.

Assumptions:

- Equal number of turns for each of the coils:

$$N = N_a = N_b = N_c$$

- Maximum magnetic ring flux linking a coil is the same for each of the phase coils:

$$\Phi_{max} = \Phi_{max,a} = \Phi_{max,b} = \Phi_{max,c}$$

Flux Linkage:

- $\lambda_a = -N_a \Phi_{max,a} \cos(\theta_{e,a}) + L i_a = -N \Phi_{max} \cos(\theta_e) + L i_a$
- $\lambda_b = -N_b \Phi_{max,b} \cos(\theta_{e,b}) + L i_b = -N \Phi_{max} \cos\left(\theta_e - \frac{2\pi}{3}\right) + L i_b$
- $\lambda_c = -N_c \Phi_{max,c} \cos(\theta_{e,c}) + L i_c = -N \Phi_{max} \cos\left(\theta_e - \frac{4\pi}{3}\right) + L i_c$

Back EMF:

$$\bullet \quad e_a = -\frac{d\lambda_a}{dt} = -\frac{d}{dt}\{-N \Phi_{max} \cos(\theta_e) + L i_a\} = N \Phi_{max} \frac{d}{dt}\{\cos(\theta_e)\} - L \frac{d}{dt}\{i_a\}$$

$$= -N \Phi_{max} \sin(\theta_e) \cdot \frac{d}{dt}\{\theta_e\} - L \frac{di_a}{dt} = -N \Phi_{max} \sin(\theta_e) \cdot \omega_e - L \frac{di_a}{dt}$$

$$\boxed{e_a = -N \omega_e \Phi_{max} \sin(\theta_e) - L \frac{di_a}{dt}}$$

$$\bullet \quad e_b = -\frac{d\lambda_b}{dt} = -\frac{d}{dt}\{-N \Phi_{max} \cos\left(\theta_e - \frac{2\pi}{3}\right) + L i_b\} = N \Phi_{max} \frac{d}{dt}\{\cos\left(\theta_e - \frac{2\pi}{3}\right)\} - L \frac{d}{dt}\{i_b\}$$

$$= -N \Phi_{max} \sin\left(\theta_e - \frac{2\pi}{3}\right) \cdot \frac{d}{dt}\left\{\theta_e - \frac{2\pi}{3}\right\} - L \frac{di_b}{dt} = -N \Phi_{max} \sin\left(\theta_e - \frac{2\pi}{3}\right) \cdot \omega_e - L \frac{di_b}{dt}$$




$$\boxed{e_b = -N \omega_e \Phi_{max} \sin\left(\theta_e - \frac{2\pi}{3}\right) - L \frac{di_b}{dt}}$$

$$\bullet \quad e_c = -\frac{d\lambda_c}{dt} = -\frac{d}{dt}\{-N \Phi_{max} \cos\left(\theta_e - \frac{4\pi}{3}\right) + L i_c\} = N \Phi_{max} \frac{d}{dt}\{\cos\left(\theta_e - \frac{4\pi}{3}\right)\} - L \frac{d}{dt}\{i_c\}$$

$$= -N \Phi_{max} \sin\left(\theta_e - \frac{4\pi}{3}\right) \cdot \frac{d}{dt}\left\{\theta_e - \frac{4\pi}{3}\right\} - L \frac{di_c}{dt} = -N \Phi_{max} \sin\left(\theta_e - \frac{4\pi}{3}\right) \cdot \omega_e - L \frac{di_c}{dt}$$

$$\boxed{e_c = -N \omega_e \Phi_{max} \sin\left(\theta_e - \frac{4\pi}{3}\right) - L \frac{di_c}{dt}}$$

Equivalent Circuits:

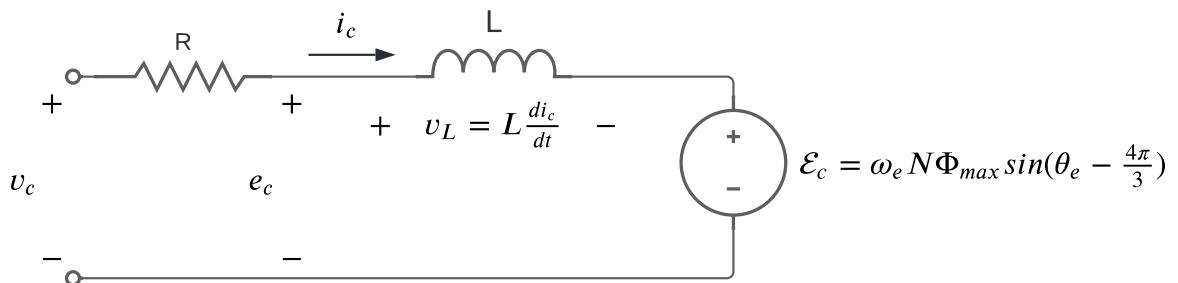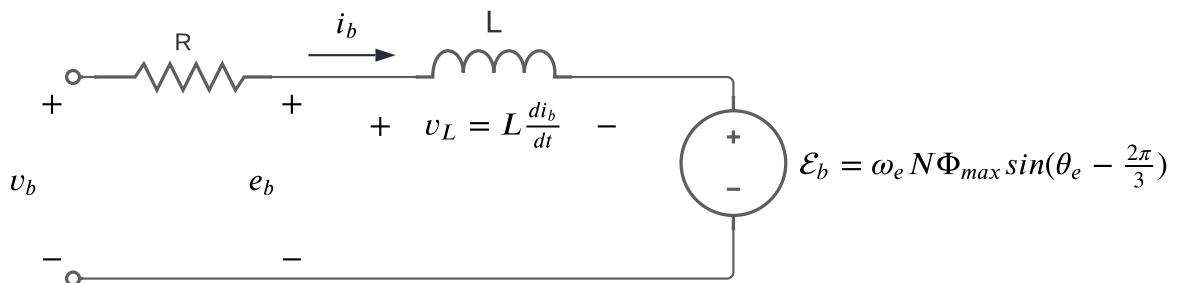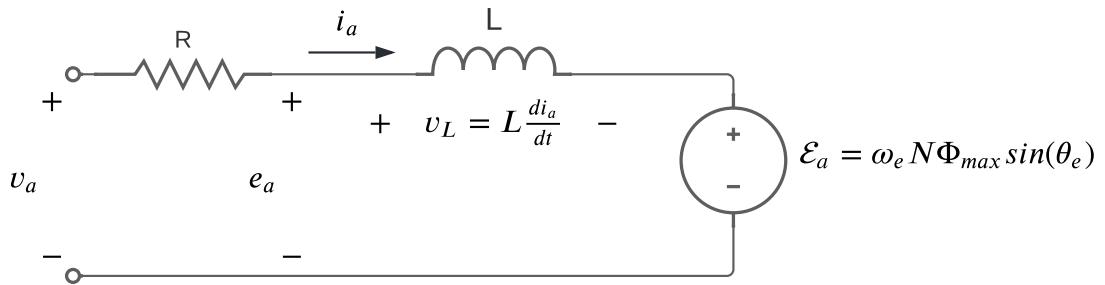

Note, the equivalent circuits also include the effects of winding resistance R , assuming that: $R = R_a = R_b = R_c$.

Notation:

- $v \rightarrow$ terminal voltage of the armature (i.e., stator) coils
- $v_L \rightarrow$ inductance of the armature coils
- $e \rightarrow$ back EMF
- $\mathcal{E} \rightarrow$ speed-dependent back EMF

Ques. 3. for phase (a)

$$\lambda_a = -N \phi_{max} \cos \theta_e + L \dot{i}_a$$

induced back EMF voltage,

$$e_a = -\frac{d \lambda_a}{dt}$$

$$= -\frac{d}{dt} (-N \phi_{max} \cos \theta_e) + L \dot{i}_a$$

$$= -N \phi_{max} \omega_e \sin \theta_e - L \frac{di_a}{dt}$$

$$e_a = N \phi_{max} \omega_e \sin \theta_e.$$

for phase (b)

$$\lambda_b = -N \phi_{max} \cos(\theta_e - \frac{2\pi}{3}) + L \dot{i}_b$$

$$e_b = -\frac{d \lambda_b}{dt}$$

$$= -N \phi_{max} \omega_e \sin(\theta_e - \frac{2\pi}{3}) + \left(-L \frac{di_b}{dt} \right)$$

$$= -N \phi_{max} \omega_e \sin(\theta_e - \frac{2\pi}{3}) - L \frac{di_b}{dt}$$

$$e_b = N \phi_{max} \omega_e \sin(\theta_e - \frac{2\pi}{3})$$

for phase C

$$\lambda_c = -N\Phi_{max} \cos(\theta_e + 2\pi/3) + L\dot{i}_c.$$

$$e_c = -\frac{d\lambda_c}{dt}.$$

$$= -\frac{d}{dt}(-N\Phi_{max} \cos(\theta_e + 2\pi/3) + L\dot{i}_c)$$

$$= -N\Phi_{max} \omega_e \sin(\theta_e + 2\pi/3) - L \frac{di_c}{dt}.$$

$$e_c = N\Phi_{max} \omega_e \cos(\theta_e + 2\pi/3)$$

$$e_c = N\Phi_{max} \omega_e \sin(\theta_e + 2\pi/3)$$

