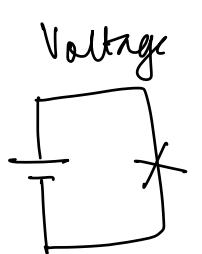


1. Overview
2. Description of System.
3. PWM & ADC
4. Basic Control System.

TA office hour : Mon 2-3 pm.

~~Prajakta~~ Mom, Wed → before 1:30 pm,  
after 3:30 pm.

Turn off some effects for ppl entering & leaving




Sources

never short

$\equiv \frac{1}{T}$  capacitors


store energy  
in electrostatic field

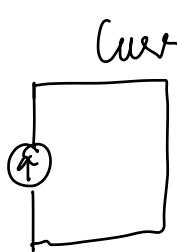


Current Sources

never open

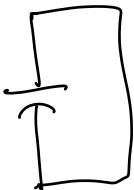
$\equiv -\infty$  inductors  
electromagnetic fields




## Overview 1.1 Using Real Time System


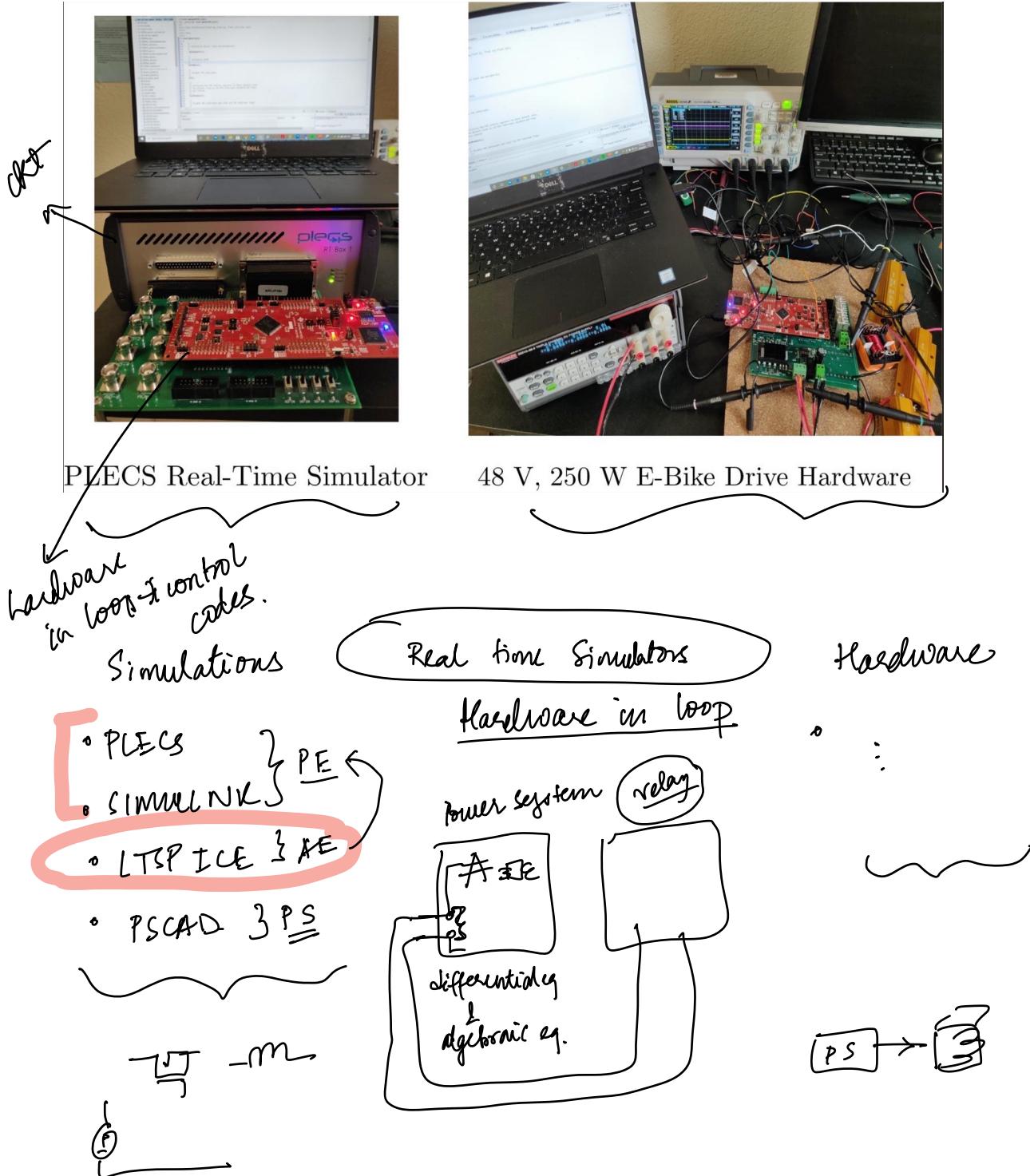


## Overview 1.2 System Description

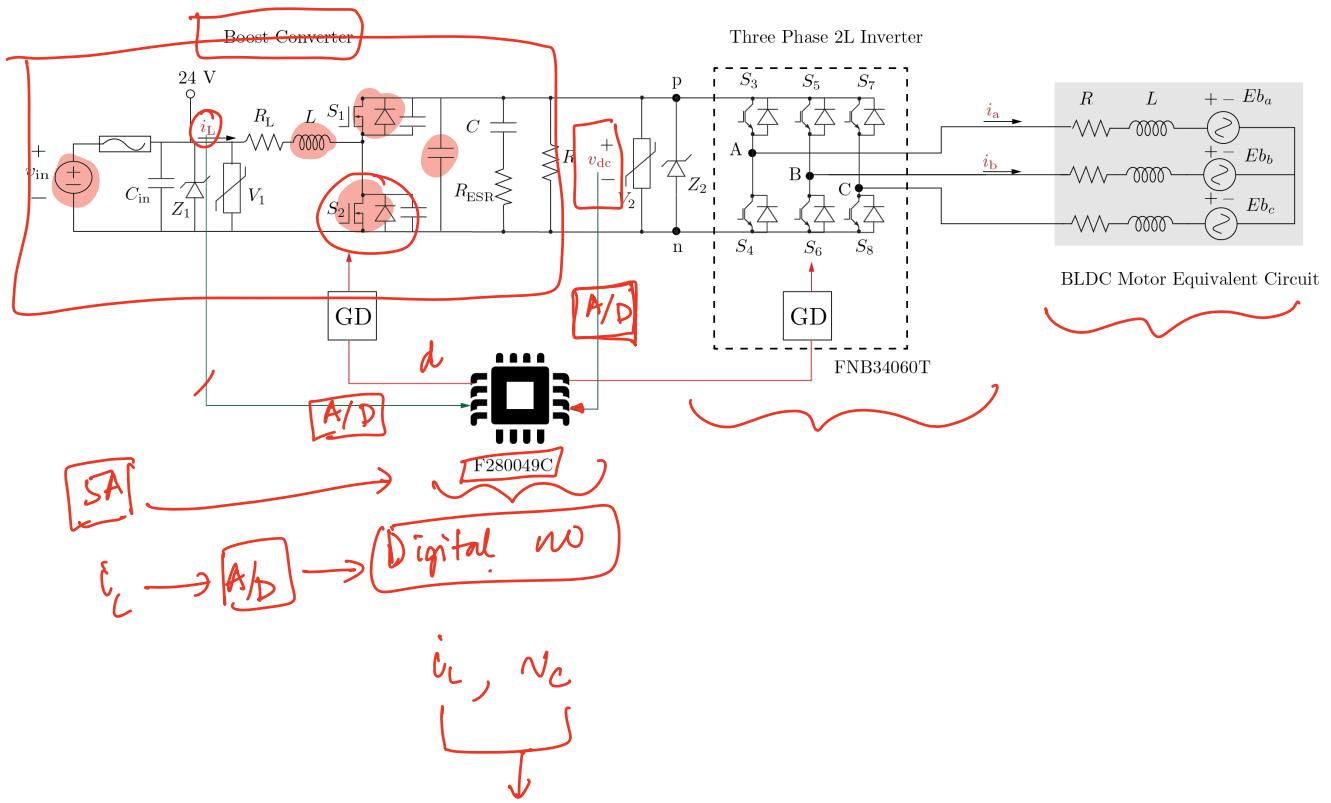

## Overview|3 Basic Diagram of Boost Converter.

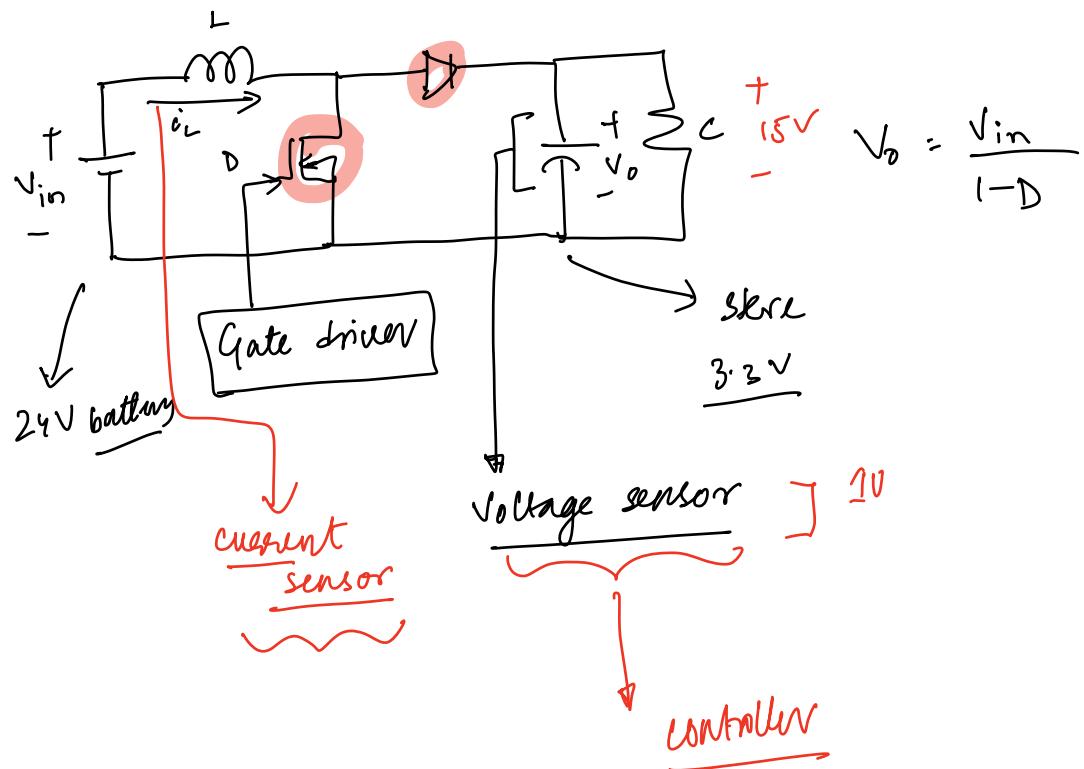

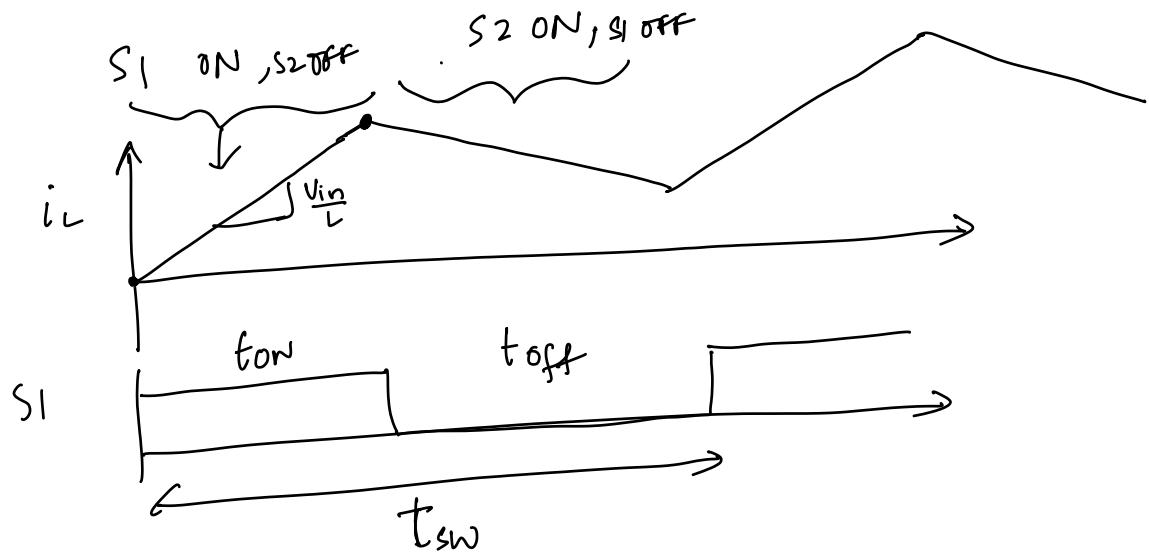
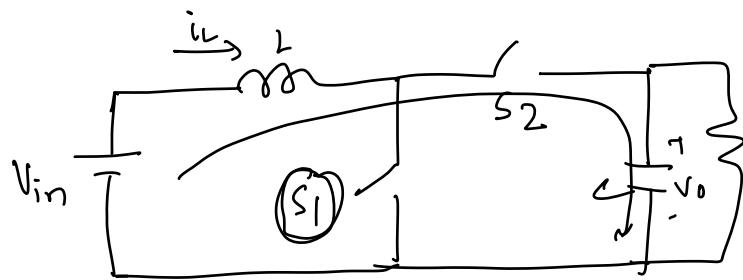


$$D = \text{Duty ratio} = \frac{t_{on}}{T_{sw}} = \frac{T_{on}}{T_{sw}} = \frac{T_{on} \cdot f_{sw}}{1}$$


$$V_{in} \left( \frac{t_{on}}{T_{sw}} \right) = (V_o - V_{in}) \left( \frac{t_{off}}{T_{sw}} \right)^{1-D}$$

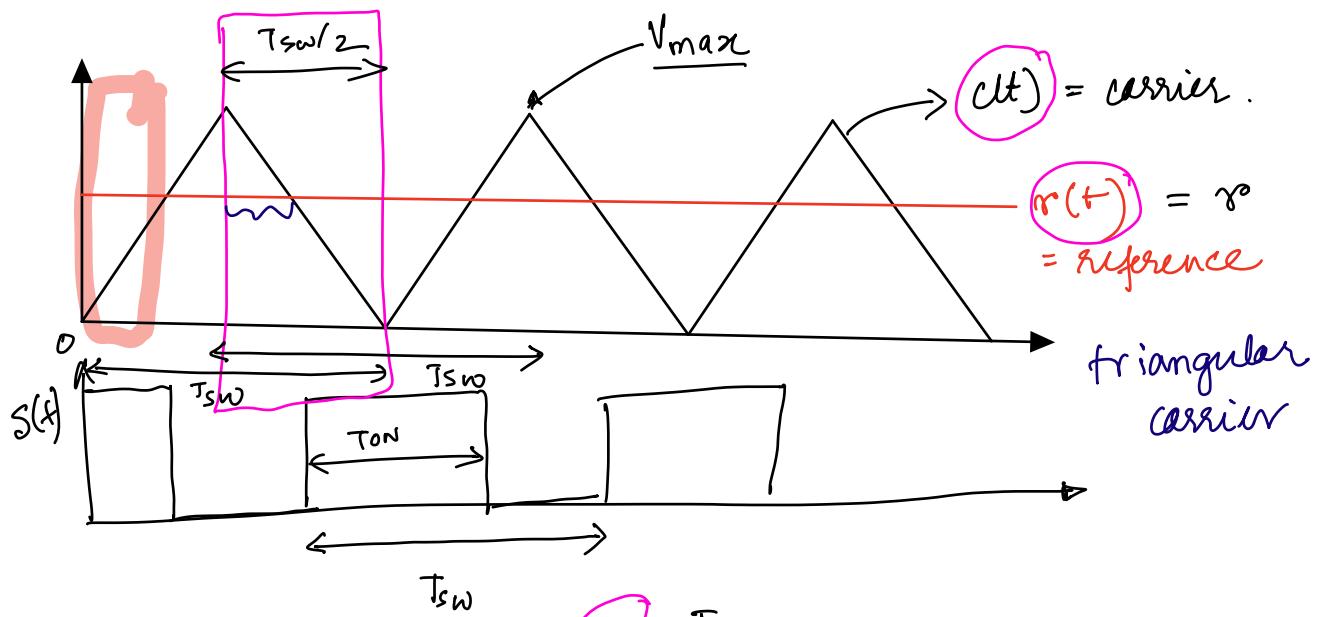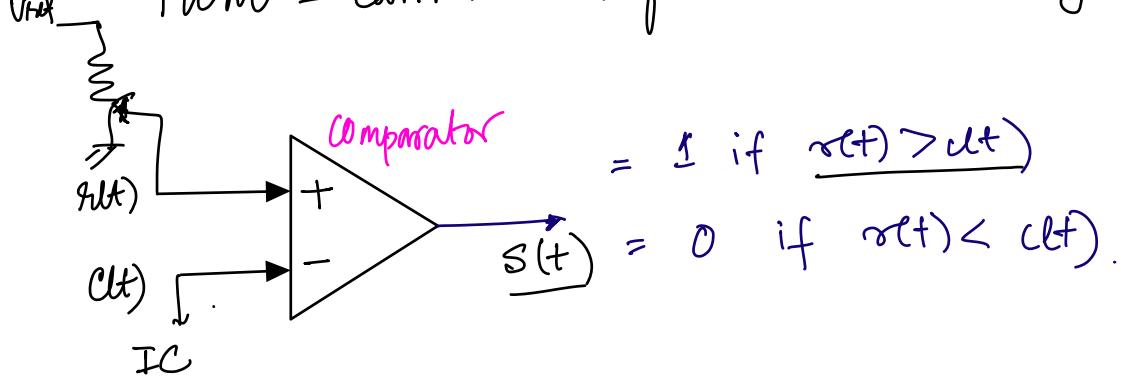
## PWFM & ADC 1.1

Vref PUFM - Carrier & reference  $\rightarrow$  Switching.



$$\alpha = \frac{T_{ON}}{T_{SW}}$$

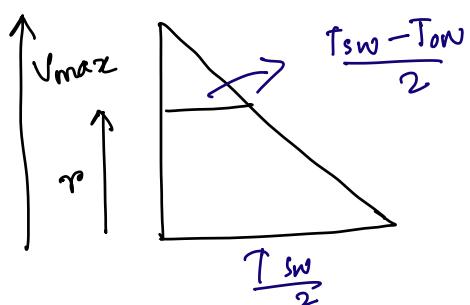

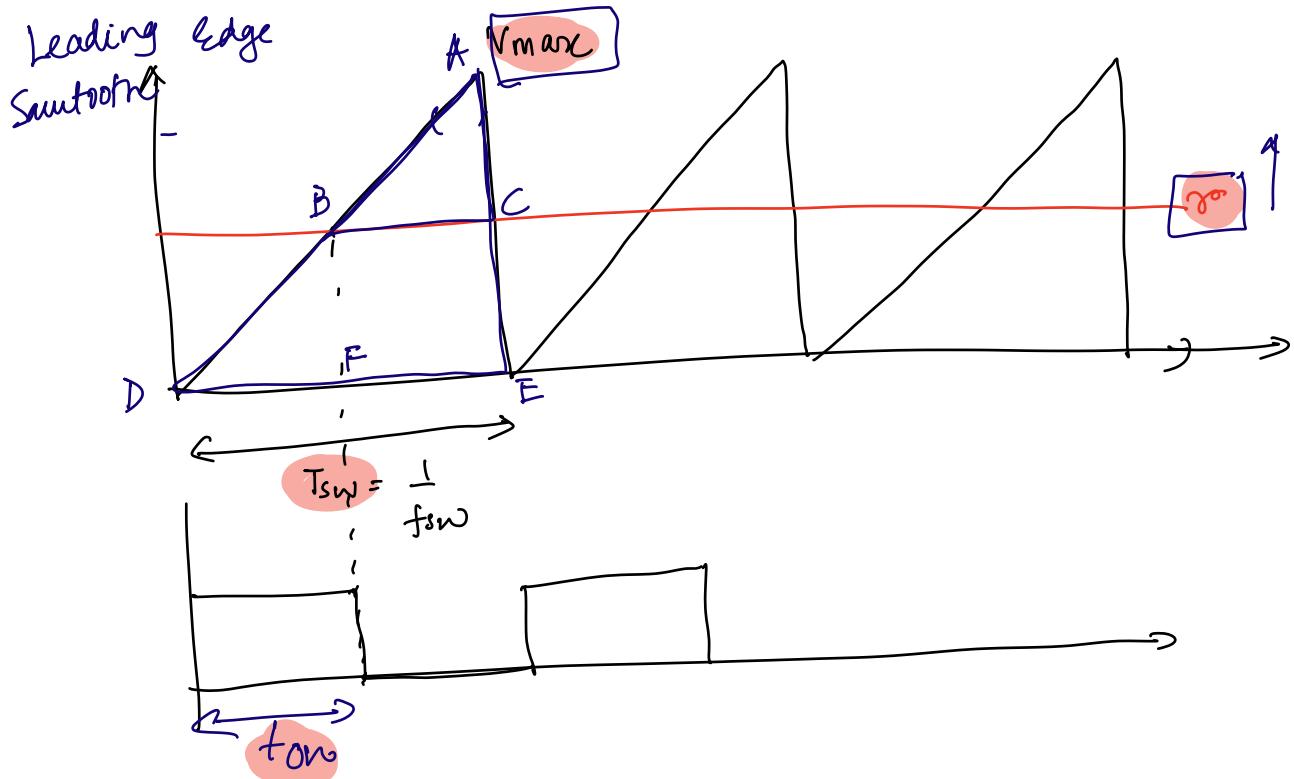





$$\Delta ABC \sim \Delta ADE$$

$$\begin{aligned} V_{\max} - r &:= \frac{AC}{BC} = \frac{AE}{DE} =: V_{\max} \\ T_{sw} - t_{on} &:= \frac{BC}{DE} =: T_{sw} \end{aligned}$$

$$\frac{V_{\max} - r}{T_{sw} - t_{on}} = \frac{V_{\max}}{T_{sw}}$$

$$\begin{aligned} D &:= \frac{t_{on}}{T_{sw}} \Rightarrow \frac{V_{\max} - r}{V_{\max}} = \frac{T_{sw} - t_{on}}{T_{sw}} \\ &\Rightarrow 1 - \frac{r}{V_{\max}} = 1 - \frac{t_{on}}{T_{sw}} \\ \therefore D &= \frac{r}{V_{\max}} \quad \boxed{D = \frac{r}{V_{\max}}} \quad \Rightarrow \frac{r}{V_{\max}} = \frac{t_{on}}{T_{sw}} = D \end{aligned}$$

## Lagging Edge sawtooth carrier

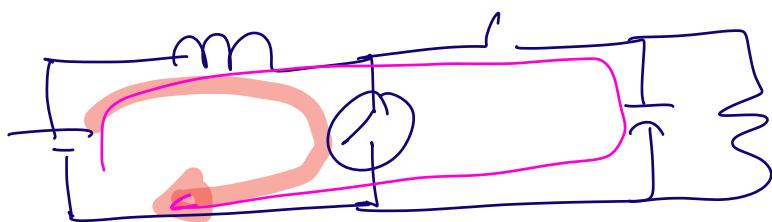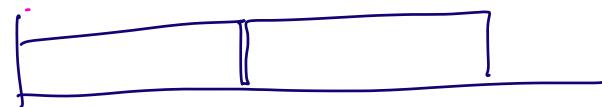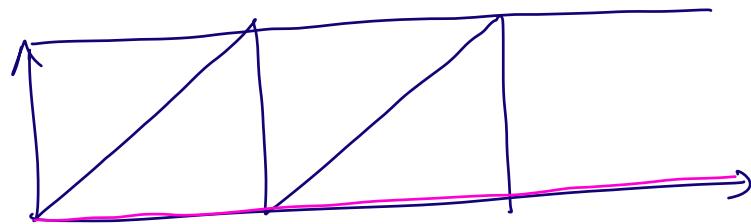
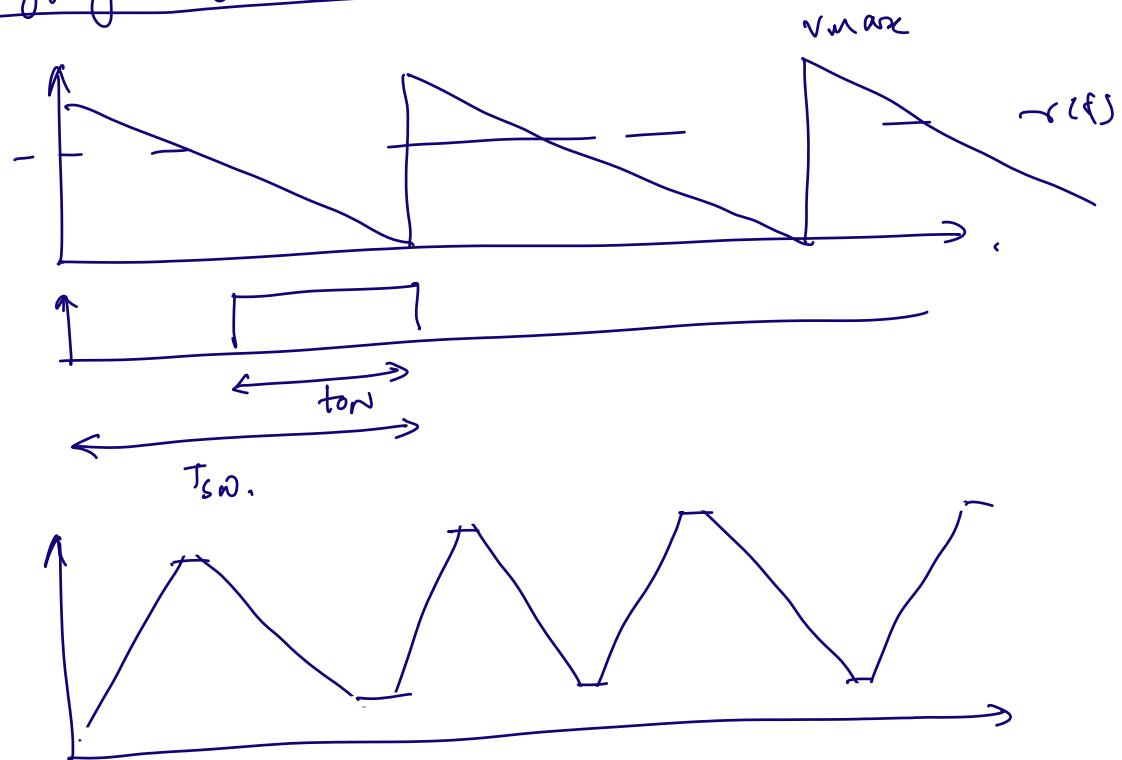


## P & A 2.1
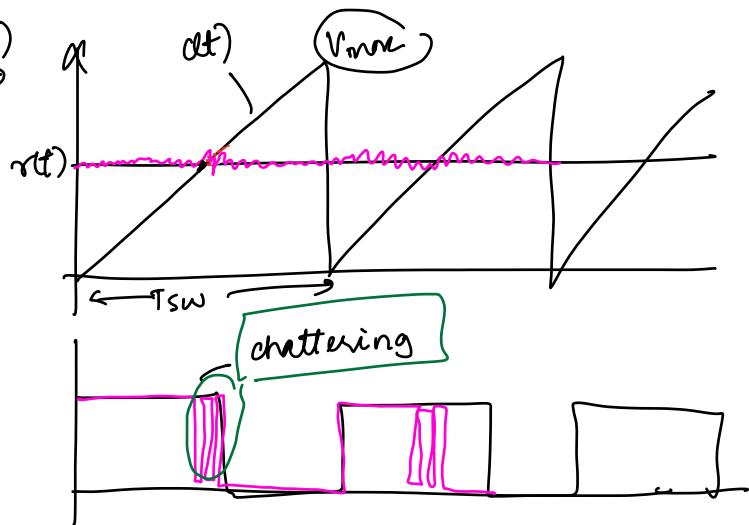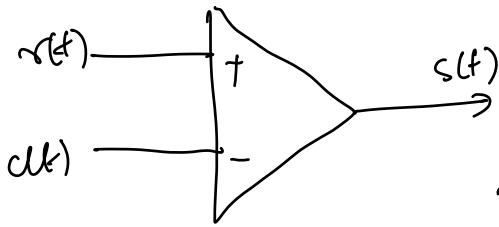
### Analog Pwm vs Digital PWM

- infinite resolution
- chattering

- no chattering
- finite resolution
- instability due to ADC interaction.







advantage

= infinite resolution


$d = \frac{r}{V_{max}}$  analog signal

$$0 < r < V_{max}$$

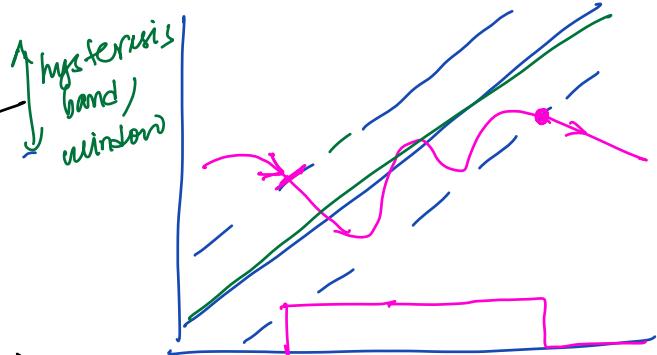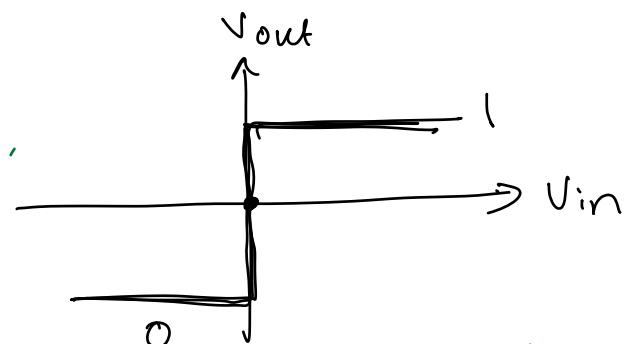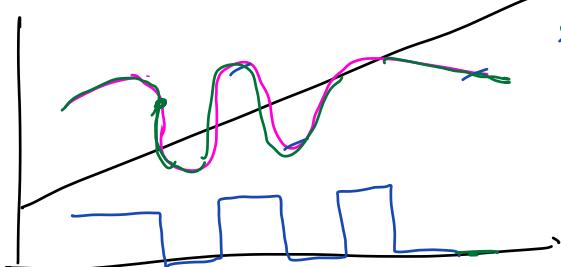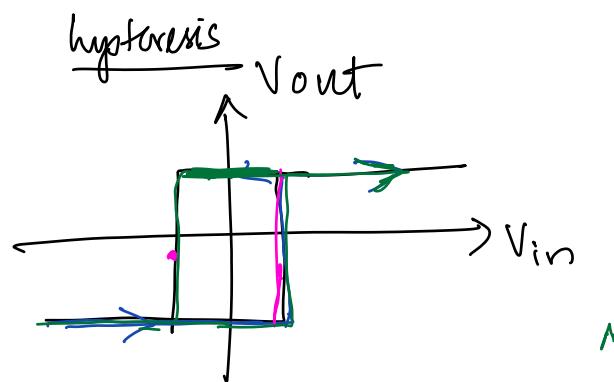

P 8 A 2.2

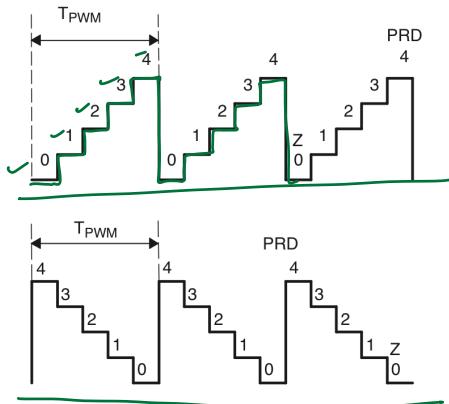
3 bits  
 $b_2 \ b_1 \ b_0$   
 $0 = 0 \ 0 \ 0$   
 $1 = 0 \ 0 \ 1$   
 $2 = 0 \ 1 \ 0$   
 $3 = 0 \ 1 \ 1$   
 $4 = 1 \ 0 \ 0$



For Up Count and Down Count  
 $T_{PWM} = (TBPRD + 1) \times T_{TBCLK}$   
 $F_{PWM} = 1 / (T_{PWM})$

bits
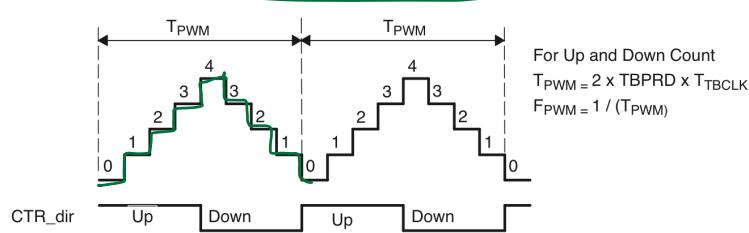
$$\begin{array}{c} b_1 \quad b_0 \\ \hline 0 = 0 \quad 0 \\ 1 = 0 \quad 1 \\ 2 = 1 \quad 0 \\ 3 = 1 \quad 1 \end{array} \} 4$$





For Up and Down Count  
 $T_{PWM} = 2 \times TBPRD \times T_{TBCLK}$   
 $F_{PWM} = 1 / (T_{PWM})$

N bits

$$2^N$$


for  $N_{pwm}$  bits,

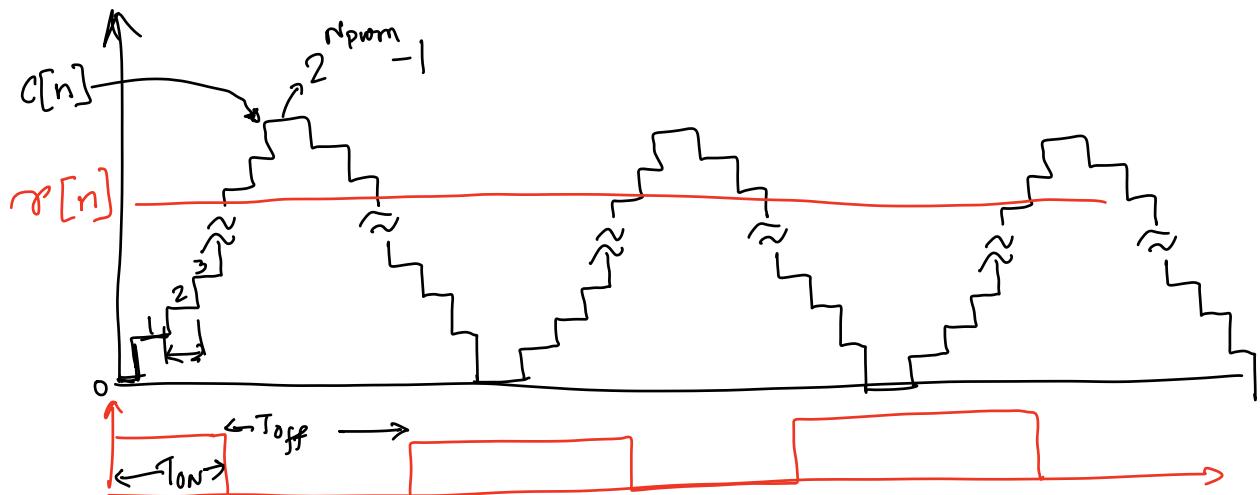
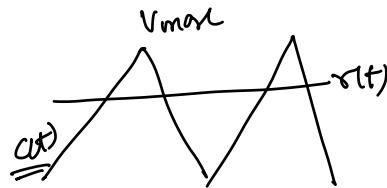
$$\begin{array}{c} N_{pwm} \\ 2 \end{array}$$



$r[n]$  = at the  $n$ th sample  $\Rightarrow$  discrete S/S.

$$N_{pwm} = 2$$

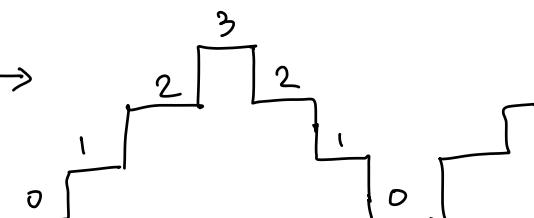

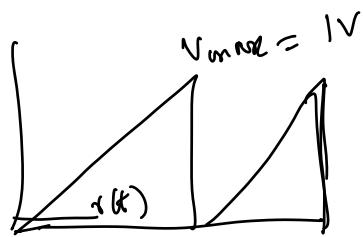
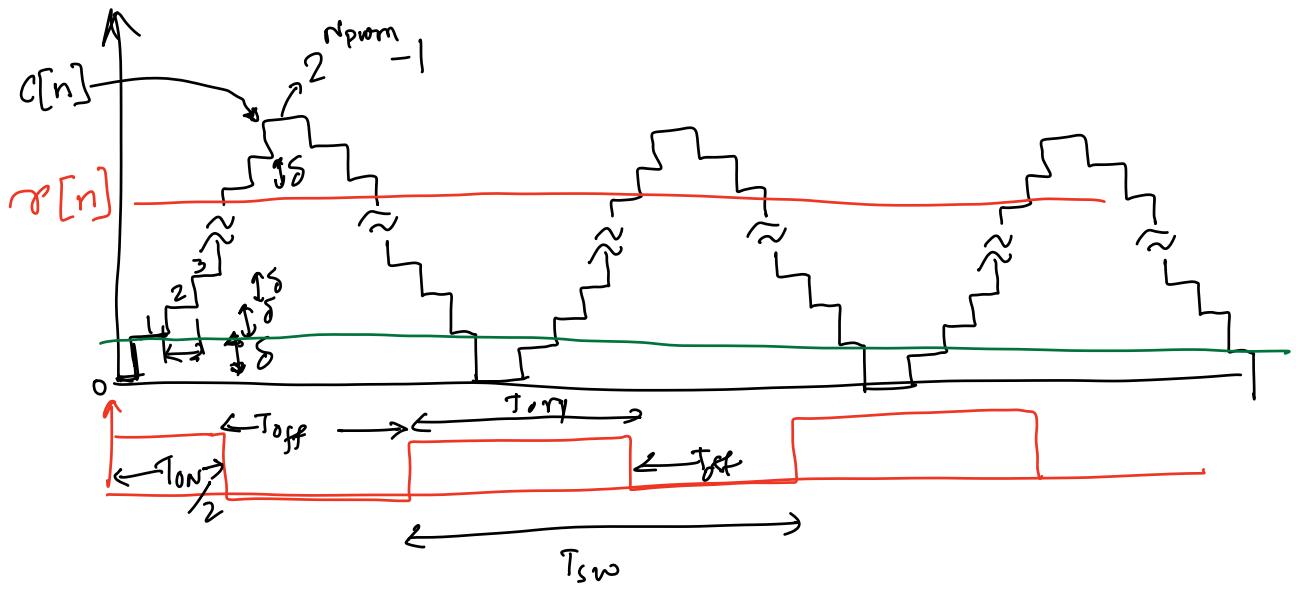


$$r(f) = 0.1 \therefore D = \frac{0.1}{1V} = 0.1$$


$$r(f) = 0.000001 \therefore D = \underline{\underline{0.000001}}$$

$$\delta = \frac{1}{2N_{\text{pwm}}} = \underline{\text{smallest duty ratio}}$$

: quantization.

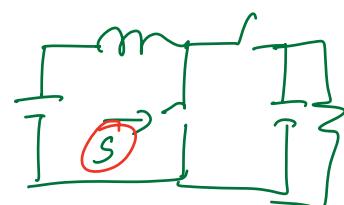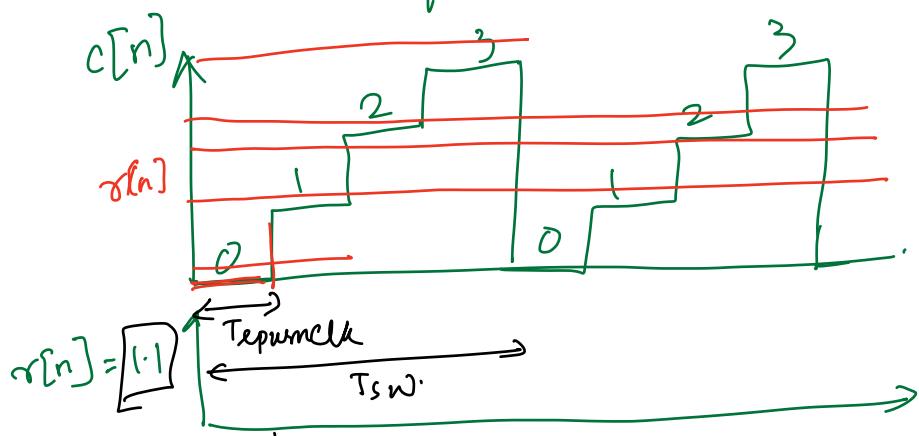

$$\delta = \frac{1}{2^2} = \frac{1}{4}$$

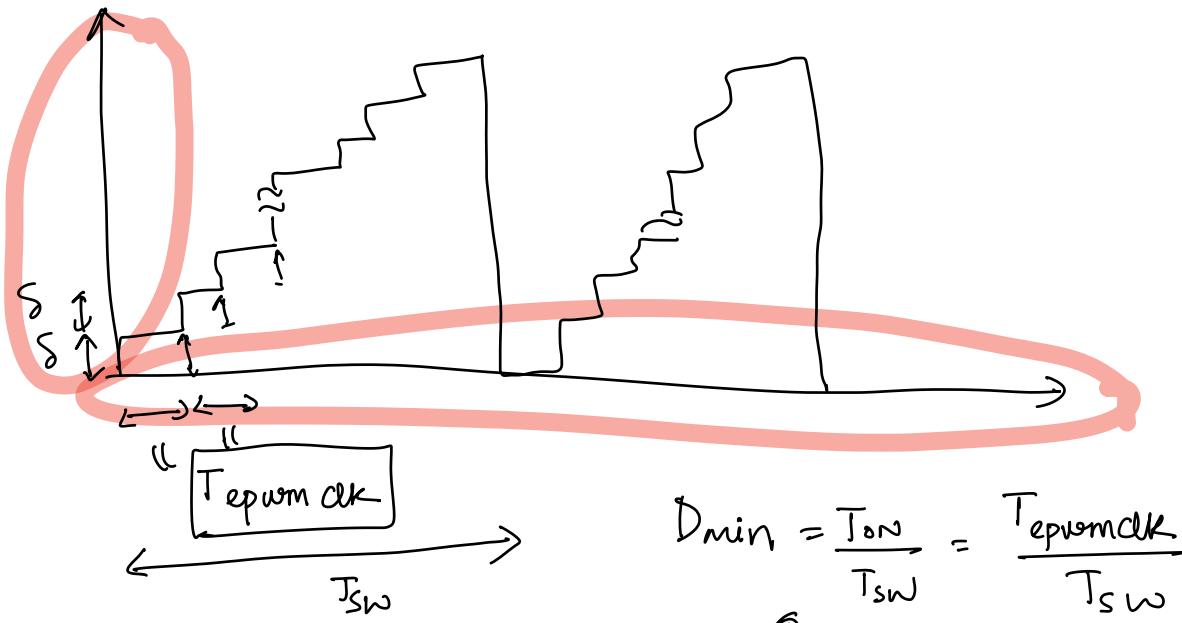


$$\delta = \frac{1}{2^{N_{pwm}}} = D_{\text{minimum}}$$

$$\frac{1}{2^{N_{pwm}}} = \frac{T_{epwm\,clk}}{T_{sw}} = \frac{f_{sw}}{\text{frequency clk}}$$

Q Boost converter. switching freq = 50 kHz.

Epwm clock = 50 MHz

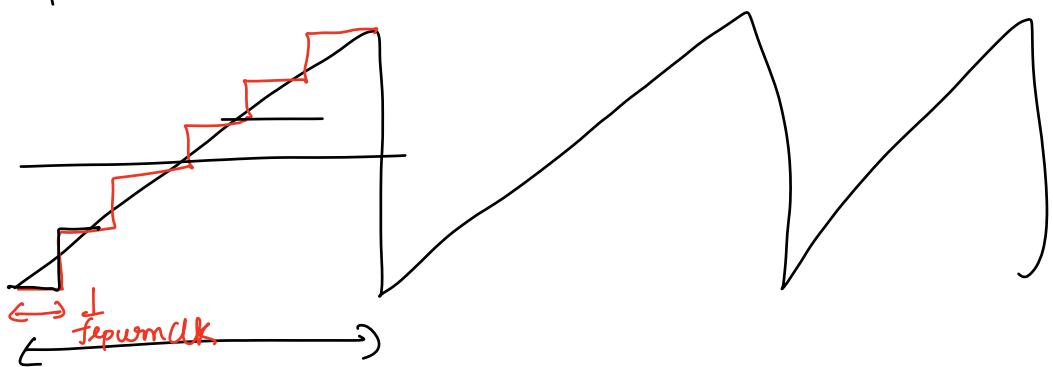


$$\frac{1}{f_{sw}} = T_s$$

$q = \text{quantization} = \text{smallest duty ratio} = \frac{f_{\text{sw}}}{f_{\text{switch}}}$

$$= \frac{50 \text{ K}}{50 \text{ M}} = \frac{1}{10^3} = \frac{1}{1000}$$

$\boxed{= 0.001}$

Boost converter

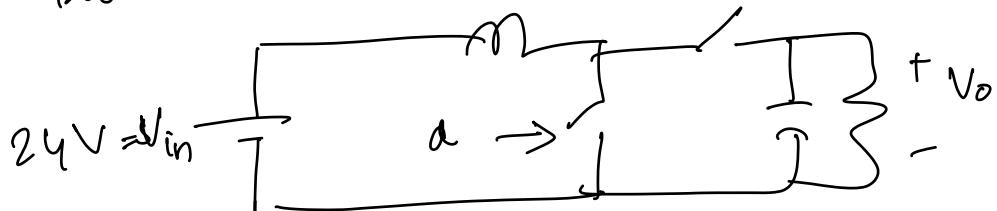

$$V_o = \frac{V_{in}}{1-D}$$

Let's say  $D = 0.5$   $V_o = \frac{24}{0.5} = 48$

$$D = 0.501 \xrightarrow{\quad} V_o = \frac{24}{1-0.501} = 48.096 \text{ V}$$

$$\Delta V_o = 48.096 \text{ V} - 48 \text{ V}$$

$\boxed{\Delta V_o = 0.096 \text{ V}}$

48.99996

$$\left. \begin{aligned} q &= \text{quantization} = \text{smallest duty ratio} = \frac{f_{sw}}{f_{epuemeck}} \\ &= \frac{50\text{K}}{50\text{M}} = \frac{1}{10^3} = \frac{1}{1000} \\ &\quad \boxed{= 0.001} \end{aligned} \right\}$$

Q: How many bits do you need?  $N_{pwm} = ?$

$$\frac{1}{2^{N_{pwm}}} = \frac{T_{epuemeck}}{T_{sw}} = \frac{f_{sw}}{f_{epuemeck}}$$

$$f_{sw} = 50\text{kHz}, \quad f_{epuemeck} = 150\text{kHz}.$$


$$\frac{1}{2^{N_{pwm}}} = \frac{50}{150} = \frac{1}{3}.$$

$$\boxed{0, 1, 2, 3} \quad N_{pwm} = \underline{2 \text{ bits}}$$

$$f_{epuemeck} = 250\text{kHz}$$

$$\boxed{\frac{1}{2^{N_{pwm}}} = \frac{50}{250} = \frac{1}{5}} \quad !! \text{Not an equality}$$

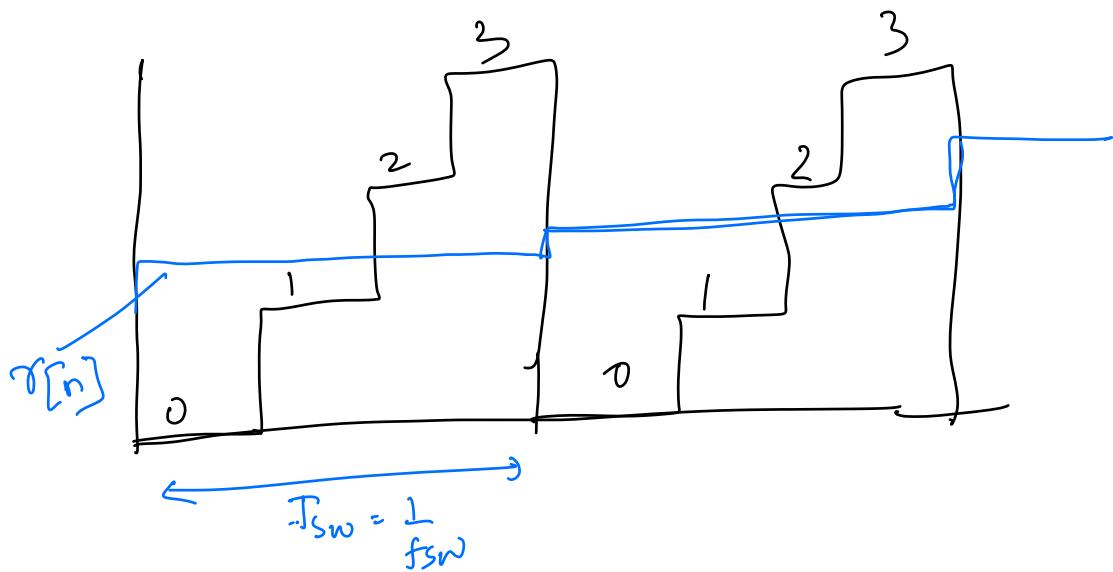
$$\boxed{2^{N_{pwm}}} > \frac{f_{epuemeck}}{f_{sw}} \Rightarrow 2^? \geq 1000 \quad \boxed{N_{pwm} = 10}$$





→ No chattering for digital PWM

→ Problem exists of limited resolution.

$\oplus$

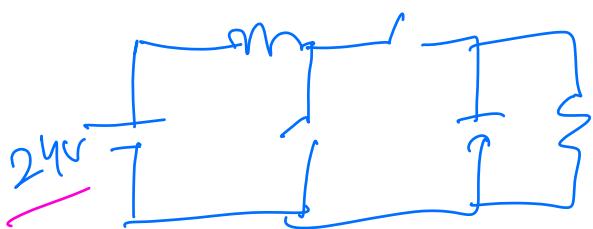


$$N_{\text{pwm}} = 2$$

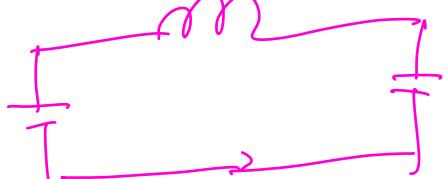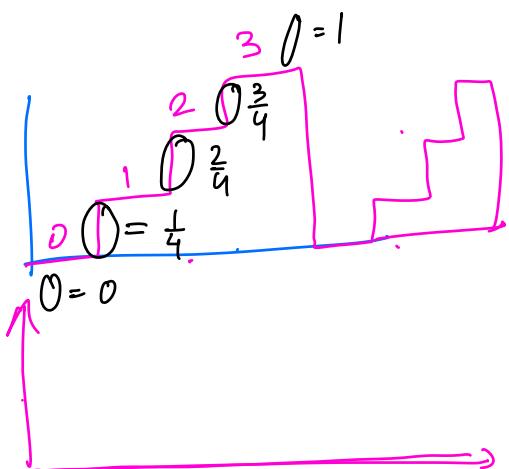

$$D_{\min} = \frac{1}{2^2} = \frac{1}{4}$$
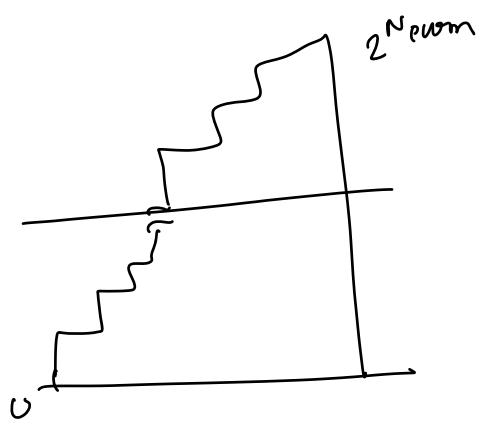
$$V_0 = ? \quad \text{possible } D = \left[ 0, \frac{1}{4}, \frac{1}{2}, \frac{3}{4}, 1 \right] \quad \left\{ 0, \frac{1}{4}, \frac{2}{4}, \frac{3}{4}, \frac{4}{4} \right\} \Rightarrow \frac{V_{\text{out}}}{24, 48, \dots}$$



$$d = 0.5$$

$$r = \frac{2^{N_{pwm}}}{2}$$

0.25

$$d = \frac{r}{V_{max}} = \frac{2^{N_{pwm}} \times d}{2^{N_{pwm}}}$$

Plum 2 ADC 1.1

"Peak-Malley Sampling"