

EE 559/400 – Power Electronics Controls, Winter 2019

Homework 4

Due Date: Friday March 15th, 2019, 5pm

Instructions. You must scan your completed homework assignment into a pdf file, and upload your file to the Canvas Assignment page by 5 pm Pacific Time on Friday March 15th, 2019. All pages must be gathered into a single file of moderate size, with the pages in the correct order. Set your phone or scanner for basic black and white scanning. You should obtain a file size of hundreds of kB, rather than tens of MB. I recommend using the “Tiny Scanner” app. Please note that the grader will not be obligated to grade your assignment if the file is unreadable or very large.

Problem 1: See Figure 1 on the next page. Consider the signal chain from a current $i(t)$, through a hall-effect sensor, an op-amp circuit, an analog to digital converter (ADC), and a subsequent inversion calculation that is designed to recover the current as $i_m[n] \approx i(t)$. Below are the system constraints, ratings, and notation to be mindful of:

- The converter is rated to consume ac current swings between $-i_{pk} \leq i \leq i_{pk}$ when transferring full power.
- The current sensor output voltage, v_s , is

$$v_s(t) = G_s i(t) + v_{dc} \quad (1)$$

where G_s is the sensor gain in units of V/A, and v_{dc} is the dc offset voltage at the sensor output.

- The op-amp has feedback and input resistors R_f and R_i , respectively. This circuit is fed by the sensor output voltage, v_s , and an adjustable dc-bias voltage v_x provided by an IC or a voltage divider. The op-amp output voltage, which is denoted as $v_{A/D}$, is fed to the ADC pin.
- The ADC has an analog sensing range between 0V and V_{FS} , and the digital output is an unsigned integer, x , with 2^n bits.

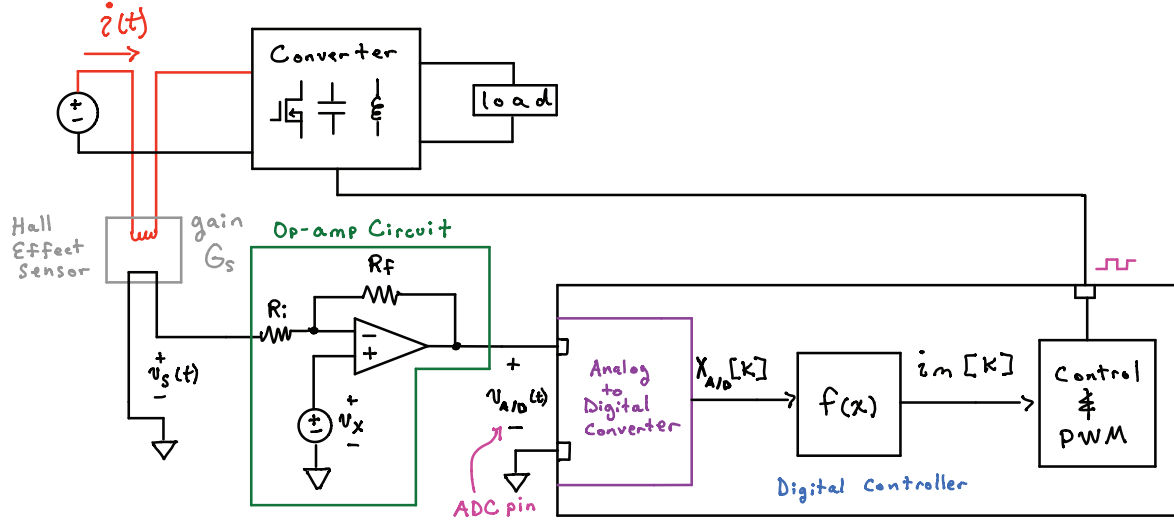


Figure 1: A physical current, $i(t)$, and its measurement signal-chain.

- (a) Derive an analytic expression for the voltage that appears across the ADC pin, $v_{A/D}$, in terms of v_x , R_f/R_i , G_s , v_{dc} , and i . Hint: Use the provided handout on the op-amp “Golden Rules.”
- (b) Consider the following design objectives:
- When $i = 0$, the ADC pin voltage should be at the midpoint $v_{A/D} = V_{FS}/2$.
 - When the current swings to the positive and negative peaks (i.e., $|i| = i_{pk}$), the ADC pin voltage equals

$$\begin{aligned} v_{A/D} &= V_{FS} - \epsilon, & \text{for } i = -i_{pk} \\ v_{A/D} &= \epsilon, & \text{for } i = i_{pk} \end{aligned}$$

where $\epsilon \ll V_{FS}/2$ is a small safety margin (typically a few percent of the ADC analog input voltage range) to prevent damage to the ADC.

Sketch the ADC pin voltage, $v_{A/D}$, and full-rated converter current, $i = i_{pk} \sin(2\pi t/T_{ac})$, over one sinusoidal AC cycle of period T_{ac} . You can ignore the effect of ripple. Clearly label $\pm i_{pk}$ points on the $i(t)$ plot. Clearly label V_{FS} , $V_{FS}/2$, and ϵ on the $v_{A/D}(t)$ plot.

- (c) Design the parameters v_x and R_f/R_i to achieve the objectives in (b). Express v_x and R_f/R_i in terms of V_{FS} , ϵ , G_s , i_{pk} and v_{dc} .
- (d) Substitute your result from (b) into (a), and show that the ADC pin voltage is

$$v_{A/D}(t) = \frac{V_{FS}}{2} \pm (?) i(t). \quad (2)$$

Fill in the blanks in red with the correct sign and specify the factor in terms of the sensor gain G_s and op-amp resistor ratio R_f/R_i .

- (e) Derive an analytic expression for $x_{A/D}[n]$ in terms of the number of bits $n_{A/D}$ and the ADC analog voltage $v_{A/D}$. To capture quantization from the ADC, use the “round(\cdot)” operator to denote the conversion to an integer value.


- (f) Using your result in (d) and (e), derive the digitally implemented formula which recovers an estimate of the physical current, which we denote as $i_m[n]$. Your result should be given in the form

$$i(t) \approx i_m[n] = mx_{A/D}[n] + b \quad (3)$$


where both m and b are written in terms of R_f/R_i , V_{FS} , G_s , and the number of bits $n_{A/D}$.

Sensing Path Design For AC Signals

Consider the signal chain:

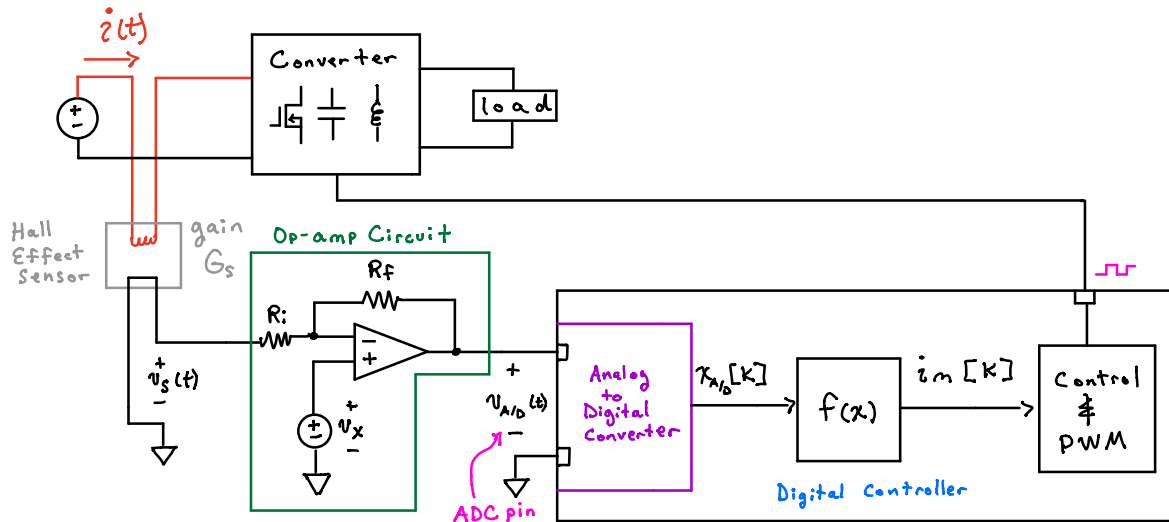

a) Closer look @ op-amp

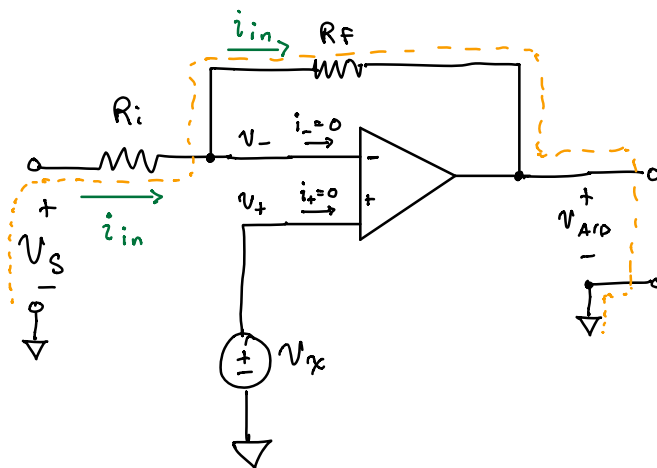

• Apply Golden Rule # 1

Since $i_- = i_+ \approx 0$

then i_{in} flows through $R_f \neq R_i$.

Look @ KVL loop

$$0 = V_s - i_{in}(R_i + R_f) - V_{A/D} \quad (1)$$

• Apply Golden Rule #2

$$\underbrace{V_- = V_+}_{\text{Rule \#2}} = \underbrace{V_x}_{\oplus \text{ terminal}} = \boxed{V_s - i_{in} R_{in}} \quad (2)$$

from input side

$$= \boxed{V_{A/D} + i_{in} R_f} \quad (3)$$

from output side
 \ominus terminal

solve for i_{in} using (2)

$$\Rightarrow i_{in} = \frac{V_s - V_x}{R_{in}} \quad (4)$$

Rearrange (3) to obtain $V_{A/D}$

$$\begin{aligned} \Rightarrow V_{A/D} &= V_x - i_{in} R_f \\ &\quad \times \text{ use (4)} \\ &= V_x - \left(\frac{V_s - V_x}{R_{in}} \right) R_f \end{aligned}$$

$$= v_x - \frac{R_f}{R_i} (v_s - v_x) \quad (5)$$

$$= v_{A/D}$$

• Use sensor equation. Recall


$$v_s = G_s i + v_{dc} \quad (6)$$

(6) \rightarrow (5) gives


$$v_{A/D} = v_x - \frac{R_f}{R_i} (G_s i + v_{dc} - v_x)$$

$$= \underbrace{v_x \left(1 + \frac{R_f}{R_i}\right) - \frac{R_f}{R_i} v_{dc}}_{\text{dc offset terms}} - \underbrace{\frac{R_f}{R_i} G_s i}_{\text{sensed signal term}} \quad (7)$$

(a)

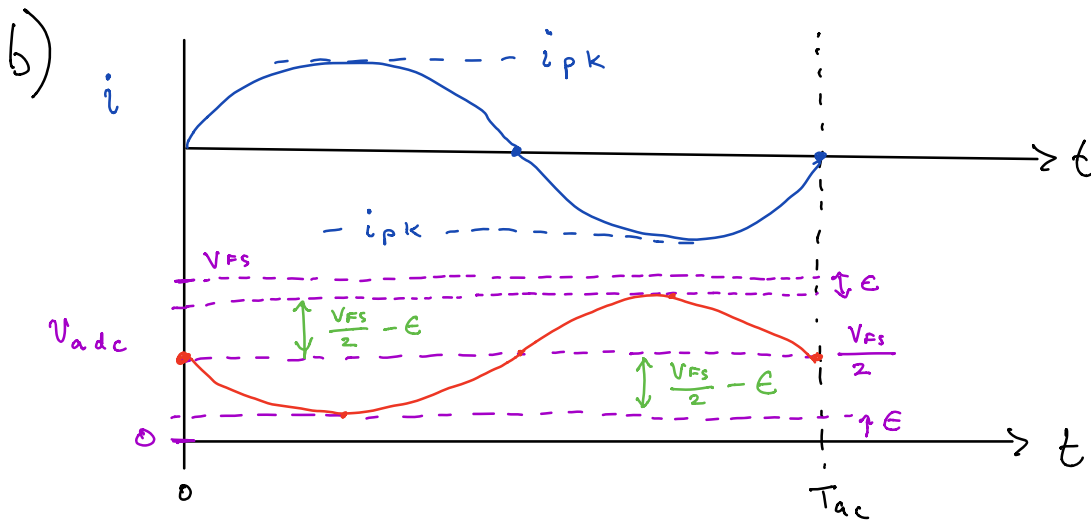

c) Look @ first objective in (b). Set $i=0$ and $V_{A10} = \frac{V_{Fs}}{2}$, then apply eq (7) from part (a).
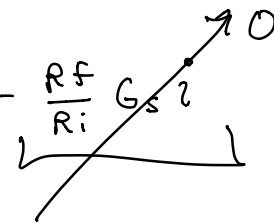
$$\underbrace{\frac{V_{Fs}}{2}}_{V_{adc}} = V_x \left(1 + \frac{R_f}{R_i} \right) - \frac{R_f}{R_i} V_{dc} - \frac{R_f}{R_i} G_s i$$


$$\Rightarrow V_x = \frac{1}{1 + \frac{R_f}{R_i}} \left(\frac{V_{adc}}{2} + \frac{R_f}{R_i} V_{dc} \right) \quad (8)$$

still need to solve for this...

Now look @ second objective in (b). See plot in (b) & notice that ac component of $V_{A10}(t)$ has a peak amplitude $\frac{V_{Fs}}{2} - \epsilon$ in both directions. Use this insight to make our lives easier. Set dc component in eq (7) to zero & $V_{A10} = \frac{V_{Fs}}{2} - \epsilon = \text{ac component}$, then evaluate when $i = -i_{pk}$ to capture peak \oplus swing.

$$\Rightarrow \frac{V_{Fs}}{2} - \epsilon = - \frac{R_f}{R_i} G_s (-i_{pk})$$

$$\Rightarrow \boxed{\frac{R_F}{R_i} = \frac{1}{G_s i_{pk}} \left(\frac{V_{Fs}}{2} - \epsilon \right)} \quad \boxed{(c)} \quad (9)$$

(9) \rightarrow (8) gives

$$\boxed{V_x = \frac{1}{1 + \frac{1}{G_s i_{pk}} \left(\frac{V_{Fs}}{2} - \epsilon \right)} \left(\frac{V_{Fs}}{2} + \frac{1}{G_s i_{pk}} \left(\frac{V_{Fs}}{2} - \epsilon \right) V_{dc} \right)} \quad \boxed{(10)} \quad \boxed{(c)}$$

(d) Put result from (c) into (a) as a sanity check.

Recall from (a), that

$$V_{A/D} = V_x \left(1 + \frac{R_F}{R_i} \right) - \frac{R_F}{R_i} V_{dc} - \frac{R_F}{R_i} G_s i$$

\times use (8) for V_x to keep things simpler

$$= \underbrace{\frac{1}{1 + \frac{R_F}{R_i}} \left(\frac{V_{Fs}}{2} + \frac{R_F}{R_i} V_{dc} \right)}_{V_x} \left(\cancel{1 + \frac{R_F}{R_i}} \right) - \frac{R_F}{R_i} V_{dc} - \frac{R_F}{R_i} G_s i$$

$$= \left(\frac{V_{Fs}}{2} + \frac{R_f}{R_i} v_{dc} \right) - \frac{R_f}{R_i} v_{dc} - \frac{R_f}{R_i} G_s \dot{i}$$

$$= \boxed{\frac{V_{Fs}}{2} - \frac{R_f}{R_i} G_s \dot{i}(t)} = v_{A/D}(t) \quad (11)$$

... I will take a few extra steps to shed further insight.

* use (9) for $\frac{R_f}{R_i}$

$$= \frac{V_{Fs}}{2} - \underbrace{\frac{1}{G_s z_{pk}} \left(\frac{V_{Fs}}{2} - \epsilon \right)}_{\frac{R_f}{R_i}} G_s \dot{i}$$

$$= \frac{V_{Fs}}{2} - \boxed{\left(\frac{V_{Fs}}{2} - \epsilon \right) \frac{\dot{i}(t)}{z_{pk}}}$$


desired offset term. Good!

this factor normalizes & scales $\dot{i}(t)$ as needed.

Success!

$$= v_{A/D}(t)$$

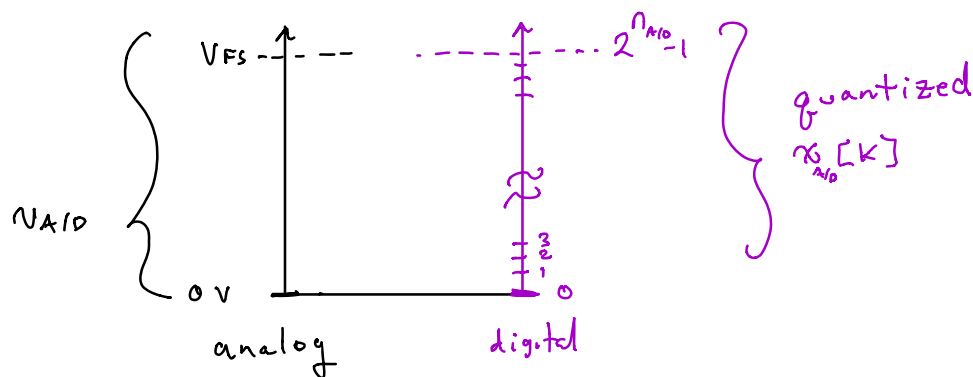- (e) Derive equation for digital value $x_{A/D}[n]$.
- Look @ analog & digital scales together



$x_{A/D}[n]$ is just a scaled version of $v_{A/D}$, of the form

$$x_{A/D}[k] = \underbrace{\text{round}}_{\text{captures quantization of ADC.}} \left(\underbrace{\frac{v_{A/D}}{V_{FS}} \cdot (2^{N_{A/D}} - 1)}_{\text{normalization \& scaling}} \right) \quad (e) \quad (12)$$

- (f) Recover i_m via a linear function.

- Ignoring quantization, (12) becomes

$$x_{A/D}[n] \approx \frac{(2^{N_{A/D}} - 1)}{V_{FS}} v_{A/D}[n]$$

* substitute (11) and let $i_m[k] \approx i(t)$

$$= \frac{2^{n_{A/D}} - 1}{V_{FS}} \left(\frac{V_{FS}}{2} - \frac{R_f}{R_i} G_s i_m[k] \right)$$

• Now solve for $i_m[k]$.

$$\Rightarrow \frac{R_f}{R_i} G_s i_m[k] = \frac{V_{FS}}{2} - \frac{V_{FS}}{2^{n_{A/D}-1}} \chi_{A/D}[k]$$

$$\Rightarrow \boxed{i_m[k] = - \frac{R_i V_{FS}}{R_f G_s (2^{n_{A/D}} - 1)} \chi_{A/D}[k] + \frac{R_i}{R_f G_s} \frac{V_{FS}}{2}}$$

\boxed{f}