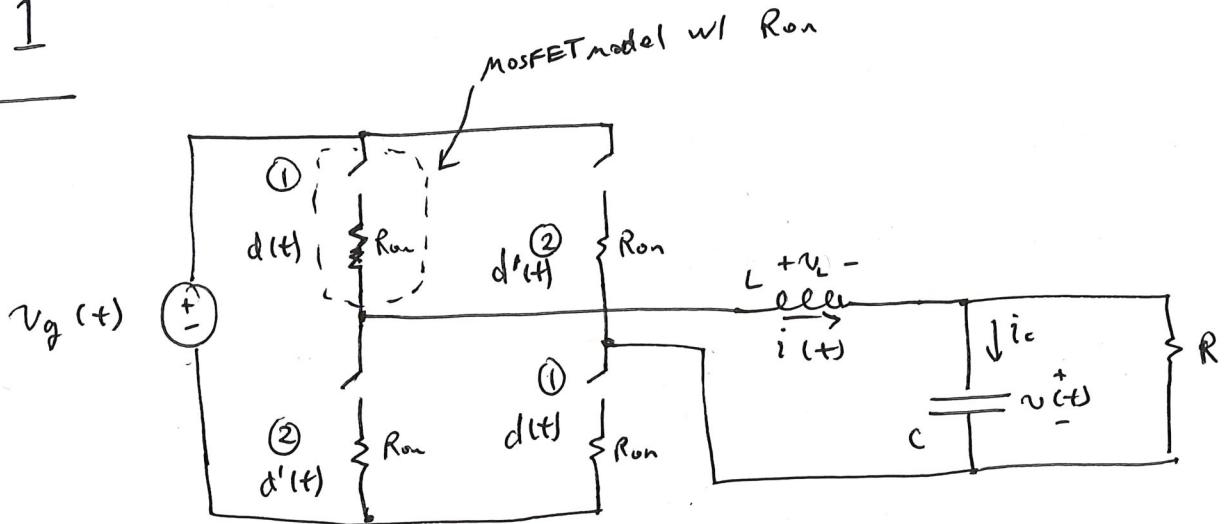


(1)

Homework # 1 solution

Problem 1




(a) Get avg equiv circuit

$$\begin{aligned}
 \left[\frac{d \langle i_L(t) \rangle}{dt} \right] &= d(t) \left(\underbrace{\langle v_g(t) \rangle - 2R_{on} \langle i(t) \rangle - \langle v(t) \rangle}_{(1)} \right) \\
 &\quad + d'(t) \left(\underbrace{-\langle v_g(t) \rangle - 2R_{on} \langle i(t) \rangle - \langle v(t) \rangle}_{(2)} \right) \\
 &= (d(t) - \underbrace{(1-d(t))}_{d'(t)} \langle v_g(t) \rangle - 2R_{on} \langle i(t) \rangle - \langle v(t) \rangle) \\
 &= (2d(t) - 1) \langle v_g(t) \rangle - 2R_{on} \langle i(t) \rangle - \langle v(t) \rangle
 \end{aligned}$$

$$\begin{aligned}
 C \frac{d \langle v(t) \rangle}{dt} &= d(t) \left(\underbrace{\langle i(t) \rangle - \frac{\langle v(t) \rangle}{R}}_{\text{eqn (1.1)}} \right) + d'(t) \left(\underbrace{\langle i(t) \rangle - \frac{\langle v(t) \rangle}{R}}_{(2)} \right) \\
 &= \langle i(t) \rangle - \frac{\langle v(t) \rangle}{R} \quad (1.2)
 \end{aligned}$$


(2)

Draw as equiv ckt

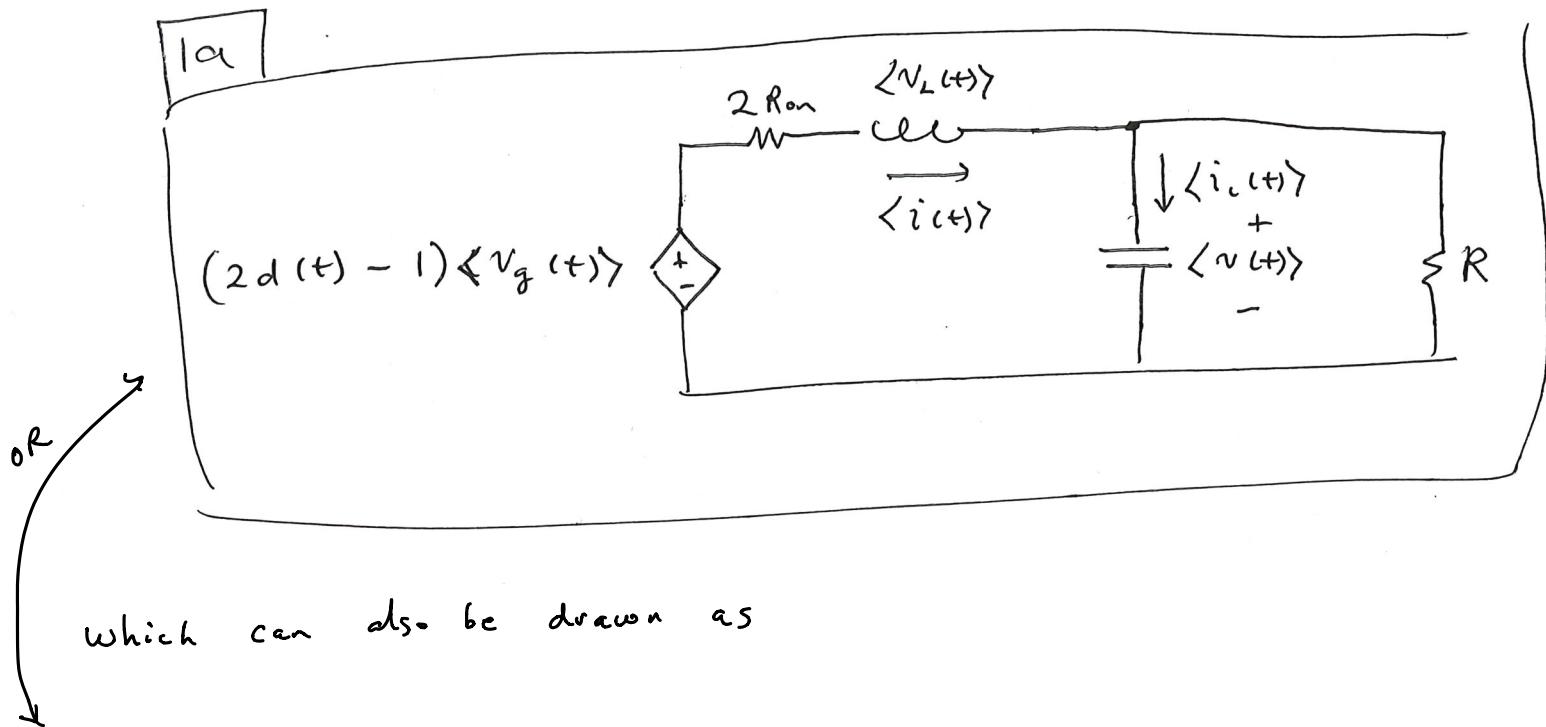(1) \textcircled{a} \rightarrow KVL for inductor(2) \rightarrow KCL for cap

or

which can also be drawn as

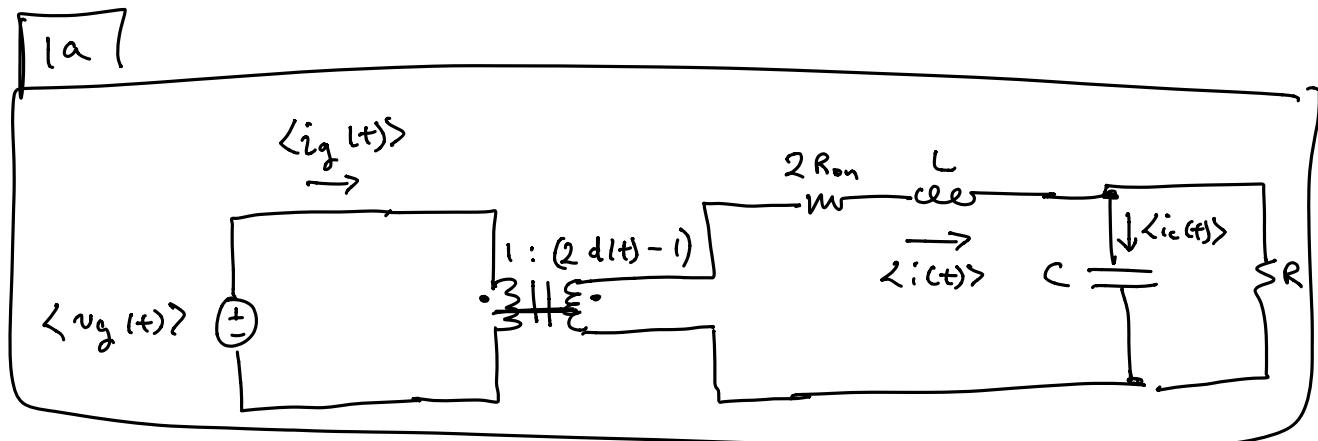

↑ This representation is more complete since it shows the input source side current too.

(b) Put into form $\dot{x} = f(x, u)$

\div (1) by L ∇ \div (2) by C to get

$$\boxed{1b} \quad \begin{aligned} \dot{x} &= \frac{d}{dt} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \frac{d}{dt} \begin{bmatrix} \langle i(t) \rangle \\ \langle v(t) \rangle \end{bmatrix} \\ &= \left[\begin{array}{l} \frac{1}{L} \left[(2a(t)-1) \langle v_g(t) \rangle - 2R\alpha \langle i(t) \rangle - \langle v(t) \rangle \right] \\ \frac{1}{c} \left[\langle i(t) \rangle - \underbrace{\frac{\langle v(t) \rangle}{R}}_{f(x, u)} \right] \end{array} \right] \\ &= \begin{bmatrix} f_1(x, u) \\ f_2(x, u) \end{bmatrix} \end{aligned}$$

where $u = \begin{bmatrix} d(t) \\ \langle v_g(t) \rangle \end{bmatrix}$

(3)

(c) Derive s.s. X given V

. Look at (1.1) - (1.2) where $d(t) = D$, $\langle V_g(t) \rangle = V_g$
 and set derivatives to zero. AKA "balance equations"
 we get!

$$0 = (2D-1)V_g - 2R_{on}I - V \quad (1.3)$$

$$0 = I - \frac{V}{R} \quad (1.3)$$

$$\text{From (1.3)} \rightarrow V = IR \quad (1.4)$$

$$(1.4) \rightarrow (1.3)$$

$$0 = (2D-1)V_g - 2R_{on}I - IR$$

$$= (2D-1)V_g - I(2R_{on} + R)$$

$$\rightarrow \boxed{I = \frac{(2D-1)V_g}{(2R_{on} + R)}} \quad (1.5)$$

$$(1.5) \rightarrow (1.4)$$

$$\boxed{V = \frac{(2D-1)V_g R}{(2R_{on} + R)}} \quad (1.6)$$

$$\rightarrow X = \begin{bmatrix} I \\ V \end{bmatrix} = \frac{(2D-1)V_g}{2R_{on} + R} \begin{bmatrix} R \\ 1 \end{bmatrix} = X \quad (1.7)$$

(d) Get linearized model. $\dot{x} \approx A(x(t) - x) + B(u(t) - u)$ (4)

• Compute A

$$A = \left[\begin{array}{cc} \frac{\partial f_1}{\partial x_1} & \frac{\partial f_1}{\partial x_2} \\ \frac{\partial f_2}{\partial x_1} & \frac{\partial f_2}{\partial x_2} \end{array} \right] \Big|_{x,u} = \left[\begin{array}{cc} \frac{\partial f_1}{\partial i} & \frac{\partial f_1}{\partial v} \\ \frac{\partial f_2}{\partial i} & \frac{\partial f_2}{\partial v} \end{array} \right] \Big|_{x,u}$$

$$= \boxed{\begin{bmatrix} -\frac{2R_{on}}{L} & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix}} = A \quad (1.8)$$

• Compute B

$$B = \left[\begin{array}{cc} \frac{\partial f_1}{\partial u_1} & \frac{\partial f_1}{\partial u_2} \\ \frac{\partial f_2}{\partial u_1} & \frac{\partial f_2}{\partial u_2} \end{array} \right] = \left[\begin{array}{cc} \frac{\partial f_1}{\partial d} & \frac{\partial f_1}{\partial v_g} \\ \frac{\partial f_2}{\partial d} & \frac{\partial f_2}{\partial v_g} \end{array} \right]$$

$$= \left[\begin{array}{cc} \frac{2}{L} \langle v_g(t) \rangle & \frac{2}{L} d(t) \\ 0 & 0 \end{array} \right] \Big|_{x,u} = \boxed{\begin{bmatrix} \frac{2}{L} V_g & \frac{2D-1}{L} \\ 0 & 0 \end{bmatrix}} = B \quad (1.9)$$

• Combine result in (c) w/ A & B:

$$\dot{x} = \underbrace{\left[\begin{array}{cc} -\frac{2R_{on}}{L} & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{array} \right]}_A \underbrace{\left[\begin{array}{c} \langle i(t) \rangle \\ \langle v(t) \rangle \end{array} \right]}_{x(t)} - \underbrace{\frac{(2D-1)V_g}{2R_{on}+R} \begin{bmatrix} R \\ 1 \end{bmatrix}}_X + \dots$$

(5)

$$+ \left[\begin{array}{cc} \frac{2}{L} V_g & \frac{2D-1}{L} \\ 0 & 0 \end{array} \right] \left(\left[\begin{array}{c} d(t) \\ (V_g(t)) \end{array} \right] - \left[\begin{array}{c} D \\ V_g \end{array} \right] \right) \quad (1.10)$$

$\underbrace{\qquad\qquad\qquad}_{B}$ $\underbrace{\qquad\qquad\qquad}_{u(t)}$ $\underbrace{\qquad\qquad\qquad}_{U}$

\boxed{Id}

e) See plots in solution simulations.

As mentioned in pdf, let $D = d(0)$ & $V_g = v_g(0)$


$$\Rightarrow D = \frac{1}{2} \text{ & } V_g = 100V \quad (1.11)$$

Plugging in (1.11) \rightarrow (1.7) we get

$$X = \frac{(2\cancel{\frac{1}{2}} - 1)100V}{2R_{on} + R} \begin{bmatrix} R \\ 1 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

Problem #2

Flyback w/ transformer model:

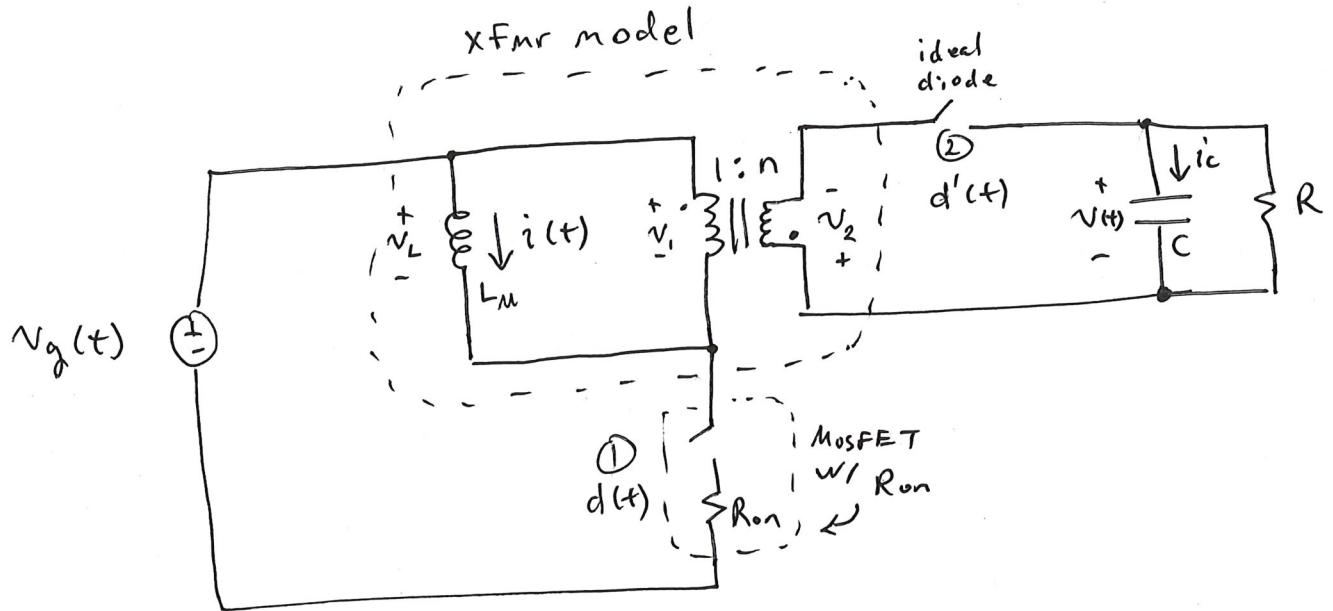

(a) Get avg ckt.

- Follow details from HWS & flyback to get RTFs of eqns below:


$$L \frac{d\langle i_L(t) \rangle}{dt} = d(t) \left(\langle v_g(t) \rangle - \langle i(t) \rangle R_{on} \right) - d'(t) \underbrace{\left(\langle v(t) \rangle \right)}_{\langle v_L \rangle} \quad (2.1)$$

and

$$C \frac{d\langle v(t) \rangle}{dt} = d(t) \left(\frac{-\langle v(t) \rangle}{R} \right) + d'(t) \left(\frac{\langle i(t) \rangle}{n} - \frac{\langle v(t) \rangle}{R} \right) = -\frac{\langle v(t) \rangle}{R} + d'(t) \frac{\langle i(t) \rangle}{n} \quad (2.2)$$


(7)

Draw as

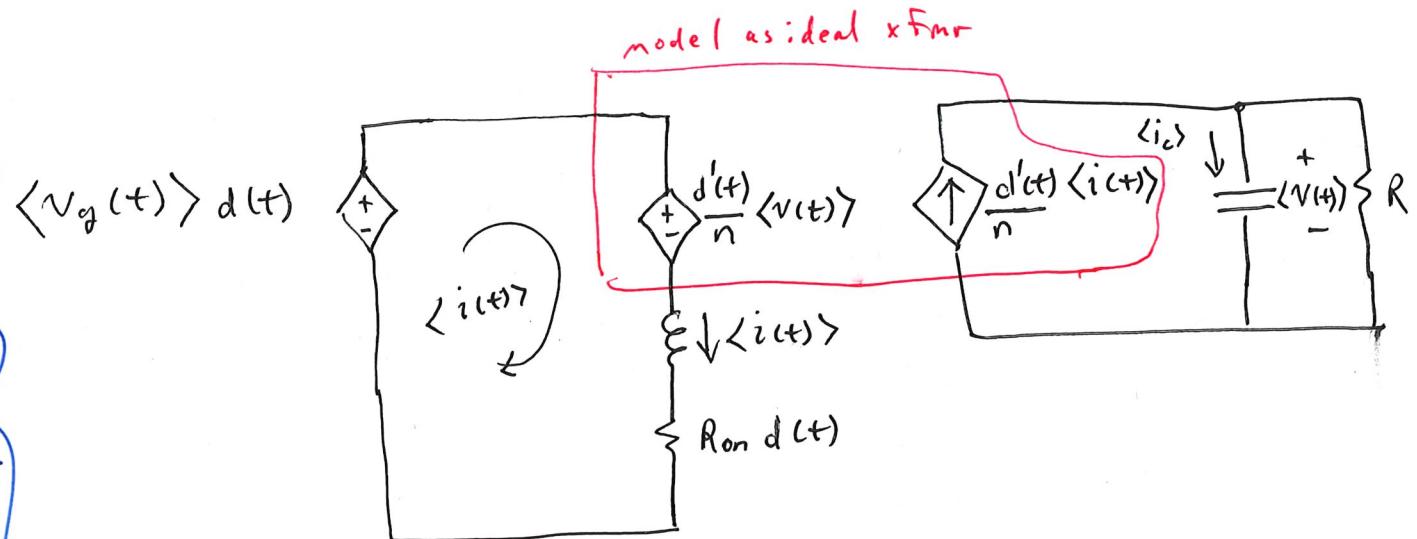

for
PLECS
simulation


2a

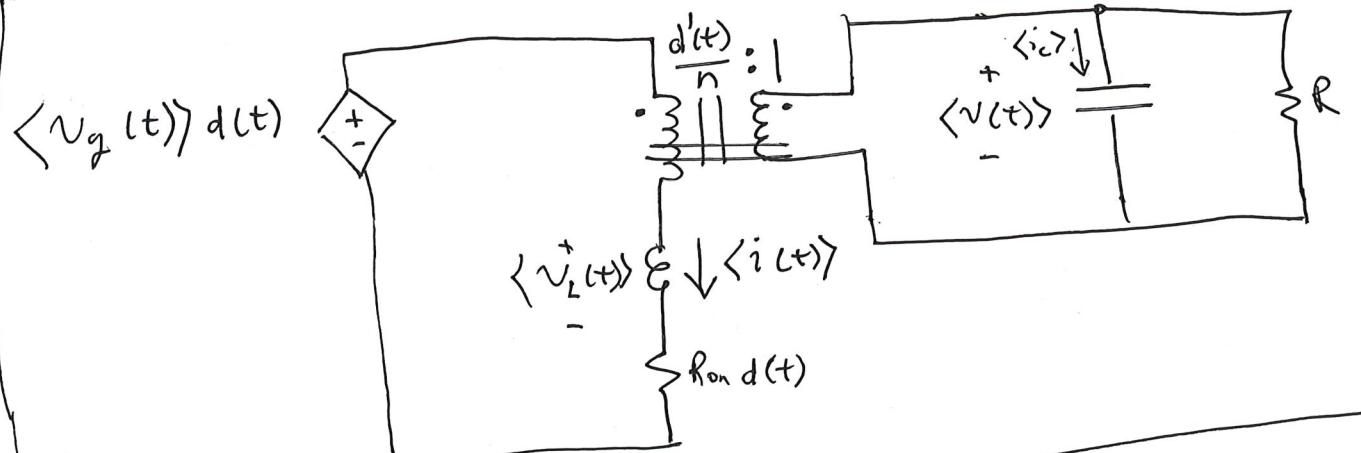

* Since PLECS doesn't have an ideal time-varying transformer,
you have to build your averaged simulation using the circuit
above



can also draw equivalently as

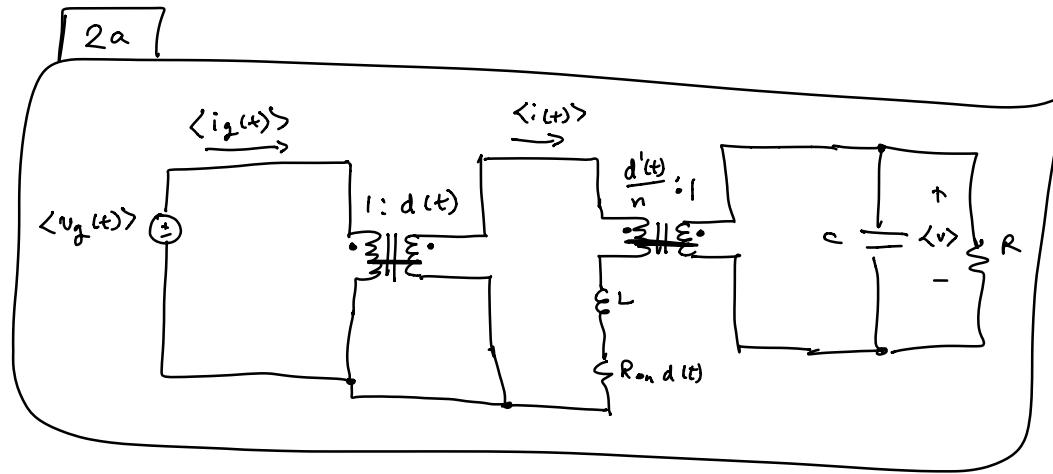

This diagram is more complete if
shows the input source.

(8)

(b) Put into form $\dot{x} = f(x, u)$

From (2.1)-(2.2) we get

$$\dot{x} = \frac{d}{dt} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \frac{d}{dt} \begin{bmatrix} \langle i(t) \rangle \\ \langle v(t) \rangle \end{bmatrix}$$

$$= \left[\begin{array}{l} \frac{1}{L} \left(d(t) \langle v_g(t) \rangle - \langle i(t) \rangle R_{on} \right) - \frac{(1-d(t))}{n} \langle v(t) \rangle \\ \frac{1}{C} \left(-\frac{\langle v(t) \rangle}{R} + (1-d(t)) \frac{\langle i(t) \rangle}{n} \right) \end{array} \right]$$

$$= f(x, u)$$

again $u = \begin{bmatrix} d(t) \\ \langle v_g(t) \rangle \end{bmatrix}$

(c) Derive S.S. X.

Solve balance equations... obtain V, I in terms of independent variables (V_g, D) . Set (2.1)-(2.2) to 0.

$$0 = D(V_g - IR_{on}) - \frac{(1-D)}{n} V \quad (2.3)$$

$$0 = -\frac{V}{R} + (1-D) \frac{I}{n} \quad (2.4)$$

Get I from (2.4),

$$I = \frac{VN}{R(1-D)} \quad (2.5)$$

 $(2.5) \rightarrow (2.3)$ to get

(4)

$$0 = D \left(V_g - \frac{V_n R_{on}}{R(1-D)} \right) - \frac{(1-D)V}{n}$$

$$= DV_g - V \left(\frac{Dn R_{on}}{R(1-D)} + \frac{(1-D)}{n} \right)$$

Solve for V

$$\rightarrow V = \frac{DV_g}{\left(\frac{Dn R_{on}}{R(1-D)} + \frac{1-D}{n} \right)}$$

$$= \frac{D(1-D) RV_g n}{D n^2 R_{on} + (1-D)^2 R} \quad (2.6)$$

$$= V$$

Put (2.6) \rightarrow (2.5)

$$I = \frac{n}{R(1-D)} \frac{D(1-D) RV_g n}{(D n^2 R_{on} + 1-D)}$$

$$\Rightarrow \frac{n^2 V_g D}{D n^2 R_{on} + (1-D)^2 R} = I \quad (2.7)$$

now put into vector form (10)

$$X = \begin{bmatrix} I \\ V \end{bmatrix} = \frac{n D V_g}{(D n^2 R_{on} + (1-D)^2 R)} \begin{bmatrix} n \\ (1-D) R \end{bmatrix} \quad (2.8)$$

2(d): Get linearized model: $\dot{x} \approx A(x(t)-x) + B(u(t)-u)$

$$A = \left[\begin{array}{cc} \frac{\partial f_1}{\partial \langle i \rangle} & \frac{\partial f_1}{\partial \langle v \rangle} \\ \frac{\partial f_2}{\partial \langle i \rangle} & \frac{\partial f_2}{\partial \langle v \rangle} \end{array} \right] \Big|_{X,U}$$

$$= \boxed{\begin{bmatrix} -\frac{1}{L} DR_{on} & \frac{-(1-D)}{L n} \\ \frac{(1-D)}{C n} & -\frac{1}{RC} \end{bmatrix}} = A \quad (2.8)$$

and,

$$B = \left[\begin{array}{cc} \frac{\partial f_1}{\partial d} & \frac{\partial f_1}{\partial \langle v_g \rangle} \\ \frac{\partial f_2}{\partial d} & \frac{\partial f_2}{\partial \langle v_g \rangle} \end{array} \right] \Big|_{X,U} = \boxed{\begin{bmatrix} \frac{1}{L} (V_g - IR_{on} + \frac{V}{n}) & \frac{1}{L} D \\ -\frac{1}{C} \left(\frac{I}{n} \right) & 0 \end{bmatrix}} = B \quad (2.9)$$

where the result in 2.8 gives us I .

(11)

Putting it all together

$$\dot{x} \approx \begin{bmatrix} -DR_{on} & -(1-D) \\ \frac{1-D}{nC} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} \langle i(t) \rangle \\ \langle V_C(t) \rangle \end{bmatrix} - \frac{nPV_g}{(n^2R_{on}+1-D)} \begin{bmatrix} n \\ (1-D)R \end{bmatrix}$$

$A \quad X$

$$+ \begin{bmatrix} \frac{1}{L}(V_g - IR_{on} + \frac{v}{n}) & \frac{1}{L}D \\ -\frac{I}{nC} & 0 \end{bmatrix} \begin{bmatrix} d(t) \\ \langle V_g(t) \rangle \\ u(t) \end{bmatrix} - \begin{bmatrix} D \\ V_g \end{bmatrix}$$

$B \quad Y$

2(d)

2(e) See simulation plots.

Code calculates I s.s. variable First... all else carries forward logically.

Contents

- [Problem 1 set up](#)
- [Problem 1 Run Simulation](#)
- [Problem 1 Plot Results](#)
- [Problem 2 Set up](#)
- [Problem 2 Run Simulation](#)
- [Problem 2 Plot Results](#)

```
clear all  
clc
```

Problem 1 set up

```
% Parameters  
fs = 25e3;  
T = 1/fs;  
L = 300e-6;  
C = 10e-6;  
R = 10;  
Ron = 15e-3;  
  
% Input values before and after step changes  
vg_before = 100;  
vg_after = 75;  
tStepVg = 20e-3;  
  
% duty cycle  
A_before = .7;  
A_after = .9;  
freq=2*pi*50;  
tStepDuty = 40e-3;  
  
% In part (c) we get the ss values below  
Vg = vg_before;  
D = .5*(1+.7*sin(freq*0));  
I = -(1-2*D)*Vg/(2*Ron+R);  
V = -R*(1-2*D)*Vg/(2*Ron+R);  
  
% State Space Set up  
A=[-2*Ron/L -1/L; 1/C -1/(R*C)];  
B=[2*Vg/L -(1-2*D)/L; 0 0];  
X=[I; V];  
U=[D; Vg];
```

Problem 1 Run Simulation

```

tStop = 60e-3;

[t_sw, x_sw, y_sw] = sim('Sim_EE452_HW6_Probl_Switched', tStop);

i_sw = x_sw(:,1);
v_sw = x_sw(:,2);

[t_avg, x_avg, y_avg] = sim('Sim_EE452_HW6_Probl_Averaged', tStop);

i_avg = x_avg(:,1);
v_avg = x_avg(:,2);

[t_ss,x_ss]=sim('Sim_EE452_HW6_Probl_StateSpace_Simulink', tStop);

i_ss=x_ss(:,1);
v_ss=x_ss(:,2);

```

Problem 1 Plot Results

```

close all

for i = 1:3

figure (i)

a1 = subplot(2,1,1);
plot(t_sw, v_sw, 'LineWidth', 1)
hold on
plot(t_avg, v_avg, 'LineWidth',2)
plot(t_ss,v_ss,'LineWidth',1)
xlabel('$t$', [s],'Interpreter','latex');
ylabel('$v$', [V],'Interpreter','latex');
legend('Switched Model', 'Averaged Model','State Space Model','Location','SouthEast')

a2 = subplot(2,1,2);
plot(t_sw, i_sw, 'LineWidth', 1)
hold on
plot(t_avg, i_avg, 'LineWidth',2)
plot(t_ss,i_ss,'LineWidth',1)
xlabel('$t$', [s],'Interpreter','latex');
ylabel('$i$', [A],'Interpreter','latex');
legend('Switched Model', 'Averaged Model','State Space Model','Location','SouthEast')

if i == 1
    linkaxes([a1 a2], 'x')
    xlim([0, tStop])
    subplot(2,1,1);
    legend('Switched Model', 'Averaged Model','State Space Model','Location','NorthEastOut
side')
    title('Single Phase Voltage Source Inverter: Entire Simulation')
    subplot(2,1,2);
    legend('Switched Model', 'Averaged Model','State Space Model','Location','NorthEastOut
side')
elseif i == 2
    linkaxes([a1 a2], 'x')

```



```

    xlim([tStepDuty - 5*T, tStepDuty + 25*T])
    subplot(2,1,1);
    title('Single Phase Voltage Source Inverter: Duty Ratio Step')
else
    linkaxes([a1 a2], 'x')
    xlim([tStepVg - 5*T, tStepVg + 25*T])
    subplot(2,1,1);
    title('Single Phase Voltage Source Inverter: Input Voltage Step')
end


end

```

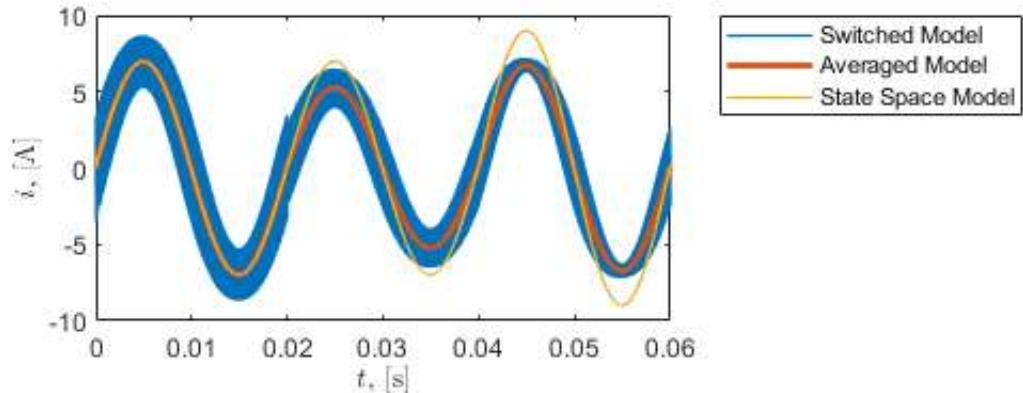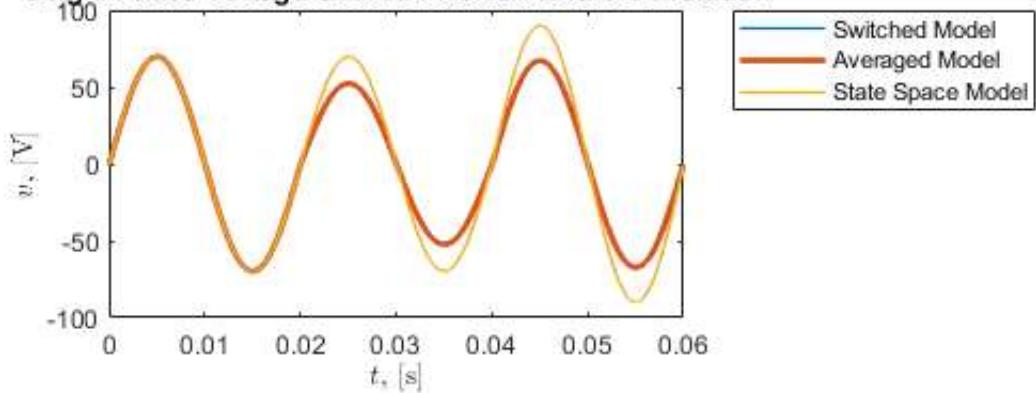
Single Phase Voltage Source Inverter: Entire Simulation



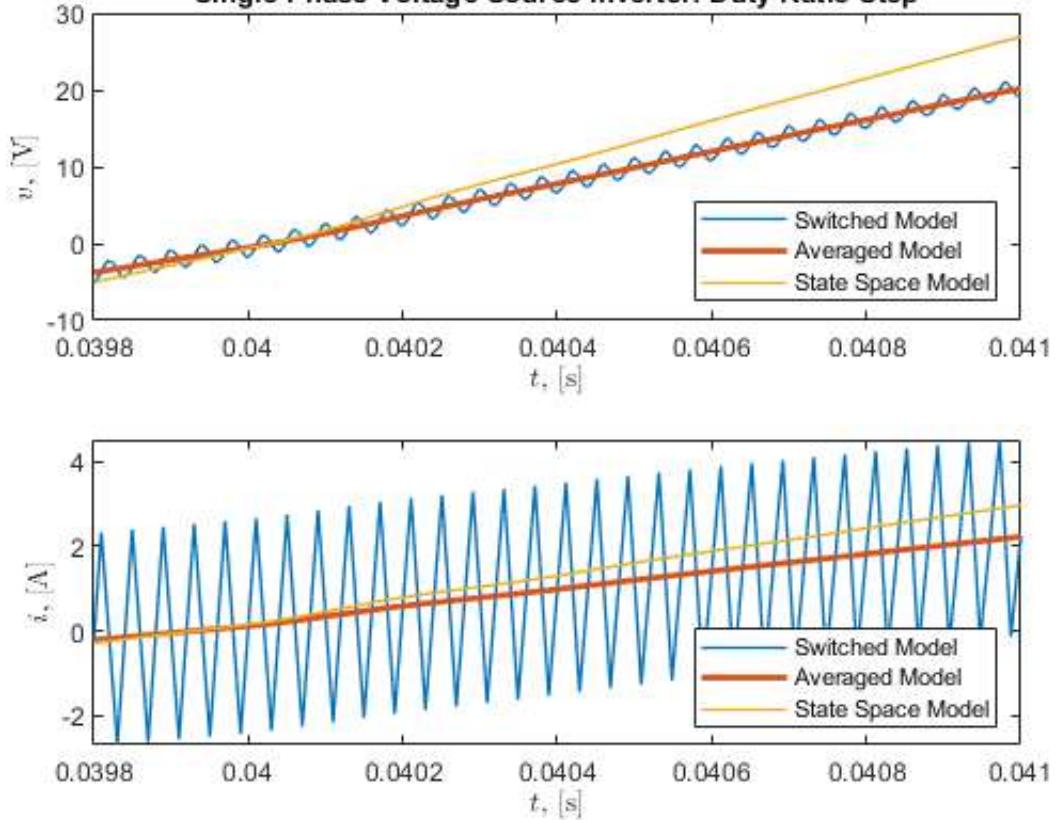Single Phase Voltage Source Inverter: Duty Ratio Step



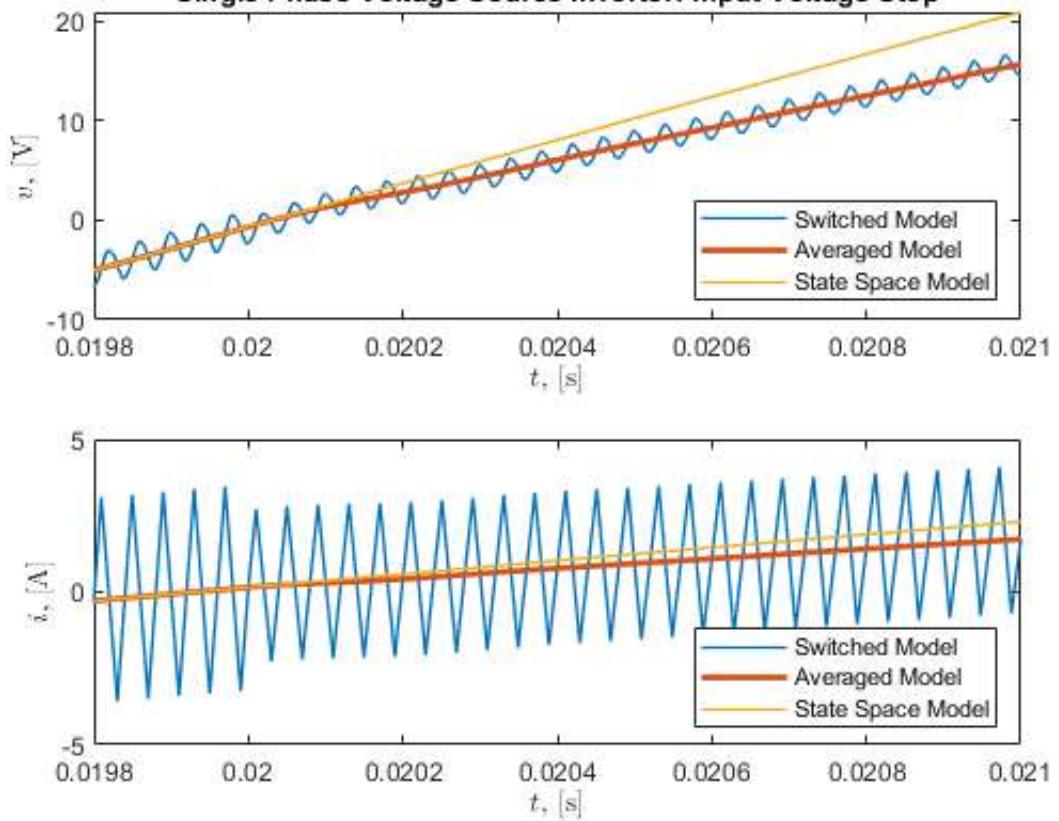Single Phase Voltage Source Inverter: Input Voltage Step



Problem 2 Set up

```

% Parameters
n=2;
Lm=300*10^-6;
tStop = 60e-3;

% duty cycle
d_before=0.5;
d_after=0.75;

% In part (c) we get the ss values below
Vg = vg_before;
D = d_before;
I = n^2*D*Vg/(D*Ron*n^2+(1-D)^2*R);
V = D*(1-D)*R*n*Vg/(D*Ron*n^2+(1-D)^2*R);

A=[-D^2*Ron/Lm -(1-D)/(Lm*n); (1-D)/(C*n) -1/(R*C)];
B=[-Ron*I/Lm+V/(Lm*n)+Vg/L D/L; -I/(C*n) 0];
X=[I; V];
U=[D; Vg];

```

Problem 2 Run Simulation

```

tStop = 60e-3;

[t_sw2, x_sw2, y_sw2] = sim('Sim_EE452_HW6_Prob2_Switched', tStop);

i_sw2 = y_sw2(:,1);
v_sw2 = y_sw2(:,2);

[t_avg2, x_avg2, y_avg2] = sim('Sim_EE452_HW6_Prob2_Averaged', tStop);

i_avg2 = y_avg2(:,1);
v_avg2 = y_avg2(:,2);

[t_ss,x_ss]=sim('Sim_EE452_HW6_Prob2_StateSpace_Simulink', tStop);

i_ss=x_ss(:,1);
v_ss=x_ss(:,2);

```

Problem 2 Plot Results

```

for i = 4:6

    figure (i)

a1 = subplot(2,1,1);
plot(t_sw2, v_sw2, 'LineWidth', 1)
hold on
plot(t_avg2, v_avg2, 'LineWidth',2)
plot(t_ss,v_ss,'LineWidth',1)
xlabel('$t$, [s]', 'Interpreter', 'latex');
ylabel('$v$, [V]', 'Interpreter', 'latex');
legend('Switched Model', 'Averaged Model', 'State Space Model')

```

```


a2 = subplot(2,1,2);
plot(t_sw2, i_sw2, 'LineWidth', 1)
hold on
plot(t_avg2, i_avg2, 'LineWidth',2)
plot(t_ss,i_ss,'LineWidth',1)
xlabel('$t$', [s],'Interpreter','latex');
ylabel('$i$', [A],'Interpreter','latex');
legend('Switched Model', 'Averaged Model','State Space Model')

if i == 4
    linkaxes([a1 a2], 'x')
    xlim([0, tStop])
    subplot(2,1,1)
    legend('Switched Model', 'Averaged Model','State Space Model','Location','NorthWest')
    title('Flyback Converter: Entire Simulation')
    subplot(2,1,2)
    legend('Switched Model', 'Averaged Model','State Space Model','Location','NorthWest')
elseif i == 5
    linkaxes([a1 a2], 'x')
    xlim([tStepDuty - 5*T, tStepDuty + 25*T])
    subplot(2,1,1)
    legend('Switched Model', 'Averaged Model','State Space Model','Location','NorthWest')
    title('Flyback Converter: Duty Ratio Step')
    subplot(2,1,2)
    legend('Switched Model', 'Averaged Model','State Space Model','Location','NorthWest')
elseif i == 6
    linkaxes([a1 a2], 'x')
    xlim([tStepVg - 5*T, tStepVg + 25*T])
    subplot(2,1,1);
    title('Flyback Converter: Input Voltage Step')
end


end

```



Flyback Converter: Entire Simulation

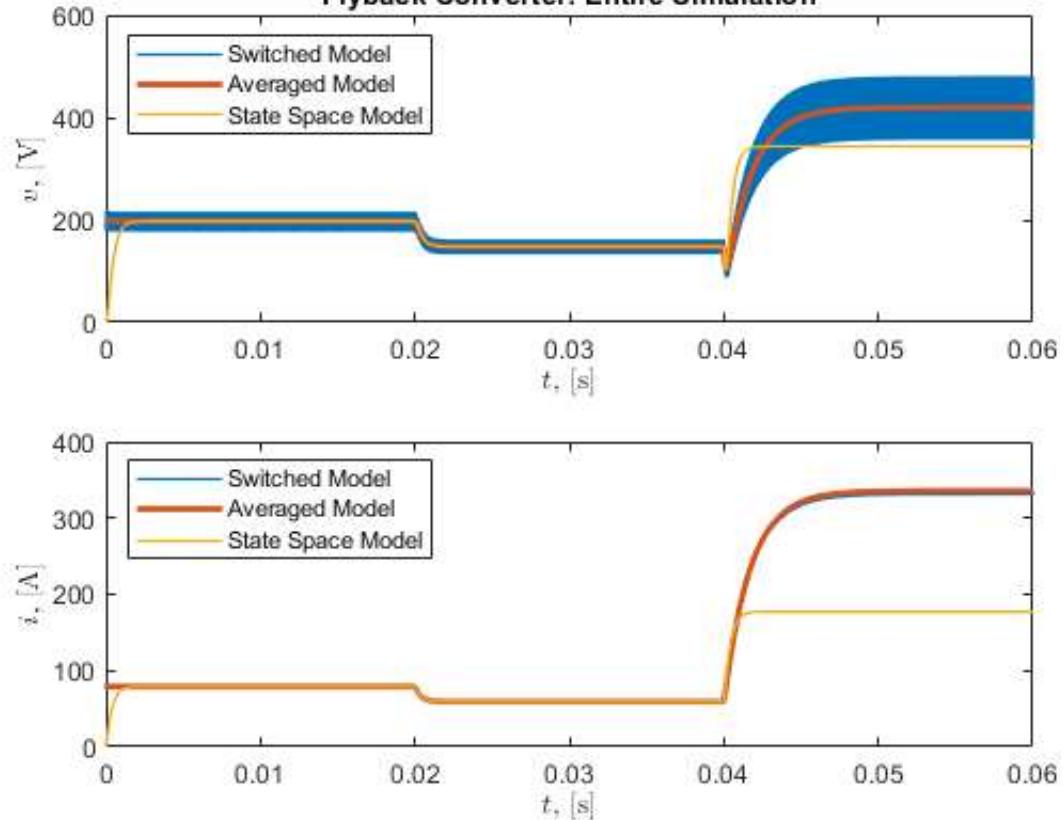

Flyback Converter: Duty Ratio Step

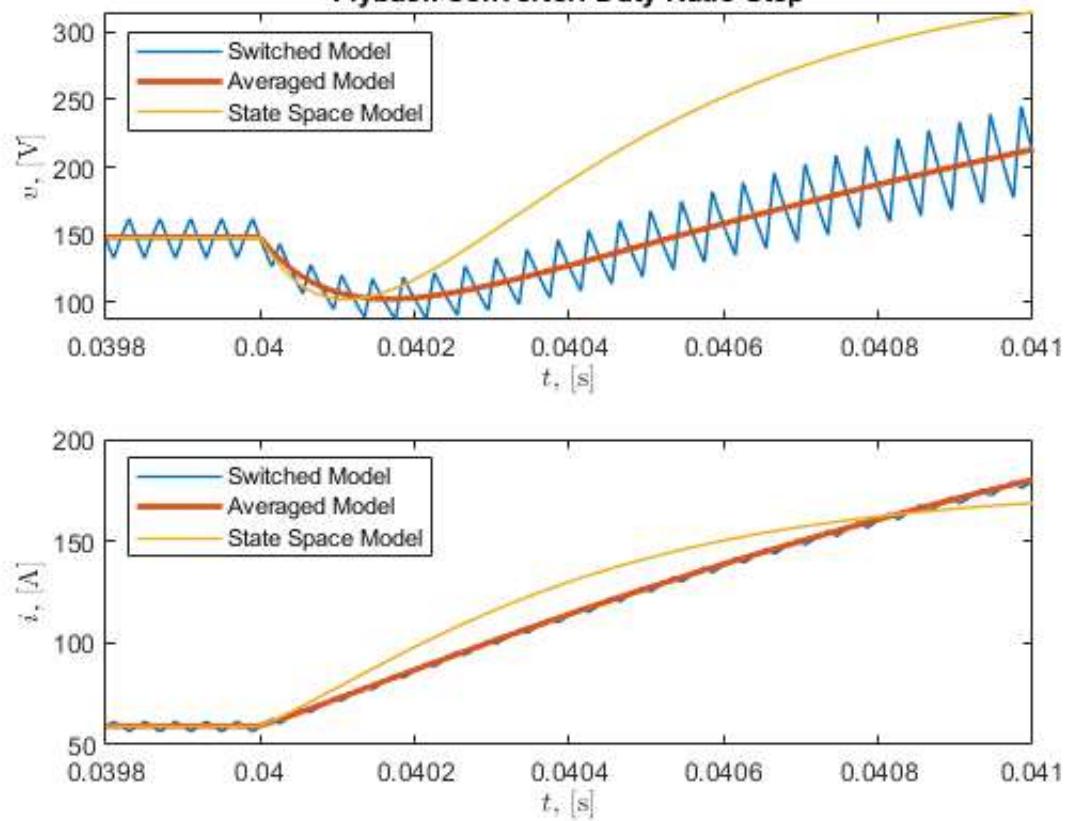

Flyback Converter: Input Voltage Step

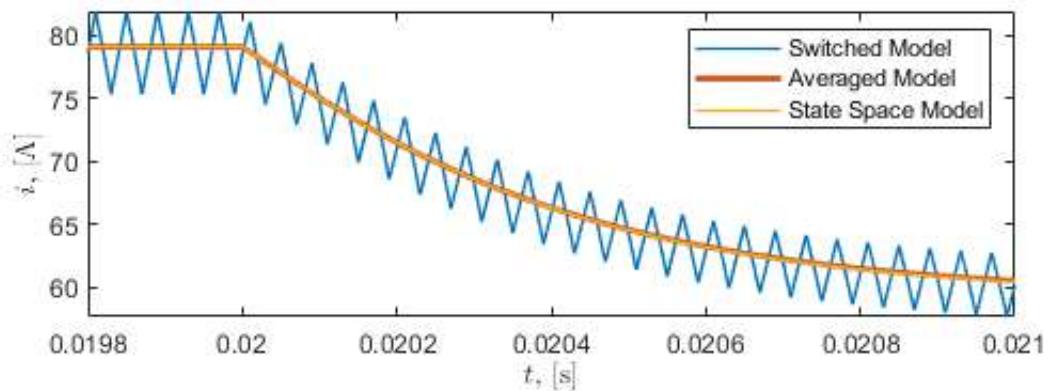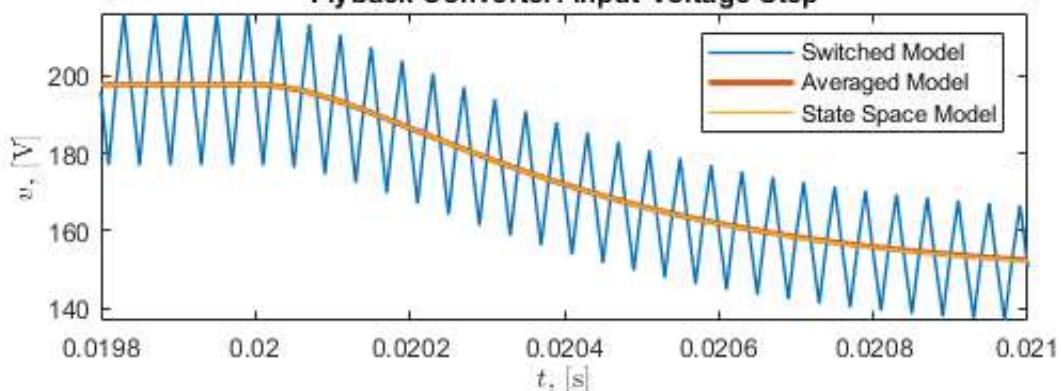

Published with MATLAB® R2018b

Hence

$$f_{sw} \leq f_{sw}_{\max} = 1 \text{ MHz}$$

2a

2b) find f_{sw}_{\min} for a 2^{16} bit counter.

- The slowest switching occurs when N_r is maximized.
- Since we have 16 bits, then

$$N_r \leq N_r_{\max} = 2^{16} = 65,536$$

- If we set $N_r = N_r_{\max}$ & plug into equation (2.1), we get

$$N_r_{\max} = \frac{f_{clk}}{2 f_{sw}}$$

$$\Rightarrow f_{sw} = \frac{f_{clk}}{2 N_r_{\max}} = \frac{100 \mu\text{Hz}}{2 \cdot 2^{16}} = \frac{100 \mu\text{Hz}}{2^{17}}$$

$$\approx 762.9 \text{ Hz} = f_{sw}_{\min}$$

2b

2c) Resolution with $N_r = 2^{16}$?

2c

$$\rightarrow f_D = \frac{1}{N_r_{\max}} = \frac{1}{2^{16}} \approx 1.52 \times 10^{-5} = f_D$$

\Rightarrow Resolution of 0.00152 %