

Lecture 4      13<sup>th</sup> January 2022

HW1 has been uploaded (files section)

Due on Thursday before class.

Revision: To obtain the small signal model.

① Draw the circuit as it appears in mode 1 & 2.

- Mode is based on switch / diode being turned on/off.

② find the state equations of circuit in mode 1 & 2.

$$\text{mode I} \left\{ \begin{array}{l} L \frac{di_L}{dt} = -f_1 \\ C \frac{dV_C}{dt} = -f_2 \end{array} \right.$$

$$\text{mode II} \left\{ \begin{array}{l} L \frac{di_L}{dt} = -f_3 \\ C \frac{dV_C}{dt} = -f_4 \end{array} \right.$$

③ Obtain the switch cycle average model.

$$\langle x(t) \rangle_{T_S} = \int_t^{t+T_S} x(\tau) d\tau$$

$$L \frac{d}{dt} \langle i_L(t) \rangle_{T_S} = f_1 \cdot d(t) + f_3 \cdot d'(t)$$

$f_1, f_2$  are functions of  $i_L, V_C, V_{in}, D, t \dots$

$$C \frac{d}{dt} \langle v_c(t) \rangle_{TS} = f_2 dt + f_4 d'(t)$$

- ④ Write every input (duty ratio, input voltage), state variable (capacitor voltage, inductor current)  
 $d = \text{sum of a large dc value + small ac perturbation}$

eg.  $d(t) = \underbrace{D}_{\text{not a fn of time}} + \underbrace{x(t)}_{\text{fn of time}}$

Substitute into eq. of step ③.

- ⓐ Equate large signal on both sides &  
 $\rightarrow$  notice  $\frac{d}{dt} X = 0$  [EE452  $\rightarrow$  steady state solution]

- ⓑ Equate small signal on both sides ( $\frac{d}{dt} \tilde{x} = 0$ )  
[EE458 - transient state solution]

$$L \frac{d\tilde{i}_L(t)}{dt} = f(t, \tilde{i}_L(t), \tilde{v}_c(t), \bar{d}(t), \tilde{v}_{in}(t), I_L, V_C, D, V_{in})$$

$$C \frac{d\tilde{v}_c(t)}{dt} = f(t, \tilde{i}_L(t), \tilde{v}_c(t), \bar{d}(t), \tilde{v}_{in}(t), I_L, V_C, D, V_{in})$$

- ⑤ We need to solve the eq. of Step ④.  
One way to do is Laplace transform.

$$SL \tilde{i}_L(s) = F(s, \tilde{i}_L(s), \tilde{v}_c(s), \tilde{d}(s), \tilde{v}_{in}(s), l_c, V_{c,d}, V_{in})$$

$$SC \tilde{v}_c(s) = F(s, \tilde{i}_L(s), \tilde{v}_c(s), \tilde{d}(s), \tilde{v}_{in}(s), l_c, V_{c,d}, V_{in})$$

⑥ Obtain transfer functions.

$$\frac{\tilde{v}_c(s)}{\tilde{d}(s)} \longrightarrow \text{set } \tilde{v}_{in}=0, \text{ substitute away } \tilde{v}_c(s)$$

$$\left[ \frac{\tilde{v}_c(s)}{\tilde{d}(s)} \right] \longrightarrow \text{''} \quad , \quad \text{''} \quad \tilde{i}_L(s)$$

$$\left[ \frac{\tilde{i}_L(s)}{\tilde{v}_{in}(s)} \right] \longrightarrow \text{set } \tilde{d}(s)=0, \dots$$

$$\left[ \frac{\tilde{v}_c(s)}{\tilde{v}_{in}(s)} \right] \longrightarrow \text{''} \quad , \quad \text{''} \quad \dots$$

## Taylor Series




① Taylor series (McLaurin series)

$$f(x) = \underline{c_0 + c_1 x + c_2 x^2 + c_3 x^3 + \dots}$$

② Fourier series

$$f(x) = c_0 + \sum_{n=1}^{\infty} (a_n \sin(nx) + b_n \cos(nx))$$

e.g.

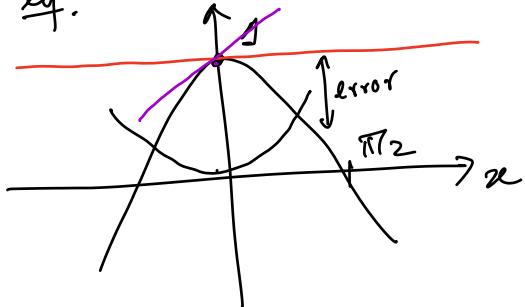

Q. How do you approximate  $\cos(x)$  near  $x=0$

$$f(x) = \boxed{\quad}$$


$$\approx \cos x$$

$$f(x) = \textcircled{1} = \cos(0)$$

$$-\sin x$$

$$f(x) = \underline{c_0 + c_1 x + c_2 x^2}$$

$$x=0 \Rightarrow f(0) = c_0 = 1.$$

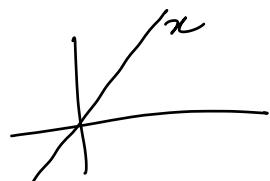

$$\left. \frac{\partial f}{\partial x} \right|_{x=0} = c_1 + 2c_2 x = 0 \quad \therefore c_1 = 0$$

$$c_1 + 2c_2 \cdot 0 = 0$$

$$f(x) = 1 + 0 \cdot x$$

$$\frac{\partial^2 f}{\partial x^2} = 2c_2 = -\cos x \Big|_{x=0} \quad \underline{-\cos x}$$

$$c_2 = -\frac{1}{2}$$

$$f(x) = 1 + 0 - \frac{1}{2}x^2 = 1 - \frac{x^2}{2}$$

Q What if I asked to find an approximation of  $\cos x$   
at  $x = \pi/4$

$$f(x) = c_0 + c_1(x - \frac{\pi}{4}) + c_2(x - \frac{\pi}{4})^2 \quad ( )^3$$

Equate true for at  $x = \pi/4$

$$\therefore f(\frac{\pi}{4}) = c_0 = \cos(\frac{\pi}{4}) \quad 3.2 \dots$$

$$\frac{df}{dx} = 0 + 2c_2(x - \frac{\pi}{4})$$

$$\left. \frac{df}{dx} \right|_{x=\frac{\pi}{4}} = 0$$

$$f(x) = f(\frac{\pi}{4}) + \left. \frac{df}{dx} \right|_{x=\frac{\pi}{4}} (x - \frac{\pi}{4}) + \frac{1}{2!} \left. \frac{\partial^2 f}{\partial x^2} \right|_{x=\frac{\pi}{4}} (x - \frac{\pi}{4})^2 \\ + \frac{1}{3!} \left. \frac{\partial^3 f}{\partial x^3} \right|_{x=\frac{\pi}{4}} (x - \frac{\pi}{4})^3 \dots$$

$$\langle v_L(t) \rangle_{T_S} = L \frac{d \langle i_L(t) \rangle_{T_S}}{dt} = \langle v_{in}(t) \rangle_{T_S} dt - \langle v_c(t) \rangle_{T_S} d'(t)$$

$$\langle i_c(t) \rangle_{T_S} = C \frac{d}{dt} \langle v_c(t) \rangle_{T_S} = \frac{\langle v_c(t) \rangle_{T_S}}{R} \cdot d(t) + \left( \frac{\langle v_c(t) \rangle_{T_S}}{R} + \langle i_L(t) \rangle_{T_S} \right) d'(t)$$

$$L \frac{d}{dt} \langle i_L(t) \rangle_{T_S} = f_1$$

$$C \frac{d}{dt} \langle v_c(t) \rangle_{T_S} = f_2$$

Let us call nominal operating point =  $\bar{x}, \bar{u}$

$$\bar{x} = \begin{bmatrix} I_L \\ V_o \end{bmatrix} = \begin{bmatrix} \frac{V_o}{D'R} \\ \frac{V_{in}}{D'} \end{bmatrix} \quad V_o = V_C$$

$$\bar{u} = \text{input} = \begin{bmatrix} D \\ V_{in} \end{bmatrix}$$

$$L \frac{d \langle i_L(t) \rangle_{T_S}}{dt} = f_1(\bar{x}, \bar{u}) = \langle v_{in}(t) \rangle_{T_S} dt - \langle v_c(t) \rangle_{T_S} d'(t) \quad \checkmark$$

$$C \frac{d \langle v_c(t) \rangle_{T_S}}{dt} = f_2(\bar{x}, \bar{u}) = -\frac{\langle v_c(t) \rangle_{T_S}}{R} + \langle i_L(t) \rangle_{T_S} d'(t)$$

$$\frac{\partial f}{\partial x} \quad x = \begin{bmatrix} \langle i_L(t) \rangle_{T_S} \\ \langle v_c(t) \rangle_{T_S} \end{bmatrix}$$

$$f = \begin{bmatrix} f_1(x, u) \\ f_2(x, u) \end{bmatrix}$$

Derivative of a scalar w.r.t. vector

$$\frac{\partial f}{\partial \underline{x}} = \begin{bmatrix} \text{vector} \\ = \end{bmatrix} \quad \left[ \begin{bmatrix} \langle i_L(t) \rangle_{TS} - I_2 \\ \langle v_c(t) \rangle_{TS} - V_c \end{bmatrix} \right] = v_o$$

$$\frac{\partial f}{\partial \underline{x}} = \begin{bmatrix} [f_1, f_2] \\ \frac{\partial f_1}{\partial \tilde{i}_L} \\ \frac{\partial f_2}{\partial \tilde{v}_c} \end{bmatrix} + \begin{bmatrix} \frac{\partial f_1}{\partial \tilde{v}_c} \\ \frac{\partial f_2}{\partial \tilde{v}_c} \end{bmatrix} \begin{bmatrix} \tilde{i}_L(t) \\ \tilde{v}_c(t) \end{bmatrix}$$

$$x = \bar{x}, \quad u = \bar{u}$$

$$\begin{bmatrix} \frac{\partial f}{\partial \underline{x}} \\ \frac{\partial f_1}{\partial \tilde{v}_{in}} \\ \frac{\partial f_2}{\partial \tilde{v}_{in}} \end{bmatrix} \begin{bmatrix} \tilde{x}(t) \\ \tilde{v}_{in} \end{bmatrix}$$

$$f(\underline{x}, \underline{u}) \xrightarrow{\begin{bmatrix} \tilde{v}_c \\ \tilde{v}_i \end{bmatrix}} \begin{bmatrix} d \\ v_{in} \end{bmatrix}$$

$$\approx \frac{\partial f}{\partial \underline{x}} \Big|_{\substack{x=\bar{x} \\ u=\bar{u}}} (\underline{x} - \bar{\underline{x}}) + \frac{\partial f}{\partial \underline{u}} \Big|_{\substack{x=\bar{x} \\ u=\bar{u}}} (\underline{u} - \bar{\underline{u}}) + \dots$$

$$\frac{\partial^2 f}{\partial \underline{x}^2} \Big|_{\substack{x=\bar{x} \\ u=\bar{u}}} (\underline{x} - \bar{\underline{x}})^2 + \frac{\partial^2 f}{\partial \underline{u}^2} \Big|_{\substack{x=\bar{x} \\ u=\bar{u}}} (\underline{u} - \bar{\underline{u}})^2 + \dots$$

ignore these.

$$f(x) = c_0 + c_1 x + c_2 x^2$$

$$\begin{bmatrix} L \frac{d i_L(t)}{dt} \\ C \frac{d v_C(t)}{dt} \end{bmatrix} = \begin{bmatrix} f_1(x, u) \\ f_2(x, u) \end{bmatrix} = \begin{bmatrix} f_1(\bar{x}, \bar{u}) \\ f_2(\bar{x}, \bar{u}) \end{bmatrix} + \frac{\partial f}{\partial x} \cdot \tilde{x} + \frac{\partial f}{\partial u} \cdot \tilde{u}$$

why?  $\tilde{x} = (x - \bar{x}) \sqrt{L}$ ,  $\tilde{u} = (u - \bar{u}) \sqrt{C}$

$$v_L = L \frac{d i_L}{dt} = 0 = f_1(\bar{x}, \bar{u}) \quad (\text{steady state soln})$$

$$i_C = C \frac{d v_C}{dt} = 0 = f_2(\bar{x}, \bar{u}) \quad (\quad " \quad )$$

$$\begin{bmatrix} \tilde{i}_L(t) \\ \tilde{v}_C(t) \end{bmatrix} = \begin{bmatrix} \langle i_L(t) \rangle_{IS} - I_L \\ \langle v_C(t) \rangle_{IS} - V_C \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} \langle i_L(t) \rangle_{IS} \\ \langle v_C(t) \rangle_{IS} \end{bmatrix} = \begin{bmatrix} \tilde{i}_L(t) + I_L \\ \tilde{v}_C(t) + V_C \end{bmatrix}$$

$$\therefore L \frac{d}{dt} \langle i_L(t) \rangle_{IS} = L \frac{d}{dt} (I_L + \tilde{i}_L(t)) = L \frac{d \tilde{i}_L(t)}{dt}$$

$$\therefore \underline{\frac{d I_L}{dt} = 0}$$

$$C \frac{d}{dt} \langle v_C(t) \rangle_{IS} = C \frac{d \tilde{v}_C(t)}{dt}$$

$$\begin{bmatrix} L \frac{d\tilde{i}_L(t)}{dt} \\ C \frac{d\tilde{v}_C(t)}{dt} \end{bmatrix}_{2 \times 1} = \begin{bmatrix} f_1(\tilde{i}_L, \tilde{v}_C, \tilde{d}, \tilde{v}_{in}, \\ I_L, v_C, D, V_{in}) \\ f_2(\dots) \end{bmatrix}_{2 \times 1} = \underbrace{\begin{bmatrix} \frac{\partial f_1}{\partial \tilde{i}_L} & \frac{\partial f_1}{\partial \tilde{v}_C} \\ \frac{\partial f_2}{\partial \tilde{i}_L} & \frac{\partial f_2}{\partial \tilde{v}_C} \end{bmatrix}_{2 \times 2} \begin{bmatrix} \tilde{i}_L \\ \tilde{v}_C \end{bmatrix}_{2 \times 1}}_{\text{jacobian}} + \underbrace{\begin{bmatrix} \frac{\partial f_1}{\partial \tilde{d}} & \frac{\partial f_1}{\partial \tilde{v}_{in}} \\ \frac{\partial f_2}{\partial \tilde{d}} & \frac{\partial f_2}{\partial \tilde{v}_{in}} \end{bmatrix}_{2 \times 2} \begin{bmatrix} \tilde{d} \\ \tilde{v}_{in} \end{bmatrix}_{2 \times 1}}_{2 \times 1}$$

$$\frac{d\langle \tilde{v}(t) \rangle}{dt} = \frac{f_1(x, u)}{L} = \frac{1}{L} \left[ \langle v_{in}(t) \rangle_{T_S} d(t) - \langle v_C(t) \rangle_{T_S} d'(t) \right] \checkmark$$

$$\frac{d\langle v_C(t) \rangle}{dt} = \frac{f_2(x, u)}{C} = \frac{1}{C} \left[ -\frac{v_C(t) \lambda_{T_S}}{R} + \langle i_L(t) \rangle_{T_S} d'(t) \right]$$

$$\begin{bmatrix} \frac{d\tilde{i}_L(t)}{dt} \\ \frac{d\tilde{v}_C(t)}{dt} \end{bmatrix} = \begin{bmatrix} f_1(\tilde{i}_L) \\ f_2(\tilde{v}_C) \end{bmatrix} = \begin{bmatrix} 0 & -d'(t)/L \\ \frac{d'(t)}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} \tilde{i}_L \\ \tilde{v}_C \end{bmatrix} + \begin{bmatrix} \frac{\langle v_{in}(t) + v_C(t) \rangle_{T_S}}{L} \frac{d(t)}{L} \\ -\frac{\langle i_L(t) \rangle_{T_S}}{C} 0 \end{bmatrix} \begin{bmatrix} \tilde{d} \\ \tilde{v}_{in} \end{bmatrix}$$

$\alpha = \bar{x}$   
 $u = \bar{u}$

$\alpha = \bar{x}$   
 $u = \bar{u}$

$$\frac{\partial \langle v_C(t) \rangle_{T_S} d'(t)}{\partial \bar{v}_C} = \frac{\partial}{\partial v_C} (\langle v_C(t) \rangle_{T_S} d'(t))$$

$$\frac{\partial}{\partial \bar{d}} \frac{1}{L} \left[ \langle v_{in}(t) \rangle_{T_S} d(t) - \langle v_C(t) \rangle_{T_S} (1-d(t)) \right] = \frac{\partial}{\partial \bar{d}} \frac{1}{L} \left[ \langle v_{in}(t) \rangle_{T_S} (D+\bar{d}) - \langle v_C(t) \rangle_{T_S} (1-D-\bar{d}) \right] = \frac{\langle v_{in}(t) \rangle_{T_S}}{L} + \frac{\langle v_C(t) \rangle_{T_S}}{L}$$

$d(t) = D + \bar{d}$

$\bar{x} = \begin{bmatrix} \bar{i}_L \\ \bar{v}_C \end{bmatrix} = \begin{bmatrix} \frac{V_0}{D+R} \\ \frac{V_{in} D}{D+R} \end{bmatrix}$

$$\begin{bmatrix} \frac{d\tilde{i}_L(t)}{dt} \\ \frac{d\tilde{v}_C(t)}{dt} \end{bmatrix} = \begin{bmatrix} 0 & -D'/L \\ \frac{D'}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} \tilde{i}_L \\ \tilde{v}_C \end{bmatrix} + \begin{bmatrix} \frac{V_{in} + V_0}{L} \\ -\frac{1}{C} \end{bmatrix}$$

$\bar{x} = \begin{bmatrix} D \\ V_{in} \end{bmatrix}$

$$\ddot{\tilde{x}} = A \tilde{x} + B \tilde{u}$$

Laplace

$$s\tilde{x}(s) - \tilde{x}(0) = A \tilde{x}(s) + B \tilde{u}(s)$$

$\downarrow_0$

$$s\tilde{x}(s) = s I \tilde{x}(s)$$

(from  $s = s I \tilde{x}(s)$ )

$$s I \tilde{x}(s) - A \tilde{x}(s) = B \tilde{u}(s)$$

$$(sI - A) \tilde{x}(s) = B \tilde{u}(s)$$

$$s = s I \tilde{x}(s)$$

$$= s I \begin{bmatrix} \tilde{w} \\ \tilde{v}_c \end{bmatrix}$$

$$\begin{bmatrix} s & 0 \\ 0 & s \end{bmatrix} \tilde{x}(s) = s \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} \tilde{w} \\ \tilde{v}_c \end{bmatrix}$$

$$\tilde{x}(s) = \xrightarrow[\text{vector}]{\text{transfer matrix}} \begin{bmatrix} (sI - A)^{-1} B \\ \tilde{x}(s) \end{bmatrix}$$

$$\begin{bmatrix} \tilde{u}(s) \\ \tilde{v}_c(s) \end{bmatrix} = \left\{ \begin{bmatrix} s & 0 \\ 0 & s \end{bmatrix} - \begin{bmatrix} 0 & -D'/L \\ D/L & -1/R_C \end{bmatrix} \right\}^{-1} \begin{bmatrix} \frac{V_{in} + V_o}{L} & P_L \\ -\frac{L}{C} & 0 \end{bmatrix} \begin{bmatrix} \tilde{w} \\ \tilde{v}_{in}(s) \end{bmatrix}$$

$$= \begin{bmatrix} s & +D'/L \\ -\frac{D'}{C} & s + \frac{1}{R_C} \end{bmatrix}^{-1} \begin{bmatrix} \frac{V_{in} + V_o}{L} & P_L \\ -\frac{L}{C} & 0 \end{bmatrix} \begin{bmatrix} \tilde{w} \\ \tilde{v}_{in}(s) \end{bmatrix}$$

$$\begin{bmatrix} a & b \\ c & d \end{bmatrix}^{-1} = \frac{1}{ad - bc} \begin{bmatrix} d & -c \\ -b & a \end{bmatrix}^T$$

$$= \frac{1}{ab - bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$$

$$= \frac{1}{s \left( s + \frac{1}{R_C} \right) + \frac{D'^2}{LC}} \begin{bmatrix} s + \frac{1}{R_C} & -D'/L \\ D'/C & s \end{bmatrix} \begin{bmatrix} \frac{V_{in} + V_o}{L} & P_L \\ -\frac{L}{C} & 0 \end{bmatrix} \begin{bmatrix} \tilde{w} \\ \tilde{v}_{in}(s) \end{bmatrix}$$

$$\begin{bmatrix} \tilde{i}_L(s) \\ \tilde{v}_c(s) \end{bmatrix} = \left( \frac{1}{s^2 + \frac{s}{RC} + \frac{D'^2}{LC}} \right) \begin{bmatrix} \left( s + \frac{1}{RC} \right) \left( \frac{V_{in} + V_o}{L} \right) + \frac{D'}{LC} I_L & \left( s + \frac{1}{RC} \right) \frac{D'}{L} \\ \frac{D'}{C} \left( \frac{V_{in} + V_o}{L} \right) - \frac{S I_L}{C} & \frac{D'^2 D}{LC} \end{bmatrix} \begin{bmatrix} \tilde{V}_{in}(s) \\ \tilde{I}_{in}(s) \end{bmatrix}$$

$$\tilde{i}_L(s) = \frac{\left( s + \frac{1}{RC} \right) \left( \frac{V_{in} + V_o}{L} \right) + \frac{D'}{LC} I_L}{s^2 + \frac{s}{RC} + \frac{D'^2}{LC}}$$

$$\frac{\tilde{i}_L(s)}{D(s)} = \frac{\left( sC + \frac{1}{R} \right) \left( \frac{V_{in} + V_o}{L} \right) + \frac{D'}{LC} I_L}{LC s^2 + \frac{sL}{R} + \frac{D'^2}{LC}}$$



$$\begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} a & b \\ c & d \end{bmatrix} \begin{bmatrix} p \\ q \end{bmatrix}$$


$$x = ap + bq$$

$$y = cq + dq$$

$$q=0 \quad \therefore \quad \frac{m}{p} = a$$

$$\frac{\tilde{i}_L(s)}{D(s)} = \frac{(V_{in} + V_C) \left( sC + \frac{1}{R} \right) + D' I_L}{s^2 LC + \frac{sL}{R} + \frac{D'^2}{LC}}$$

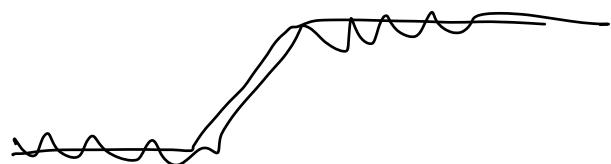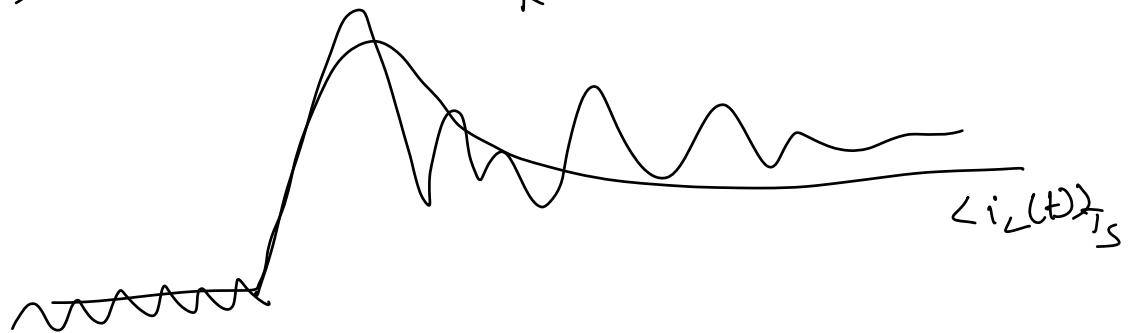

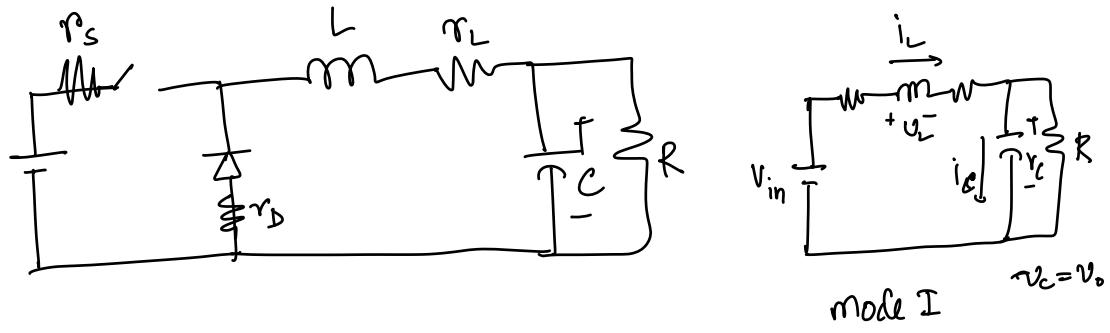


Mode I

$$L \frac{di_L}{dt} = v_{in} - v_c - r_s i_L - i_L \cdot r_L$$

$$C \frac{dv_c}{dt} = i_L - \frac{v_c}{R}$$

Mode II

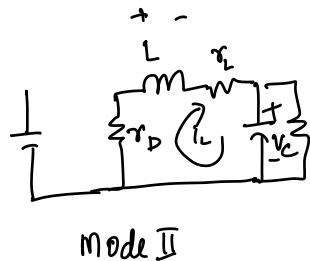

$$L \frac{di_L}{dt} = -i_L r_L - i_L r_D - v_c$$

$$C \frac{dv_c}{dt} = i_L - \frac{v_c}{R}$$

$$L \frac{di_L}{dt} + r_s = d(t) \left[ v_{in} - v_c - r_s i_L - i_L \cdot r_L \right] + d'(t) \left[ -i_L r_L - i_L r_D - v_c \right]$$

$$C \frac{dv_c}{dt} = d(t) \left[ i_L - \frac{v_c}{R} \right] + d'(t) \left[ i_L - \frac{v_c}{R} \right] \\ = i_L - \frac{v_c}{R}$$

$$\bar{u} = ? = \begin{bmatrix} D \\ v_{in} \end{bmatrix}$$

$$\bar{x} = ? = \begin{bmatrix} I_L \\ v_c \end{bmatrix}$$

$$D \left[ v_{in} - v_c - r_s i_L - i_L \cdot r_L \right] \\ + D' \left[ -i_L r_L - i_L r_D - v_c \right] = 0 \quad \textcircled{1}$$

$$I_L = \frac{v_c}{R} \quad \textcircled{2}$$

$$I_L = \underline{\hspace{2cm}}$$

$$V_C = \underline{\hspace{2cm}}$$

$$\dot{x}(t) = A \Big|_{\begin{array}{l} x=\bar{x} \\ u=\bar{u} \end{array}} \tilde{x}(t) + B \Big|_{\begin{array}{l} x=\bar{x} \\ u=\bar{u} \end{array}} \tilde{u}(t)$$

$$\frac{d\tilde{i}_L}{dt} = \frac{1}{L} \left[ d(t) \left[ V_{in} - V_C - r_s i_L - i_L r_L \right] + d'(t) \left[ -i_L r_L - i_L r_D - V_C \right] \right] = f_1.$$

$$\frac{d\tilde{V}_C}{dt} = \frac{1}{C} \left\{ i_L - \frac{V_C}{R} \right\} = f_2$$

$$\begin{bmatrix} \frac{d\tilde{i}_L}{dt} \\ \frac{d\tilde{V}_C}{dt} \end{bmatrix} = \begin{bmatrix} \frac{\partial f_1}{\partial \tilde{i}_L} & -\frac{d(t)r_s - r_L - d'(t)r_D}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} \tilde{i}_L \\ \tilde{V}_C \end{bmatrix} + \begin{bmatrix} \tilde{i}_L \\ \tilde{V}_C \end{bmatrix}_{x=\bar{x}, u=\bar{u}}$$

$$\begin{bmatrix} \frac{1}{L} \left( V_{in} - V_C - r_s i_L - i_L r_L \right) \\ \frac{i_L r_L + i_L r_D + V_C}{L} \end{bmatrix} = \frac{d(t)}{L} \begin{bmatrix} \tilde{i}_L \\ \tilde{V}_C \end{bmatrix} + \begin{bmatrix} \tilde{V}_{in} \\ 0 \end{bmatrix}_{x=\bar{x}, u=\bar{u}}$$

$$\dot{x} = \underbrace{\begin{bmatrix} -\frac{D(r_s + r_D) - r_L}{L} \\ \frac{1}{C} \end{bmatrix}}_A \tilde{x} + \underbrace{\begin{bmatrix} -\frac{1}{L} \\ -\frac{1}{RC} \end{bmatrix}}_B \tilde{u}$$

$$\begin{bmatrix} \frac{1}{L} \left( V_{in} + I_L (r_s + r_D) \right) \\ 0 \end{bmatrix} = \underbrace{\begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix}}_D \tilde{u}$$

$$\tilde{v}(s) = (sI - A)^{-1} B u(s) \Rightarrow \begin{bmatrix} \tilde{v}(s) \\ \tilde{v}_c(0) \end{bmatrix} = (sI - A)^{-1} B \begin{bmatrix} \tilde{i}_c \\ v_{in}(s) \end{bmatrix}$$

$$\begin{bmatrix} \tilde{v}_c(s) \\ \tilde{v}_{in}(s) \end{bmatrix} = \frac{1}{\Delta} \begin{bmatrix} s + \frac{1}{RC} & \frac{1}{L} \\ -\frac{1}{C} & s + \frac{D(r_s+r_D)+r_L}{L} \end{bmatrix} \begin{bmatrix} \frac{1}{L}(v_{in} + I_L(-r_s+r_D)) & \frac{1}{L} \\ 0 & D \end{bmatrix} \begin{bmatrix} \tilde{v}_{in} \\ \tilde{i}_c \end{bmatrix}$$

$$\Delta = \left( s + \frac{1}{RC} \right) \left( s + \frac{D(r_s+r_D)+r_L}{L} \right) + \frac{1}{LC}$$

$$\frac{\tilde{v}_c(s)}{\tilde{v}_{in}(s)} = \frac{\left( s + \frac{1}{RC} \right) \frac{1}{L} (v_{in} + I_L(-r_s+r_D))}{\Delta}$$

$$s^2 + \dots$$

$$\frac{\tilde{v}_c(s)}{\tilde{v}_{in}(s)} =$$

$$\frac{\tilde{i}_c(s)}{\tilde{v}_{in}(s)} =$$

$$\boxed{\dot{x} = Ax + Bu}$$

Sample code for:

① symbolic inverse.

② solving ODE