

EE 458 – Power Electronics Controls

Homework 3

Kevin Egedy

1 Boost Converter Computations

Find the small signal output voltage to duty ratio transfer function as defined,

$$G_{vd}(s) = G_0 \frac{1 - \frac{s}{w_z}}{1 + \frac{s}{Qw_0} + \left(\frac{s}{\omega_0}\right)^2}.$$

Volt-Seconds

$$\langle v_L(t) \rangle = L \frac{d}{dt} \langle i(t) \rangle = \left[\left(\langle v_g(t) \rangle \right) d(t) + \left(\langle v_g(t) \rangle - \langle v(t) \rangle \right) d'(t) \right]$$

$$\langle v_L(t) \rangle = L \frac{d}{dt} \langle i(t) \rangle = \left[\langle v_g(t) \rangle - \langle v(t) \rangle d'(t) \right]$$

$$V = \frac{V_g}{D'}$$

Charge Balance

$$\langle i_C(t) \rangle = C \frac{d}{dt} \langle v(t) \rangle = \left[\left(\frac{-\langle v(t) \rangle}{R} \right) d(t) + \left(\langle i(t) \rangle - \frac{\langle v(t) \rangle}{R} \right) d'(t) \right]$$

$$\langle i_C(t) \rangle = C \frac{d}{dt} \langle v(t) \rangle = \left[\frac{-\langle v(t) \rangle}{R} + \langle i(t) \rangle d'(t) \right]$$

$$I = \frac{V}{D'R} = \frac{V_g}{D'^2 R}$$

System Inputs

$$\dot{x} = \frac{d}{dt} \begin{bmatrix} \langle \hat{i}(t) \rangle \\ \langle \hat{v}(t) \rangle \end{bmatrix} = \frac{1}{L} \begin{bmatrix} \langle v_g(t) \rangle - \langle v(t) \rangle d'(t) \\ \frac{-\langle v(t) \rangle}{R} + \langle i(t) \rangle d'(t) \end{bmatrix}$$

System Output $\hat{y}(s)$

$$\hat{y}(s) = \left(C(sI - A)^{-1}B + E \right) \hat{u}(s)$$

$$A = \left[\begin{array}{cc} \frac{\partial f_1}{\partial x_1} & \frac{\partial f_1}{\partial x_2} \\ \frac{\partial f_2}{\partial x_1} & \frac{\partial f_2}{\partial x_2} \end{array} \right] \Big|_{x,u} = \left[\begin{array}{cc} \frac{\partial f_1}{\partial \langle \hat{i}(t) \rangle} & \frac{\partial f_1}{\partial \langle \hat{v}(t) \rangle} \\ \frac{\partial f_2}{\partial \langle \hat{i}(t) \rangle} & \frac{\partial f_2}{\partial \langle \hat{v}(t) \rangle} \end{array} \right] \Big|_{x,u} = \left[\begin{array}{cc} 0 & \frac{-D'}{L} \\ \frac{D'}{C} & \frac{-1}{RC} \end{array} \right]$$

$$B = \left[\begin{array}{cc} \frac{\partial f_1}{\partial u_1} & \frac{\partial f_1}{\partial u_2} \\ \frac{\partial f_2}{\partial u_1} & \frac{\partial f_2}{\partial u_2} \end{array} \right] \Big|_{x,u} = \left[\begin{array}{cc} \frac{\partial f_1}{\partial \hat{d}(t)} & \frac{\partial f_1}{\partial \langle \hat{v}_g(t) \rangle} \\ \frac{\partial f_2}{\partial \hat{d}(t)} & \frac{\partial f_2}{\partial \langle \hat{v}_g(t) \rangle} \end{array} \right] \Big|_{x,u} = \left[\begin{array}{cc} \frac{V}{L} & \frac{1}{L} \\ \frac{-I}{C} & 0 \end{array} \right] = \left[\begin{array}{cc} \frac{V_g}{D'L} & \frac{1}{L} \\ \frac{-V_g}{D'^2 RC} & 0 \end{array} \right]$$

System Output expressed in equivalent $G(s)$

$$\hat{y}(s) = \left(C(sI - A)^{-1}B + E \right) \hat{u}(s)$$

$$\hat{y}(s) = G(s)u(s)$$

$$G(s) = \begin{bmatrix} G_{id}(s) & G_{ig}(s) \\ G_{vd}(s) & G_{vg}(s) \end{bmatrix}$$

$$= \begin{bmatrix} \left(\frac{V_g}{D'} \right) \frac{RCs + 2}{RLCs^2 + Ls + D'^2 R} & \frac{RCs + 1}{RLCs^2 + Ls + D'^2 R} \\ \left(\frac{-V_g}{D'^2} \right) \frac{Ls - D'^2 R}{RLCs^2 + Ls + D'^2 R} & \frac{D'R}{RLCs^2 + Ls + D'^2 R} \end{bmatrix}$$

Small signal output voltage to duty ratio transfer function

$$G_{vd}(s) = G_0 \frac{1 - \frac{s}{w_z}}{1 + \frac{s}{Qw_0} + \left(\frac{s}{\omega_0} \right)^2}$$

$$G_{vd}(s) = \left(\frac{V_g}{D'^2} \right) \frac{D'^2 R - Ls}{D'^2 R + Ls + RLCs^2} = \left(\frac{V_g}{D'^2} \right) \frac{1 - \frac{L}{D'^2 R} s}{1 + \frac{L}{D'^2 R} s + \frac{RLC}{D'^2 R} s^2} = \left(\frac{V_g}{D'^2} \right) \frac{1 - \frac{s}{\frac{D'^2 R}{L}}}{1 + \frac{s}{\left(D'R\sqrt{\frac{C}{L}} \right) \left(\frac{D'}{\sqrt{LC}} \right)} + \frac{s^2}{\left(\frac{D'}{\sqrt{LC}} \right)^2}}$$

Parameter Value

$$G_0 \quad \frac{V_g}{D'^2}$$

$$\omega_z \quad \frac{D'^2 R}{L}$$

$$Q \quad D'R\sqrt{\frac{C}{L}}$$

$$\omega_0 \quad \frac{D'}{\sqrt{LC}}$$

2 Stability

Describe the stability of the system $G_{vd}(s)$, under the following conditions.

Parameter	Value
V_{in}	24V
V_{out}	48V
P_{out}	250W
f_{sw}	100kHz
L	1.25mH
C	250 μF

With this system,

$$\begin{aligned}
 P_{out} &= I^2 R = \left(\frac{V}{D'R} \right)^2 R \\
 R &= \frac{V^2}{P_{out} D'^2} = 37 \Omega \\
 \omega_z &= \frac{D'^2 R}{L} = 7373 \text{ Hz} \\
 \omega_0 &= \frac{D'}{\sqrt{LC}} = 894 \text{ Hz}
 \end{aligned}$$

2.1 Reduce current ripple $i(t)$: stability decreases

Current ripple is defined by $\frac{i_L}{dt} \propto \frac{1}{L}$.

Increasing L results in smaller w_z since $w_z \propto \frac{1}{L}$.

Increasing L results in smaller w_0 since $w_0 \propto \frac{1}{\sqrt{L}}$.

The phase margin decreases thus the system stability decreases.

2.2 Decrease output power to 100W: stability increases

Power is defined as $P_{out} = I^2 R$ such that I is 1.58x ($\sqrt{2.5}$) smaller than the original value.





Output current I is defined as $I = \frac{V}{D'R}$ where R and V is held constant (problem doesn't state output voltage has changed).

Then D' is inversely proportional to I such that it increases when power is decreased.

Increasing D' results in larger w_z since $w_z \propto D'^2$.

Increasing D' results in larger w_0 since $w_0 \propto D'$.

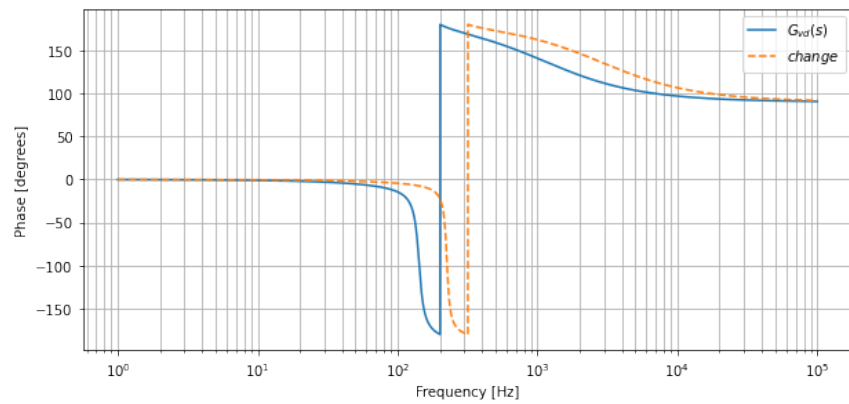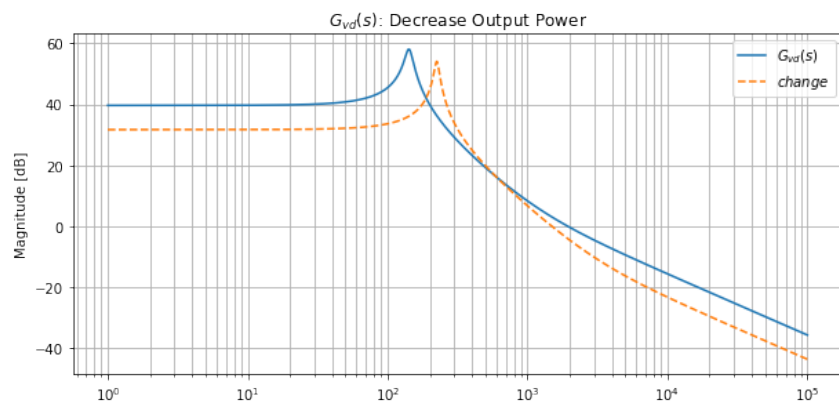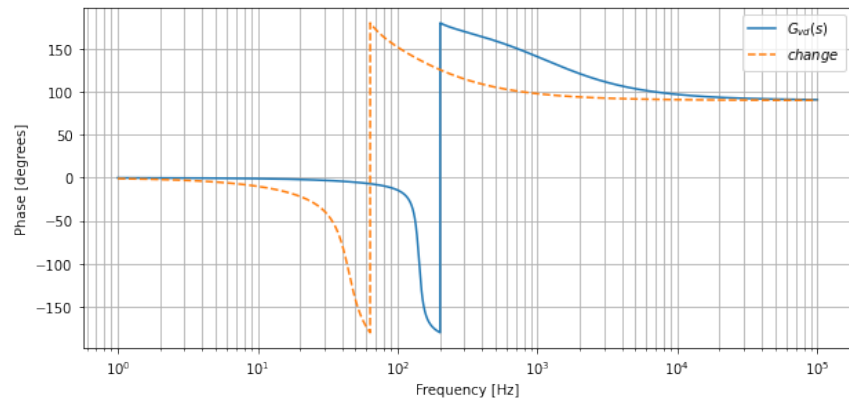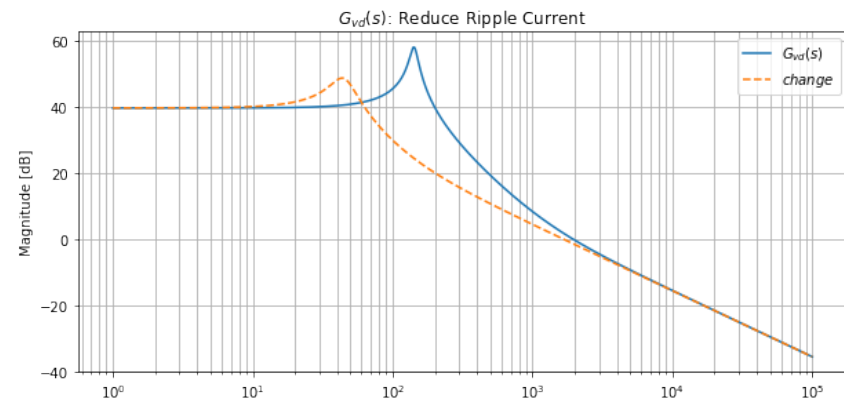The phase margin increases thus the system stability increases.



2.3 Decrease switching frequency to 10kHz: stability unchanged

The zeros or poles have no dependence on switching frequency and no ripple requirements are defined.

Thus stability remains unchanged.

2.4 Decrease output voltage to 30V: stability increases


Output voltage is defined as $V = \frac{V_g}{D'}$ where V_g is held constant (problem doesn't state it has changed).

Then D' is inversely proportional to V such that it increases when output voltage is decreased.

Increasing D' results in larger w_z since $w_z \propto D'^2$.

Increasing D' results in larger w_0 since $w_0 \propto D'$.

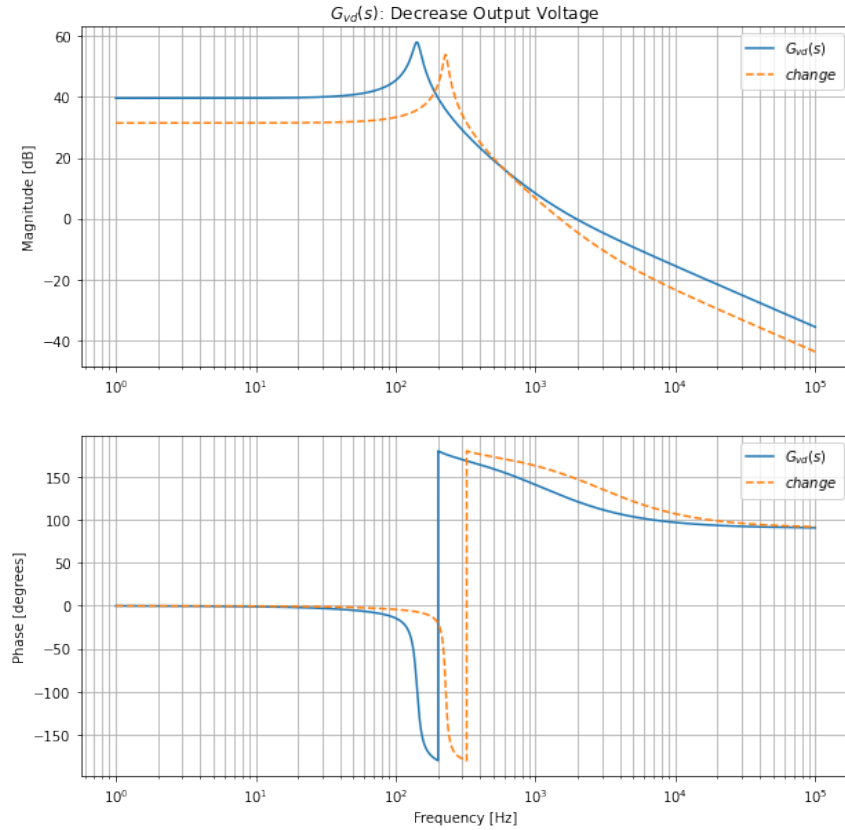The phase margin increases thus the system stability increases.






3 Transfer Functions

$$G_1(s) = 100 \frac{1}{1 + \frac{s}{2\pi \cdot 1kHz}}$$

$$G_2(s) = \frac{1}{1 + \frac{s}{2\pi \cdot 10kHz}}$$
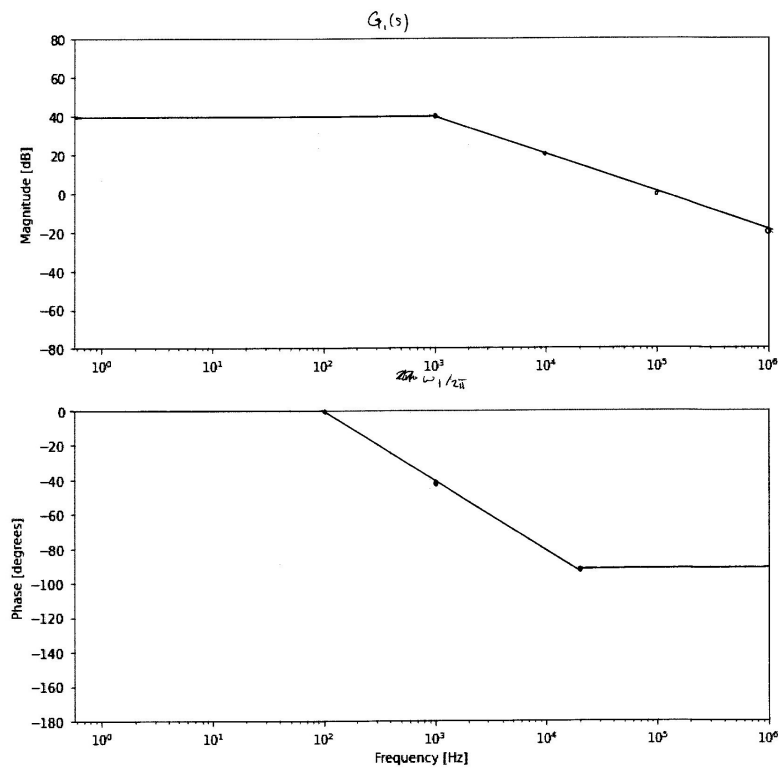
$$G_1(s)G_2(s) = G_0 \left(\frac{1}{1 + \frac{s}{\omega_1}} \right) \left(\frac{1}{1 + \frac{s}{\omega_2}} \right) = 100 \frac{1}{\left(1 + \frac{s}{2\pi \cdot 1kHz}\right) \left(1 + \frac{s}{2\pi \cdot 10kHz}\right)}$$



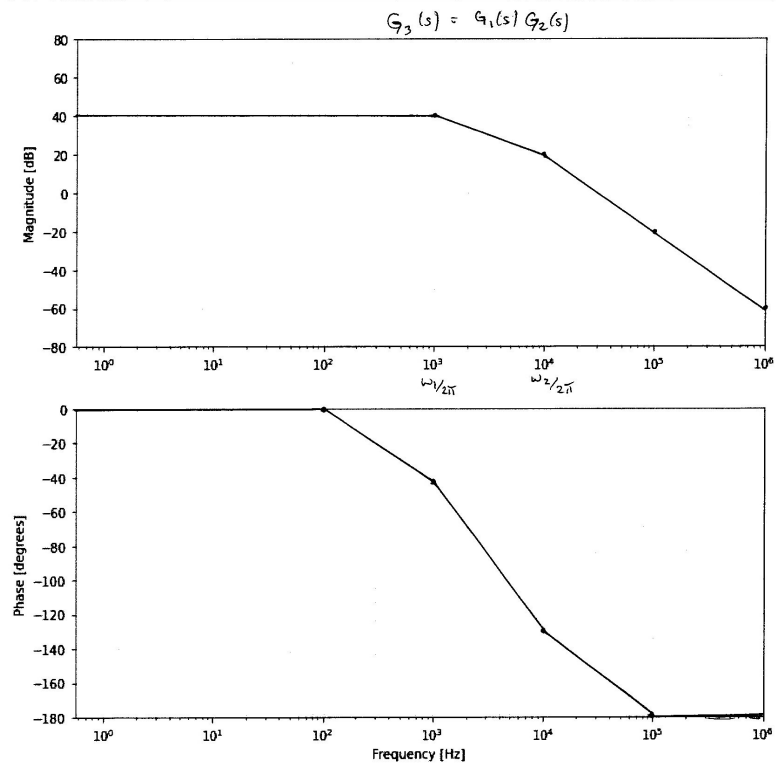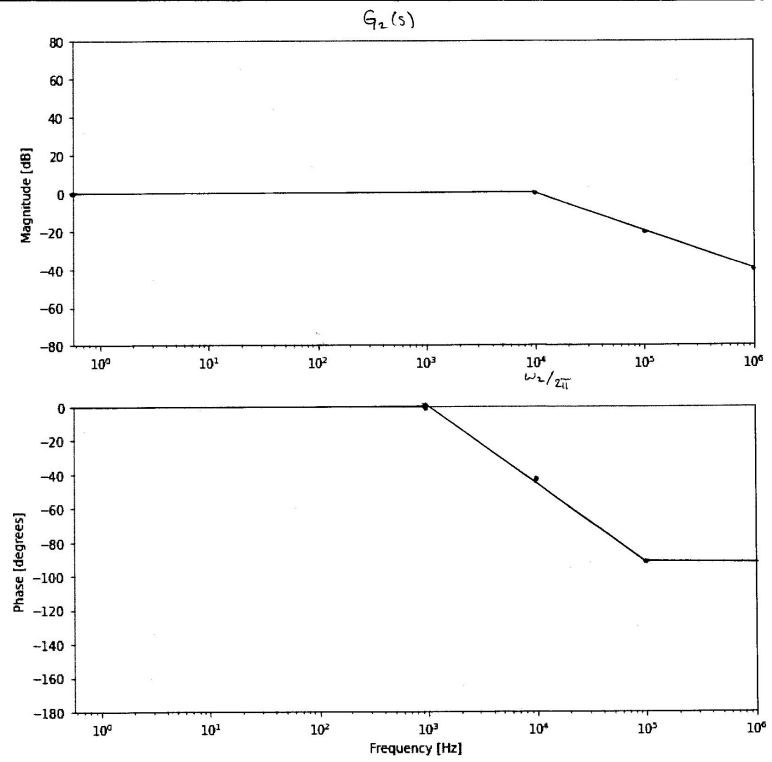

4 ADC and PWM

4.1 Digital Integer Value $x_{A/D}$

$$V_{FS} = 3V$$

$$n_{A/D} = 12bits$$

$$v_{A/D} = 0.75V$$

$$x_{A/D} = \left(\frac{v_{A/D}}{V_{FS}} \right) 2^{n_{A/D}} = \left(\frac{0.75}{3} \right) 2^{12} = 1024$$

4.2 Voltage Resolution $q_{A/D}$

$$q_{A/D} = \frac{v_{A/D}}{2^{n_{A/D}}} = 0.000732V = 0.732mV$$

4.3 T_{hold}

$$T_{sw} = 100kHz$$

$$T_{ctrl} = T_{A/D} + T_{comp} + T_{hold} = T_{sw}$$

$$\frac{1}{100kHz} = \frac{50}{100MHz} + \frac{500}{100MHz} + T_{hold}$$

$$T_{hold} = \frac{1}{100kHz} - \frac{50}{100MHz} - \frac{500}{100MHz}$$

$$T_{hold} = 10\mu s - 0.5\mu s - 5\mu s$$

$$T_{hold} = 4.5\mu s$$

$$\frac{T_{hold}}{T_{ctrl}} = \frac{4.5\mu s}{10\mu s} = 0.45$$

4.4 T_{ctrl}, T_{mod}, T_d

$$T_{clk} = 100MHz$$

$$T_{ctrl} = 10\mu s = 1000T_{clk}$$

$$T_{mod} = D'T_{sw} = D' \cdot 1000T_{clk}$$

$$T_d = T_{A/D} + T_{comp} + T_{hold} + T_{mod}$$

$$Td = T_{ctrl} + T_{mod}$$

$$T_d = (1 + D')1000T_{clk} = (2 - D)1000T_{clk}$$

4.5 see figure

4.6 see figure

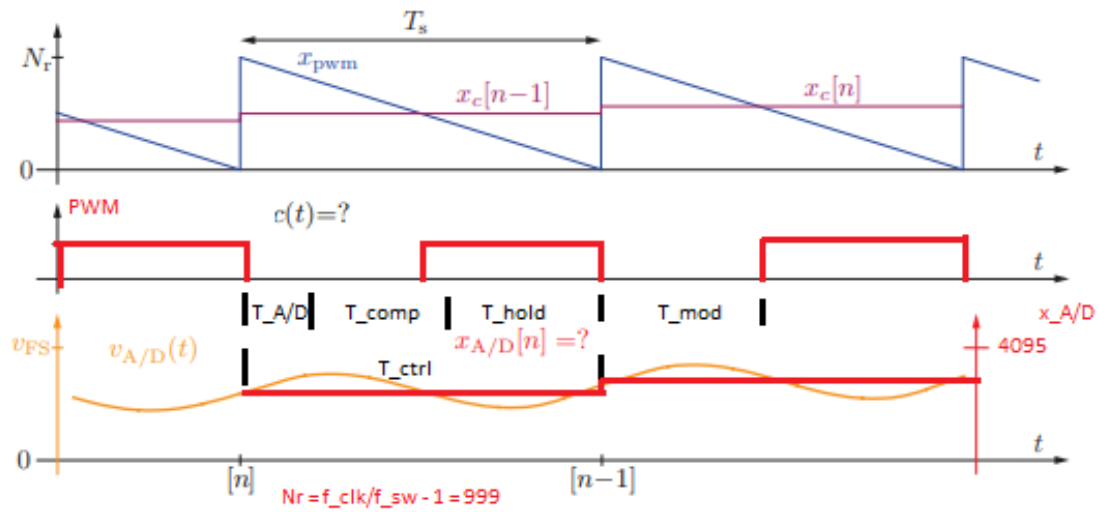


Figure 2: Digital system waveforms for Problem 3.